

EVERYDAY

DECEMBER 1994

WITH

PRACTICAL

ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

FULLY S.O.R. £2.15

EPE FRUIT MACHINE

**MICROCONTROLLER
DESIGN THAT
REALLY PAYS OUT!**

UNIVERSAL DIGITAL CODE LOCK

**over 20,000
possible combinations**

SPACEWRITER

**Write Christmas
messages in the air**

VIDEO MODULES

**Horizontal and Vertical
Wipers plus Audio Mixer**



PC PAL VGA to TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and sware. £49.95. Ideal for laptops or a cheap upgrade.

EMERGENCY LIGHTING UNIT Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased. 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11.

GUIDED MISSILE WIRE. 4,200 metre reel of ultra thin 4 core insulated cable, 28lbs breaking strain, less than 1mm thick! Ideal alarms, intercoms, fishing, dolls house's etc. £14.99 ref MAG15P5

SINCLAIR C6 13" WHEELS Complete with centre bearing (cycle type), tyre and inner tube. £6 ea ref MAG6P10. Ideal go kart **300v PANELMETER** 70X60X50MM, AC, 90 degree scale. Good quality meter. £5.99 ref MAG6P14. Ideal for monitoring mains etc.

ASTEC SWITCHED MODE PSU BM41012 Gives +5 @ 3.75A, +12 @ 1.5A, -12 @ 4A. 230/110, cased, BM41012. £5.99 ref AUG6P3.

TORRIDIAL TX 30-0-30 480VA, Perfect for Mosfet amplifiers etc. 120mm dia 55mm thick. £18.99 ref APR19.

AUTO SUNCHARGER 155x300mm solar panel with diode and 3metre lead fitted with a cigar plug. 12v 2watt. £9.99 ea ref AUG10P3.

FLOPPY DISCS DSDD Top quality 5.25" discs, these have been written to once and are unused. Pack of 20 is £4 ref AUG4P1.

MOD WIRE Perfect for repairing PCB's, wire wrap etc. Thin insulated wire on 500m reels. Our price just £9.99 ref APR10P8.

12v MOVING LIGHT Controller. Made by Hella, 6 channels rated at 90watts each. Speed control, cased. £34.99 ref APR35.

ECLATRON FLASH TUBE As used in police car flashing lights etc, full spec supplied, 60-100 flashes a min. £9.99 ref APR10P5.

24v AC 96WATT Cased power supply. New. £13.99 ref APR14.

MILITARY SPEC GEIGER COUNTERS Unused and straight from Her Majesty's forces. £50 ref MAG50P3.

STETHOSCOPE Fully functioning stethoscope, ideal for listening to hearts, pipes, motors etc. £6 ref MAR6P6.

OUTDOOR SOLAR PATH LIGHT Captures sunlight during the day and automatically switches on a built in lamp at dusk. Complete with sealed lead acid battery etc. £19.99 ref MAR20P1.

ALARM VERSION Of above unit comes with built in alarm and pir to deter intruders. Good value at just £24.99 ref MAR25P4.

CLOCKMAKER KIT Hours of fun making your own clock, complete instructions and everything you need. £7.99 ref MAR8P2.

CARETAKER VOLUMETRIC Alarm, will cover the whole of the ground floor against forced entry. Includes mains power supply and integral battery backup. Powerful internal siren, will take external bell if req'd. Retail £150+, ours? £49.99 ref MAR50P1.

TELEPHONE CABLE White 6 core 100m reel complete with a pack of 100 clips. Ideal 'phone extns etc. £7.99 ref MAR8P3.

IBM PC CASE AND PSU Ideal base for building your own PC. Ex equipment but OK. £9.99 each REF: JUN10P2.

MICRODRIVE STRIPPER Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. £2 each ref JUN2P3.

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: MAG6P8

SOLID STATE RELAYS Will switch 25A mains. Input 3.5-26v DC 57x43x21mm with terminal screws £3.99 REF MAG4P10

300DPI A4 DTP MONITOR Brand new but shop soiled so hence bargain price! TTL/ECL inputs, 15" landscape, 1200x1664 pixel complete with circuit diag to help you interface with your projects. JUST £14.99. REF JUN15P2.

MULTICORE CABLE 300 metre reel of grey 8 core cable ideal for 'phones, intercoms, computers, alarms etc. Comes in special dispensing container to avoid tangles. £15 ref AUG15.

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

ULTRAMINI BUG MIC 6mmx3.5mm made by AKG, 5-12v electret condenser. Cost £12 ea, Our? four for £9.99 REF MAG10P2.

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back anodised metal case. £79 each REF JUN79

GX4000 GAMES MACHINES returns so ok for spares or repair £9 each (no games). REF MAG9P1

C64 COMPUTERS Returns, so ok for spares etc £9 ref MAG9P2

FUSELAGE LIGHTS 3 foot by 4" panel 1/8" thick with 3 panels that glow green when a voltage is applied. Good for night lights, front panels, signs, disco etc. 50-100v per strip. £25 ref MAG25P2

ANSWER PHONES Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF MAG18P1. PSU £5 ref MAG5P12

SWITCHED MODE PSU ex equip, 60w +5v @ 5A, -5v @ 5A, +12v @ 2A, -12v @ 5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF MAG7P1

PLUG IN PSU 9V 200mA DC £2.99 each REF MAG3P9

PLUG IN ACORN PSU 19v AC 14w £2.99 each REF MAG3P10

POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9

ACORN ARCHIMEDES PSU +5v @ 4.4A. on/off sw uncased, selectable mains input, 145x100x45mm £7.99 REF MAG7P2

GEIGER COUNTER KIT Low cost professional twin tube, complete with PCB and components. Now only £19 REF AUG19.

9v DC POWER SUPPLY Standard plug in type 150ma 9v DC with lead and DC power plug. price for two is £2.99 ref AUG3P4.

AA NICAD PACK encapsulated pack of 8 AA nicad batteries (tagged) ex equip, 55x32x32mm. £3 a pack. REF MAG3P11

13.8V 1.9A psu cased with leads. Just £9.99 REF MAG10P3

360K 6.25 brand new half height floppy drives IBM compatible industry standard. Just £6.99 REF MAG7P3

PPC MODEM CARDS. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

INFRA RED REMOTE CONTROLLERS Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

TOWERS INTERNATIONAL TRANSISTOR GUIDE. A very useful book for finding equivalent transistors, leadouts, specs etc. £20 REF: MAG20P1

SINCLAIR C6 MOTORS We have a few left without gearboxes.

NEW BULL ELECTRONICS STORE IN WOLVERHAMPTON

55A WORCESTER ST TEL 0902 22039

Spec is 12v DC 3,300rpm £25 ref MAG25.

*****NEW PRODUCT*****

200 WATT INVERTER Converts 10-15v DC into either 110v or 240v AC. Fully cased 115x36x156mm, complete with heavy duty power lead, cigar plug, AC outlet socket. Auto overload shutdown, auto short circuit shutdown, auto input over voltage shutdown, auto input under voltage shutdown (with audible alarm), auto temp control, unit shuts down if overheated and sounds audible alarm. Fused reversed polarity protected. output frequency within 2%, voltage within 10%. A extremely well built unit at a very advantageous price!!! Price is £64.99 ref AUG65.

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

MAINS CABLE Precut black 2 core 2 metre lengths ideal for repairs, projects etc. 50 metres for £1.99 ref AUG2P7.

COMPUTER COMMUNICATIONS PACK Kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PCs over along distance. Complete kit £15.99 ref MAR16P2.

MINI CYCLOPS PIR 52x62x40mm runs on PP3 battery complete with shrill sander. Cheap protection at only £5.99 ref MAR6P4.

ELECTRIC MOTOR KIT Comprehensive educational kit includes all you need to build an electric motor. £9.99 ref MAR10P4.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG8P1 2 x PP3 req'd.

***MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range of up to 2 kilometres in open country. Units measure 22x52x155mm. Complete with cases and earpieces. 2xPP3 req'd. £30.00 pair REF: MAG30.

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

LQ3500 PRINTER ASSEMBLIES Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc etc In fact everything bar the case and electronics, a good stripper! £5 REF: MAG5P3 or 2 for £8 REF: MAG8P3

SPEAKER WIRE Brown 2 core 100 foot hank £2 REF: MAG2P1

LED PACK of 100 standard red 5m leds £5 REF MAG5P4

UNIVERSAL PC POWER SUPPLY complete with flyleads, switch, fan etc. Two types available 150w at £15 REF: MAG15P2 (23x23x23mm) and 200w at £20 REF: MAG20P3 (23x23x23mm)

***FM TRANSMITTER** housed in a standard working 13A adapter!! the bug runs directly off the mains so lasts forever! why pay £700? or price is £26 REF: MAG26 Transmits to any FM radio.

***FM BUG KIT** New design with PCB embedded coil for extra stability. Works to any FM radio. 9v battery req'd. £5 REF: MAG5P5

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER originally made to retail at £79 each, these units are designed to convert and ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? Price is just £3 REF: MAG3P1

100 WATT MOSFET PAIR Same spec as 25K343 and 2SJ413 (8A, 140v, 100w) 1 N channel, 1 P channel, £3 a pair REF: MAG3P2

TOP QUALITY SPEAKERS Made for Hi Fi televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality. £2 each REF: MAG2P4 or 4 for £6 REF: MAG6P2

TWEETERS 2" diameter good quality tweeter 140R (ok with the above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

AT KEYBOARDS Made by Apricot these quality keyboards need just a small mod to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price £6 REF: MAG6P3

PC CASES Again mixed types so you take a chance next one off the pile £12 REF: MAG12 or two the same for £20 REF: MAG20P4

HEADPHONES Ex Virgin Atlantic. 8 pairs for £2 REF: MAG2P8

PROXIMITY SENSORS These are small PCB's with what look like a source and sensor LED on one end and lots of components on the rest of the PCB. Complete with flyleads. Pack of 5 £3 REF: MAG: 3P5 or 20 for £8 REF: MAG8P4

*SOME OF OUR PRODUCTS MAY BE UNLICESABLE IN THE UK

SNOOPERS EAR? Original made to clip over the earpiece of telephone to amplify the sound-it also works quite well on the cable running along the wall! Price is £5 REF: MAG5P7

DOS PACKS Microsoft version 3.3 or higher complete with all manuals or price just £5 REF: MAG5P8 Worth it just for the very comprehensive manual! 5.25" only.

DOS PACK Microsoft version 5 Original software but no manuals hence only £3 REF: MAG3P6 5.25" only.

PIR DETECTOR Made by famous UK alarm manufacturer these are hi spec, long range internal units. Slight marks on case and unboxed (although brand new) £8 REF: MAG8P5

WINDUP SOLAR POWERED RADIO AM/FM radio complete with hand charger and solar panel! £14 REF: MAG14P1

MOBILE CARPHONE £5.99 Well almost! complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: MAG6P6

ALARM BEACONS Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! £5 REF: MAG5P11

FIRE ALARM CONTROL PANEL High quality metal cased alarm panel 350x165x80mm. With key. Comes with electronics but no information. sale price 7.99 REF: MAG6P6

REMOTE CONTROL PCB These are receiver boards for garage door opening systems. Another use? £4 ea REF: MAG4P5

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF: MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experiments! 30 m for £12.99 ref MAG13P1

LOPTX Line output transformers believed to be for IBM hi res colour monitors but useful for getting high voltages from low ones! £2 each REF: MAG2P12 bumper pack of 10 for £12 REF: MAG12P3.

HEATSINKS (finned) TO220, designed to mount vertically on a pcb 50x40x25mm you can have a pack of 4 for £1 ref JUN1P11.

WATERPROOF JUNCTION BOX 65mm dia 33mm deep. Four cable entry exit points (adjustable for any size cable) snap fit lid. Ideal for TV, satellite use. £2 ea ref APR2 or 6 for £10 ref APR10P7.

BOTH SHOPS OPEN 9-5.30 SIX DAYS A WEEK

INFRARED LASER NIGHT SCOPES

Second generation image intensifier complete with hand grip attachment with built in adjustable laser lamp for zero light conditions. Supplied with Pentax 42mm camera mount and normal eye piece. 1.6kg, uses 1xPP3, 3xAA's (all supplied) & £245+Vat

NEW HIGH POWER LASERS

15mW, Helium neon, 3 switchable wave lengths. .63um, 1.15um, 3.39um

(2 of them are infrared) 500:1 polarizer built in so good for holography. Supplied complete with mains power supply. 790x65mm. Use with EXTREME CAUTION AND UNDER QUALIFIED GUIDANCE. £349+Vat.

*****WE BUY SURPLUS STOCK*****

TURN YOUR SURPLUS STOCK INTO CASH. IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR COMPLETE FACTORY CLEARANCE.

1994 CATALOGUE.

MINIMUM GOODS ORDER £5.00. TRADE ORDERS FROM GOVERNMENT, SCHOOLS, UNIVERSITIES & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30 DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILLINGLY GIVEN FOR QUANTITIES HIGHER THAN THOSE STATED.

3FT X 1FT 10WATT SOLAR PANELS

14.5v/700mA

£33.95

(PLUS £2.00 SPECIAL PACKAGING CHARGE)

TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE APPLICATIONS. SOME OF WHICH MAY BE CAR BATTERY CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANYWHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: MAG34

PORTABLE RADIATION DETECTOR

£49.99

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook. Ref MAG50.

BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX

BN3 5QT

MAIL ORDER TERMS: CASH PO OR CHEQUE WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY

TELEPHONE ORDERS WELCOME

TEL: 0273 203500

FAX: 0273 323077






ISSN 0262 3617
PROJECTS...THEORY...NEWS...
COMMENT...POPULAR FEATURES...

VOL. 23 No. 12 DECEMBER 1994

EVERYDAY WITH PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

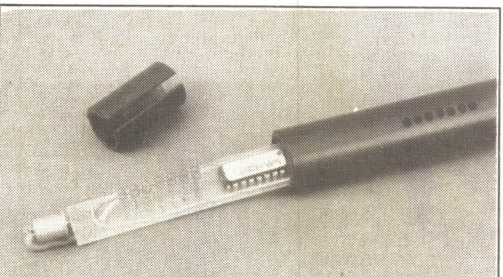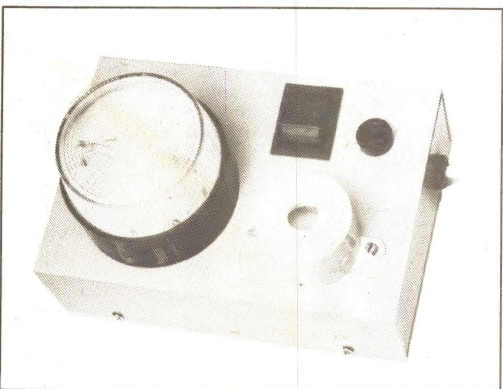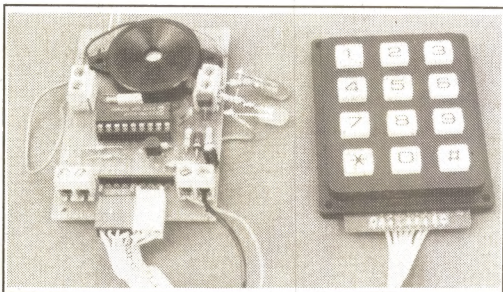**The No. 1 Independent Magazine for Electronics,
Technology and Computer Projects**



© Wimborne Publishing Ltd 1994. Copyright in all drawings, photographs and articles published in **EVERDAY with PRACTICAL ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Projects

- SPACEWRITER WAND** by Mark Stuart **906**
Conjure up Yule-tide micro-magic messages at your finger tips
- EPE FRUIT MACHINE - 1** by Brett Gossage and Julyan Ilett **909**
Put down the chips and latch onto Las Vegas for a real cash payout
- UNIVERSAL DIGITAL CODE LOCK** by Bart Trepak **944**
Stack the numbers in favour of your home security
- VIDEO MODULES - 2** by Robert Penfold **954**
Horizontal and vertical image wipers, and a 4-Channel Audio Mixer
- RODENT REPELLER** by Terry de Vaux-Balbirnie **964**
A brilliant noisy send-off for Mr. Mouse!

Series

- CIRCUIT SURGERY** by Alan Winstanley **920**
Advice on making your own p.c.b.s and winding inductors
- ELECTRONICS FROM THE GROUND UP - 3** **924**
by Mike Tooley B.A.
First steps in understanding electronics, with optional computer aided design software
- TECHNIQUES - ACTUALLY DOING IT** by Robert Penfold **934**
A beginner's guide to choosing the right tools for the task
- INTERFACE** by Robert Penfold **952**
The page for computer enthusiasts
- AMATEUR RADIO** by Tony Smith G4FA1 **976**
CIS callsigns, and 1994 in retrospect

Features

- EDITORIAL** **905**
- INNOVATIONS** **916**
Everyday news from the world of electronics
- SHOPTALK** with David Barrington **918**
Component buying for EPE projects
- FOX REPORT** by Barry Fox **936**
Has PC standardisation doomed the Apple-Mac?
- EMBEDDED CONTROLLERS** by John Davies B.Sc. **941**
Single-task computer chips are finding wider application roles
- NEW TECHNOLOGY UPDATE** by Ian Poole **950**
Glass-on-silicon chips enhance communications technology
- ELECTRONICS PRINCIPLES II SOFTWARE** **962**
Educational software - plus Electronics PC Toolbox 2.0 and GCSE Mathematics
- ELECTRONICS VIDEOS** **963**
Our range of educational videos to complement your studies
- DIRECT BOOK SERVICE** **971**
A wide range of technical books available by mail order
- PRINTED CIRCUIT BOARD SERVICE** **975**
PCBs for EPE projects - some at sale price!
- INDEX FOR VOLUME 23** **979**
- ADVERTISERS INDEX** **984**

FREE
BULL ELECTRICAL 1995 CATALOGUE (96-pages)
BANDED WITH MAGAZINE

Our January '95 issue will be published on Friday,
2 December 1994. See page 895 for details.

Readers Services • Editorial and Advertisement Departments **905**

Surplus always
wanted for cash!


THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

LOW COST PC's - ALL EXPANDABLE - ALL PC COMPATIBLE

THE OFFER OF 1994!

Surplus always
wanted for cash!

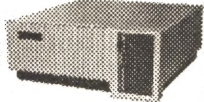

SPECIAL BUY

AT 286

40Mb HD + 3Mb Ram

LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. *Only to Run!*
Order as HIGRADE 286

ONLY £149.00 (E)

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£32.95
NE2000 Ethernet (thick, thin or twisted) network card	£49.00

FLOPPY DISK DRIVES 3.5" - 8"

5.25" from £22.95 - 3.5" from £24.95

Massive purchases of standard 5.25" and 3.5" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3.5" supported on your PC).

3.5" Panasonic JU3634 720K or equivalent	£24.95(B)
3.5" Mitsubishi MF355C-L 1.4 Meg. Laptops only *	£36.95(B)
3.5" Mitsubishi MF355C-D 1.4 Meg. Non laptop	£29.95(B)
5.25" Teac FD-55GFR 1.2 Meg	£29.95(B)
5.25" BRAND NEW Mitsubishi MF501B 360K	£22.95(B)
* Data cable included in price.	
Shugart 800/801 8" SS refurbished & tested	£195.00(E)
Shugart 851 8" double sided refurbished & tested	£250.00(E)
Mitsubishi M2894-63 8" sided switched NEW	£250.00(E)
Mitsubishi M2896-63 8" DS slimline NEW	£285.00(E)
Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply. Ideal as exterior drives!	£499.00(F)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte of hard disk storage! Full industry standard SMD Interface. Ultra high speed data transfer and access time, replaces Fujitsu equivalent model. Complete with manual. Only

3.5" FUJII FK-309-26 20mb MFM I/F RFE	£59.95(C)
3.5" CONNER CP3024 20 mb IDE I/F (or equiv) RFE	£69.95(C)
3.5" CONNER CP3044 40mb IDE I/F (or equiv) RFE	£99.00(C)
3.5" RODIME R030575 45mb SCSI I/F (Mac & Acorn)	£99.00(C)
5.25" MINISCRIBE 3425 20mb MFM I/F (or equiv) RFE	£49.95(C)
5.25" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95(C)
5.25" CDC 94205-51 40mb HF MFM I/F RFE tested	£89.95(C)
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00(E)
Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95	

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND
& VIDEO
TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£32.95
TELEBOX ST as ST but with integral speaker	£36.50
TELEBOX MB Multiband VHF-UHF-Cable - Hyperband tuner	£69.95
For overseas PAL versions state 5.0 or 6.0mhz sound specification.	
*For cable / hyperband reception Telebox MB should be connected to cable type socket. Shipping code on all Teleboxes is (B)	

FANS & BLOWERS

MITSUBUSHI MMF-D6D12DL 60 x 25 mm 12v DC	£4.95 10 / £42
MITSUBUSHI MMF-09B12DH 92 x 25 mm 12v DC	£5.95 10 / £53
PANCAKE 12-3.5 92 x 18 mm 12v DC	£7.95 10 / £69
EX-EQUIP 120 x 38mm AC fans - tested specify 110 or 240 v	£6.95
EX-EQUIP 80 x 38mm AC fans - tested specify 110 or 240 v	£45.95
VERO rack mount 10 x 19" fan tray specify 110 or 240v	£79.95
IMHOFF B26 1900 rack mnt 30 x 19" Blower 110/240v NEW	£79.95
Shipping on all fans (A), Blowers (B), 50,000 Fans Ex Stock CALL	

IC's TRANSISTORS DIODES

OBSOLETE - SHORT SUPPLY - BULK

5,000,000 items EX STOCK

For MAJOR SAVINGS - SAE or CALL FOR LATEST LIST

Issue 12 of Display News now available - send large SAE - PACKED with bargains!


display
-ELECTRONICS-

LONDON SHOP
Open Mon-Sat 9:00-5:30
215 Whitehorse Lane
South Norwood
LONDON SE25

DISTEE © The Original
FREE On line Database
Info on 1000's of items
V21, V22, V22 BIS
081 679 1888


ALL MAIL & OFFICES
Open Mon-Fri 9:00-5:30
Dept EE. 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

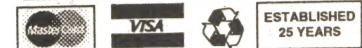ALL ENQUIRIES
081 679 4414
FAX 081 679 1927



All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Carriage charges (A)=£3, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge (A)ALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1994. E & O E.

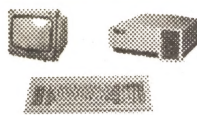PC SCOOP COMPLETE COLOUR SYSTEM ONLY £99.00



A massive bulk purchase enables us to bring you a COMPLETE ready to run colour PC system at an unheard of price! The Display Electronics PC99 system comprises of fully compatible and expandable XT PC with 256k of RAM, 5 1/4" 360K floppy disk drive, 12" CGA colour monitor, standard 84 key keyboard, MS DOS and all connecting cables - just plug in and go! Ideal students, schools or anybody wishing to learn the world of PC's on an ultra low budget. Don't miss this opportunity. Fully guaranteed for 90 Days.

Order as PC99COL £99.00 (E)

Optional Fitted extras: 640K RAM	£29.00
2nd floppy drive, specify 5 1/4" 360K or 3 1/2" 720K	£29.95
Above prices for PC99 only.	

VIDEO MONITOR SPECIALS

Superb quality 14" FOREFRONT MTS-9600 SVGA Multisync - Multimode monitor 0.28" dot pitch with resolution of 1024 x 768. The multi mode input allows direct connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COM-MODORE (including Amiga 1200), ARCHIMEDES etc. The H version will also function with the ATARI in all modes inc HI RES monochrome. Complete with text!

switching for WP use (possible minor screen burns) Syncs down to 15 kHz. Supplied in EXCELLENT little used condition with full 90 day guarantee.

Order as MTS-9600 / H for ATARI £159.00 (E)

All modes as above Order as MTS-9600 / S £139.00 (E)
ELECTROHOME ECM-12115BU 12" VGA multisync monitor with resolution 640 x 480. Multi input selection; Spin CGA/ EGA; 15 pin VGA or 5 BNC connectors. 0.31 pitch. Compatible with PCs, Amiga, Atari and others. In good used condition (possible minor screen burns). 90 day guarantee. £99.00 (E)

KME 10" high definition colour monitors. Nice tight 0.28" dot pitch for superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13.5" x 12" x 11". Only £125 (E)
Good used condition. 90 day guarantee.
KME 10" as above for PC EGA standard £145.00 (E)

NEC CGA 12" colour IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive tone ribbed grey plastic case measuring 15" x 13" x 12". The front cosmetic bezel has been removed for contractual reasons.
Only £49.00 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

9" Mono cased, Black & White for CCTV Used / Tested. £49.00 (C)

DC POWER SUPPLIES

10,000 Power Supplies Ex Stock
Call for info / list

Power One SPL200-5200P 200 watt (250 v peak). Semi open frame giving +5v 35A, -5v 1.5A, +12v 4A (8A peak), -12v 1.5A, +24v 4A (8A peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE.	£85.00 (B)
Power One SPL130. 130 watts. Selectable for 12v (4A) or 24 v (2A). 5v @ 20A. & 12v @ 1.5A. Switch mode. New.	£59.95 (B)
Astec AC-8151 40 watts. Switch mode. +5v @ 2.5A. +12v @ 2A. -12v @ 0.1A. 6-1/4" x 4" x 1-3/4" RFE tested	£22.95 (B)
Lambda LYS-PV-12 200 watt switch mode +12V DC @ 20A semi enclosed. 10" x 5" x 5". RFE and fully tested.	£59.95 (C)
Conver AC130. 130 watt hi-grade VDE spec. Switch mode +5v @ 15A, -5v @ 1A, +12v @ 6A, 27 x 12.5 x 6.5cm. New.	£49.95 (C)
Bosher 13090. Switch mode ideal for drives & system. +5v @ 6A, +12v @ 2.5A, -12v @ 0.5A, -5v @ 0.5A.	£29.95 (C)
Farnell G6/40A. Switch mode. 5v @ 40A. Encased	£95.00 (C)

SPECIAL INTEREST

INTEL SBC486/133SE Multibus 486 system. 8Mb Ram	£1975
Zeta 3220-05 A0 4 pen HPGL RS232 last drum plotter	£2100
Avitel VDA-3100 Video Distribution Amps. 1 in 92 out	£575
Trio 0-18 vdc bench PSU. 30 amps. New	£470
Fujitsu M3041 600 LPM band printer	£1950
VG Electronics 1035 Decoding Margin Meter Rack	£3750
Andrews LARGE 6 m Satellite Dish & mount (For Voyager)!	£950
RED TOP IR Hand seeking missile (not armed !!)	£470
Tektronix 1L30 Spectrum analyser plug in	£330
Thurlby LA 160B logic analyser	£375
GEC 1.5kw 115v 60hz power source	£950
Burk 2Kw 400 Hz 3 phase frequency converter	£850
Anton Pillar 75 KW 400 Hz 3 phase frequency converter	POA
Newton Derby 70 KW 400 Hz 3 phase frequency converter	POA
Nikon PL2 Projection lens meter/scope	£750
Sekonic SD 150H 18 channel digital Hybrid chart recorder	£1995
HP 7580A A1 8 pin HPGL high speed drum plotter	£1850
Kenwood DA-3501 CD tester, laser pickup simulator	£350
Computer MCA1613APC 16mm auto iris lenses 'C' mount	£125
Seaward PAT 2000 dual voltage computerised PAT tester	£585

One of the most amazing surplus deals that we ever been able to offer you! The Philips VP410 LaserVision player, in as new condition, unit features full computer control, Plays standard 12" LaserVision disks with startling visual and audio quality in two channel stereo or mono. When controlled by a computer, it may also be used as a versatile high quality storage / retrieval medium. It will play back either LaserVision CAV (active play) or CLV (Long Play) discs (which covers most types of commercially available video discs). Some of the many features of this incredible machine are:

RS-232 INTERFACE	RGB / COMPOSITE VIDEO OUTPUT
BNC+SCART INTERFACE	PAL / RGB DECODER
IR+WIRELESS REMOTE CONTROL	FAST RANDOM ACCESS

SPECIAL PURCHASE Only £399.00 (F)

BBC Model B APM Board

WIN £100
CASH!


£100 CASH FOR THE MOST
NOVEL DEMONSTRABLE
APPLICATION

BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large similar systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board! It is supplied complete with a connector panel which brings all the I/O's to 'D' and BNC type connectors - all you have to do is provide +5 and +12 v DC. The APM consists of a single PCB with most major ic's socketed. The ic's are too numerous to list but include a 6502 / 6512 CPU, RAM and an SAA5050 teletext chip. Three 27128 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information to the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Appx. dms: main board 13" x 10". I/O board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only £29.95
2 for £53 (B)

19" RACK CABINETS

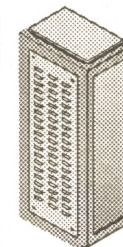Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have

ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in bays
Overall dimensions are: 77-1/2" H x 32-1/2" D x 22" W. Order as:
Rack 1 Complete with removable side panels. £295.00 (G)
Rack 2 Rack, Less side panels £175.00 (G)

Over 1000 racks in all sizes from stock!
Call with your requirements.

LOW COST RAM UPGRADES

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disk supplied. In good used condition fully tested and guaranteed. Order as: ABOVE CARD £59.95 (A1)
Windows compatible. Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in Order as: ABOVE CARD £59.95 (A1)
Rack above 640K DOS limit. Complete with data. £32.95 (A1)
Order as: XT RAM UPG. 256K £38.95 (A1)
1 MEG x 9 SIMM 9 chip 120ns only £29.95 (A1)

No Break Uninterruptible PSU's

Brand new and boxed 230 volts 1 KVA uninterruptible power supply from system from Densel. Model MUD 1085-AHBB. Complete with sealed lead acid batteries in matching case. Approx time from interrupt is 15 minutes. Complete with full manual.
Order as: MUD 1 £575.00 (G)


EMERSON ACCUCARD UPS, brand new 8 Bit half length PC compatible card for all IBM XT/AT compatibles. Card provides DC power to all internal system components in the event of power supply failure. The Accucard software provided uses only 6k of base RAM and automatically copies all system, expanded and video memory to the hard disk in the event of loss of power. When power is returned the machine is returned to the exact status when the power failed! The unit features full self diagnostics on boot and is supplied with full fitting instructions and manual. Normal price £189.00

Only £99.00 (B) or 2 for £195 (C)

MAGNETIC FIELD DETECTOR

Modern man is ever more often exposed to a variety of alternating magnetic fields of various frequencies, emanating from the huge variety of electrical and electronic devices which now form an integral part of life. Over the last few years these fields have become a source of concern to some people, who feel that constant exposure to them may constitute a hazard to health. A vast amount of research on this has been carried out, much of it by the electricity authorities who are understandably concerned about the safety of their product, but to date results have been inconclusive.

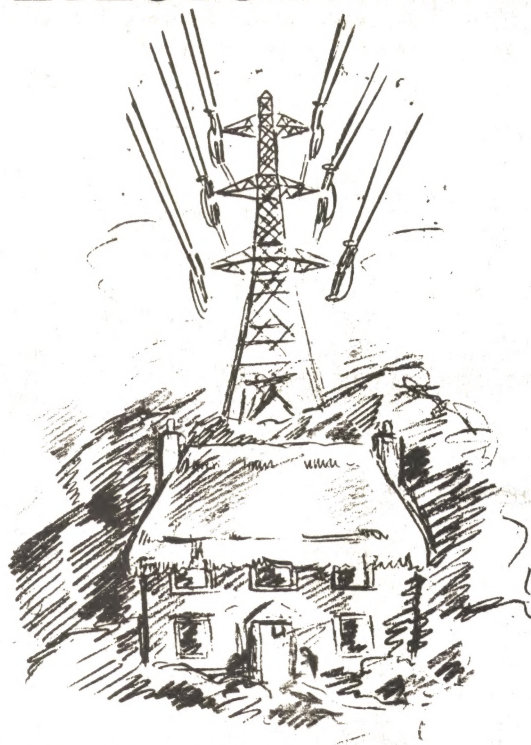However, since these fields cannot generally be seen, felt or heard, a means of detecting them may be useful to those who wish to minimise their exposure to this sort of risk. This relatively simple and inexpensive unit gives both an audible and visual (i.e.d. bargraph) indication of field strength.



ELECTRONIC TRACK CLEANER

Dirt on model railway track often produces erratic train speed and can cause a low speed train to come to a grinding halt. High quality controllers are less prone to this problem than very basic types, but if a significant length of track is affected, contact can be lost with the train, and it will come to a halt.

The best solution to the dirt problem is to simply keep the track scrupulously clean, but this can be quite difficult and time consuming. An alternative approach is to keep the track as clean as reasonably possible, and to use an electronic track cleaner to "zap" any remaining small amounts of dirt on the tracks.

This "zapping" is done by applying a high voltage across the tracks when the train goes out of electrical contact with the track. Although using a high voltage across the tracks might seem to be dangerous, this voltage is at a high impedance. The available current is therefore very low, and the equipment is incapable of giving even a moderate electric shock or of damaging the train.

MOVING DISPLAY METRONOME

The traditional mechanical metronome, with its weighted swinging-arm provides an audio and visual indication of beats per minute, but many simple electronic metronomes often overlook the visual aspect, with at best, a flash from an i.e.d. on every beat. This project fills this shortfall. It is based on a 4067 16-channel analogue multiplexer/demultiplexer with a ten i.e.d. display.

When the arm of a mechanical metronome swings from side to side it appears to slow down towards the end of its travel. To simulate this motion electronically, the outer i.e.d.s of the display stay on for longer. This produces an effective moving dot display similar to its mechanical counterpart. The metronome "clicks" are produced by a piezo electric buzzer.

EVERYDAY WITH PRACTICAL ELECTRONICS

OUR JANUARY '95 ISSUE WILL BE PUBLISHED ON FRIDAY, 2nd DECEMBER

E
L
E
C
T
R
O
N
I
C
S

HART

HART AUDIO KITS – YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HART KITS give you the opportunity to build the very best engineered hifi equipment there is, designed by the leaders in their field, using the best components that are available.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

In short HART is your 'friend in the trade' giving you, as a knowledgeable constructor, access to better equipment at lower prices than the man in the street.

You can buy the reprints and construction manual for any kit to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

Our list will give you fuller details of all our Audio Kits, components and special offers.

AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hifi system. This kit is your way to get £K performance for a few tenths of the cost! Featured on the front cover of 'Electronics Today International' this complete stereo power amplifier offers World Class performance allied to the famous HART quality and ease of construction. John Linsley Hood's comments on seeing a complete unit were enthusiastic:- "The external view is that of a thoroughly professional piece of audio gear, neat elegant and functional. This impression is greatly reinforced by the internal appearance, which is redolent of quality, both in components, and in layout." Options include a stereo LED power meter and a versatile passive front end giving switched inputs using ALPS precision, low-noise volume and balance controls. A new relay switched front end option also gives a tape input and output facility so that for use with tuners, tape and CD players, or indeed any other 'flat' inputs the power amplifier may be used on its own, without the need for any external signal handling stages. 'Slave' and 'monobloc' versions without the passive input stage and power meter are also available. All versions fit within our standard 420 x 260 x 75mm case to match our 400 Series Tuner range. ALL six power supply rails are fully stabilised, and the complete power supply, using a toroidal transformer, is contained within a heavy gauge aluminium chassis/heat sink fitted with IEC mains input and output sockets. All the circuitry is on professional grade printed circuit boards with roller tinned finish and green solder resist on the component ident side, the power amplifiers feature an advanced double sided layout for maximum performance. All wiring in this kit is pre-terminated, ready for instant use!

RLH11 Reprints of latest articles.....£1.80
K1100CM HART Construction Manual.....£5.50

LINSLEY HOOD 1400 SERIES ULTRA HIGH-QUALITY PREAMP

Joining our magnificent 80 Watt power amplifier now is the most advanced preamplifier ever offered on the kit, or indeed made-up marketplace. Facilities include separate tape signal selection to enable you to listen to one programme while recording another, up to 7 inputs, cross recording facilities, class A headphone amplifier, cancellable 3-level tone controls and many other useful functions, all selected by high quality relays. For full details see our list.

LINSLEY HOOD 'SHUNT FEEDBACK' R.I.A.A. MOVING COIL & MOVING MAGNET PICKUP PREAMPLIFIERS



Modern, ultimate sound systems are evolving towards built-in preamplifiers within or near the turntable unit. This keeps noise pickup and treble loss to a minimum. We now offer two units, both having the sonically preferred shunt feedback configuration to give an accurate and musical sound, and both having the ability to use both moving magnet and moving coil cartridges.

Kit K1500 uses modern integrated circuits to achieve outstanding sound quality at minimal cost. The very low power requirements enable this unit to be operated from dry batteries and the kit comes with very detailed instructions making it ideal for the beginner. K1500 Complete kit with all components, printed circuit board, full instructions and fully finished case.....£67.99

Instructions only.....£2.80
Kit K1450 is a fully discrete component implementation of the shunt feedback concept and used with the right cartridge offers the discerning user the ultimate in sound quality from vinyl disks. Can be fitted inside our 1400 Preamp, used externally or as a standalone unit. It has a higher power requirement and needs to be powered from our 1400 Series preamplifier or its own dedicated power supply.

K1450 Complete Discrete Component RIAA Phono Preamp.....£109.58
Factory Assembled and Tested.....£159.58

K1565 Matching Audio Grade Power Supply with potted toroidal transformer and limited shift earthing system.....£79.42
Factory Assembled and Tested.....£118.42

U1115 Power Interconnect Cable.....£7.29

SPECIAL OFFER

PRECISION Triple Purpose TEST CASSETTE TC1D.

Are you sure your tape recorder is set up to give its best? Our latest triple purpose test cassette checks the three most important tape parameters without test equipment. Ideal when fitting new heads.

A professional quality, digitally mastered test tape at a price anyone can afford.

Test Cassette TC1D Our price only £10.99

DISK-COUNT Classical CD's.

Many New Titles This Month

Top quality, Full Digital (DDD) Compact Disks of the great classical favourites. Like everyone else we didn't like the idea of paying silly prices for CD's. After a long search we have now located a source of top quality classical recordings at prices that make you suspect the quality – until you try them! Send for our list of titles.

HART PCB SOLDERING PRACTICE KIT

Your chance to learn or try your soldering skills on a real Hart printed circuit board! This kit comes with a range of modern components, a typical Hart quality PCB, a roll of the correct grade of solder and your full learning guide. It enables the enthusiast who is uncertain of his, or indeed her, ability to put together and solder a printed circuit to try their hand first at minimum cost.

The instructions explain the right technique and guide even an absolute beginner through the seemingly daunting, but in fact very simple, art of making a good soldered joint.

The Hart Printed Circuit Board Soldering Practice Kit represents excellent value for money at only £4.99.

Send or 'phone for your copy of our FREE List of these and many other Kits & Components. Enquiries from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Just write or telephone your requirements to sample the friendly and efficient HART service. Payment by cheque, cash or credit card. A telephoned order with your credit card number will get your order on its way to you THAT DAY.

Please add part cost of carriage and insurance as follows:—INLAND Orders up to £20 - £1.50,

Orders over £20 - £3.50. Express Courier, next working day £10.

OVERSEAS - Please see the ordering information with our lists.

TECHNICAL BOOKSHELF

The Following are a Small Selection of the Books we Offer. Full Details are in our Free List.

"THE ART OF LINEAR ELECTRONICS", John Linsley Hood.

Just Out! Hot Off the Press, the definitive electronics and audio book by the renowned John Linsley Hood. This 300+ page book will give you an unparalleled insight into the workings of all types of audio circuits. Learn how to read circuit diagrams and understand amplifiers and how they are designed to give the best sound. The virtues and vices of passive and active components are examined and there are separate sections covering power supplies and the sources of noise and hum. As one would expect from this writer the history and derivation of audio amplifier circuitry have an entire chapter, as does test and measurement equipment.

Copiously illustrated this book is incredible value for the amount of information it contains on the much neglected field of linear, as opposed to digital, electronics. Indeed it must be destined to become the standard reference for all who work, or are interested in, this field.

SPECIAL OFFER. With each book purchased you may request a FREE extended index, written by the Author, exclusively from HART.

0-7806-0868-4 £16.95

Don't forget most of our kits have reprints of articles by John Linsley Hood that you can purchase separately.

"TOWERS' INTERNATIONAL TRANSISTOR

SELECTOR". This will give you the specification, pin connections, case outline, manufacturer, equivalents and substitutes for over 27,000 European, American and Japanese transistors. Latest update 4 offers over 2,000 new entries plus surface mount cross index. 1990 432 Pages. 247 x 173.

0-572-01062-1 £19.95

"DIGITAL AUDIO AND COMPACT DISC

TECHNOLOGY" 2nd Edition. Baert, Theunissen

and Vergult. (SONY Europe).

A thoroughly well written book covering the whole field of recording media starting with the Phonograph right through to modern professional PCM digital recording systems with particular and extensive coverage on the compact disc. All aspects of the recording and reproduction processes are explained with separate chapters on such things as compact disc encoding and the use of cross interleave Reed-Solomon error correction code (CIRC). This book is of course essential reading for engineers and students involved in the field but its very low prices makes it ideal for the enthusiast of recorded music who wants to know more about the hidden processes going on in his CD player.

1992/94 248 Pages. 247 x 190.

0-7506-0614-2 £17.95

INTRODUCING DIGITAL AUDIO CD, DAT AND

SAMPLING 2nd Edition. Ian R. Sinclair.

For enthusiasts, technicians and students. Covers CD and DAT, Philips DCC and Sony Mini Disc, the digital techniques involved are explained non-mathematically.

Digital audio involves methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and methods are explained, but the mathematical background and theory are avoided other than to state the end product. This second edition has been updated to include sections on oversampling methods and bitstream techniques. The opportunity has also been taken to add a glossary of technical terms.

1992 168 Pages. 217 x 138. 64 line drawings.

ISBN 1870775 22 8 £7.95

"THE ART OF SOLDERING", R. Brewster.

Absolutely essential reading for anyone who ever picks up a soldering iron. Written from knowledge gained in a lifetime in the field, this is the first book ever solely devoted to this essential and neglected skill for all electronic enthusiasts. Covers everything from the correct choice of soldering iron and solder to the correct procedures to follow with many illustrations and practical exercises.

0-85935-324-3 £3.95

"HOW TO USE OSCILLOSCOPES & OTHER TEST

EQUIPMENT", R.A. Penfold, 112 pages. 178 x 111.

Publ. 1989.

BP267 £3.50

Postage on Single Books is £1.50 except for The Art of Linear Electronics, Digital Audio and Compact Disc Technology and The Towers International Transistor Selector which are £3.50. Two, or more, books are only £4.50, any size, any quantity.



QUALITY
AUDIO KITS

24 hr. SALES LINE
(0691) 652894


ALL PRICES
INCLUDE
UK/EC VAT

HART
HART ELECTRONIC KITS LTD.
6 PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

Data Acquisition for your PC


Easy to use, low cost data acquisition products that allow your PC to be used as a range of useful test and measurement instruments, or as an advanced data logger. Easy installation via a parallel port except the ADC-16 which connects to the serial port. They require no power supply. Take up no expansion slots. Each comes with a comprehensive manual. Software drivers are included for users who wish to write their own software. Software supplied on 3.5" disk.

PicoScope 'Virtual instrument' software.

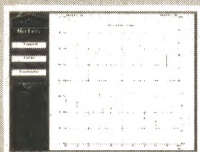

Storage scope with trigger, timebase, rulers and offset. Real time spectrum analysis with min/max frequency and signal averaging. Multiple meters on screen (digital and bargraph). Printer and file handling support.

PicoLog

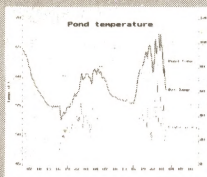

Advanced data logging software package. Collect store, display and print data from one sample per millisecond to one per day. Record average, min/max or scaled values (linear, equation, table look-up). Report types; monitor (with min/max alarms), y-t graphs, x-y graphs, tabulation.

NEW SLA-16 Logic Analyser

Pocket sized 16 channel Logic Analyser



SLA-16 with power supply and cables £219

- Connects to PC serial port, ideal for desktops or notebooks.
- Supplied with easy to use software, power supply and cables.
- High Speed - up to 50MHz sampling.
- Internal and external clock modes.
- 8K Trace Buffer.

NEW ADC-100 Virtual Instrument

Dual Channel 12 bit resolution



- Digital Storage Scope
- Spectrum Analyser
- Frequency Meter
- Chart Recorder
- Data Logger
- Voltmeter

The ADC-100 offers both a high sampling rate (100kHz) and a high resolution. It is ideal as a general purpose test instrument either in the lab or in the field. Flexible input ranges ($\pm 200\text{mV}$ to $\pm 20\text{V}$) allows the unit to connect directly to a wide variety of signals.

ADC-100 with PicoScope £199
with PicoScope & PicoLog £209

ADC-10

1 Channel 8 bit

- Lowest cost
- Up to 22kHz sampling
- 0-5V input range

The ADC-10 gives your computer a single channel of analog input. Simply plug into the parallel port and your ready to go.

ADC-10 with PicoScope £49
PicoScope & PicoLog £59

Carriage UK free, Overseas £6
Oscilloscope Probes (x1, x10) £10
Existing ADC 10/11/12/100 users can add PicoLog for £25

ADC-11

11 Channel 10 bit

- Digital output
- Up to 18kHz sampling
- 0-2.5V input range

The ADC-11 provides 11 channels of analog input in a case slightly larger than a matchbox. It is ideal for portable data logging using a "notebook" computer.

ADC-11 with PicoScope £85
PicoScope & PicoLog £95

ADC-12

1 Channel 12 bit

- High resolution
- Up to 17kHz sampling
- 0-5V input range

The ADC-12 is similar to the ADC-10 but offers an improved 12 bit (1 part in 4096) resolution compared to the ADC-10's 8 bit (1 part in 256).

ADC-12 with PicoScope £85
PicoScope & PicoLog £95



ADC-10 Simply plug into the parallel port and your ready to go.

ADC-16

8 Channel 16 bit+sign

- Highest resolution
- 2Hz sampling - 16bit
- $\pm 2.5\text{V}$ input range

The ADC-16 has the highest resolution of the range, it is capable of detecting signal changes as small as $40\text{ }\mu\text{V}$. Pairs of input channels can be used differentially to reject noise. Connects to serial port.

ADC-16 with PicoLog £115

PICO TECHNOLOGY



Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ

Tel: 01954 - 211716

Fax: 01954 - 211880




Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT

Take the


Quickroute

from
£99.00


to successful PCB &
Schematic Design

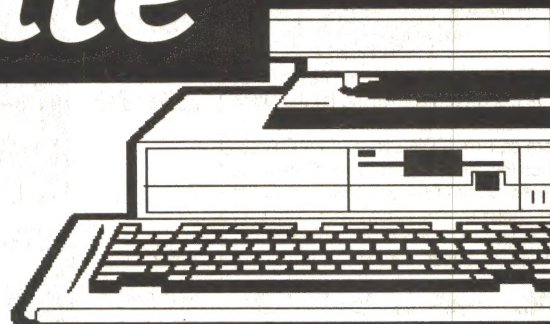

Design PCBs and Schematics quickly

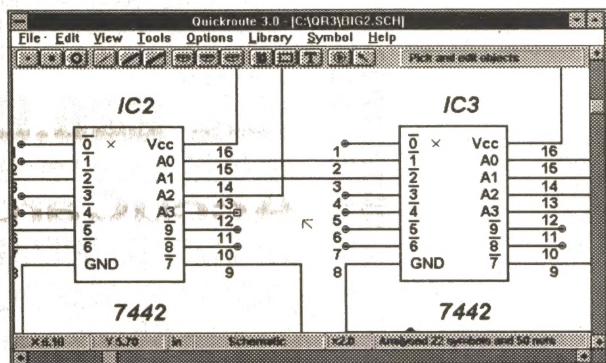

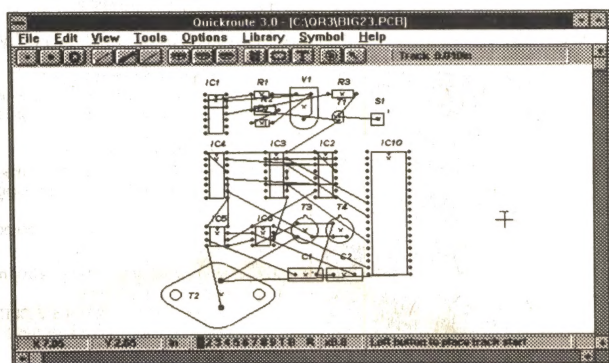
After schematic capture, components can be re-arranged prior to manual or automatic routing.



	Auto Router Max Layers	Schematic Capture	Gerber & NC-Drill	Design Size K nodes
DESIGNER	2 Standard	None	None	10
DESIGNER+	2 Medium	None	Export	20
PRO	8 Fast	Standard	Export	30
PRO+	8 Fast	Advanced	Export/ Import*	40

*PRO+ can import Gerber files

All versions include an auto-router.

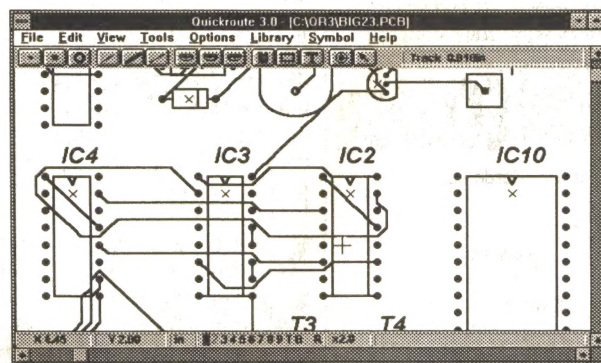

Telephone or FAX POWERware on 061 449 7101

POWERware, 14 Ley Lane,
Marple Bridge, Stockport,
SK6 5DD, UK.

Quickroute 3.0 for Windows 3.1

DESIGNER £99.00 DESIGNER+ £149.00

PRO £199.00 PRO+ £299.00

All prices exclude post & packing, and V.A.T.

DEMO
DISK
Available

**OUT
NOW!**

1995 catalogue - 196 pages of stunning offers. only £2, or free with order



Z5887 Amongst the pile of 'Ties in Tins', we've discovered something for the ladies - pure silk scarves. Identical tin, but the 68cm square 100% silk scarf by Camelia James (by appointment to the Queen, no less) is in a attractive grey-blue with darker blue border. The scarf alone would probably sell for a tenner - our price for this beautiful silk squire and the tin is just

£4.95

MINI FM RADIO



FM1 Just 20mm thick and 45mm dia, this receiver has auto-seek tuning - keep pushing the button till you reach the station of your choice. Uses 3V lithium battery (supplied), and comes with twin earphones.

£7.99

RELAY OFFER

Z3762 Standard BT type relay - our type W831 - except 9V coil. Usually £1.95. Special Bargain Price



£1.00 100+
0.60



**ELECTRONIC
ANTI-DAZZLE
MIRROR**

ECLIPSE

Removes headlight dazzle from behind
Dips in 1/10 second
Sensitivity selector
Battery operated, easily fitted
Complete with accessories

Order Code: Z5693

£7.95



A range of videos of interest to railway enthusiasts, all at the same price - £7.95

(a) Rare footage 1950's, 1960's

Z5878 Vintage Steam Scrapbook Vol 1

Z5879 Vintage Steam Scrapbook Vol 2

(b) Romney Hythe & Dymchurch Railway

Z5880 Vintage Steam Remembered Vol 1

Z5881 Vintage Steam Remembered Vol 2

Z5882 Vintage Steam Remembered Vol 3

(c) Miscellaneous

Z5883 Vintage American Locos

Z5884 GWR


Z5885 The Last British Trains - Blackpool



Remote Control Deal


Left:
Z5876

Right:
Z5879

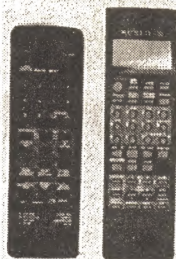

Left:
Z5887

Right:
Z5888

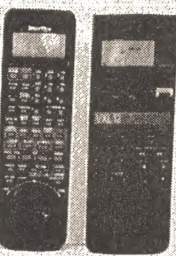

Just purchased a few thousand TV/VCR remote controls - and what a mixture they are. All brand new, they fall into three broad categories - (a) basic; (b) with LCD and (c) the bells and whistles brigade. Unfortunately, most manufacturers' seem reluctant to print their name on these handsets, so we haven't a clue for which machines they are intended. Hopefully, the table below will give some idea. Being realistic, we're aware not many of these will be wanted as replacements in any case, but just for the spare parts, and the low prices reflect this. In order to shift them fairly quickly, we've decided to offer them (wait for it, wait for it) in a PACK (What a surprise). Yes, another amazing GREENWELD offer. Enough buttons to zap the world!

Code	Man'r	Type	Lang	Description	Price
(a) Basic controller with no display - all take 2 x AAA cells					
Z5875		RC07	F	20 buttons	£2.00
Z5876		RC08	E	34 buttons	£2.00
Z5877				35 buttons	£2.00
Z5878		RC44	F	37 buttons	£2.00
(b) Controller with LCD - all take 2 x AA cells					
Z5879	Matsui	VX2700	E	39 buttons	£3.00
Z5880		RCD	E	37 buttons	£3.00
Z5881		RCF	E	38 buttons	£3.00
Z5882		RCK	E	36 buttons	£3.00
Z5883		RCL	E	38 buttons	£3.00
Z5884		RCW	E	24 buttons	£3.00
Z5885	EasyP		E	40 buttons inc. Sat	£4.00
Z5886	Two		E	49 buttons. For twin deck VCR	£5.00
(c) Controllers with LCD and extras					
Z5887	Show View			45 buttons. With jog/shuttle control 2 x AA cells	£8.00
Z5888		VXL12	E	32 buttons. With built in speech chip giving instructions. Also acts as talking clock, giving day and time at the touch of a button. 4 x AA cells	£9.95
Z5889			G	As above	£4.95
Z5890			F	As above	£4.95

E = English; F = French; G = German

SCOPE CLEARANCE!

Few only Hitachi Oscilloscopes to clear! We are discounting these owing to ever increasing prices and decreasing sales

Model	List	Clearance
V212	£399	£350
V223	£599	£450
V522	£745	£575
V525	£999	£750

Phone Nos: **SALES 01703 236363**; Technical 325999; Accounts 231003; Fax (All depts) 236307; FaxOnDemand 236315*

*To obtain latest lists, info etc, just dial 0703 236315 from any fax machine and follow instructions.

All 1 off and pack prices include VAT, qty prices do not. P&P £3 per order (£9.50 next day). Min Credit Card £12; Official Orders welcome from Education - min invoice charge £15. Payment accepted by cheque, PO, cash, book tokens, Access, Visa, Connect. Our stores (over 10,000 sq ft) have enormous stocks. We are open from 8-5.30 Mon-Sat. Come and see us!

GREENWELD

ELECTRONIC
COMPONENTS



27D Park Road Southampton SO15 3UQ

POWER SUPPLY BARGAIN

One of the best power supplies we've seen for the money - this 397 watt switch mode beauty is of the highest quality, made by Delta Electronics Inc. Removed from equipment, but in excellent condition (less than a year old!) the unit is totally enclosed in a steel case 340x152x152mm. It has an IEC mains inlet with suppressor fitted and on/off mains rocker switch, and all outputs are on leads with power connectors.

Now for the spec:

Inputs: 100-120V @ 10A

or 200-240V @ 6A,

switchable

on front panel.


Outputs:

+5V @ 40A

+12V @ 15A

-5V @ 1A

-12V @ 1A

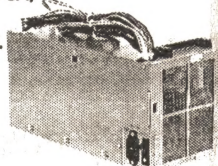


A 12V DC 120x120mm fan is fitted at the rear of the case. Current distributor price of the unit of this ilk would be around £400!

OUR PRICE £29.95

SAVE 92%! Order Code: Z9157

AccuCard™ UNINTERRUPTIBLE POWER SUPPLY

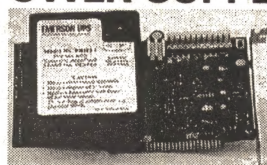

For all IBM and 100% compatible PCs up to 386

* Low cost alternative to expensive bulky external PSU

* Occupies only 6k of memory

* Uses only one half card slot

* Provides DC power to all internal system components

* On board logic and memory chips

* Automatic self-diagnostics run on the board, battery and software every time system is booted up

* Easy USER installable directions

* Protects against DC power supply failure

* Protects against accidental unplugging or switching off

* Supplied complete with cable and connectors, and software on 3.5" disk

Please note this card will not support disk doubling or space saving software

This essential piece of kit has a current

list price of £213.85 - we have


a few hundred only at just

£69.95

Order Code Z9252

MINI EXTN SPEAKER

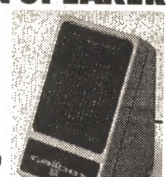Z5740 Plastic housing 100x75x73mm with 1.5m lead fitted with 3.5mm plug. Ideal for plugging into ear-piece of cheap radios for a massive improvement in sound quality, and great, too, for multimedia computers. Individually boxed. Free 3.5mm stereo plug with each pair purchase!



PRICE PER PR

£2.95

100+ prs (no free plug) 1.20

BTEC
Certificated



TUTOR
Supported

DISTANCE LEARNING COURSES

Update and reskill at home or in your workplace training centre with these highly practical industrially approved short courses. There is no travelling so commence at any time on

Electronic Testing & Fault Diagnosis
Analogue Electronics
Digital Electronics
Fibre/Optoelectronics
Programmable Logic Controllers

Courses are supplied with NCT training workbooks, audio cassette lecturettes, PCB's, instruments, tools, components and leads as necessary for each course. Continuous tutor support and **BTEC** certification is available as an option from NCT. Individual course certificates can be credited towards a **BTEC** Continuing Education Certificate which is at **NVQ level 4**. For the latest information on courses and your options write or telephone:

National College of Technology, NCT Ltd., PO Box 11
Wendover, Bucks. Tel: (0296) 624270



TRANSMITTERS

AT LAST. A comprehensive, easy to follow guide to building short range transmitters and surveillance devices. Packed with useful information and circuits.

★ Only **£3.95** inc p&p.

(Some of the circuits included cannot be used legally in the UK)

KITS

All kits come with pre-drilled PCBs and high spec. components.

MICRO FM TRANSMITTER (a). 1 mile range, 80-100MHz preset inc. mic., very small (2"3cm) **£6.95**

MICRO FM TRANSMITTER (b). Variable mic. sens., tunable 90-110MHz, 1 mile range **£7.95**

FM TRACKER. Transmits an audio tone for direction finding, tracking etc. 80-110MHz **£8.50**

FM RECEIVER (a). Tiny high quality FM radio. Will drive headphones direct (not inc) **£10.90**

FM RECEIVER (b). As (a) but with 3 watt audio output and tuning LED **£12.60**

CRYSTAL RADIO. Includes tuner, earphone, ferrite aerial, etc. **£6.90**

AM RADIO. Single chip radio for headphones (not inc.) **£8.90**

AUDIO POWER AMPS **3 WATT** low cost for intercoms etc **£4.95**
15 WATT General purpose upgrade **£8.95**

40 WATT High quality, HD 0-003%, switch on mute ideal for compact disc **£15.50**

150 WATT Rugged and powerful MOSFET design. PA/sound systems **£22.95**

PREAMPS ETC

GENERAL PURPOSE PREAMP. Variable gain 9-25V 40mV max in **£4.00**

ULTRA LOW NOISE. For high quality mixers, mics etc 9-25V **£4.50**

SMALL SIGNAL. Sensitive FET preamp for piezo transducers **£3.90**

ACTIVE TONE. 12dB c/b bass and treble with variable gain **£8.95**

7 BAND EQ. 150Hz-18KHz for EQ units and tone control, includes on-board preamp and pots. Variable gain **£12.95**


NOISE GATE. Dynamic noise reduction system. Variable input and cut off level. Will accept instruments, tape decks etc **£15.95**

MUSIC KITS. Full range of on-board units for guitars and other instruments. Tone boosters, active circuitry, transducers. Send for list.

Prices include P&P. **Mail Order Only.** Make cheques and postal orders payable to:



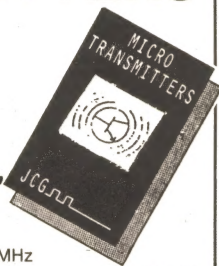PO Box HP79, Woodhouse Street, Leeds LS6 3XN



SYSTEM 200 DEVICE PROGRAMMER

SYSTEM: Programs 24, 28, 32 pin EPROMS, EE-PROMS, FLASH and Emulators as standard, quickly, reliably and at low cost.

Expandable to cover virtually any programmable part including serial E², PALS, GALS, EPLD's and microcontrollers from all manufacturers.

DESIGN: Not a plug in card but connects to the PC serial or parallel port; it comes complete with powerful yet easy to control software, cable and manual.

SUPPORT: UK design, manufacture and support. Same day dispatch, 12 month warranty. 10 day money back guarantee.



**ASK FOR FREE
INFORMATION
PACK**



MQP ELECTRONICS Ltd.
Unit 2, Park Road Centre,
Malmesbury, Wiltshire, SN16 0BX UK
TEL. 0666 825146 FAX. 0666 825141

GERMANY 089/4602071
NORWAY 0702-17890
ITALY 02 92 10 3554
FRANCE (1)69.41.28.01
IRELAND 1-2800395
SWEDEN 08-590-32185
Also from **ELECTROSPEED UK**

At last, a fully functional upgradeable PCB CAD system to suit any budget. Substantial trade-in discounts are available against other "professional" PCB design packages ...

... call now for details.

Board Capture

Schematic Capture Design Tool

£395

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

BoardMaker

BoardMaker1 - Entry level


£95

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking


BoardMaker2 - Advanced level

£295

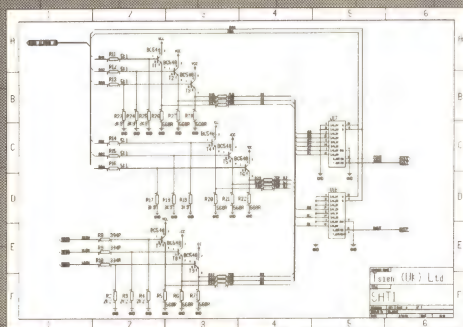- All the features of BoardMaker1 +
- Full netlist support - BoardCapture, OrCad, Schema, Tango, CadStar and others
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC



NEW

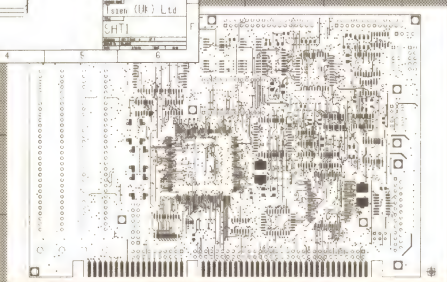

BoardRouter

Gridless re-entrant autorouter

£200

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom white routing

Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)

Call, write or fax for more information

or a full evaluation kit

Tsien (UK) Limited

Aylesby House


Wenny Road, Chatteris

Cambridge

PE16 6UT

Tel (0354) 695959

Fax (0354) 695957

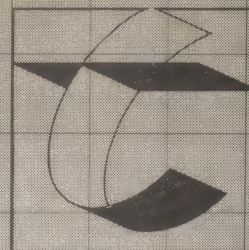

tsien



SHOP OPEN 9-5 MON-FRI. CLOSED SAT --- OFFICIAL ORDERS WELCOME

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with μ C control of all timing functions and advanced pulse separation techniques.

- New circuit design 1994
- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847.....£63.95

DIGITAL LCD THERMOSTAT

A versatile thermostat using a thermistor probe and having an I.C.D. display. MIN/MAX memories, -10 to 110 degrees celsius, or can be set to read in Fahrenheit. Individually settable upper and lower switching temperatures allow close control, or alternatively allow a wide 'dead band' to be set which can result in substantial energy savings when used with domestic hot water systems. Ideal for greenhouse ventilation, or heating control, aquaria, home brewing, etc. Mains powered, 10A SPCO relay output. Punched and printed case.

KIT 841.....£29.95

PORTABLE ULTRASONIC PEST SCARER

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

KIT 842.....£22.56

DIGITAL CAPACITANCE METER

A really professional looking project. Kit is supplied with a punched and printed front panel, case, p.c.b. and all components. Quartz controlled accuracy of 1%. Large clear 5 digit display and high speed operation. Ideal for beginners - as the μ F, nF and pF ranges give clear unambiguous read out of marked and unmarked capacitors from a few pF up to thousands of μ F.

KIT 493.....£39.95

ACOUSTIC PROBE

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches, and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers, and nosey parkers.

KIT 740.....£19.98



1000V & 500V INSULATION TESTER


Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms. Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848.....£32.95

MOSFET MkII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A

Based on our MkI design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.

KIT 845.....£64.95

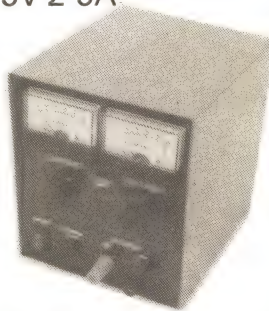

ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS
- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT Ref. 812.....£14.81

'COMSTEP' P.C. COMPUTER STEPPING MOTOR INTERFACE

An exciting project supplied with two 200 step motors, interface board, and easy to use P.C. software. Allows independent control of both motors - speed, direction, number of steps, and half/full step mode. Connects to computer parallel port. Requires 12V 1A D.C. supply and printer lead.

KIT 846 (with 2 motors)£62.99 (Printer lead £5.00)

IONISER

A highly efficient mains powered Negative Ion Generator that clears the air by neutralising excess positive ions. Many claimed health benefits due to the ioniser removing dust and pollen from the air and clearing smoke particles. Costs virtually nothing to run and is completely safe in operation. Uses five point emitters.

KIT 707.....£17.75

BAT DETECTOR

An excellent circuit which reduces ultrasound frequencies between 20 and 100 kHz to the normal (human) audible range. Operating rather like a radio receiver the circuit allows the listener to tune-in to the ultrasonic frequencies of interest. Listening to Bats is fascinating, and it is possible to identify various different types using this project. Other uses have been found in industry for vibration monitoring etc.

KIT 814.....£21.44

SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube + instructions for message loading.

KIT 849.....£16.99

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790.....£28.51

MOSFET 25V 2.5A POWER SUPPLY

High performance design has made this one of our classic kits. Two panel meters indicate Volts and Amps. Variable from 0-25 Volts and current limit control from 0-2.5A. Rugged power MOSFET output stage. Toroidal mains transformer.

KIT 769.....£56.82

INSULATION TESTER

A reliable and neat electronic tester which checks insulation resistance of wiring and appliances etc., at 500 Volts. The unit is battery powered, simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. A very popular college project.

KIT 444.....£22.37

DIGITAL COMBINATION LOCK

Digital lock with 12 key keypad. Entering a four digit code operates a 250V 16A relay. A special anti-tamper circuit permits the relay board to be mounted remotely. Ideal car immobiliser, operates from 12V. Drilled case, brushed aluminium keypad.

KIT 840.....£19.86

E.E. TREASURE HUNTER P.I. METAL DETECTOR MKI

Magenta's highly developed & acclaimed design. Quartz crystal controlled circuit MOSFET coil drive. D.C. coupled amplification. Full kit includes PCB, handle, case & search coil.

- KIT INC. HEADPHONES
- EFFICIENT CMOS DESIGN
- POWERFUL COIL DRIVE



- DETECTS FERROUS AND NON-FERROUS METAL - GOLD, SILVER, COPPER ETC.
- 190mm SEARCH COIL
- NO 'GROUND EFFECT'

KIT 815.....£45.95

HAMEG HM303 30 MHz DUAL TRACE OSCILLOSCOPE & COMPONENT CHECKER

Western Europe's best selling oscilloscope - now improved. It now features 30MHz bandwidth, triggering to 100MHz and 2mV/div sensitivity.

Sharp bright display on 8 x 10cm screen with internal graticule. Special component tester built in - allows capacitors, resistors, transistors, diode, and many other components to be checked at a glance.

As with its predecessor, the QUALITY OF THIS INSTRUMENT IS OUTSTANDING. It is supported with a two year warranty covering parts and labour. If you are buying an oscilloscope, this is the one. It costs a fraction more than some others, but it is far far superior. Supplied with test probes, mains lead, and manual.

£392.00 + £68.60 VAT Includes FREE Next-day delivery (Cheques must be cleared)

EDUCATIONAL BOOKS & PACKS

ADVENTURES WITH ELECTRONICS

The classic book by Tom Duncan used throughout schools. Very well illustrated, ideal first book for age 10 on. No soldering. Uses an S.DEC breadboard.

Book & Components £28.95, Book only £7.25

FUN WITH ELECTRONICS

An Osborne book, wonderfully illustrated in colour. Component pack allows 6 projects to be built and kept. Soldering is necessary. Age 12 on, or younger with adult help. Book & Components £20.88, Book only £2.95

30 SOLDERLESS BREADBOARD PROJECTS


A more advanced book to follow the others. No soldering. Circuits cover a wide range of interests.

Book & Components £30.69, Book only £2.95

DC MOTOR/GEARBOXES

Ideal for robots, buggies, and many other mechanical projects. Min. plastic gearbox with 1.5-4.5V DC motor. 6 ratios can be set up.

Small type MGS.....£4.77

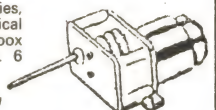

STEPPING MOTORS


For computer control via standard 4 pole unipolar drivers.

MD38 - miniature 48 steps per rev.....£9.15

MD35 1/4 - standard 48 steps per rev.....£12.99

MAGENTA

Teach-In '93

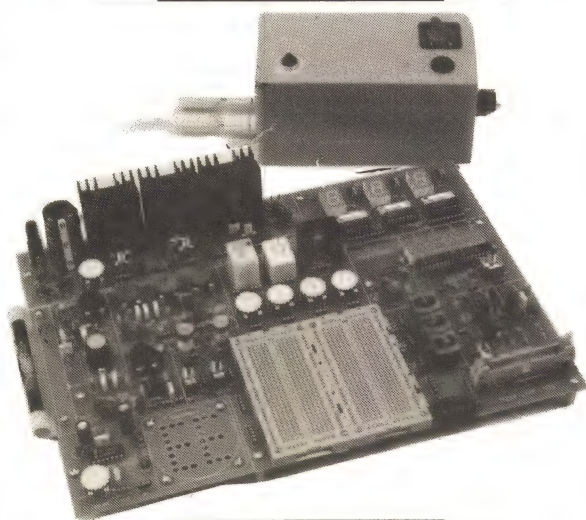

MINI LAB KITS

ALL COMPONENTS TO ASSEMBLE
THE EPE MINI LAB.

Follow this exciting educational series as
featured in EPE through 1993.

Full set of reprints£4.60

Components are supplied in packs to keep
ordering simple.

A full MINI LAB consists of ML1, ML3, ML5,
ML6. These are available at a special
combined price of.....£114.99
or less the p.c.b.

ML2, ML3, ML5, ML6 at.....£104.99

The transformer unit ML4 is also needed....£21.45

KIT ML1 MINI-LAB P.C.B. + all components
inclusive of breadboard for
Part 1 (Nov. '92).....£49.95

KIT ML2 All Components for Part 1 less
p.c.b.....£39.95

KIT ML3 Power Supply components.....£19.95

KIT ML4 Transformer unit.....£21.45

KIT ML5 L.E.D. Voltmeter, signal
generator, audio amplifier and
555 timer.....£33.95

KIT ML6 Logic probe, display, radio
tuner.....£17.95


(Note: batteries not included)

All prices include V.A.T. Add £3.00 p&p.

Tel: 0283 565435 Fax: 0283 546932

MAGENTA

Teach-In '93

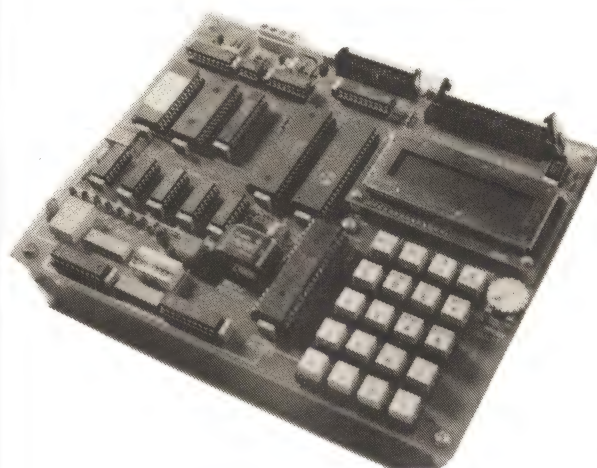

MICRO LAB KITS

ALL COMPONENTS TO ASSEMBLE
THE EPE MICRO LAB.

A 6502 Microprocessor trainer with many
features. Accompanied by an excellent set
of tutorial articles and a manual.

Repair/fault-finding help assured when you
buy your kit from us.

Full MICRO LAB kit including PC Board,
EPROM, PAL, & Manual.

MIC 1£149.95

(Also available less PCB etc. if required).

Full set of reprints.....£3.00

BUILT & TESTED

Full MICRO LAB AS MIC1 (above)

MIC1B.....£179.95

Professionally assembled, inspected,
cleaned and tested. Full back-up service,
spares, etc available.

All prices include V.A.T. Add £3.00 p&p.

Tel: 0283 565435 Fax: 0283 546932

ESR ELECTRONIC COMPONENTS

Station Road, Cullercoats,

Tyne & Wear NE30 4

Tel. 091 251 436

Fax. 091 252 2296

74LS00-Series			4000 Series			TRANSISTORS			LINEAR ICs			EPROMS & RAMS			SOLDERING IRONS			RF CONNECTORS		
74LS00	£0.22	4000	£0.17	2N1613	£0.31	BC181E	£0.33	BD534	£0.47	CA311E	£0.28	2716	£4.46	£4.66	Antex Soldering Irons	£8.19	BNC Solder Plug 50R	£0.93		
74LS01	£0.14	4001	£0.20	2N1711	£0.26	BC204C	£0.72	BD535	£0.50	CA324	£0.35	2732	£4.64	£4.84	M 12 Watt	£8.19	BNC Solder Plug 75R	£0.96		
74LS02	£0.25	4002	£0.17	2N1893	£0.29	BC206B	£0.72	BD536	£0.65	CA355	£0.25	27128-20	£4.68	£4.88	C15 Watt	£8.18	BNC Crimp Plug 50R	£0.68		
74LS03	£0.14	4006	£0.10	2N2218A	£0.20	BC207C	£0.72	BD537	£0.65	CA341CE	£0.25	27128-20	£4.68	£4.88	G18 Watt	£8.41	BNC Crimp Plug 75R	£0.68		
74LS04	£0.14	4007	£0.18	2N2219A	£0.21	BC208	£0.72	BD538	£0.65	CA347CE	£0.25	2764-25	£3.00	£3.20	CS17 Watt	£8.31	BNC Solder Skt	£1.08		
74LS05	£0.14	4008	£0.31	2N2222A	£0.18	BC209A	£0.72	BD550	£0.53	CA3046	£0.37	2764-25	£3.16	£3.36	XS 25Watt	£8.41	BNC Chassis Skt	£0.80		
74LS08	£0.23	4009	£0.19	2N2646	£0.80	BC212	£0.08	BD707	£0.42	CA3080	£0.72	27128-20	£4.22	£4.42	S14 Stand	£2.97	PL259 5.2mm	£0.62		
74LS09	£0.14	4010	£0.23	2N2904A	£0.25	BC212L	£0.08	BD807	£0.80	CA3130	£0.98	27526-20	£4.99	£5.19	35Watt Gas Iron	£15.26	PL259 11mm	£0.68		
74LS10	£0.14	4011	£0.26	2N2905A	£0.23	BC212BL	£0.08	BDX32	£1.78	CA3130E	£0.98	27526-20	£4.21	£4.41	Low Cost 15 Watt Iron	£3.90	RDR UHF socket	£0.68		
74LS107	£0.23	4012	£0.27	2N2907	£0.20	BC213	£0.08	BDX33	£0.45	CA3140	£0.31	27526-20	£4.21	£4.41	Desolder Pump	£3.00	SCRH OHF socket	£0.68		
74LS107	£0.23	4013	£0.24	2N2926	£0.16	BC213CL	£0.08	BDX34C	£0.50	CA3240	£0.41	27526-20	£4.21	£4.41	Antistatic Pump	£4.25	F Plug RG58	£0.30		
74LS11	£0.17	4014	£0.30	2N3053	£0.27	BC214	£0.08	BDX53C	£0.47	ICL7621	£1.70	27526-20	£4.21	£4.41	225WG 0.5kg Solder	£7.40	F Plug RG6	£0.27		
74LS112	£0.24	4015	£0.31	2N3054	£0.90	BC214L	£0.08	BDX54C	£0.50	ICM7555	£0.43	27526-20	£4.21	£4.41	18SWG 0.5kg Solder	£6.60	N Plug RG8	£1.60		
74LS112	£0.24	4016	£0.18	2N3055	£0.62	BC237B	£0.09	BF180	£0.31	ICM7556	£0.43	27526-20	£4.21	£4.41	1mm 3yds Solder	£0.62	N Socket RG8	£1.40		
74LS114	£0.21	4017	£0.35	2N3440	£0.50	BC238C	£0.09	BF182	£0.31	ICM7557	£0.43	27526-20	£4.21	£4.41	Desolder Braid	£0.87	BNC Crimp Pliers	£17.44		
74LS114	£0.21	4018	£0.27	2N3441	£0.50	BC239C	£0.09	BF183	£0.31	ICM7558	£0.43	27526-20	£4.21	£4.41						
74LS122	£0.31	4019	£0.49	2N3703	£0.10	BC251	£0.13	BF194	£0.19	LF351N	£0.43	27526-20	£4.21	£4.41						
74LS122	£0.31	4020	£0.31	2N3704	£0.10	BC252	£0.13	BF195	£0.19	LF353	£0.43	27526-20	£4.21	£4.41						
74LS125	£0.21	4021	£0.31	2N3705	£0.10	BC261B	£0.24	BF244	£0.35	LM358N	£0.27	27526-20	£4.21	£4.41						
74LS126	£0.21	4022	£0.32	2N3706	£0.24	BC262B	£0.24	BF257	£0.33	LM377	£0.27	27526-20	£4.21	£4.41						
74LS13	£0.14	4023	£0.16	2N3771	£1.44	BC267B	£0.30	BF259	£0.33	LM380N	£1.12	27526-20	£4.21	£4.41	Photo Resist Aerosol Spray	£4.47	Transfer Eraser (Alfac)	£0.55		
74LS13	£0.14	4024	£0.21	2N3772	£1.44	BC303	£0.10	BF361	£0.30	LM381	£0.27	27526-20	£4.21	£4.41	Developing/Etching Tray	£1.35	Opaque Drafting Film (A4)	£0.46/shet		
74LS132	£0.31	4025	£0.15	2N3773	£1.79	BC308	£0.10	BF365	£0.38	LM386	£0.48	27526-20	£4.21	£4.41	Plastic Tweezers	£0.55	Tin Plating Powder 90g	£12.93		
74LS133	£0.36	4026	£0.59	2N3819	£0.40	BC327	£0.10	BF423	£0.13	LM387	£1.60	27526-20	£4.21	£4.41	Transfer Sponular (Alfac)	£0.70	PCB Polishing Block	£1.84		
74LS136	£0.16	4027	£0.18	2N3820	£0.66	BC328	£0.10	BF451	£0.19	LM392N	£0.79	27526-20	£4.21	£4.41	Clear Drafting Film (A4 size)	£0.44/shet	Small Knife + spare blade	£0.39		
74LS136	£0.16	4028	£0.22	2N3904	£0.10	BC337	£0.10	BF459	£0.29	LM393N	£0.79	27526-20	£4.21	£4.41	Ferric Chloride (0.5kg)	£2.45	Allac Transfers - full range in stock			
74LS136	£0.16	4029	£0.40	2N3905	£0.10	BC338	£0.10	BF469	£0.36	LM748CN	£0.31	27526-20	£4.21	£4.41	UV Exposure Unit 2x8W	£76.31	How to Make PCBs			
74LS14	£0.25	4030	£0.17	2N3906	£0.10	BC340	£0.10	BF479	£0.29	LM1458	£1.56	27526-20	£4.21	£4.41	Etch Resist Pen (High Q)	£0.78	(Book)	£2.50 - No VAT		
74LS147	£1.26	4033	£0.56	2N5296	£0.57	BC461	£0.40	BFX85	£0.32	LM3914	£2.70	27526-20	£4.21	£4.41						
74LS148	£0.70	4034	£1.24	2N5321	£0.57	BC463	£0.29	BFY50	£0.29	LM3915	£2.70	27526-20	£4.21	£4.41						
74LS15	£0.14	4035	£0.31	2N6107	£0.60	BC478	£0.32	BFY52	£0.26	MC3340	£1.60	27526-20	£4.21	£4.41	64mm x 25mm	£0.27	81mm x 60mm	£3.30		
74LS151	£0.25	4040	£0.29	2N6126	£0.30	BC479	£0.32	BFY51	£0.28	MC3458	£1.60	27526-20	£4.21	£4.41	64mm x 95mm	£0.27	175mm x 42mm	£1.74		
74LS153	£0.31	4041	£0.27	2N6127	£0.30	BC480	£0.32	BFY52	£0.28	MC3458	£1.60	27526-20	£4.21	£4.41	95mm x 127mm	£1.50	175mm x 67mm	£5.56		
74LS154	£0.70	4041	£0.31	2N6128	£0.28	BC516	£0.22	BS170	£0.21	NE556N	£0.39	27526-20	£4.21	£4.41	95mm x 143mm	£4.80	203mm x 75mm*	£7.36		
74LS155	£0.25	4042	£0.28	2N6129	£0.45	BC517	£0.20	BSW66	£1.35	NE567N	£0.36	27526-20	£4.21	£4.41	119mm x 454mm	£6.20	* Supplied on mounting plate with terminal posts			
74LS156	£0.36	4044	£0.35	2N6130	£0.37	BC527	£0.20	BU126	£1.70	NE5532	£0.80	27526-20	£4.21	£4.41						
74LS157	£0.22	4046	£0.35	2N6131	£0.34	BC528	£0.20	BU205	£1.82	NE5534	£0.80	27526-20	£4.21	£4.41	6mm Thick					
74LS158	£0.21	4047	£0.25	2N6132	£1.67	BC537	£0.27	BU208A	£1.24	TBA120S	£0.90	27526-20	£4.21	£4.41	PHOTO RESIST GASKET FIBRE					
74LS160	£0.48	4048	£0.28	2N6133	£0.92	BC546C	£0.09	BU326A	£1.51	TBA810S	£0.69	27526-20	£4.21	£4.41	Single Sided	£1.58	Double Sided	£1.20		
74LS161	£0.48	4049	£0.22	2N6134	£0.16	BC548C	£0.08	BU501	£1.54	TBA820M	£0.69	27526-20	£4.21	£4.41	6x12"	£6.92	£5.15	£4.46		
74LS162	£0.44	4050	£0.43	2N6135	£0.15	BC549C	£0.10	BU508A	£1.76	DA2002	£1.04	27526-20	£4.21	£4.41	9x12"	£6.93	£7.77	£5.19		
74LS163	£0.32	4051	£0.43	2N6136	£0.15	BC550C	£0.10	BU526	£2.24	DA2030	£1.04	27526-20	£4.21	£4.41	12x12"	£8.07	£9.81	£8.30		
74LS164	£0.26	4052	£0.40	2N6137	£0.13	BC550C	£0.10	BU806	£1.36	LO61	£0.35	27526-20	£4.21	£4.41	160x100mm	£1.94	£2.20	£2.00		
74LS165	£0.48	4053	£0.40	2N6138	£0.16	BC556C	£0.08	BU848	£0.78	LO62	£0.35	27526-20	£4.21	£4.41	203x114mm	£2.52	£2.78	£2.78		
74LS170	£0.30	4054	£0.56	2N6139	£0.17	BC558C	£0.08	IRF540	£1.80	LO64	£0.72	27526-20	£4.21	£4.41	220x100mm	£2.58	£2.88	£2.88		
74LS173	£0.24	4055	£0.34	2N6140	£0.17	BC559C	£0.08	IRF740	£1.63	LO71CP	£0.68	27526-20	£4.21	£4.41	233x220mm	£5.67	£6.41	£6.41		
74LS175	£0.24	4060	£0.48	2N6141	£0.41	BC560B	£0.09	LM1101S	£2.11	LO72CP	£0.68	27526-20	£4.21	£4.41	233x160mm	£3.99	£4.41	£4.41		
74LS190	£0.25	4066	£0.24	2N6142	£0.11	BC637	£0.21	LMJ301	£1.80	LO82CP	£0.64	27526-20	£4.21	£4.41						
74LS191	£0.24	4067	£1.96	2N6143	£0.18	BC638	£0.21	LMJ301	£1.80	LO82CP	£0.64	27526-20	£4.21	£4.41						
74LS192	£0.42	4068	£0.16	2N6144	£0.32	BC640	£0.21	LMJ340	£0.40	LO84CN	£0.46	27526-20	£4.21	£4.41						
74LS193	£0.24	4069	£0.20	2N6145	£0.36	BC641	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS195	£0.24	4070	£0.17	2N6146	£0.36	BC642	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS196	£0.24	4071	£0.22	2N6147	£0.25	BC643	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS197	£0.24	4072	£0.17	2N6148	£0.25	BC644	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS20	£0.16	4073	£0.17	2N6149	£0.25	BC645	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS21	£0.14	4074	£0.17	2N6150	£0.25	BC646	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS22	£0.14	4075	£0.17	2N6151	£0.25	BC647	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS221	£0.40	4077	£0.17	2N6152	£0.25	BC648	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS240	£0.32	4078	£0.20	2N6153	£0.25	BC649	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS241	£0.32	4079	£0.20	2N6154	£0.25	BC650	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS242	£0.32	4082	£0.21	2N6155	£0.25	BC651	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS243	£0.30	4085	£0.28	2N6156	£0.25	BC652	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS244	£0.32	4086	£0.26	2N6157	£0.25	BC653	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS245	£0.36	4089	£0.55	2N6158	£0.25	BC654	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS247	£0.32	4093	£0.18	2N6159	£0.25	BC655	£0.21	LMJ350	£0.42	UA733	£0.64	27526-20	£4.21	£4.41						
74LS251	£0.24	4094	£0.31	2N6160	£0.25	BC656	£0.21	LMJ350	£0.42											

CALL IN – OPEN: MON-FRI 8.30-5.00 SAT 10.00-5.00

EVERYDAY WITH PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

VOL. 23 No. 12 DECEMBER '94

Editorial Offices:

EVERYDAY with PRACTICAL ELECTRONICS EDITORIAL,
ALLEN HOUSE, EAST BOROUGH, WIMBORNE
DORSET BH21 1PF

Phone: Wimborne (01202) 881749

Fax: (01202) 841692, DX: Wimborne 45314.

See notes on **Readers' Enquiries** below – we regret that lengthy technical enquiries cannot be answered over the telephone. Due to the cost we cannot reply to queries by Fax.

Advertisement Offices:

EVERYDAY with PRACTICAL ELECTRONICS
ADVERTISEMENTS,

HOLLAND WOOD HOUSE, CHURCH LANE,

GREAT HOLLAND, ESSEX CO13 0JS.

Phone/Fax: (01255) 850596

STANDARDS

So many of us have been caught out when various standards fight it out in the market place. It happened with VHS and Betamax and I, for one, have an old Betamax recorder that still works well sitting in my loft. It is about to happen again with Digital Compact Cassette and Minidisc and it looks as though PCs are now winning over Apple Macs.

In *Fox Report* this month Barry Fox is fairly forthright on the possible imminent death of the Apple Mac. While it still reigns supreme in the publishing world (although all of our typesetting is done on PCs) it does appear to be on its way out elsewhere. Our recent free gift of *Electronics Workbench* software resulted in a couple of requests from colleges for a free Apple Mac disc – not available I'm afraid, although the full package is available in a Mac version.

On further investigation it appears that some colleges have equipped themselves totally with Apple Mac equipment – when I mentioned this to others in education and educational software suppliers the reaction was “are they in the real world?” Unfortunately it is a fact of life that out in the business world the PC is the *de facto* standard and while I can see that in the past Macs have been easier to use that does not help students when they need to work for a living.

GET REAL

“Dodo Apple”, as Barry puts it, may not become a reality, only time will tell, but students must get to grips with the realities of DOS and Windows and possibly quite soon Chicago on a PC. It is time for our educational system to come to terms with educating students for the real world, particularly in the technological subjects, using the tools they will have to use in industry. Fortunately this is already happening in many areas but in some colleges it appears that the buying decisions are being made on ease of use in the classroom, rather than on criteria which will affect the ability of the student to function in the real world.

Mike Kenward

SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £24. Overseas: £30 (£47.50 air-mail). Cheques or bank drafts (in £ sterling only) payable to Everyday with Practical Electronics and sent to EPE Subscriptions Dept., Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749. **Subscriptions start with the next available issue.** We accept Access (MasterCard) or Visa payments, minimum credit card order £5.

BACK ISSUES

Certain back issues of EVERYDAY ELECTRONICS, PRACTICAL ELECTRONICS and EVERYDAY with PRACTICAL ELECTRONICS (from Nov '92 onwards) are available price £2.30 (£3 overseas surface mail) inclusive of postage and packing per copy – **£ sterling only please.** Visa and Access (MasterCard) accepted, minimum credit card order £5. Enquiries with remittance, made payable to Everyday with Practical Electronics, should be sent to Post Sales Department, Everyday with Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF Tel: 01202 881749. In the event of non-availability one article can be photostatted for the same price. *Normally sent within seven days but please allow 28 days for delivery.* We have sold out of Jan, Feb, Mar, Apr, May, June, Oct, & Dec 88, Mar, May & Nov 89, Mar 90, April, Aug & Sept 91 Everyday Electronics, and can only supply back issues from Jan 92 to Aug 92 (excluding Mar 92) of Practical Electronics. Dec 92, Jan, Feb and March 93 Everyday with Practical Electronics are also unavailable.

BINDERS

New style binders to hold one volume (12 issues) are now available from the above address for £5.95 plus £3.50 post and packing (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). *Normally sent within seven days but please allow 28 days for delivery.*

Payment in £ sterling only please. Visa and Access (MasterCard) accepted, minimum credit card order £5. Send or phone your card number and card expiry date with your name and address etc.

Editor: MIKE KENWARD

Secretary: PAM BROWN

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Editorial: Wimborne (01202) 881749

Advertisement Manager:

PETER J. MEW, Frinton (01255) 850596

Advertisement Copy Controller:

DEREK NEW, Wimborne (01202) 882299

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope** or a **self addressed envelope and international reply coupons**. Due to the cost we cannot reply to queries by Fax.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that **we cannot provide data or answer queries on projects that are more than five years old.**

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY with PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; overseas readers should check local laws.



SPACEWRITER WAND

by MARK STUART

Sky writing with a Santalight!

THIS project follows the current vogue of optical effects and illusions such as the 3-D "Magic Eye" type currently featured in books and magazines worldwide. It uses the well known effect of "persistence of vision" to allow a single row of l.e.d.s to write words in the air. The effect is not difficult to view. With practised movement of a "wand" containing a row of seven l.e.d.s, an easily readable display is produced - especially in a darkened room.

PRINCIPLE

As the display relies on "persistence of vision" for its effect, if a bright light is moved quickly across the field of vision, a single continuous streak is seen. A row of seven bright l.e.d.s would produce seven parallel streaks. To write a message, the l.e.d.s are switched on and off rapidly during their travel so that the streaks become dashes. Timing the switching of each l.e.d. correctly allows dashes of different lengths and positions to be produced forming letters.

REALISATION

A microcontroller is ideal for this kind of job. A program containing all the necessary time delays for the pulses is relatively easy to produce, and the l.e.d.s can be driven directly from the microcontroller's output pins.

As the movement of the wand is by hand, and the l.e.d.s are switched at a fixed rate, the message may be compressed or stretched depending on the speed of movement. Ideally, the message should start and finish in the same position, so that repeated waves of the wand produce identical displays. In practice this is impossible, and so the display is arranged to appear as a "one shot" single event each time the wand is moved. To detect the movement of the wand, a mercury tilt switch is used. As soon as motion begins, the tilt switch becomes a short circuit and starts the display sequence.

An input pin on the microcontroller reads the tilt switch.

A second pin provides a serial input facility to allow user defined messages to be entered into memory.

The wand is tubular, being made from a short length of plastic electrical conduit. This is convenient as it is an almost ideal housing for the batteries, but construction is more complicated than just using a plastic box. An on/off switch is not required as the circuit drain is negligible provided the wand is stored with the tilt switch in the open circuit condition.

Other possible arrangements for the display suggest themselves, especially those which include some form of mechanical movement such as a turntable, pendulum, or rotating mirror, combined with a reed switch and magnet to produce a reliable and repeatable start position. The circuit is adaptable to all of these applications, and the tilt switch can be replaced by any appropriate type of switching device.

CIRCUIT DETAILS

The full circuit diagram for the Spacewriter Wand is shown in Fig. 1. As with a lot of circuits using a microcontroller there are very few components. The l.e.d.s are driven directly from the

output of microcontroller IC1 and share a single low value limiting resistor R3. This is mainly to protect IC1 from overcurrent in the event of a fault. Special low current l.e.d.s are used. These are very efficient at current levels right down to 2mA and are bright.

The brightness is limited mainly by the supply voltage at 3V. At 6V the brightness is much higher, but the length of the wand is increased by the extra batteries and may be too long.

IC1 is a CMOS microcontroller which operates at very low current levels. In this application, the current is reduced to a minimum by using a 40kHz clock fre-

quency instead of the normal 4MHz. This is possible because the amount of processing power needed is very small. Even at 40kHz there is plenty of time for the microcontroller to do its job.

Resistor R2, capacitors C1 and C2, and crystal X1 provide the clock frequency determining components. The oscillator circuitry is contained within IC1.

A single input pin (pin 6) is required for the tilt switch, S1. The input has a built in pull-up resistor so that the pin is normally held at logic 1 level. Closing the tilt switch pulls down the pin to logic 0 and starts the display sequence.

Two other input pins are used. Pin 18 allows data to be sent to the microcontroller from a computer serial (RS232) output. This allows a message to be loaded into RAM and displayed automatically. The message, once loaded, is maintained as long as the batteries are not removed. Resistor R1 and diode D1 protect the input from excessive voltage levels. Pin 17 is used to set IC1 to receive serial data. It is normally held at logic 1 by resistor R4 but must be shorted to 0V whenever data is being loaded.

CONSTRUCTION


A single printed circuit board holds all the components. This board is available from EPE PCB Service, code 921. The p.c.b. component layout and full size copper foil master track pattern is shown in Fig 2.

The board has been made as small as practically possible to fit into a piece of 20mm plastic electrical conduit. Alternative mounting arrangements such as cardboard tubes or plastic overflow pipes may, of course, be used. A transparent perspex tube would give a very interesting appearance. If the tubular form of construction is too fiddly, the display works quite well stuck on a strip of wood, using an ordinary 4 x AA battery holder, and a few rubber bands!

Whichever method of assembly is used, do not fit any components to the board until the drilling and mechanical work has been completed. The board is useful as a template, and is easier to handle before assembly.

For use in a tube, it is very important to set the l.e.d.s in the board to exactly the right height. This allows the board to be slipped into the tube and then pushed upwards so that the l.e.d.s locate into seven pre-drilled 3mm diameter holes.

The hole positions can be marked most accurately with a sharp needle using the unassembled board as a template. Stick the board to the outside of the tube with tape before marking the centres so that move-

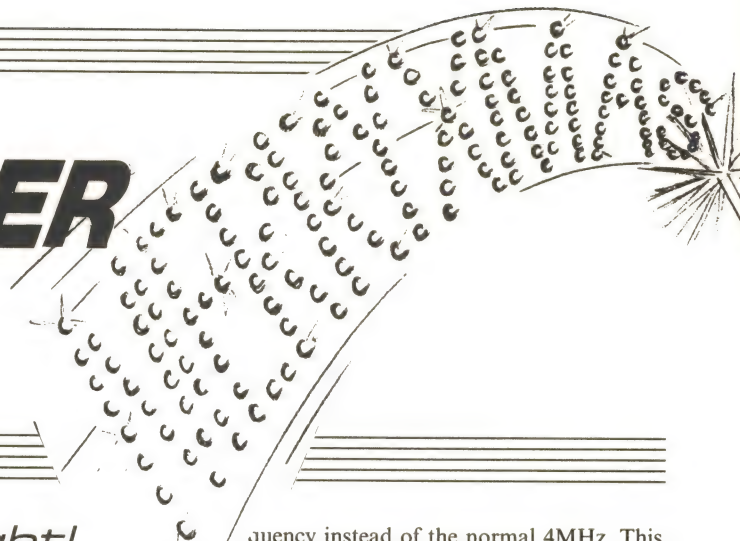

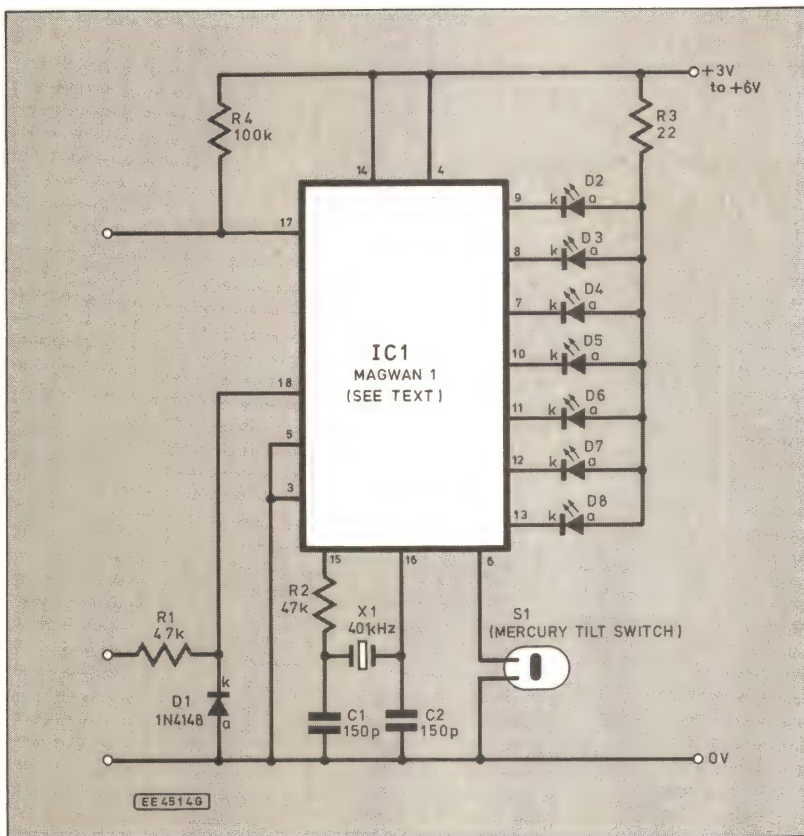


Fig. 1. Complete circuit diagram for the Spacewriter Wand.

ment is minimised and the holes are aligned as well as they can be. Do this very carefully as the l.e.d.s cannot be adjusted easily if the holes are out of line. If alignment does cause problems, larger holes can be used to allow some slack.

The board should be positioned in the tube to allow for three AA type batteries to be fitted. It is permissible to use four batteries for a brighter display, but in most situations three are adequate.

The positive battery terminal connects to a thin piece of metal bent over the end of the board at the battery connection end. Make sure that the metal chosen can be soldered, and that it does not have a transparent plastic coating. Most tin cans are suitable and can be cut with strong scissors.

The tilt switch, S1, needs to be fitted "upside down" as shown in the component layout drawing. Two lengths of stiff wire are needed to extend the connections and should be insulated with short lengths of sleeving. Good quality silicon rubber sleeving was used in the prototype, it is flexible, and does not melt when soldered.

In use it was found that the initial "flick" as the tube was moved causes the mercury inside the switch to rise to the top, bridge the contacts, and start the display. This was contrary to the initial idea which was to use the switch conventionally and allow the mercury to roll over the contacts as the tube was tilted. It seems that the inertia and low viscosity of the mercury makes it respond quickly even to relatively slow movements (is that why it's called quicksilver?).

SOLDERING ON

The l.e.d.s must all be fitted the right way round. The long lead is normally the anode and goes to the long strip of track as shown in Fig 2. The height above the board is best determined by trial and error and should allow the board to be inserted and removed easily from the tube. Experiment with just

one, and then mount the others at the same height. To aid alignment, the holes drilled in the tube can be used from the outside to hold the l.e.d.s in place whilst soldering. Use of sticky tape to hold the tube to the workbench is helpful, and allows the job to be done with just two hands.

Once the l.e.d.s have been fitted and the circuit board can be moved in and out of place, the remaining components can be added. The resistors are all miniature surface mount components. They are not difficult to solder, provided the pads onto which they sit have been tinned. Also, it is

COMPONENTS

Resistors

R1, R2 47k (2 off)

R3 22

R4 100k

All surface mount types

See
SHOP
TALK

Capacitors

C1, C2 150p sub.min ceramic (2 off)

Semiconductors

D1 1N4148 signal diode

D2 to D8 sub.min. high brightness l.e.d.

IC1 pre-programmed microcontroller (see Shoptalk)

Miscellaneous

X1 40kHz crystal

S1 mercury tilt switch

Printed circuit board available from EPE PCB Service, code 921; length of 20mm plastic tubing 20mm diameter (see text); AA-type battery (3 off); connecting wire, solder, etc.


Approx cost
guidance only

£17

strongly recommended that a fine-tipped soldering iron is used.

A needle or other sharp instrument can be used to hold the resistor in position while one end is soldered. Once the solder has set, solder the other end. Be careful not to get both ends hot together, or the resistor will slide about all over the place. This can be turned to advantage to remove a resistor wrongly positioned. Simply heat both ends by moving the soldering iron from one to the other in quick succession. The resistor will loosen and can be lifted off with a needle.

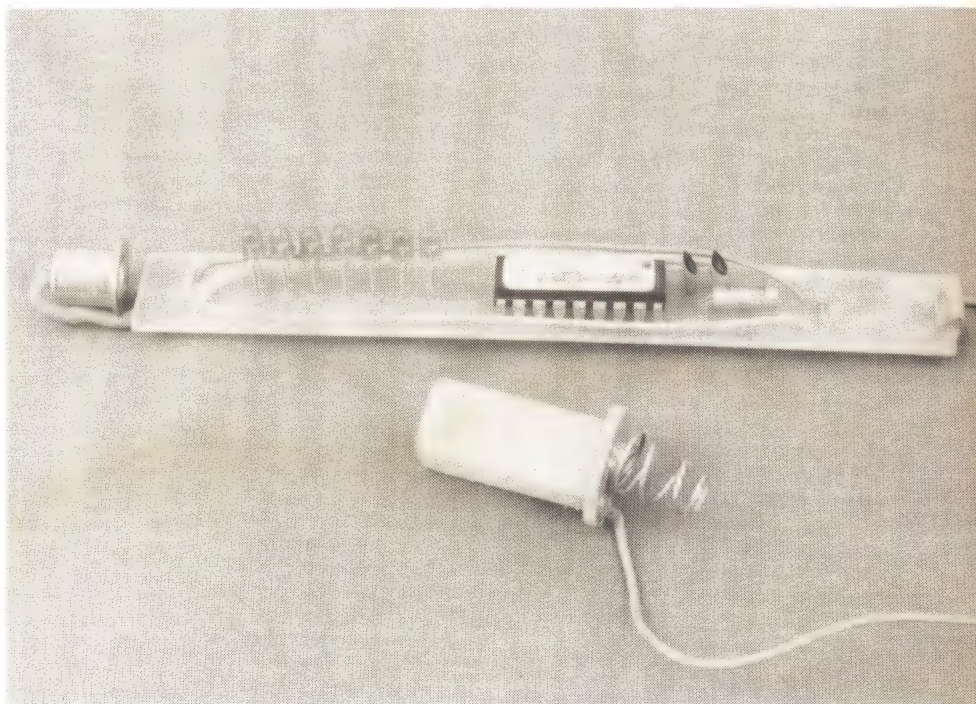There are four wire links which run from the holes at one end of the board to pads at the other. This is to allow the tilt switch and serial input connections to be at the top end of the board. There is not enough board space to allow proper tracks to be used. Ordinary thin solid core connecting



The assembled Spacewriter Wand p.c.b. showing "wood dowelling" battery connector.

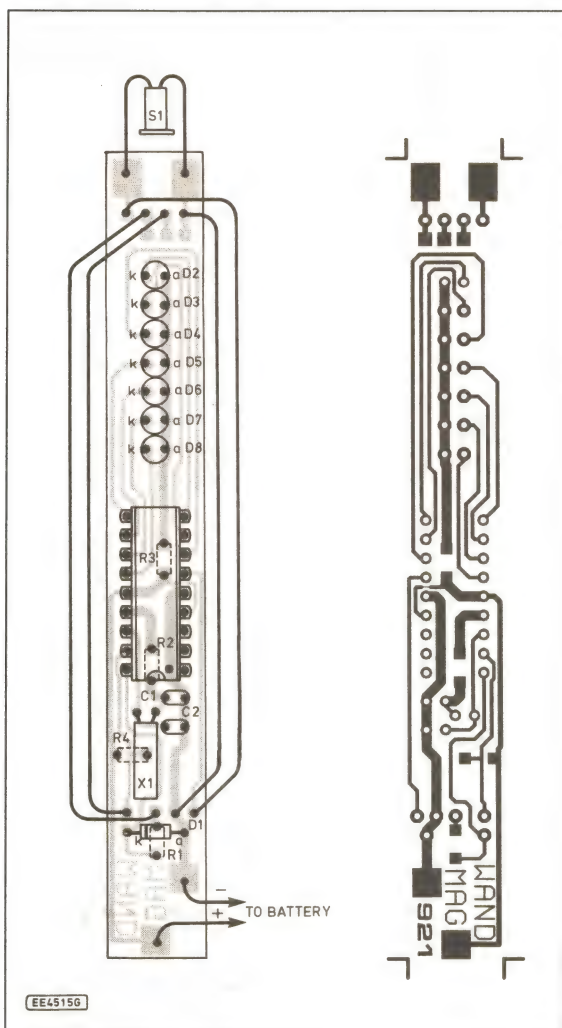


Fig. 2. Printed circuit board component layout and full size copper foil master track pattern.

wire can be used, and laid along the sides of the other components as shown.

To keep the board height low, IC1 must be soldered in position. Make sure it is the right way round! A mistake here will be difficult to put right.

With all components fitted, the board should be tested. The test procedure is described later. Once tested and working, proceed with the mechanical assembly.

TUBULAR MOUNTING

The positive battery connection is made directly to the end of the board as already explained. The negative connection is made via a flexible lead from the board to a connecting spring at the distant end of the batteries. This spring is held in place by being soldered to a metal disc which just fits inside the tube. A long flexible wire connects it to the negative contact point on the board.

The tube length must be cut carefully to give just the right amount of spring compression with the l.e.d.s on the board aligned correctly with their holes in the tube. This is done by setting up the board, the retaining plugs and the batteries alongside a piece of tubing and marking out the correct length. Be sure to have the l.e.d.s aligned in their holes so that everything is positioned accurately.

The top and bottom ends of the board are retained by a 30mm pieces cut from the end of a spare length of tube. Each piece is cut along its length and a section removed so that it closes down to become a tight

inside fit like an internal circlip. One piece is pushed down over the tilt switch until it touches the top edge of the board, the other is pushed in to retain the batteries and their negative connection spring.

Permanent fixing with glue was not necessary, as the tubing is quite springy and holds its position well. A short length of wood dowelling was needed, glued to the underside of the disc supporting the negative connection. This was to keep the disc aligned correctly, preventing it from flipping over onto its edge.

To keep the board in position with the l.e.d.s aligned in their holes, a small piece of foam sponge can be pushed down the tube behind the board using a knitting needle. Be careful not to use any more force than necessary, and not to damage the surface mounted components or wire links.

The tube ends can be covered using moulded end caps, or adapting bicycle handlebar end plugs. This type of hardware can usually be found without too much difficulty.

TESTING

Assuming the assembly of the board is complete, the first thing to do is double check all of the soldering and the component identification. Once everything is in order, connect a 4.5V supply and check that the circuit does not draw excessive current. If a multimeter is not available, a small bulb in series with the supply will light if there are any bad short circuits.

If the current is in order, it should be possible to get the l.e.d.s to flash by tilting the board and closing the tilt switch. A simple voltage check at IC1 pin 6 can be made to see if the tilt switch is working. Normally the voltage should be 4.5V, and it will switch to 0V when the switch closes.

If the circuit refuses to flash the l.e.d.s, disconnect the supply, wait about one minute, and reconnect. If the circuit still

does not work, check that the l.e.d.s are the right way round, and that they light individually when their corresponding pin on IC1 is short circuited to 0V. As it is such a simple circuit, there is very little to go wrong, and so faults are unlikely. An oscilloscope, if available, can be used to check the crystal oscillator which should be producing a 4.5V peak to peak sine wave at 40kHz.

Once the l.e.d.s are flashing, the effect can be tested by moving the wand from left to right across the field of view. The best effect is obtained in a dimly lit room, and is easier to see when the eyes are fixed in one position by looking at a stationary object behind the display. The speed of movement is largely down to trial and error, but should be easy to establish. The display speed is a compromise between speed of movement and persistence of vision. Too slow, and a row of moving l.e.d.s appears, too fast, and the wand has to be moved too quickly.

The default display is "MERRY XMAS". Apologies to those who prefer not to abbreviate, but for the display to be read easily, the full word *Christmas* is too long!

OTHER MESSAGES

After Christmas, the display can be used for its main purpose by programming it with any 16-digit message. The message is loaded simply by sending serial ASCII code at 300 baud into pin 18 of IC1, whilst connecting pin 17 to 0V.

Any serial communication can be used, provided it sends data without handshaking, at 300 baud, no parity, eight bits and one stop bit. *Procomm* was used in the original, this has an ASCII download option and was configured as "300,N,8,1" according to the "Set Modem Parameters" screen. The first 16 codes to arrive are loaded, and everything else is discarded. Only capital letters, numbers, and spaces are available for display, others are ignored.

No handshaking or other reverse communication is used, because the message is so short and errors unlikely.

Three pads at the top of the board allow the serial connection to be made. A small 3-way 0.1 inch socket is suitable on a short flying lead. A special computer lead is then needed to pick up the computer 0V and TXD pins from the chosen serial port.

Finally, this is a novel display which must have a variety of interesting uses, about which we would be pleased to hear from you! □



Spacewriter board half-inserted into mounting tube. Note the holes for the l.e.d.s, and the retaining "plug".

EPE FRUIT MACHINE



BRETT GOSSAGE and JULYAN ILETT ≡ **Part 1** ≡

A coin operated fruit machine that really pays out!

HAVING had a keen interest in fruit machines (also known as "slots", "automatics" or "one arm bandits") for as long as the authors can remember, they have always had it in mind to construct one. At a very early age, mechanical designs constructed using Meccano or Lego were attempted, but met with limited success, so an electronic machine was the obvious alternative.

Many years ago, an all TTL system was proposed, but if even the simplest of features were to be included, the circuitry would have been very complex. Some time later, a microprocessor design was considered, but it still would have involved considerable hardware and a hefty power supply.

PAYOFF

Now, finally, a design based around a single chip PIC16C57 microcontroller has become possible, and has resulted in a simple circuit, with battery power capability and plenty of space left for the single most important feature – a *real payout mechanism*.

This design, which it is believed fits into the "executive toy" category, makes use of two simple-to-construct plastic coin mechanisms, a coin detector and a coin payout mechanism. Both mechanisms are designed to work with the new small five pence piece. This coin was chosen for two reasons. First, the Fruit Machine had to be reasonably inexpensive to play while at the same time offering a high value jackpot. Second, since the five pence coin is the smallest, lower value coins will not fit through the slot, so no reject mechanism is required.

ANIMATED FRUIT

In order to minimise the number of mechanical components, large 7-segment displays are used instead of "reels" to reproduce the "fruit" symbols. Animation techniques have been used to give the "reels" a realistic spinning action, and software algorithms have been designed to simulate the inertia and friction of an equivalent mechanical system.

The fruit symbols are passed through the displays from top to bottom, quickly at first, then progressively more slowly until stationary. The three reels have been given different characteristics, so that the left reel

stops first, followed by the centre reel and then the right reel.

To add further realism, the sound of the reels clicking against ratchets as they spin has been simulated too. Features including "hold" and "gamble" have been incorporated which appear at random introducing an element of skill into the game.

A mechanical arm, used to start the reels spinning, has been rejected in favour of a "start" button in line with the more up-to-date designs of fruit machine. Naturally, the machine cannot be started until at least one coin has been inserted. Several coins can be inserted if desired, and are registered as "credits" inside the machine.

A set of eight l.e.d.s called the *Feature l.e.d.s* are normally used to indicate the credits but are also used to liven up the machine by flashing various sequences prior to payout and when the machine is not being played.

PAYING OUT

The Fruit Machine has an average payout of about 75 per cent and so is capable of making a profit. Interestingly, commercial machines are bound by law to return a minimum percentage of the stake,


typically 70 per cent to 90 per cent, to the player. The exact value is indicated on the front of the machine. Since it does not make commercial sense to payout more than this, the odds are manipulated to maintain this percentage with great accuracy, it does not matter whether you play to win or lose.

This design does not monitor the payout, it is genuinely random and skilful play will increase the payout rate, although never above 100 per cent! For this reason, the Fruit Machine would make an ideal money box for a child who should ultimately discover the futility of gambling!

PROFESSIONAL PRESENTATION

The Fruit Machine is housed in a standard ABS plastic box measuring 220mm x 150mm x 60mm approx. A specially commissioned full-colour self-adhesive front panel is available which considerably enhances the machine's appearance. All the electronics including the displays and switches are mounted on a single sided p.c.b. measuring 100mm x 140mm approx. which is available from the *EPE PCB Service*, code 914.

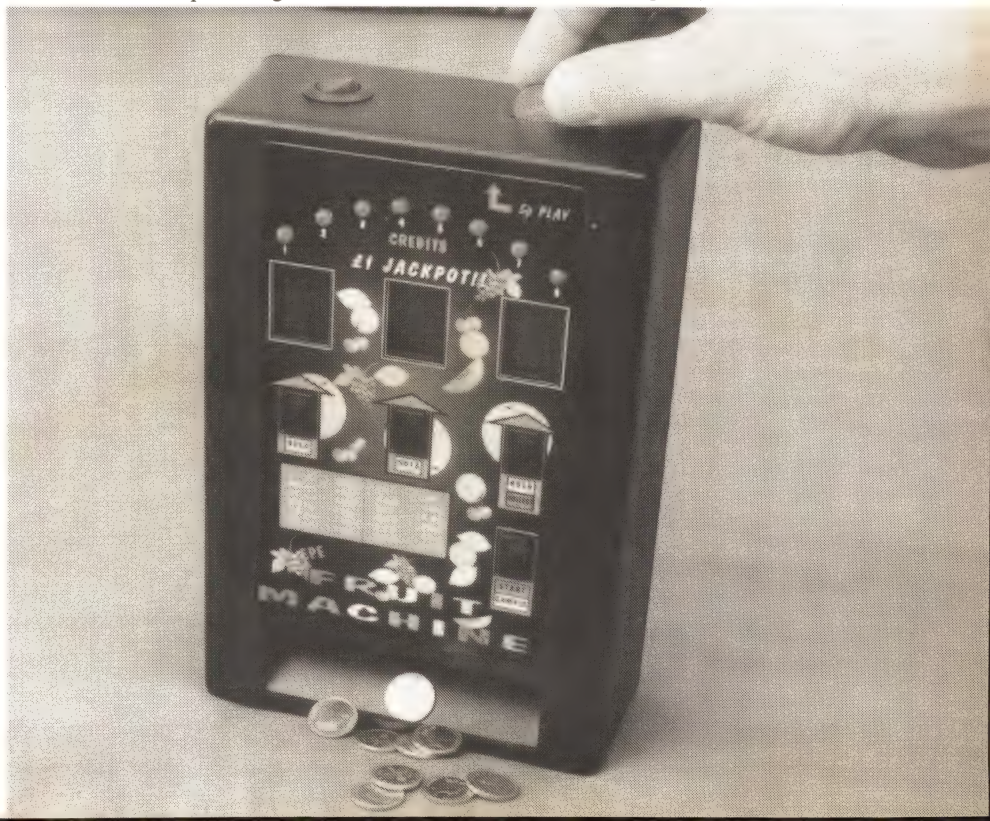The specially programmed PIC16C57 microcontroller is available from the authors, price £12, and the colour front panel is £2 (see Shoptalk).



MODE MANAGEMENT

The Fruit Machine's microcontroller continually manages a number of different tasks. These include multiplexing of the display matrix, monitoring the switches and coin detector, and controlling the piezo and servo outputs. In addition to this, "mode" control and the complex task of animating the three reels must also be carried out.

The program flowchart is shown in Fig. 1. At any one time, the Fruit Machine can be in one of seven different modes, *idle*, *sequence*, *spin*, *win*, *payout*, *gamble* or *nudge*. When the machine is first switched on, the *idle* mode is entered. If there are no credits, i.e. no coins have been inserted, the machine switches to the *sequence* mode after two seconds to encourage play.

Inserting a coin takes the machine back to the *idle* mode. In this mode, all three reels are stationary, and the program waits for the *start* button to be pressed. If the *hold* feature is active, the three *hold* lights will flash and the *hold* buttons will be active.

When the *start* button is pressed, the machine enters the *spin* mode. Next, a random number generator decides which combination of fruits the reels will stop at. Whether or not a win will be given and its value is decided even before the reels start spinning!

When all three reels have stopped, the winning line is analysed and the machine

enters either the *win* mode, or returns to the *idle* mode if the game is lost. The *win* mode consists simply of a short sound and light sequence, after which the *payout* mode is entered. In the case of wins with three fruits the same, the *gamble* mode may be entered. Here, the win is either collected or gambled up or down. The *nudge* mode just steps all three reels forward or backward by one fruit.

In the *payout* mode, the "odds" table is read and a counter is set up to pay out the required number of coins. The servo motor is then moved to and fro and the counter decremented until it reaches zero. After payout, the Fruit Machine returns to the *idle* mode.


The random number generators, used to decide the winning line and to control the *hold* and *gamble* features, are simply fast counters which cycle continuously and are read each time the start button is pressed. It is impossible to anticipate the values of the counters, however, making it impossible to cheat!

IN A SPIN

A "mechanical analogy" of one of the Fruit Machine's reels is shown in Fig. 2. Although the system is essentially "all software", the algorithms of the *spin* mode were closely modelled on the equivalent mechanical system shown. The principles used are best described using this analogy, simply publishing parts of the source code would make very dull reading indeed!

The three reels each have six fruit symbols, but a total of 30 individual steps. This enables a reel to be displayed part way between two fruits for animation purposes, although the reel cannot stop in this position. Each reel has a speed parameter which is used to step the reel forward at a constant rate. Each time a reel is stepped, the piezo electric sounder output is toggled giving a "click" sound.

Initially, the reel is set spinning at a constant speed, then, after a short period, the speed parameter is decremented at a constant rate which slows the reel down. To ensure that the reel stops accurately on the fruit, rather than half way between two fruits, slowdown is delayed until the selected fruit passes through the win line. The complete slowdown process then takes exactly two revolutions until the speed parameter reaches zero and the reel stops.

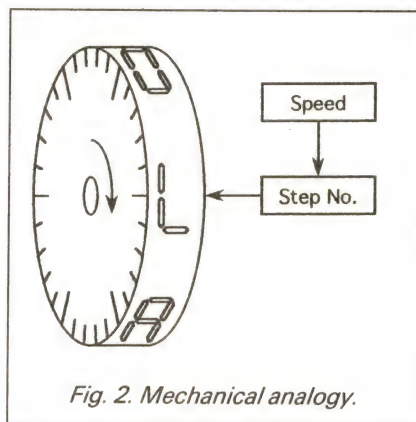

MECHANICS

Since the Fruit Machine handles real coins, the job of getting them into and out of the machine requires a couple of mechanical devices.

Insertion of coins is handled by the coin detector mechanism. This uses a simple infra-red beam which is broken as the coin drops through. Whilst this design does not have any obvious security features, tampering is countered by measuring the time for which the beam is broken. Durations outside of a "window" value are rejected thereby ignoring the insertion of "inappropriate" objects.


Coins are paid out by the coin payout mechanism which uses a simple sliding tray to pull the coins, one at a time, from the bottom of the coin stack. It is driven by a servo motor, the type typically used in radio controlled models.

Both the coin detector mechanism and the coin payout mechanism are constructed, very simply, out of sheet plastic available from most model shops. A length of plastic pipe is required for the coin stack which is easily obtained in the form of overflow pipe for water tanks, available from builders merchants.

COMMERCIAL SCENE

The design of the Fruit Machine was, to a certain extent, inspired by the techniques used in commercial machines. For this reason, and by way of a small diversion, it may be interesting to take a look at the way these fascinating machines work.

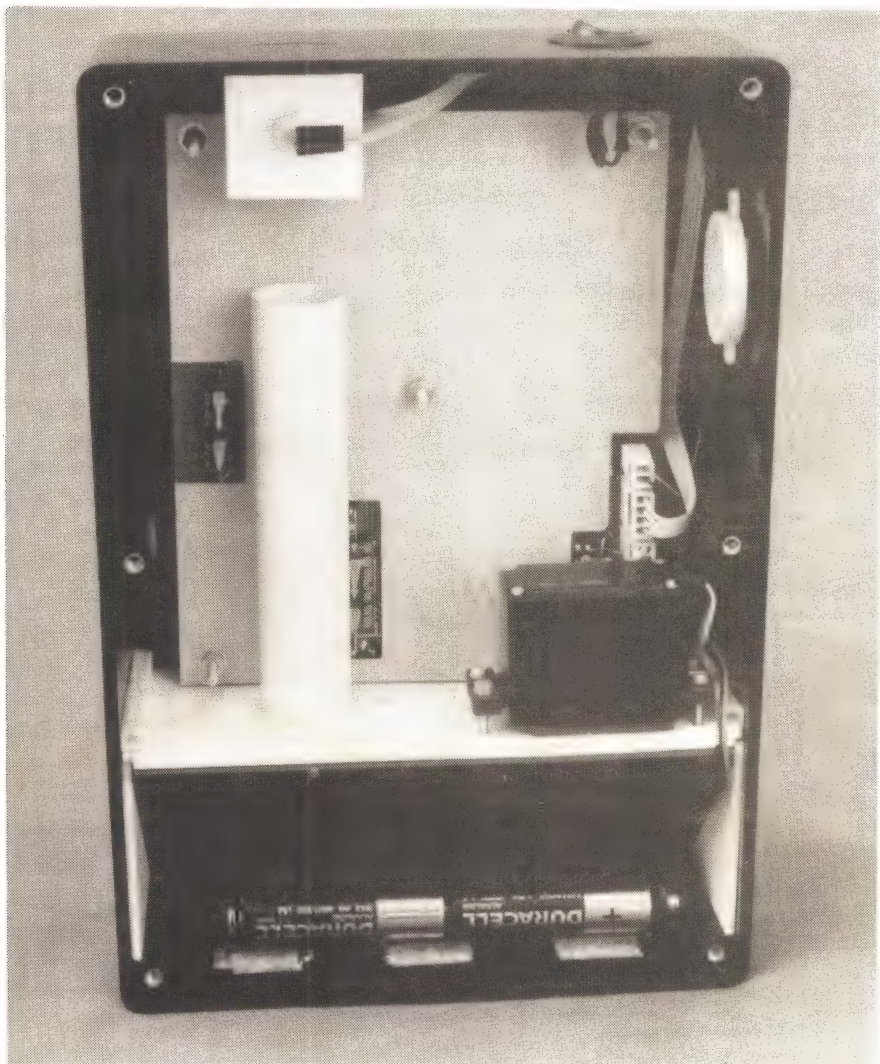Unlike early mechanical machines, which used electricity just to illuminate the front glass, modern machines are based entirely around complex microprocessor circuitry. The CPU board will typically contain a



Interior of the Fruit Machine showing the "mechanical mechanism" to be described next month.

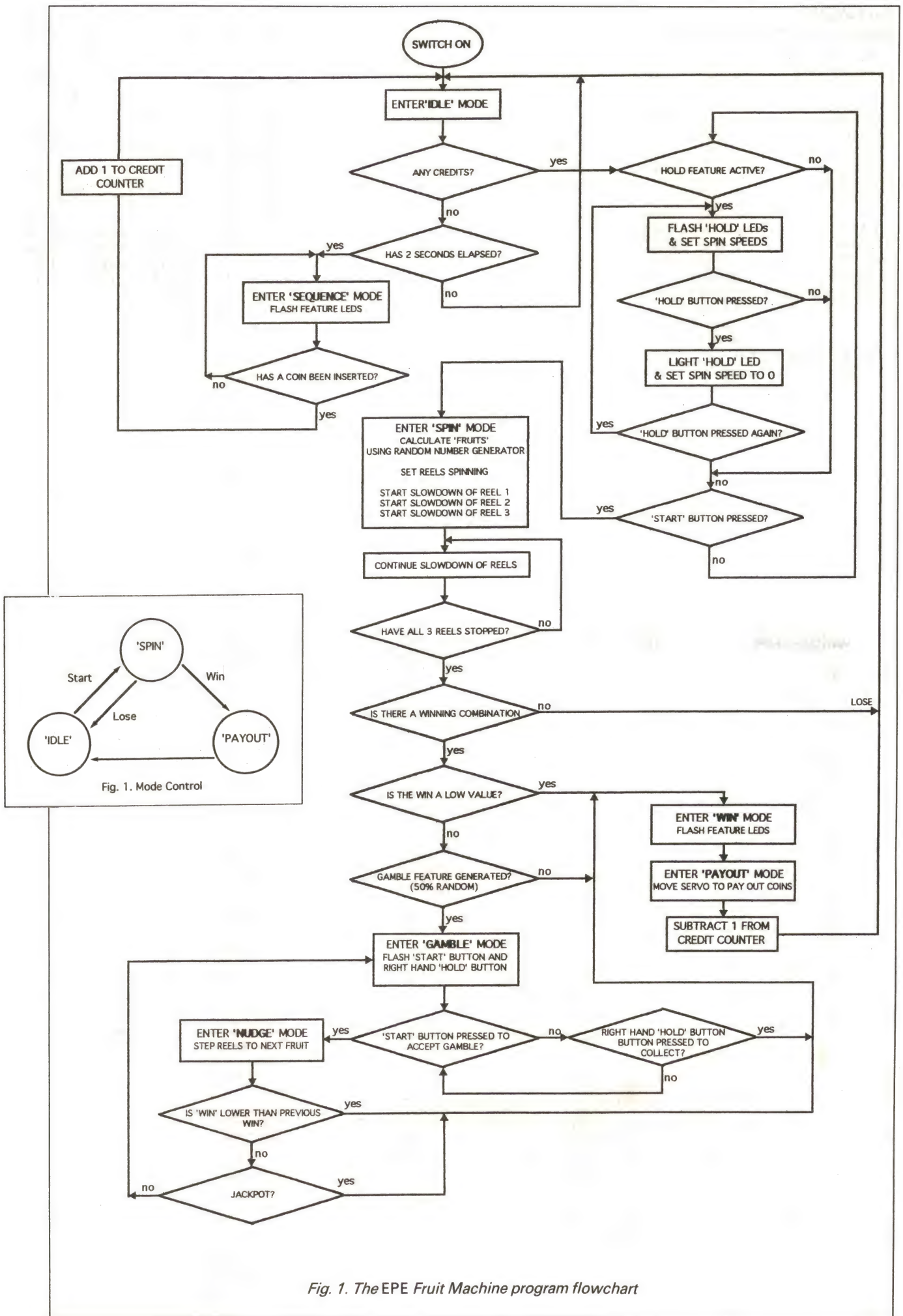


Fig. 1. The EPE Fruit Machine program flowchart



Z80 or 68000 processor and the usual EPROM and RAM. Battery backed RAM or EEPROM may be used to maintain "odds" data during power off.

A large number of power transistors will be present to drive solenoids, stepper motors and the matrix of light bulbs which illuminate the reels and feature panels on the front glass. A sound effects chip may also be present.

The reels are, of course, mechanical, but being of an ultra light weight construction, have virtually no inertia and are controlled directly by the CPU using stepper motors. The speed of rotation and the point at which they stop is under CPU control. Any random behaviour here comes from random number generators in the software.

A large number of miniature filament lamps, which sit behind the front glass, are connected up in a matrix of rows and columns. Unlike l.e.d.s, these lamps conduct in both directions and therefore each lamp requires a series diode, which may be mounted in the lamp holder.

COIN DETECTION

Detecting the insertion of coins in commercial machines may be handled in two different ways.

The mechanical method uses an elaborate mechanism employing a counter-balanced cradle into which the coin drops, tipping the cradle over and sending the coin down a channel towards a microswitch which registers a credit.

Coins that are too small drop straight through the cradle and into the coin return chute, whereas large coins get stuck, requiring use of the coin reject lever. This forces open the whole mechanism allowing any large item to drop straight through. Additional safeguards include a magnet which attracts ferrous metal objects such as washers.

Modern coin detectors use a simple slide fitted with a number of coils through which a range of different coins can be passed. The coin changes the inductance of the coils as it passes, generating a unique signal for each coin.

Only coins with recognised signatures are accepted, a solenoid diverts alien devices to the reject chute. Once a valid coin has been detected, its signature is used to divert it down one of several different chutes.

A solenoid operated plastic paddle diverts the coin initially down one of two

chutes, then two more paddles, mechanically linked and controlled by a further solenoid, split the two chutes into four. In this way, two solenoids operating in a binary fashion, can sort up to four different coins into four plastic tubes.

COIN PAYOUT

The coin payout mechanisms, of which there are likely to be four, are situated at the bottom of the tubes in which the coins stack. They are similar in design to the one used in this project, although they use a metal slide moved by a solenoid.

The solenoids are massive, each about the size of a mains transformer and are typically operated from 50 or 60 volts. Tremendous pulling power is required to slide a coin out from the bottom of a stack containing a couple of hundred coins.

All this gadgetry is housed in a tall cabinet made of chipboard with glass front panels. Several locks are employed to prevent access to a number of large plastic buckets sitting in the bottom of the machine which collect the coins that overflow from the coin stacks.

Commercial fruit machines are expensive items of equipment, although when situated in the right places, are capable of making a healthy profit.

CIRCUIT DESCRIPTION

The full circuit diagram for the EPE Fruit Machine is shown in Fig. 3.

A microcontroller is ideally suited for a project like this, to control the various Input and Output (I/O) devices found in the design. The amount and complexity of the software, and the memory required (2K), determine the specific controller, and this was chosen to be the 28-pin PIC16C57 manufactured by Arizona Microchip. The PIC16C57 (IC1) has three "ports" A, B and C, (one four-bit, A, and two eight-bit, B and C, where any bit can be configured as an input or an output) all of which are used (see Fig. 3).

The seven lines RB0 to RB6 are set up as outputs (port B), and drive the seven segments of each main "fruit" display, "a" to "g". The displays are multiplexed such that "segment" data is output via port B on lines RB0 to RB6. Then the appropriate "digit" drive bit on one of the four lines of port A (RA0 to RA3) switches transistors TR1 to TR4 in turn to sink current, lighting up the "digit" (the fourth digit corresponds to the "feature" l.e.d.s).

Segment drive "h" (RB7), which is usually the decimal point on 7-segment displays, is not connected as such, but is routed off to the l.e.d.s within the hold switches. Drive current to each of the segments is limited via resistors R1 to R8.

Each segment of the four displays is "overdriven" in turn by about four times its maximum rated current. This is acceptable and is done to increase the brightness of the displays. Because each segment is only on for a quarter of the time, there is no risk of damage to the displays or the drive transistors.

The clock circuit for IC1 uses a simple ceramic resonator for stability, and consists of components X4, C1 and C2. This generates a clock frequency of 1MHz.

The start and hold switches S1 to S4 "ground" the input lines RC4 to RC7 of port C (IC1) when pressed, and are otherwise pulled "high" by R32 to R36.

The servo requires two pulse trains of 1ms and 2ms at 50Hz for the "collect"

and "payout" positions respectively, for the coin mechanism. These are generated using a CMOS 7556 dual timer chip (IC2).

The first timer in the chip (IC2a) is connected as an oscillator, generating the 50Hz via resistors R24, R25 and capacitor C3. This 50Hz output is connected to the trigger input of the second timer (IC2b), which

COMPONENTS

Resistors

R1 to R8	56 (8 off)
R9 to R20	2k7 (12 off)
R21, R22	220 (2 off)
R23, R24, R28	4k7 (3 off)
R26, R29, R31	10k (3 off)
R30	15k
R25	100k
R27	150k
R32 to R36	4k7 (s.i.l. resistor pack)

See
SHOP
TALK
Page

Potentiometers

VR1, VR2	10k sub-min. preset (2 off)
----------	-----------------------------

Capacitors

C1, C2	22p disc ceramic (2 off)
C3, C9	100n disc ceramic (2 off)
C4, C5	10n disc ceramic (2 off)
C6 to C8	1000µ axial elect. 10V (3 off)

Semiconductors

D1	1N4148 signal diode
D2 to D5	1N4001 rectifier diode (4 off)
LED 5	min Infra red l.e.d.
LED 6 to LED 13	5mm l.e.d. std. (yellow) (8 off)
X1 to X3	0-8in. 7-segment display (common cathode) (3 off)
TR1 to TR5	BC548 npn silicon (5 off)
TR6 to TR13	BC558 pnp silicon (8 off)
TR14	min Infra red phototransistor
X4	1MHz ceramic resonator
IC1	PIC 16C57 (see text)
IC2	7556 dual CMOS timer

Miscellaneous

S1 to S4 (LED1 to LED4)	p.c.b. switch with internal l.e.d. (4 off)
S5	round rocker switch (black)
MO1	servo motor (Futaba FP.S14B)
PL1, PL2, PL4	p.c.b. 2-way plug (3 off)
PL5	p.c.b. 3-way plug
PL3	p.c.b. 4-way plug
SK1, SK2, SK4	p.c.b. 2-way skt (3 off)
SK5	p.c.b. 3-way skt
SK3	p.c.b. 4-way skt
28-pin i.c. socket; 14-pin i.c. socket; battery holder 4xAA (long type); battery clip (PP3 type); box ABS MB6; l.e.d. display filter (red); plastic sheet 0-060in. white; plastic sheet 0-080in. white; plastic sheet 0-080in. black; plastic tube 6mm diameter, 1 strip; plastic tube 21mm diameter, 100mm; plastic glue; paper clip; solder etc.; printed circuit board available from the EPE P.C.B. Service, code 914.	

Approx cost
guidance only

£65

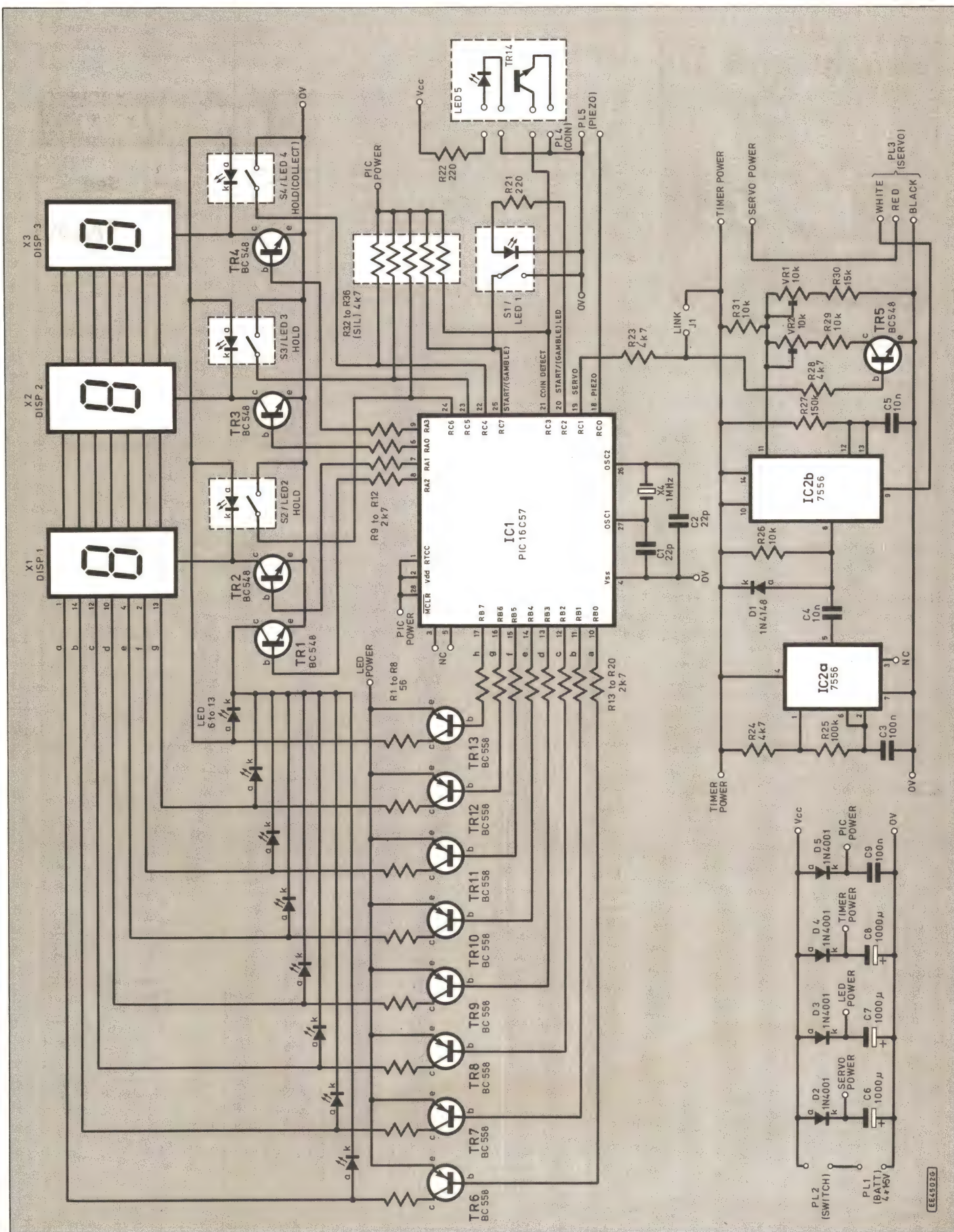


Fig. 3. Complete circuit diagram (less servo motor) for the EPE Fruit Machine. Note that resistors R32 to R36 are contained in a single s.i.l. package.


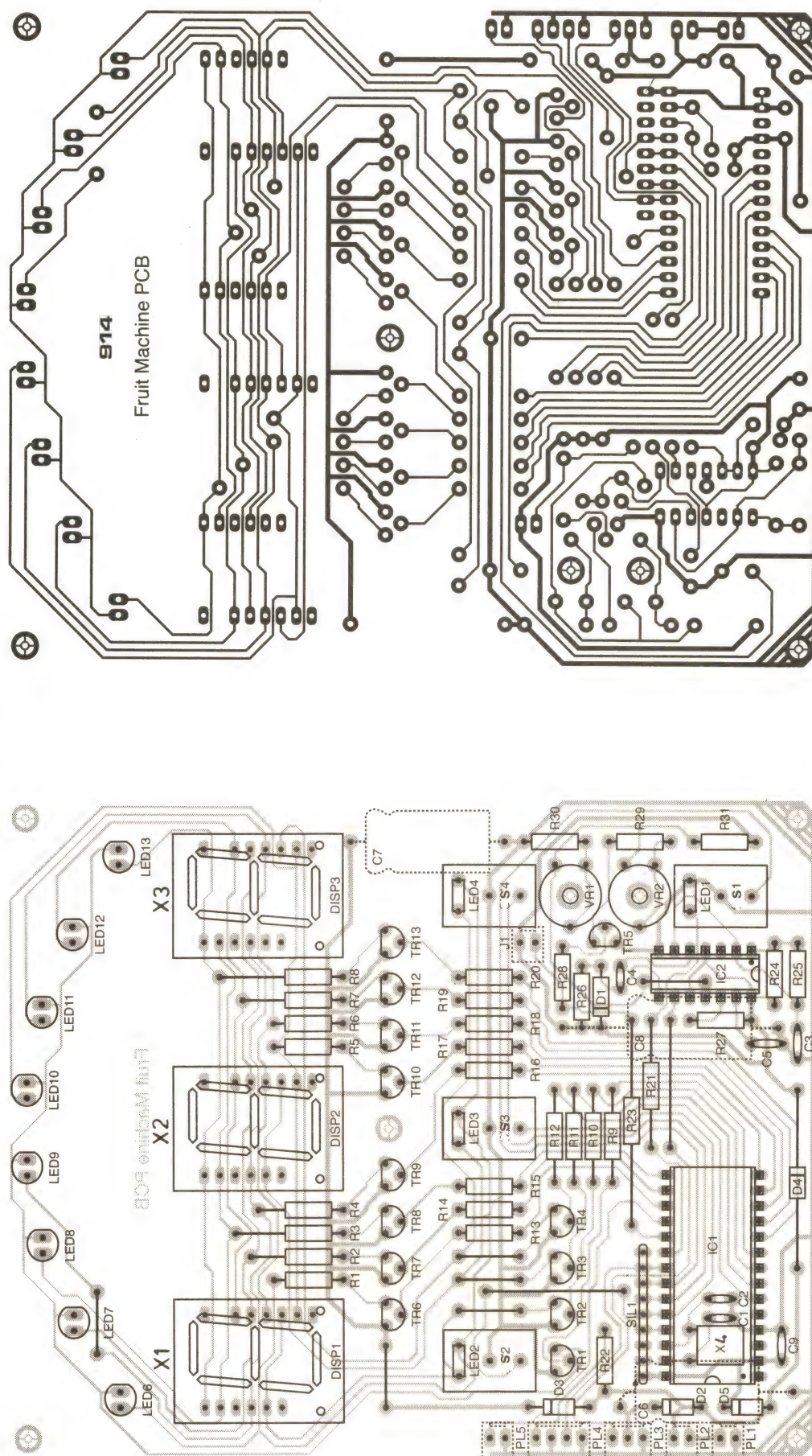
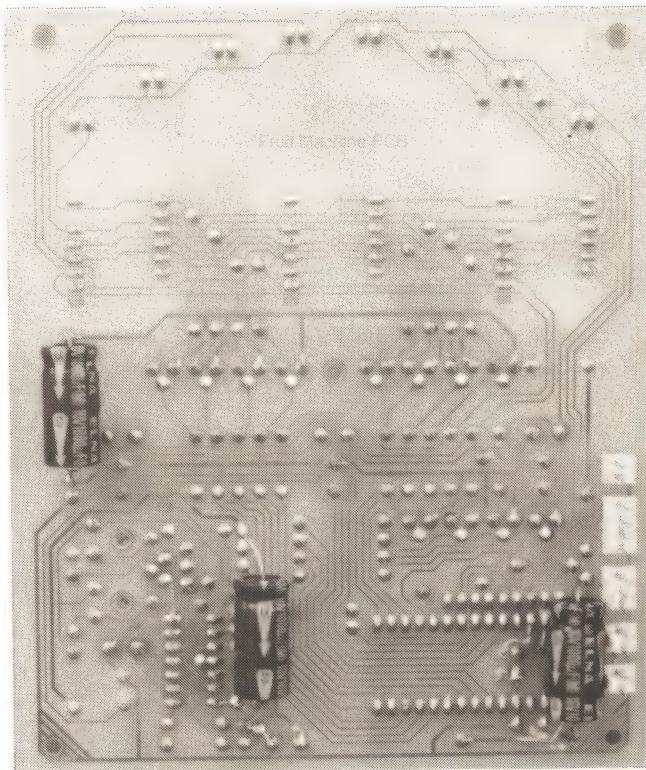


Fig. 4. Fruit Machine printed circuit board component layout and full size underside copper foil master pattern. This board is available from the EPE PCB Service, code 914.

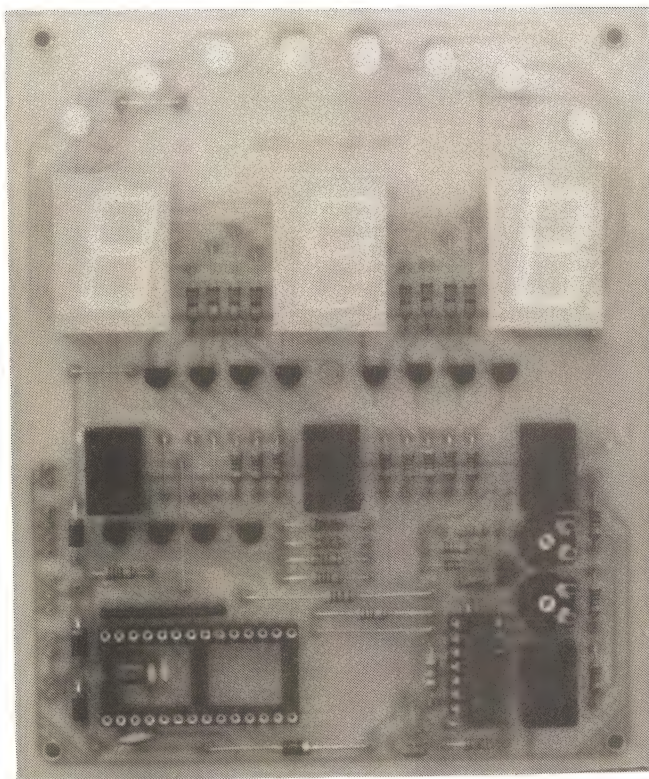

Top and underside views of the completed p.c.b. Note the electrolytic capacitors and connectors on the underside.

is connected in monostable mode, giving the correct pulse width determined by resistor R27 and capacitor C5. The voltage at the reference pin (pin 11), is adjusted by preset VR1 to obtain the 2ms pulse. TR5 is switched on via link J1 to select a parallel resistor pair which generates the 1ms pulse train, and this is adjusted using preset VR2 (see "Testing" – next month).

There are four isolated power supplies to power the l.e.d.s, servo, timer and microcontroller i.c.s. In each case, a diode "taps off" the battery supply (D2 to D5), isolating and localising any interference. Each supply is smoothed and decoupled with a capacitor (C6 to C9). The diode in the "PIC power" section (D5) reduces the maximum voltage for IC1 to a safer working level, as a new set of four batteries may exceed the 6V maximum supply rating for this i.c.

Sound is generated as a square wave, by toggling a bit (RC0) on IC1 at an appropriate frequency, (depending on the feature), and this signal is connected directly to the piezo electric sounder.

P.C.B. ASSEMBLY

The printed circuit board (p.c.b.) component layout and foil master pattern is shown in Fig. 4.

Due to the nature of construction, some of the components are not mounted flush on the p.c.b, notably the, *feature* l.e.d.s. As a rough guide, the legs of these eight yellow l.e.d.s should be cut to a length of 16mm, and then should be soldered as high off the p.c.b. as possible.

The eight *feature* l.e.d.s, the three *hold* switches and the *start* switch all protrude from the front panel of the box, thus the cut-outs need to be quite accurately made so that the p.c.b. will make a snug fit. The main displays have a red filter fitted in front of them. This increases the contrast of the displays, and it really works! It fits in one piece behind the cut-outs in the front panel of the box. Note that these cut-outs are actually smaller than the displays themselves.

Construction proceeds by first fitting the seven links, and all the resistors including

the presets. Then fit the capacitors, diodes and transistors, displays and l.e.d.s. Finally fit the switches, but note that the green l.e.d. in the *start* switch needs to be turned around. This can be done quite easily by disassembling the switch housing with a small watchmakers screwdriver, and it is easier than it sounds!

Note that some components are fitted underneath the microcontroller chip (IC1). Next fit the sockets for the microcontroller, and the 7556 timer (IC2). Finally, fit the three 1000µ capacitors on the back of the p.c.b. and fit the i.c.s when required, during testing.

The connectors are also mounted on the reverse side of the p.c.b, and because the p.c.b. is single-sided, care should be taken when soldering the plug pins to it. It may be easier to push the pins of the connector until they protrude equally from either side of the plastic mounting, and then solder them to the p.c.b, pushing the plastic part of the connector flush to the p.c.b. last.

Next Month: Mechanical assembly and testing.

EVERYDAY WITH PRACTICAL ELECTRONICS

SUBSCRIPTION ORDER FORM

Annual subscription rates (1994/5): UK £24.00.
Overseas £30 (surface mail) £47.50 (airmail)

To: Everyday with Practical Electronics,
Allen House, East Borough, Wimborne, Dorset BH21 1PF

Name

Address

I enclose payment of £ (cheque/PO in £ sterling only).

payable to Everyday with Practical Electronics
Access or Visa No.



--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Signature.....

Card Ex. Date

Please supply name and address of cardholder if different from the subscription address shown below. **Subscriptions can only start with the next available issue.** For back numbers see the Editorial page.

**WHY NOT
MAKE IT A GIFT -
EVERY MONTH?**


Post code.....

12/94

ENHANCED AIR/SEA SAFETY

British enterprise vibrantly leads the international high-flyers

by Hazel Cavendish

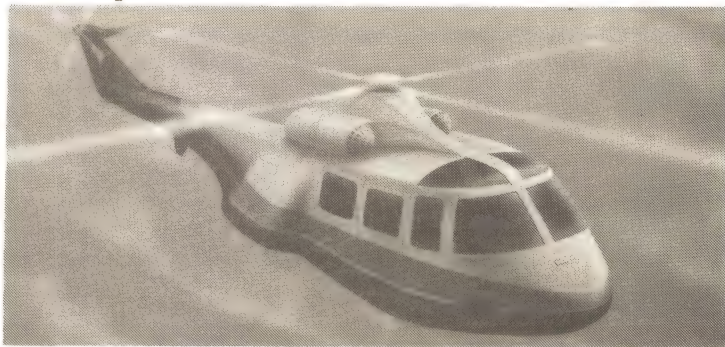

LAST year the small Hampshire engineering firm of Stewart Hughes won a Queen's Award for Export Achievement by increasing its export sales from £266,000 to £2.71 million in three years. The increase was largely through their R & D into a method of detecting mechanical faults in helicopters at an early stage. This was an exercise which also won them the American Helicopter Society's Harry T. Jensen award for contributing towards the safety of aircraft.

The Company, established 14 years ago, originated as a department of Southampton University. Both Chairman Ron Stewart and his M.D. Tony Hughes had worked in the University's Institute of Sound and Vibration, specialising in the diagnosis of machinery faults by analysing vibration signals. Their development of this technique has resulted in the unique design of a box for helicopters to be used as part of the Flight Data Recorder which controls the Crash Protection Unit.

The approach they use is the HUMS system (Health Usage Monitoring Systems). Incorporating Inmos transputers, the latest generation of the system carries out continuous automatic vibration analysis of the components within the helicopter drive train, thereby helping to detect mechanical faults at an early stage.

A factor of considerable importance is the ability of the system to distinguish one gear from another. "It is important to

know which gear is faulty," says Consultant Systems Engineer Max Hadley, "otherwise a signal indicating merely that the gearbox was faulty would mean having to change the whole box, dismantle it completely and inspect every gear. It is essential that aircraft are able to be turned around quickly, and with this system the faulty part can be identified instantly and replaced with minimum delay while the aircraft is in service."

The system uses software called the Flight Regime Recogniser which also looks at data signals from additional sensors throughout the aircraft. These too are recorded in the Crash Protection Memory, made by Penny and Giles of Dorset.

More advanced technology using Xilinx 4000 FPGAs (Field Programmable Gate Arrays) has been developed to meet military specifications for 100 systems supplied to the Canadian Defence forces for a fleet of helicopters ordered from Bell Helicopter.

"These FPGA devices are interesting because the data held within them can be readily reconfigured in situ," says Mr Hadley. "When the system is switched on, the first thing the software does is to load the hardware configuration into the FPGA which then starts the main software. It is a highly complicated system configuring from a common set of data which contains that for the FPGAs and the software for the Inmos processors. All this data can be uploaded into

the box via a connector in the front panel from a special adapter card which can be plugged into a lap-tap PC. All the software and FPGA configuration is held in flash memory within the box.

"As far as I know, we are the first company anywhere to use transputers in a certified piece of civil avionics. The idea of systems being able to be programmed in the field without having to go back to manufacturers to have a chip removed and a new one soldered in, is just taking off."

This autumn the Company also landed a six-figure contract with the American Defence Department by designing "a little black box" the size of a standard pack of corn-flakes which will monitor the cooling system of a Spruce class destroyer, a task previously done by personnel.


Stewart Hughes beat off the competition from top US companies specialising in electronic technology with its Intelligent Sensor Interface, which Max Hadley, who directed the development, describes as "a complete Star-Trek type of automated maintenance."

Handy Third Hand

The new Panavise JR is a vice that is more like a third hand than a tool. Work can be moved through three planes without removing it from the vice. The head is designed to rotate and swivel 360 degrees, and is able to pivot 210 degrees. One turn of the control knob, and you are able to securely position your work exactly where you want it.

The parallel closing jaws have an opening from 0mm to 730mm and are made of strong fibre reinforced thermal plastic for careful but firm holding of your work. The vice weighs in at only 567g, yet the body is made of cast zinc which provides a firm base that can also be bolted down. Its versatility makes it perfect for dozens of uses such as soldering, drilling, painting, gluing, assembling, fly-tying, repair, and even industrial use; ideal for the professionals, weekend professionals and do-it-yourselfers alike.

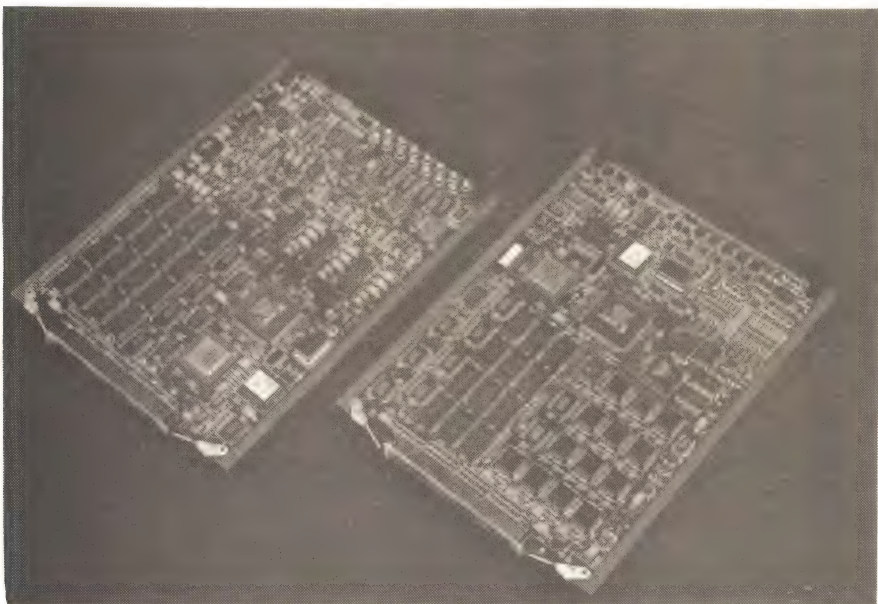The Panavise JR has a retail price of £23.44 (including VAT) and is available from many hardware stores, hobby and model shops, or with £4.95 carriage from Longs Ltd., Dept EPE, Hanworth Lane Trading Estate, Chertsey, Surrey KT16 9LZ. Tel: 0932 561241.



Circuit boards showing the use of Xilinx FPGAs in Systems developed by Stewart Hughes for use in helicopters servicing the North Sea oil rigs.

AF PDM AMPLIFIER

The first in a range of modular PDM (Pulse Duration Modulation) audio frequency amplifiers for experimenters and systems engineers has been introduced by D-Systems.

The appeal of PDM modules lies in their versatility. They work by encoding the audio signal as a proportional variation in the mark/space ratio of a high frequency power switch and decoding passively at the output. The system encodes the whole audio signal without sampling.

The audio performance is up to the standards of the best hi-fi amplifiers available and distortion is almost completely second harmonic and mostly below 0.2 per cent. This generally excellent performance, and the high efficiency and low standby current consumption, makes the modules suitable for general purpose battery-powered monitoring use, possibly in remote locations using solar powered supplies. They can also be used as booster amplifiers for personal stereos.

The first of D-System's PDM modules is the PMI which operates on a single 9V or 12V rail with quiescent current drain of only 400 microamps. Full power bandwidth is 10Hz to 100kHz at 6W into 3ohms with a conversion efficiency of more than 90 per cent. Sensitivity is 0.7V r.m.s. input for full rated output. The price of the PMI is £14.35, inclusive of post and packing.

For further information contact D-Systems, Dept EPE, Moss Drive, Haslingfield, Cambridge CB3 7JB. Tel: 0223 871555.



Tactile Audio

A new radio cassette player-recorder has arrived onto the market designed specifically for those people with visual or physical disabilities who find consumer products complicated and difficult to operate.

Designed and manufactured by Clarke & Smith Industries and commissioned by the British Wireless for the Blind Fund, this user friendly product incorporates many special features which are of particular benefit to elderly, visually impaired and disabled people.

For example, the three waveband radio cassette - f.m., m.w. and l.w. - has a very simple operating layout. Its large, easy-to-grip operating controls in the high colour contrast of yellow on grey, are generously spaced to be easily distinguishable and carry tactile symbols for easy identification.

An audible rising/falling tuning tone on the digital push button indicates the radio band position, and an audible "cue" and "review" facility helps the user to locate a particular position on a cassette tape. In addition, a large yellow safety knob sits on the end of the aerial, a surprisingly common danger for those with failing sight or with young children.

Along with these special features, this hard-wearing radio cassette has all the facilities such as five preset stations for each waveband, allowing up to fifteen stations to be stored. It has a high quality four inch speaker, is mains or battery operated and is easily serviceable.

For further information contact: Jane Marren, Clarke & Smith Industries, Dept. EPE, Melbourne House, Melbourne Road, Wallington SM6 8SD. Tel: 081 669 4411.

The savings start here!

£1.50
OFF!

Use this coupon to claim a
£1.50 discount on up to
THREE tickets
to the
Christmas
Computer
Shopper
Show



1 - 4 December 1994
Grand Hall, Olympia, London.



Sponsored by Computer Shopper Magazine

Show opening times

Thursday 1 - Saturday 3 December	10.00am - 6pm
Sunday 4 December	10.00am - 5pm

Photocopies not valid. Valid on entry to show only.

I am claiming £1.50 off 1 ☐ or 2 ☐ or 3 ☐ tickets. PLEASE TICK.

TRY THE INTERNET!

You are sure to have heard about the Internet, the information highway and the global village, but do you really know what it means and how you can access it? You can find out more by going to the Christmas Computer Shopper Show at Olympia and visiting Carrera Technology who will allow you to access the network direct from their stand.

On their stand will be displayed the first Internet-ready PCs in the UK with Easynet software and a US Robotics Sportster modem pre-installed. Hooking up to the Net then becomes simply a matter of plugging the machine into a phone line.

As a special show promotion, Carrera Technology will also be offering free vouchers for use in the newly opened central London cafe, Cyberia - the UK's first cybercafe - which has a range of Internet-ready PCs.

To help you visit the show we are pleased to include above a special voucher which allows you £1.50 off the entry ticket price. The show is to be held at the Grand Hall, Olympia, London from the 1st to the 4th of December 1994.

For more information, please contact Helen Sheffield on 081 742 2828.

Lithium saves iceman!

Lithium cells supplied by Saft Nife helped the remarkable Rupert Hadow to return from the polar ice safely after the 32-year-old Scot failed earlier this year to walk 410 miles, unaided, to the North Pole. Temperatures of -45°C and two falls into arctic water ended this year's attempt after 24 days, but the long-life, low-temperature lithium cells, in battery packs assembled by Woolsey Electronics of Bideford, continued to power radiocommunications and satellite navigation equipment perfectly.

Not all applications are as gruelling as the Sector Ice Man Challenge, but Saft Nife's high energy density, lightweight and reliable LSH lithium cells are ideal power sources for emergency applications for medium and high drain use, and where high start-up voltages are required after long storage periods.

For further information contact: Antoinette Leach, Saft Nife Ltd., Dept. EPE, Station Road, Hampton, Middlesex TW12 2BY. Tel: 081-979 7755.

SHOP TALK

with David Barrington

EPE Fruit Machine

Apart from the pre-programmed microcontroller, several other components required to complete the *EPE Fruit Machine* need special mention and may not be obtainable locally.

Starting with the most important device first, the ready programmed PIC16C57 controller chip is available from the authors, price £12. The coloured, self-adhesive front panel overlay is also available from the same source for the sum of £2. Please add 50p for UK p&p and £2.50 for Overseas postage and packing. Orders should be sent to: **Dept EPE, 28 Blisworth Close, Yeadon, Hayes, Middlesex, UB4 9RF. MAIL ORDER ONLY.**

The 0.8in. 7-segment displays must be the "common cathode" types. The ones used in the model are designated HDSP3405. An alternative type is the RS588-960 (code) stocked by **Electromail**, the RS mail order outlet.

The servo motor is the Futaba type FB.S14B and should be stocked by most good model shops. A range of low voltage servos are stocked by **Magenta Electronics** and one of these may work here but they have not been tried in the unit.

The switches with an integral l.e.d. are Maplin type JU04E (red) and JU05F (green). On/off switch also came from above, code JR96E.

The printed circuit board is available from the *EPE PCB Service*, code 914.

Universal Code Lock

The *Universal Code Lock* circuit has been designed to operate with virtually any keyboard as long as it has a matrix formation, i.e. rows and columns, and is not one with a

common connection. Choice of keypad will, of course, depend on application.

The choice of small keypad is quite large and people like **Bull Electrical**, **Greenweld**, **Maplin**, in fact, most of our component advertisers should be able to offer a suitable type. The solenoid/lock mechanism may have to be purchased from your local hardware/DIY store, but someone like Bull or Greenweld may have one hidden away amongst their vast stocks of unusual items.

The custom programmed PIC1654RC microcontroller i.c. is available from the designer - Mail Order Only - for the sum of £9.50 including postage. Customers outside Europe are asked to add an extra £2 for postage. Orders should be sent to: **B. Trepak, Dept EPE, 20 The Avenue, London, W13 8PH.**

The printed circuit for the Code Lock is available from the *EPE PCB Service*, code 922 (See page 975).

Video Modules

All components listed for the Wiper modules and the Audio Mixer, this month's *Video Modules* projects, appear to be "off-the-shelf" items and should be obtainable from your regular component supplier/advertiser. The printed circuit boards are available from the *EPE PCB Service*, codes 916 (Horiz. Wiper), 917 (Vert. Wiper) and 918 (Audio Mixer).

The case shown housing the modules is not specified as it was felt readers may care to choose their own, also it usually sells for over £30. The one used by the author is known as a "1U" type and measures 432mm (W) x 45mm (H) x 254mm (D), the front plate is, of course, 19 inch (482mm)

wide. This was originally purchased many months ago from **Rackz Products** (☎ 0749 840102). Most of our advertisers will be able to offer something similar.

Rodent Repeller

The main outlay for constructors of the *Rodent Repeller* project will be the purchase of the Xenon flash unit. This was selected from the range of "burglar alarm accessories" stocked by **Maplin** and is the "clear" version of the low profile Xenon Flasher, code ZC16S (clear).

The "scare" buzzer was also obtained from the above source and is the High Power Buzzer, code FK84F. This has a claimed operating range of 3V to 24V d.c. and an output power of 103dB at one metre. One further point, the sounder must be the type with internal drive circuitry - other types will not work here.

It is important to use a good quality mains transformer which also has an adequate current rating. This will remain cool in operation during continuous use. Suitable transformers are listed by **Greenweld** (code 88-0255) and **Maplin** (code YN15R). The printed circuit board is available from the *EPE PCB Service*, code 913. Finally, pay special attention to the notes about **mains wiring**, its the unwanted visitors we want to remove!

Spacewriter Wand

Another special pre-programmed chip is called for this month in the novel *Spacewriter Wand*, the first of our offerings for the festive season. This device is only available from **Magenta**.


A complete kit of parts, including p.c.b. and chip loaded with the message Merry Xmas, for the *Spacewriter Wand* is available from **Magenta** for the sum of £16.99 plus £3 post and packing. **Magenta Electronics, Dept EPE, 135 Hunter Street, Burton-on-Trent, Staffs, DE14 2ST. Kitcode 849.**

The printed circuit board is obtainable from the *EPE PCB Service*, code 921.

QUANTEK FC2000

ULTRA HIGH SENSITIVITY FREQUENCY COUNTER/FINDER

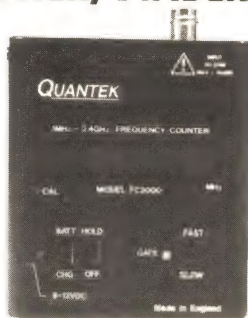- ★ 1MHz - 2.4GHz
- ★ Sensitivity less than 1mV from 10MHz to 800MHz
- ★ 2 Gate/measurement periods
- ★ Display hold switch
- ★ Bright 8 digit LED display
- ★ Charge & Gate LEDs
- ★ Aluminium case - 100 x 87 x 28mm
- ★ 700mAh Ni-cad batteries
- ★ Maximised sensitivity for measuring transmitted radio signals at a distance
- ★ Supplied with mains adaptor/charger & telescopic antenna



ONLY **£119**
+ £5 P&P
MADE IN UK
12 Months Guarantee

TO ORDER CALL
021 457 7994
FAX ORDERS **021 457 9745**

QUANTEK ELECTRONICS


1678 BRISTOL ROAD SOUTH, BIRMINGHAM B45 9TZ





OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX ★ 031 667 2611

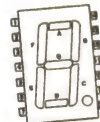The supplier to use if you're looking for:-



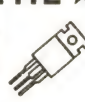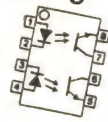A WIDE RANGE OF
★ COMPONENTS AIMED AT THE ★
HOBBYIST



★ COMPETITIVE VAT INCLUSIVE ★
PRICES



★ MAIL ORDER - generally by ★
RETURN OF POST



★ FRIENDLY SERVICE ★



OPEN:

Monday-Thursday 9.15 - 6.00


Friday 9.15-5.00

Saturday 9.30-5.00



EASY-PC, Schematic and PCB CAD

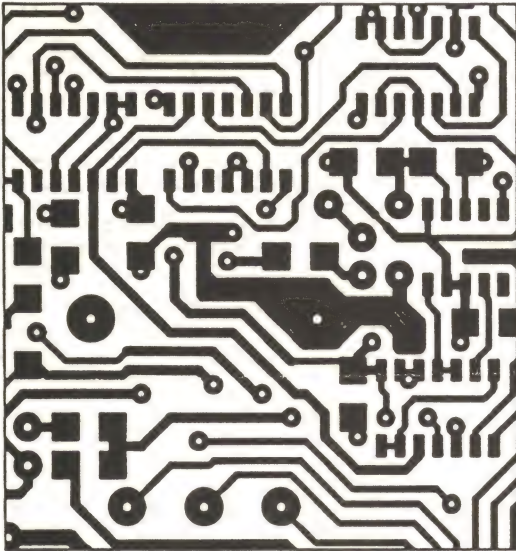Over 18,000 Installations
in 80 Countries World-wide!




- Runs on:- PC/XT/AT/ 286/ 386/ 486 with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design:- Single sided, Double sided and Multi-layer (8) boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Tech Support - free.
- Superbly easy to use.

**Still
Only
£98.00!**

Plus P&P+VAT




**BRITISH
DESIGN
AWARD
1989**

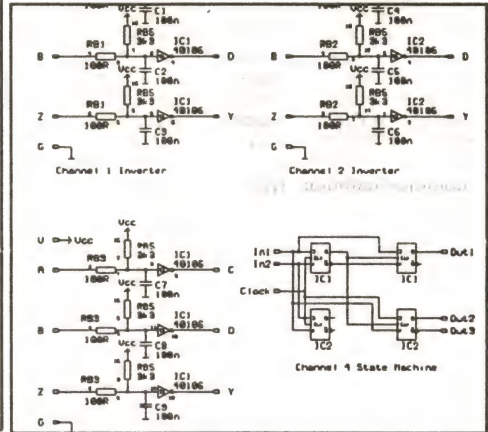

Options:-500 piece Surface Mount Symbol Library £48,
1000 piece Symbol Library £38, Gerber Import facility £98.

Electronic Designs Right First Time?

Integrated Electronics CAD

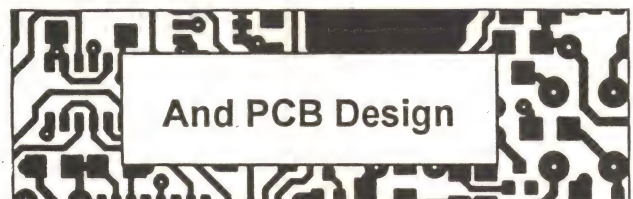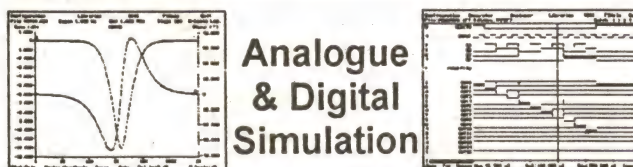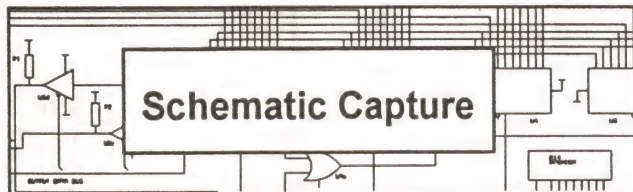

Affordable Electronics CAD

EASY-PC: Entry level PCB and Schematic CAD.	\$195.00	£98.00
EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III and PULSAR.	\$375.00	£195.00
EASY-PC Pro' XM: Extended Memory Version - Greatly increased capacity	\$475.00	£245.00
PULSAR: Digital Circuit Simulator ~ 1500 gate capacity.	\$195.00	£98.00
PULSAR Professional: Digital Circuit Simulator ~ 50,000 gate capacity.	\$375.00	£195.00
ANALYSER III: Linear Analogue Circuit Simulator ~ 130 node capability	\$195.00	£98.00
ANALYSER III Professional: Linear Analogue Circuit Simulator ~ 750 node capability.	\$375.00	£195.00
Z-MATCH for Windows: NEW Windows based Smith-Chart program for RF Engineers.	\$475.00	£245.00
FILTECH: Active and Passive Filter Design program	\$275.00	£145.00
We operate a no penalty upgrade policy. You can upgrade at any time to the professional version of a program just for the difference in price.		
	US\$ prices include Post and Packing.	UK£ prices exclude P&P and VAT

Prices from UK£195 / US\$375

For full information, please write, phone or fax:-

Number One Systems

UK/EEC: Ref. EVD, HARDING WAY, ST.IVES, CAMBS., ENGLAND, PE17 4WR.

Telephone UK: 0480 461778 (7 lines) Fax: 0480 494042 International +44 480 461778

USA: Ref. EVD, 1795 Granger Avenue, Los Altos, CA 94024


Telephone/Fax: (415) 968 9306

- TECHNICAL SUPPORT FREE FOR LIFE
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

MASTERCARD, VISA Welcome.

CIRCUIT SURGERY

ALAN WINSTANLEY

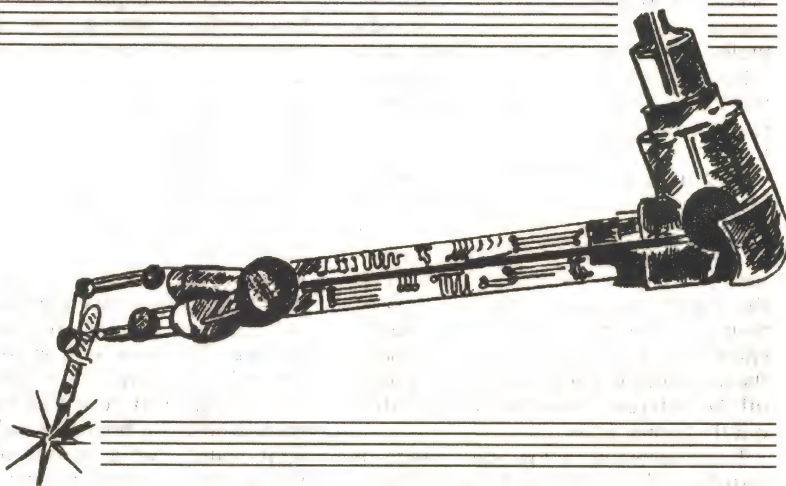

Welcome once again to our popular column devoted to readers' problems and circuit suggestions. This month, we offer some advice to those constructors who fabricate their own printed circuits boards at home, and help with a query on winding your own inductors.

THIS month's edition of *Circuit Surgery* marks my first year at the helm of our "agony column" – I hope readers continue to find it varied, interesting and helpful. Remember, this is *your* column, so if you have any suggestions for circuit ideas which you would like us to investigate, or any topical comments which you would like to make, please write to *Circuit Surgery* at the editorial address.

All wound up

We have a mixture of both theoretical and practical topics this month, starting with a query from a budding radio amateur in South Africa. **Mark Lamprecht** of Durban, 4001 Natal posed a question relating to the techniques for winding simple coils.

I've just started a course in Amateur Radio and am really keen to build my own equipment. However, I've discovered a problem when trying to construct inductors and hope you can offer some advice. Suppose an inductor is, say, 100µH in value – then how many turns of wire is that? What gauge wire can I use? Is there a formula that one could apply or is it a case of hit and miss? I would be very grateful for any helpful suggestions you could offer.

There isn't a particular problem when winding inductors, thanks partly to the availability of ferrite core kits which permit you to custom-wind these components to a high degree of accuracy. For example the "RM" series or similar ferrite cores are available in kit form from several of our advertisers (see later).

The unit of inductance is the Henry, symbol H, named after the American physicist Joseph Henry who was credited with the discovery of the principle of self-inductance in 1832 (data: Microsoft Encarta™). The usual units of measurement of inductance are these:

milliHenry (mH, 1×10^{-3} Henrys)

microHenry (µH, 1×10^{-6} Henrys)

nanoHenry (nH, 1×10^{-9} Henrys)

The inductance of a coil is proportional to the *square* of the number of turns on the core, and it's desirable to

use the largest diameter gauge of enamelled copper wire which can be accommodated on the chosen core. A larger diameter wire has a larger cross sectional area together with a lower electrical resistance than a narrower gauge. So it's best to wind on the thickest wire possible which the core will allow, for the specified number of turns.

This brings us to the next question, how many turns? The formula you need is the following:

$$N = \sqrt{\frac{L}{A_L}}$$

where N is the required number of turns, L is the desired inductance and A_L is the *specific inductance* of the ferrite core – in effect, a measure of the inductance per turn.

A useful data sheet no. K5774 is published by RS/ Electromail which describes their own product selection. If you know the number of turns required, the data sheet will help to choose the appropriate core and also the gauge of the wire.

Praying mantissa!

The parameter A_L is an inductance factor which is specific to each type of core. It could range typically from 160nH to 400nH or more. A particular trap in the above equation concerns the value of L which, if the data specifies A_L in nH, must be stated in *nanoHenry*s also. If for example Mark's coil is 100µH, you can convert this to nanoHenry's quite easily using "scientific notation" which saves having to write lots of noughts. Here's a quick reminder:

$$\begin{aligned} L &= 100\mu\text{H} = 100 \times 10^{-6} \text{ Henrys} \\ &= 1 \times 10^{-4} \text{ Henrys in scientific notation. Convert this to nH.} \end{aligned}$$

Mathematicians will know that the "1" is termed the mantissa whilst the 10^{-4} is the exponent. In order to multiply numbers together using scientific notation, one multiplies the mantissas together whilst adding the powers (exponents). Recall that nanoHenry's are

expressed as 10^{-9} Henrys. Working backwards from all this, a value of 1×10^{-4} Henrys equals $1 \times 10^5 \times 10^{-9}$ Henrys – i.e. 1×10^5 *nanoHenry*s. The less academic conversion factor is simply $1\text{nH} = 0.001\mu\text{H}$, implying that 100µH is equivalent to 100,000 nH (1×10^5). Take your pick, depending on your mathematical inclinations.

The choice of ferrite core may sometimes depend on the frequency of operation. In some applications (e.g. power supply filters), the d.c. current becomes relevant too and this also determines the wire gauge. For this example let's select the smallest pot core in the range, which has a value for A_L of 160nH.

To fabricate a 100µH inductor, we can use the above formula to calculate the required number of turns and we obtain a figure of just 25 turns (i.e. the square root of 625). Tables included in the data sheet tell us that the specified pot core (RS Order Code 228-214) will accept 25 turns of a maximum wire diameter of 0.56mm (approximately 24 standard width gauge), so that's the optimum wire gauge to plumb for when selecting the enamelled copper wire.

Several of our regular advertisers stock a comprehensive range of inductors; ferrites and other r.f. components. In particular, ElectroValue Ltd (☎0784 442253) deserve a special mention because of their comprehensive range of Siemens ferrites whilst CirKit Distribution (☎0992 448899) are the UK stockists of Toko products.

Several others, including Maplin, also list a useful selection of components. You could possibly check out a modest book entitled *Coil Design and Construction Manual* published by Babani which is listed by our own *Direct Book Service* (code BP160), price £2.50 plus P&P. This might help further.

P.C.B. techniques

Back in the September issue I touched on the subject of making your own printed circuit boards (p.c.b.s) using the ultra violet system. Whilst the *EPE PCB*

Service is as popular as ever, we're of course well aware that many readers do prefer the satisfaction of etching and fabricating the boards for themselves at home. I've received several letters from readers asking for some advice on this topic.

If you decide to dabble with p.c.b. production yourself you can adopt one of two approaches. Either use a "direct etch" method, whereby etch resistant transfers are physically applied to the copper foil of a "blank" p.c.b. — then immerse the whole board in ferric chloride etchant for a period to remove the unwanted copper. Afterwards, polish off the etch resist transfers and then drill out the copper pads.

I can recommend the *Alfac* range of transfers, which are listed both by Greenweld (☎0703 236363) and ElectroValue Ltd (☎0784 442253). They are used exactly like rub-down lettering.

This method is fine for quicker one-off boards but there are several drawbacks: the artwork is destroyed each time after etching, so it's really irksome if you need to produce a small quantity of boards; if you find you've made a mistake, error correction is impossible after etching, so you have to start all over again — the same applies if you find that you want to modify the circuit after performing some circuit trials. You can't save the artwork for reference in the future, and it's extremely inconvenient if not impossible to originate the artwork if the circuit is complex.

To relieve this tedium you can use the ultraviolet (UV) technique, though it's more expensive and a little more complex. For the benefit of less experienced readers, Fig. 1 is a basic illustration showing how the UV system works.

The desired copper track pattern is first drafted onto a clear acetate or polyester film, again *Alfac* transfers are ideal here. This means that the artwork can be amended now or in the future, and can be re-used to produce more of the same design at a later date. You can also copy magazine artwork using the same system, by tracing it from the page.

A blank p.c.b. is used which has to be coated with a special UV photo-sensitive lacquer. Either buy pre-sensitised boards (which I much prefer to work with) or use a special aerosol spray-on coating. The next step is to place the artwork "positive" over the prepared board (right way round of course!) and then expose the board to an ultraviolet light source for a period of typically between ten to twenty minutes or so.

The exposed board is subsequently developed either using a proprietary developer or a weak solution of Sodium Hydroxide (domestic caustic soda). This will dissolve away the UV lacquer which has been subjected to UV light, so all that will remain is photo-resist lacquer which had been masked by the p.c.b. artwork. The lacquer is resistant to etchant and the board can be etched in ferric chloride in the usual way.

With the unwanted copper now removed, a quick swab of acetone (nail varnish remover) afterwards will dissolve away the lacquer to reveal the copper foil track pattern, and the board may now be drilled to obtain a really crisp, professional finish.

P.C.B.s exposed!

Of course, you need a UV light source for this technique and you might consider making your own. I previously suggested the *UV Exposure Unit* we

published back in October 1991. Reader **Frank Bagshawe** of Buxton, Derbyshire had a few useful tips for those contemplating building an exposure unit for themselves:

The project you recommended for the construction of a UV light box is straightforward apart from the winding of the transformer. My difficulties with winding this led me to purchase a fluorescent tube driver from Maplin (Auto Light YZ35Q), similar types are also available from Greenweld as single or twin tube types L1652 or L1655.

The 8W UV tubes themselves were sourced from Maplin (FJ55K). This combination of parts works satisfactorily from a 12V mains power supply. However, I have come across boards which are said to react to daylight — could you give a few tips on exposure times for these boards?

Thanks for the information on your alternative approach to making a UV light unit. As far as timing's concerned, when you're exposing a photo-resist board to ultra violet light it's essential that the UV is allowed to penetrate through the entire depth of the lacquer so that it reacts thoroughly.

Exposure value

Failure to expose for long enough will result in just the surface layer of the lacquer developing away, and a residue of resist will remain on the board rendering it useless for etching. It takes a little experience to familiarise oneself with the technique, and how long you expose for depends on the combination of UV power, the thickness of the photo-resist lacquer and the distance between the light source and the board.

Mr. Bagshawe mentioned that some boards are available which could be exposed using ordinary daylight. Perhaps so — but it's strictly a matter of trial and error as it relies on the UV content of natural daylight. It depends on the time of day (and year), the weather, and where you live!

I doubt if anyone will ever obtain consistent and repeatable results simply by using daylight, especially in the British climate where the only thing predictable about it is that it's unpredictable! Without a doubt an exposure unit will save a lot of heartache — and you can do it at night!

It's probably a good idea to err on the side of caution by over-exposing the board somewhat, to ensure that the photo-resist reacts all the way through. In theory, serious *over-exposure* will only cause problems when the UV light penetrates *through* the artwork if the light-proof symbols are not sufficiently opaque, or by undermining the transfers at their edges and affecting the lacquer underneath.

The latter is only likely to be a problem if your design has very fine copper conductors: they may then be etched away completely in places. Under-exposure is likely to be much more of a nuisance.

I find that etch-resistant aerosol sprays can cause a variety of problems. Because the coating on the p.c.b. may be considerably thicker (and not necessarily uniform), exposure times may be incon-

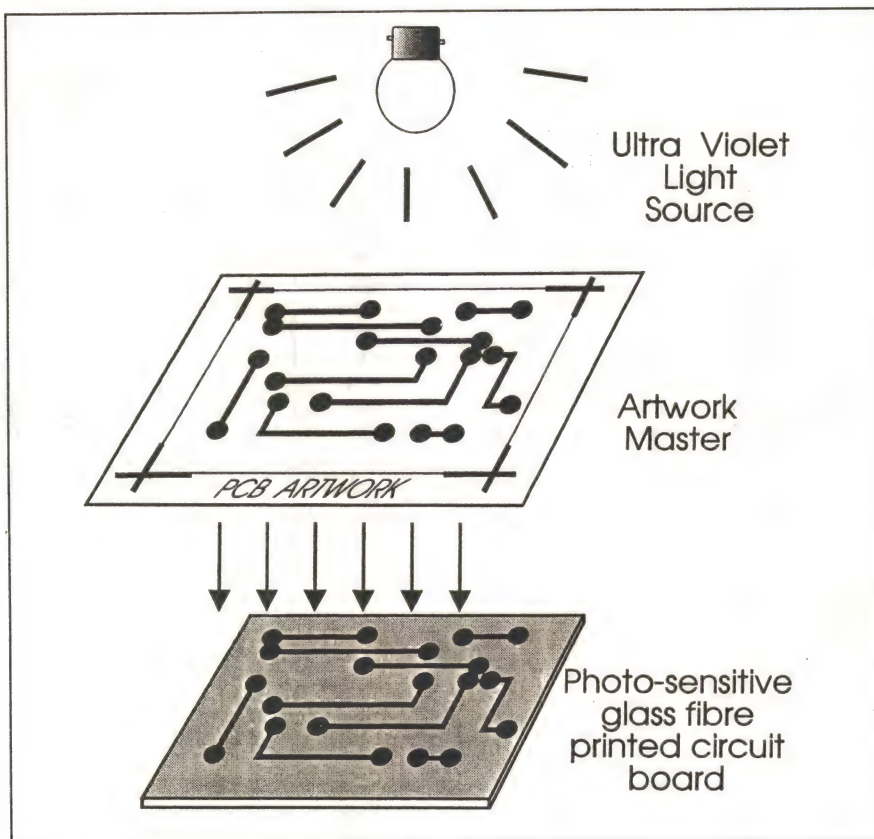


Fig. 1. Basic UV method of p.c.b. fabrication: 1 Expose to UV light through artwork. 2 Develop. 3 Etch.

sistent and sometimes I find that I have under-exposed.

It's wise to experiment with some scrap board to find the optimum exposure times and generally become acquainted with the behaviour of the spray lacquer. A period of 20 to 30 minutes exposure has been known, but it depends on the power of your UV exposure unit. Sprays are handy though if you have ruined a pre-sensitised board for any reason, when at least you can try to re-use the blank board again.

My own UV unit has two 8W tubes which is fine for my needs, and a period of roughly 15 minutes seems average for ready-coated boards. Incidentally, I described a simple constructional project *UV Exposure Timer* in the July 1992 issue of *Everyday Electronics*. The mains-powered unit offers switched time delays between 2 to 24 minutes for your ultra violet light box and helps to ensure that you avoid accidentally under-exposing your boards. The circuit board (only) for this project is still available from the *EPE PCB Service*, Code No. 797.

Alternative UV unit

Steve Knight – author of the excellent *Calculation Corner* series which has been widely applauded by readers – dropped in and suggested an alternative for a DIY mains powered UV unit. Steve suggests:

I found the best bet is to get hold of an ordinary 300W UV Sunlamp from a chemists or wherever, and fit it in an open box as per the sketch of Fig. 2. The dimensions aren't critical and the box is made from odd pieces of chipboard.

Paint the inside matt black and off you go! I suggest give the lamp a few minutes to warm up, and with the board about 10 inches/ 25cms away, I find that five minutes is the required time.

It's worth investigating Steve's idea as the cost savings over a commercial unit are substantial. You *MUST* however take suitable precautions when dealing with ultra violet light. It can damage eyesight and therefore you should not gaze at the light with the naked eye. (We strongly suggest that, for personal safety, a curtain or hinged flap is placed across the front opening of the unit. Ed.)

I would also warn novices of the dangers of using ferric chloride etchant – please wear gloves and goggles and avoid splashing this corrosive fluid on anything.

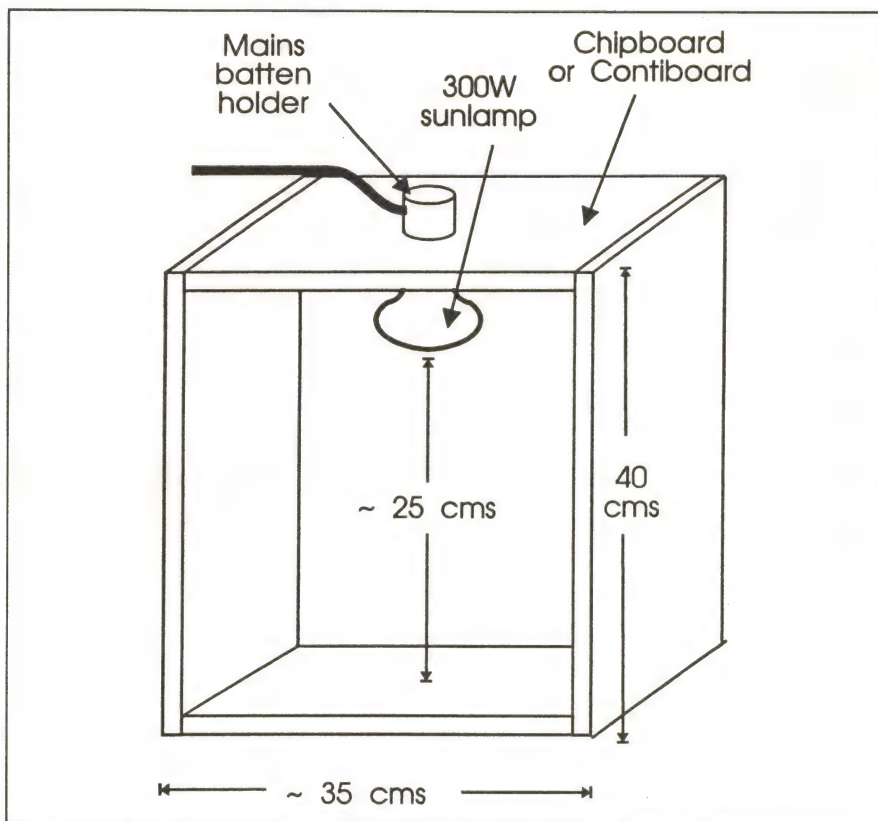


Fig. 2. UV exposure cabinet made with surplus chipboard and a 300W sunlamp. Take care not to view the UV light with the naked eye.

GCSE Support

Many GCSE Electronics/Design & Technology students write to the *Surgery* at this time of year seeking assistance with their chosen project. I'm only too happy to pass on a few pointers wherever possible, but *Circuit Surgery* does not provide specific circuits for projects as it is imperative that students research and develop the circuitry for themselves.

Our 12-part educational series *Teach-In '93* was specially written to support GCSE and Advanced Level Electronics, and as part of the course we designed the *Teach-In Mini Lab* and the advanced *Micro Lab* training units. We're pleased to say that because of demand we have now released the series as a complete book, available from your local *New-sagent* or from the *Direct Book Service*. Hobbyists and constructors will also find it useful for brushing up on theory, and the completed *Mini Lab* forms a complete test-bed to help you develop your own circuits.

Finally this month, don't forget our re-introduced *Ingenuity Unlimited* column – if you have any circuit ideas of your own for possible inclusion then please send a brief description (preferably typewritten or word-processed) with neat diagrams showing relevant component values, to myself at the following address. Ideas must be the readers' own work and we will pay between £10 to £50 for all circuits used depending on their length and technical merit. We will publish a selection at suitable intervals.

Send your circuit ideas to Alan Winstanley, *Ingenuity Unlimited*, *Everyday with Practical Electronics*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BH21 1PF. Or you can write to *Circuit Surgery* at the same address.

Next Time

In the next *Surgery*, I hope to look at regulated power supply design together with heatsink calculations, and more!

EVERYDAY WITH PRACTICAL ELECTRONICS

NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of
Everyday with Practical Electronics for me each month.

Everyday with Practical Electronics is published on the first Friday of each month and distributed by Seymour.
Make sure of your copy of EPE each month – cut out this form, fill it in and hand it to your newsagent.

Signed

Name and Address
(BLOCK CAPITALS PLEASE)

Tandy®

YOUR ELECTRONIC HOBBY SHOP Techcessories



**Dual Display
DMM**

£49.99

Features large LCD Display with 32 segment bargraph. Data hold, range hold, diode and continuity check.
22-167



**Jumbo Display
DMM**

£29.99
Until 24/12/94 Normally £49.99

Features JUMBO LCD display, capacitance and transistor HFE checks, 20 megohms resistance.
22-7215



**FET
Multimeter**

£44.99

Features continuity sounder, jumbo 5" tri-colour scale, fuse protection, 1V and 100µA DC ranges.
22-220



**Range-Doubler
Multimeter**

£34.99

50KDC sensitivity, 20 megohms resistance. Range doubler switch gives greater accuracy.
22-214



DMM With PC Interface
ONLY £69.99
With this voucher

Normal Price £79.99

△ Features 41-dot Bargraph Display

△ Frequency Counter To 200 KHz

△ Includes PC Software And Connection Cable
22-182

£10 OFF VOUCHER

NAME _____ ADDRESS _____ POST CODE _____
Present this voucher at any Tandy store or participating Dealer. May not be combined with any other coupon offer. Only one voucher per visit. No photocopies accepted. Not redeemable for cash. Offer expires on 31/12/94. InterTAN UK Ltd, Tandy Centre, Leamore Lane, Walsall, West Midlands WS2 7PS

Power Supply

NEW LOW PRICE

£29.99

△ 13.8 VDC Regulated Supply.
Rated At 5 Amps Continuous Output
△ Ideal For Powering Most Mobile CB's
Car Stereos etc 22-7101



**WIDE RANGE OF COMPONENTS IN STOCK
WIDE RANGE OF HOBBY KITS IN STORE**

**Tandy
there's
more**

welcome



over 500 stores and dealers nationwide

Credit facilities subject to acceptance. Full written details available from InterTAN UK Ltd, Tandy Centre, Leamore Lane, Walsall, WS2 7PS. Typical APR 29.8 (Variable). Payment by direct debit. Credit facilities may not be available in all Dealer outlets. Prices may vary at dealers. Offers subject to availability.

SOLDERING IRONS

FROM £4.99

Ⓐ Gas Soldering Iron.

Provides up to 60 minutes of use per fill. Refillable in seconds using butane lighter gas.

64-2160.....£19.99

Ⓑ 17 Watt Soldering Iron.

64-7118.....£14.99

Ⓒ 12 Watt Soldering Iron.

Features non-slip finger section for a reliable grip.

64-7113.....£12.99

Ⓓ 20 Watt Soldering Iron.



As above.

64-7114.....£14.99

Ⓔ 30 Watt/12VDC Soldering Iron.

Ideal for people on the move as this soldering iron can be plugged into a car cigarette lighter.

64-2105.....£4.99

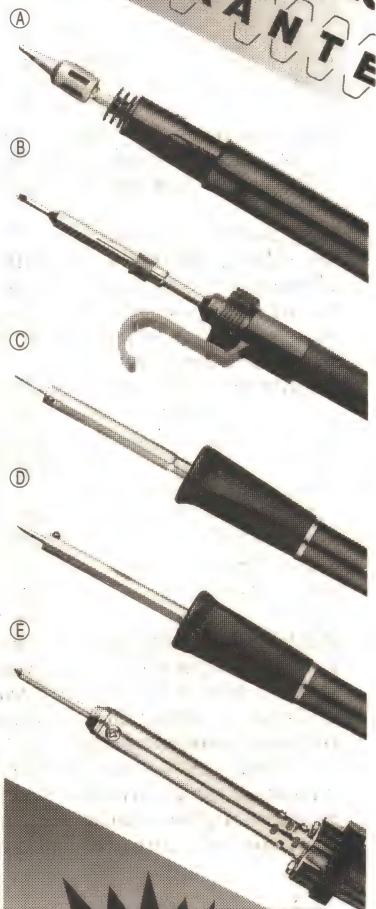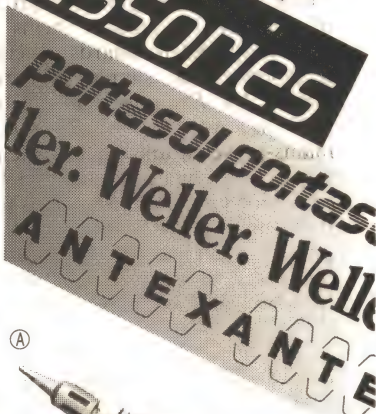

**FULL CATALOGUE
AVAILABLE
FROM YOUR
LOCAL TANDY
STORE**

Electronics from the Ground Up

Mike Tooley, BA

Part 3

ELECTRONICS from the Ground Up is designed to provide you with a comprehensive and up-to-date introduction to the world of electronics. The series is based on *Electronics Workbench*, a remarkable new software package that lets you use your PC to build and test a wide range of circuits. A special low-cost version of this software (with all the parts and test instruments

needed to complete the series) is available to readers, see later for how to order.


In this third part we introduce semiconductor diodes. We investigate the behaviour of half-wave and full-wave rectifiers and develop these into complete power supply circuits incorporating smoothing and voltage regulation.

SEMICONDUCTORS

Atoms contain both negative charge carriers (electrons) and positive charge carriers (protons). Electrons each carry a single unit of negative electric charge whilst protons each exhibit a single unit of positive charge. Since atoms normally contain an equal number of electrons and protons, the net charge present will be zero. For example, if an atom has eleven electrons, it will also contain eleven protons. The end result is that the negative charge of the electrons will be exactly balanced by the positive charge of the protons.

Electrons are in constant motion as they orbit around the nucleus of the atom. Electron orbits are organised into shells. The maximum number of electrons present in the first shell is two, in the second shell eight, and in the third, fourth, and fifth shells it is 18, 32, and 50 respectively. In electronics, only the electron shell furthestmost from the nucleus of an atom is important. It is important to note that the movement of electrons only involves those present in the outer *valence shell*.

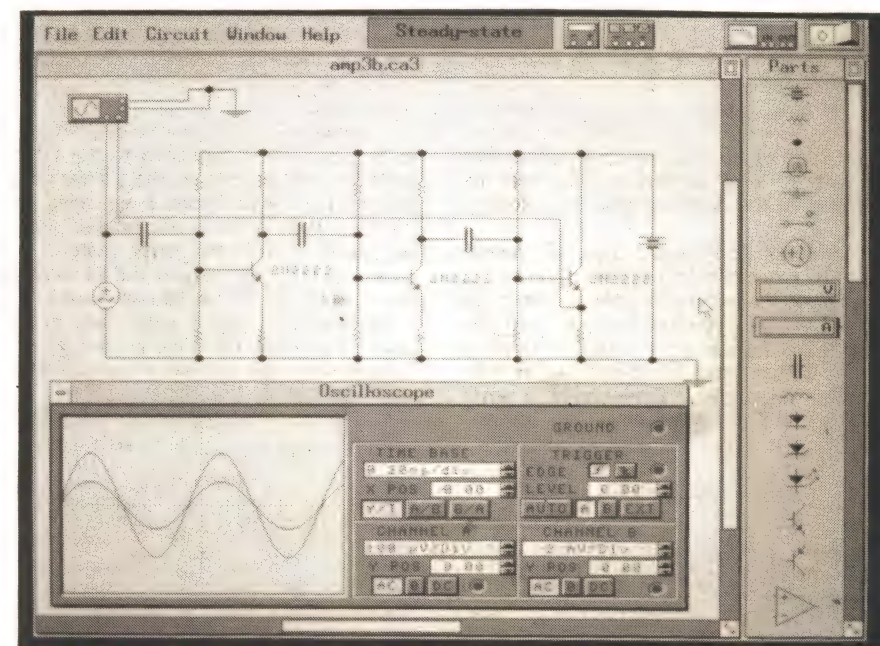If the valence shell contains the maximum number of electrons possible the electrons are rigidly bonded together and the material has the properties of an insulator. If, however, the valence shell does not have its full complement of electrons, the electrons can be easily loosened from their orbital bonds, and the material has the properties associated with an electrical conductor.



An isolated silicon atom contains four electrons in its valence shell. When silicon atoms combine to form a solid crystal, each atom positions itself between four other silicon atoms in such a way that the valence shells overlap from one atom to another. This causes each individual valence electron to be shared by two

atoms, as shown in Fig. 3.1. By sharing the electrons between four adjacent atoms, each individual silicon atom *appears* to have eight electrons in its valence shell. This sharing of valence electrons is called *covalent bonding*.

In its pure state, silicon is an insulator because the covalent bonding rigidly holds all of the electrons leaving no free (easily loosened) electrons to conduct current. If, however, an atom of a different element (i.e., an *impurity*) is introduced that has five electrons in its valence shell, a surplus electron will be present. These *free electrons* become available for use as *charge carriers* and they can be made to move through the lattice by applying an external potential difference to the material.

Similarly, if the impurity element introduced into the pure silicon lattice has three electrons in its valence shell, the absence of the fourth electron needed for proper covalent bonding will produce a number of spaces into which electrons can fit. These spaces are referred to as *holes*. Once again, current will flow when an external potential difference is applied to the material.

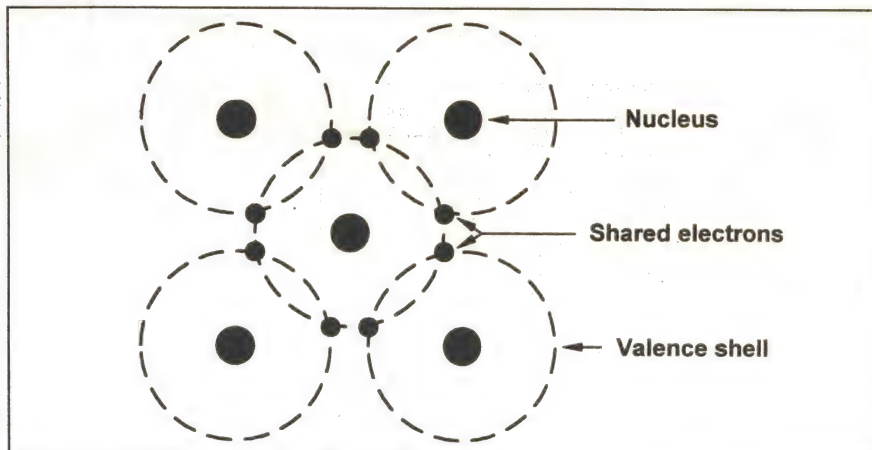


Fig. 3.1 Lattice showing covalent bonding.

Regardless of whether the impurity element produces surplus electrons or holes, the material will no longer behave as an insulator neither will it have the properties that we normally associate with a metallic conductor. Instead, we call the material a *semiconductor* – the term simply indicates that the substance is no longer a good insulator or a good conductor but is somewhere in between!

The process of introducing an atom of another (impurity) element into the lattice of an otherwise pure material is called *doping*. When the pure material is been doped with an impurity with five electrons in its valence shell (i.e., a *pentavalent impurity*) it will become an *n-type* material. If, however, the pure material is doped with an impurity having three electrons in its valence shell (i.e., a *trivalent impurity*) it will become *p-type* material. *N-type* semiconductor material contains an excess of negative charge carriers, and *p-type* material contains an excess of positive charge carriers.

DIODES

When a junction is formed between *n-type* and *p-type* semiconductor materials, the resulting device is called a diode. This component offers an extremely low resistance to current flow in one direction and an extremely high resistance to current flow in the other. This characteristic allows the diode to be used in applications that require a circuit to behave differently according to the direction of current flowing in it.

An ideal diode would pass an infinite current in one direction and no current at all in the other direction. In addition, the diode would start to conduct current when the smallest of voltages was present. In practice, a small voltage must be applied before conduction takes place. Furthermore a small *leakage current* will flow in the "reverse"

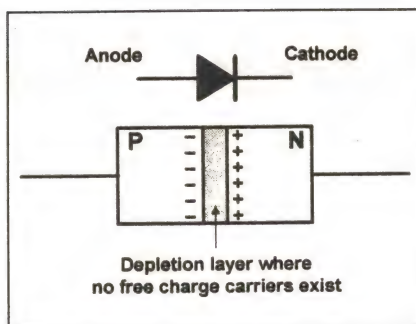


Fig. 3.2 P-N junction diode.

direction. This leakage current is usually a very small fraction of the current that flows in the "forward" direction.

If the *p-type* semiconductor material is made positive relative to the *n-type* material by an amount greater than its *forward threshold voltage* (about 0.7V if the material is silicon and 0.2V if the material is germanium), the diode will freely pass current. If, on the other hand, the *p-type* material is made negative relative to the *n-type* material, virtually no current will flow unless the applied voltage exceeds the maximum (breakdown) voltage that the device can withstand. Note that a normal diode will be destroyed if its *reverse breakdown voltage* is exceeded.

A semiconductor junction diode is shown in Fig. 3.2. The connection to the *p-type* material is referred to as the *anode* whilst that to the *n-type* material is called the *cathode*. With no externally applied potential, electrons from the *n-type* material will cross into the *p-type* region and fill some of the vacant holes. This action will result in the production of a region either side of the junction in which there are no free charge carriers. This zone is known as the *depletion region*.

A junction diode in which the anode is made positive with respect to the cathode is shown in Fig. 3.3. In this *forward-biased*

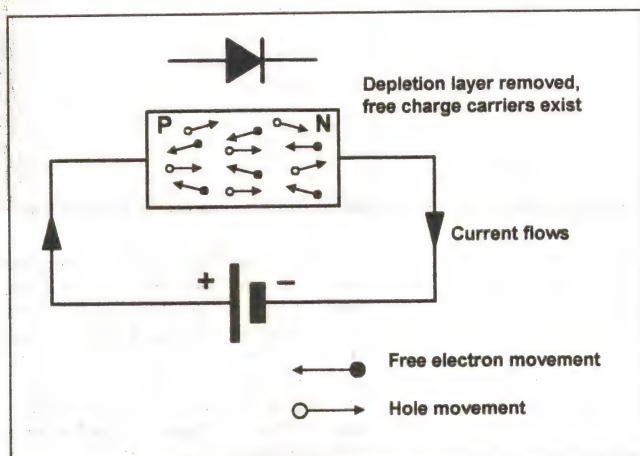


Fig. 3.3 Forward biased P-N junction.

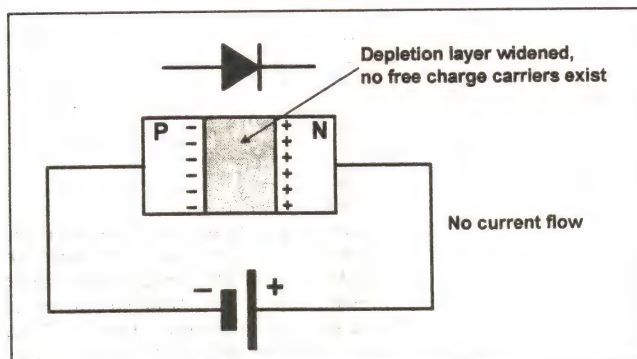


Fig. 3.4 Reverse biased P-N junction.

condition, the diode freely passes current. A diode with the cathode made positive with respect to the anode is shown in Fig. 3.4. In this *reverse-biased* condition, the diode passes a negligible amount of current. In the freely conducting forward-biased state, the diode acts rather like a closed switch. In the reverse-biased state, the diode acts like an open switch.

If a positive voltage is applied to the *p-type* material, the free positive charge carriers will be repelled and they will move away from the positive potential towards the junction. Likewise, the negative potential applied to the *n-type* material will cause the free negative charge carriers to move away from the negative potential towards the junction.

When the positive and negative charge carriers arrive at the junction, they will attract one another and combine (recall that unlike charges attract). As each negative and positive charge carrier combine at the junction, a new negative and positive charge carrier will be introduced to the semiconductor material from the voltage source. As these new charge carriers enter the semiconductor material, they will move toward the junction and combine. Thus, current flow is established and it will continue for as long as the voltage is applied.

As stated earlier, the forward threshold voltage must be exceeded before the diode will conduct. The forward threshold voltage must be high enough to completely remove the depletion layer and force charge carriers to move across the junction. With silicon diodes, this forward threshold voltage is approximately 0.6V to 0.7V. With germanium diodes, the forward threshold voltage is approximately 0.2V to 0.3V.

Typical characteristics for small germanium and silicon diodes are detailed in Fig. 3.5. It is worth noting that diodes are limited by the amount of forward current and reverse voltage they can withstand. This limit is based on the physical size and construction of the diode.

In the case of a reverse biased diode, the *p-type* material is negatively biased relative to the *n-type* material. In this case, the negative potential applied to the *p-type* material

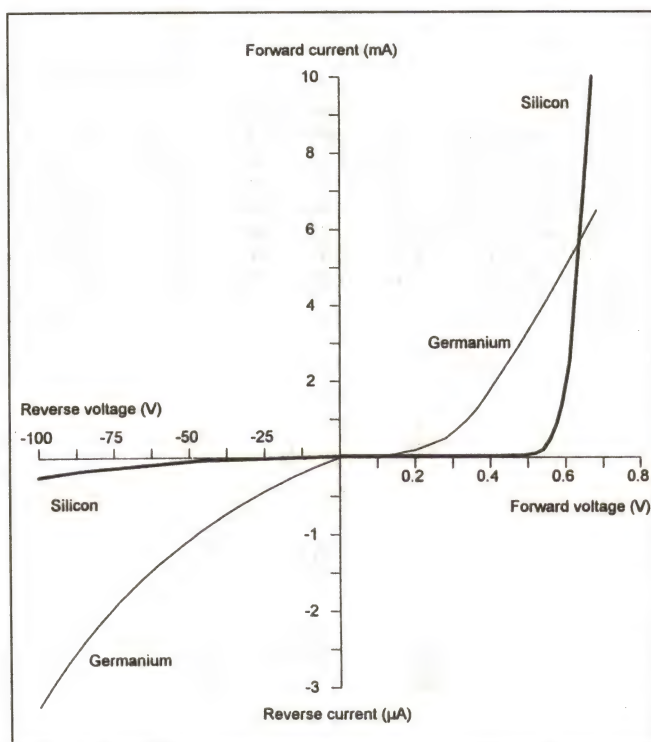


Fig. 3.5 Typical diode characteristics.

attracts the positive charge carriers, drawing them away from the junction. Likewise, the positive potential applied to the *n*-type material attracts the negative charge carriers away from the junction. This leaves the junction area depleted; virtually no charge carriers exist. Therefore, the junction area becomes an insulator, and current flow is inhibited.

The reverse bias potential may be increased to the reverse breakdown voltage for which the particular diode is rated. As in the case of the maximum forward current rating, the reverse breakdown voltage is specified by the manufacturer. The reverse breakdown voltage is usually very much higher than the forward threshold voltage.

A typical general-purpose diode may be specified as having a forward threshold voltage of 0.6V and a reverse breakdown voltage of 200V. If the latter is exceeded, the diode may suffer irreversible damage. It is also worth noting that, where diodes are designed for use as rectifiers, manufacturers often quote peak inverse voltage (p.i.v.) or maximum reverse repetitive voltage rather than maximum reverse breakdown voltage.

Practical assignment 3.1: Diode characteristics

In this practical assignment you will investigate the characteristics of a typical silicon diode.

Objectives:

- 3.1.1 To plot the forward characteristic graph for a silicon diode
- 3.1.2 To estimate the forward voltage drop for a silicon diode at given values of current

Instructions:

1. Connect the circuit shown in Fig. 3.6 using a 0.6V battery.

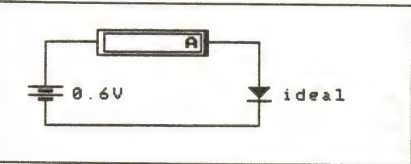


Fig. 3.6. Circuit for Assignment 3.1.

2. Switch on the power to your circuit and measure the current flowing. Record the value of current in Table 3.1.
3. Repeat steps 1 and 2 using battery voltages of 0.625V, 0.65V, 0.675V, 0.7V, 0.725V and 0.75V. Measure and record the current for each value of applied voltage.
4. Use the results from Table 3.1 to plot a graph showing forward current (mA) plotted against applied voltage (V).
5. Use the graph to determine the forward voltage drop for a current of (a) 1mA, (b) 10mA, and (c) 100mA.

Conclusions:

To what extent have the objectives for this assignment been met? Comment on

Table 3.1 Measured values for Assignment 3.1

Voltage (V)	0V	0.6V	0.625V	0.65V	0.675V	0.7V	0.725V	0.75V
Current (A)	0							

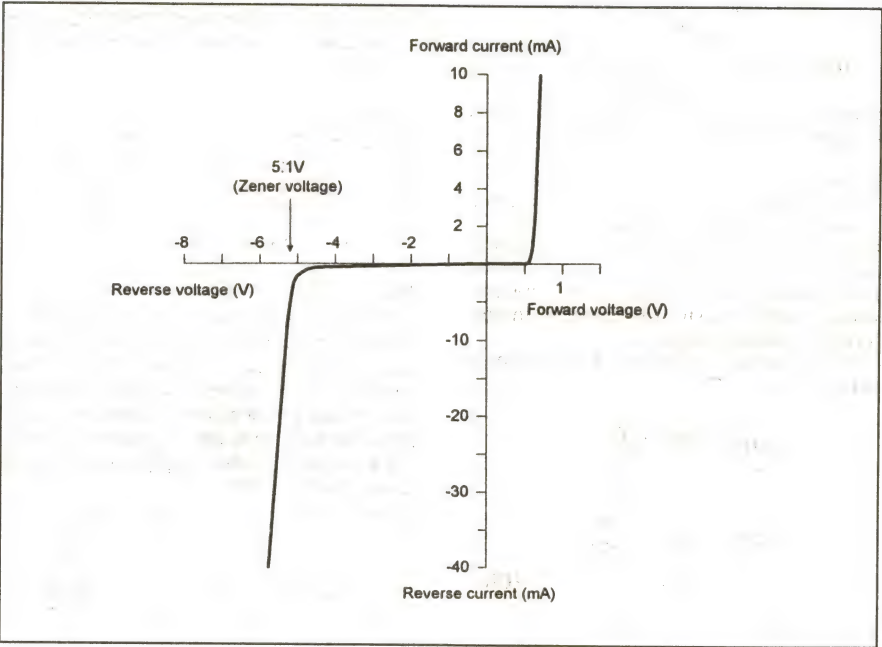


Fig. 3.7 Typical characteristics for a 5.1V Zener diode.

the shape of the graph. Is the shape similar to the one you would expect? If not, why not?

ZENER DIODES

Zener diodes are heavily doped silicon diodes which, unlike normal diodes, exhibit an abrupt reverse breakdown at relatively low voltages (typically less than 6V). A similar effect occurs in less heavily doped diodes. These *avalanche diodes* also exhibit a rapid breakdown with negligible current flowing below the avalanche voltage and a relatively large current flowing once the avalanche voltage has been reached. For avalanche diodes, this breakdown voltage usually occurs at voltages above 6V. In practice, however, both types of diode are referred to as Zener diodes. A typical characteristic for a 5.1V Zener diode is shown in Fig. 3.7.

Whereas reverse breakdown is a highly undesirable effect in circuits that use conventional diodes, it can be extremely useful in the case of Zener diodes where the breakdown voltage is precisely known. When a diode is undergoing reverse breakdown and provided its maximum ratings are not exceeded the voltage appearing

across it will remain substantially constant (equal to the nominal Zener voltage) regardless of the current flowing. This property makes the Zener diode ideal for use as a *voltage regulator*.

A simple voltage regulator is shown in Fig. 3.8. Resistor R_S is included to limit the Zener current to a safe value when the load is disconnected. When a load (R_L) is connected, the Zener current (I_Z) will fall as current is diverted into the load resistance. The output voltage (V_O) will remain at the Zener voltage until regulation fails at the point at which the potential divider formed by resistors R_S and R_L produces a lower output voltage that is less than V_Z . The ratio of R_S to R_L is thus important.

As the circuit begins to fail to regulate:

$$V_Z = V_{IN} \times \frac{R_L}{R_L + R_S}$$

where V_{IN} is the unregulated input voltage. Thus the *maximum* value for R_S can be calculated from:

$$R_{Smax} = R_L \times \left(\frac{V_{IN}}{V_Z} - 1 \right)$$

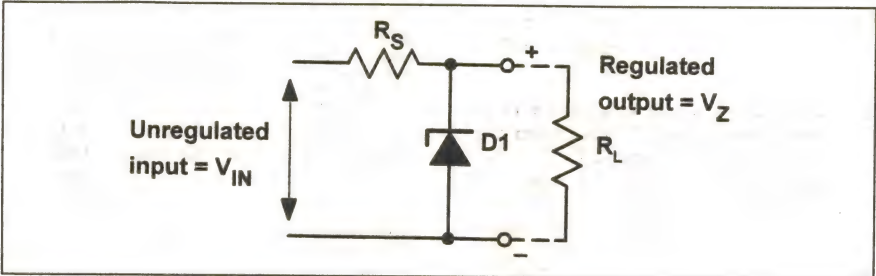


Fig. 3.8 Simple Zener diode voltage regulator circuit.

The power dissipated in the Zener diode, $P_Z = I_Z \times V_Z$, hence the *minimum* value for R_S can be determined from the "off-load" condition when:

$$R_{Smin} = \frac{V_{IN} - V_Z}{I_Z} = \frac{V_{IN} - V_Z}{(P_{Zmax}/V_Z)}$$

$$= \frac{(V_{IN} - V_Z) \times V_Z}{P_{Zmax}}$$

$$\text{thus } R_{S\min} = \frac{(V_{IN} \times V_Z) - V_Z^2}{P_{Z\max}}$$

where $P_{Z\max}$ is the maximum rated power dissipation for the Zener diode.

Example

A 5V Zener diode has a maximum rated power dissipation of 500mW. If the diode is to be used in a simple regulator circuit to supply a regulated 5V to a load having a resistance of 400Ω, determine a suitable value of series resistor for operation in conjunction with a supply of 9V.

First we should determine the maximum value for R_S :

$$R_{S\max} = R_L \times \left(\frac{V_{IN}}{V_Z} - 1 \right)$$

$$\begin{aligned} \text{thus } R_{S\max} &= 400\Omega \times \left(\frac{9V}{5V} - 1 \right) \\ &= 400 \times (1.8 - 1) = 320\Omega \end{aligned}$$

Now to determine the minimum value for R_S :

$$\begin{aligned} R_{S\min} &= \frac{(V_{IN} \times V_Z) - V_Z^2}{P_{Z\max}} = \frac{(9 \times 5) - 5^2}{0.5} \\ &= \frac{45 - 25}{0.5} = 40\Omega \end{aligned}$$

Hence a suitable value for R_S would be 150Ω (roughly mid-way between the two extremes).

Practical assignment 3.2: Zener diode characteristics

In this practical assignment you will investigate the characteristics of a typical Zener diode.

Objectives:

- 3.2.1 To plot the characteristic graph for a Zener diode
- 3.2.2 To estimate the Zener voltage for a Zener diode

Instructions:

1. Connect the circuit shown in Fig. 3.9 using a 4V battery.

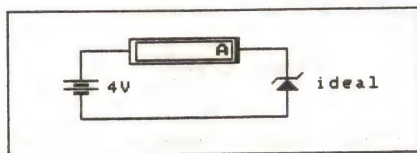


Fig. 3.9 Circuit for Assignment 3.2.

2. Switch on the power to your circuit and measure the current flowing. Record the value of current in Table 3.2.
3. Repeat steps 1 and 2 using battery voltages of 4.25V, 4.5V, 4.75V, 5V, 5.25V, 5.5V. Measure and record the current for each value of applied voltage.
4. Use the results from Table 3.2 to plot a graph showing reverse current (mA) plotted against applied voltage (V).

Table 3.2 Measured values for Assignment 3.2

Voltage (V)	0V	4V	4.25V	4.5V	4.75V	5V	5.25V	5.5V
Current (A)	0							

5. Use the graph to determine the Zener voltage at a nominal reverse current of 50mA.

Conclusions:

To what extent have the objectives for this assignment been met? Comment on the shape of the graph. Is the shape similar to the one you would expect? If not, why not?

RECTIFIERS

Diodes are commonly used to convert alternating current (a.c.) to direct current (d.c.), in which case they are referred to as *rectifiers*. The simplest form of rectifier circuit makes use of a single diode and, since it operates on only either positive or negative half-cycles of the supply, it is known as a *half-wave rectifier*.

The switching action of diode D1 results in a pulsating output voltage which is developed across the load resistor (R_L). Since the mains supply is at 50Hz, the pulses of voltage developed across R_L will also be at 50Hz even if only half the a.c. cycle is present. During the positive half-cycle, the diode will drop the 0.7V forward threshold voltage. However, during the negative half-cycle the peak a.c. voltage will be dropped across D1 when it is reverse biased. This is an important consideration when selecting a diode for a particular application.

Assuming that the secondary winding of transformer T1 provides 12V r.m.s., the peak voltage output from the transformer's secondary winding will be given by:

$$V_{pk} = 1.414 \times V_{r.m.s.} = 1.414 \times 12V = 16.968V$$

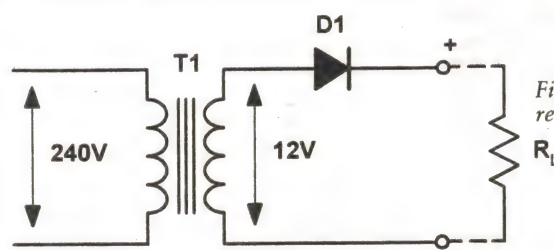


Fig. 3.10 Simple half-wave rectifier circuit.

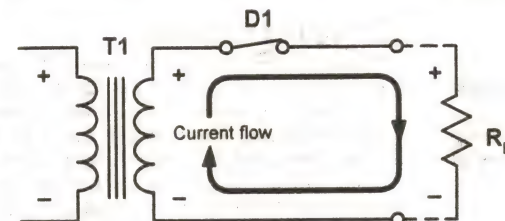


Fig. 3.11a Half-wave rectifier circuit with diode D1 conducting (positive going half cycles of secondary voltage).

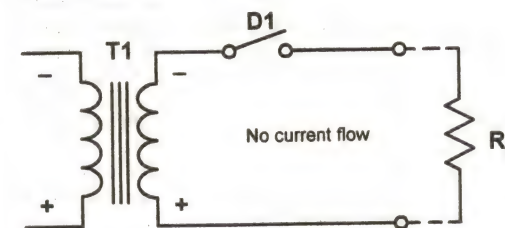


Fig. 3.11b Half-wave rectifier circuit with diode D1 not conducting (negative going half cycles of secondary voltage).

Fig. 3.10 shows a simple half-wave rectifier circuit. Mains voltage (240V) is applied to the primary winding of a stepdown transformer (T1). The secondary winding of T1 steps down the 240V r.m.s. to 12V r.m.s. (the turns ratio of T1 will thus be 240/12 or 20:1). Diode D1 will only allow the current to flow in the direction shown (i.e., from anode to cathode). Diode D1 will be forward-biased during each positive half-cycle (relative to common) and will effectively behave like a closed switch. When the circuit current tries to flow in the opposite direction, the voltage bias across the diode will be reversed, causing the diode to act like an open switch (see Fig. 3.11a and Fig. 3.11b respectively).

The peak voltage applied to diode D1 will thus be approximately 17V. The negative half-cycles are blocked by D1 and thus only the positive half-cycles appear across resistor R_L . Note, however, that the actual peak voltage across R_L will be the 17V positive peak being supplied from the secondary on T1, minus the 0.7V forward threshold voltage dropped by D1. In other words, positive half-cycle pulses having a peak amplitude of 16.3V will appear across resistor R_L .

Fig. 3.12 shows a considerable improvement to the circuit of Fig. 3.10. The capacitor, C1, has been added to ensure that the output voltage remains at, or near, the peak voltage even when the diode is not conducting. When the primary voltage is first applied to transformer T1, the first positive half-cycle output from the secondary will charge C1 to the peak value seen across R_L . Hence C1 charges to 16.3V at the peak of the positive half-cycle. Because C1 and R_L are in parallel, the voltage across R_L will be the same as that across C1.

The time required for capacitor C1 to charge to the maximum (peak) level is determined by the charging circuit time

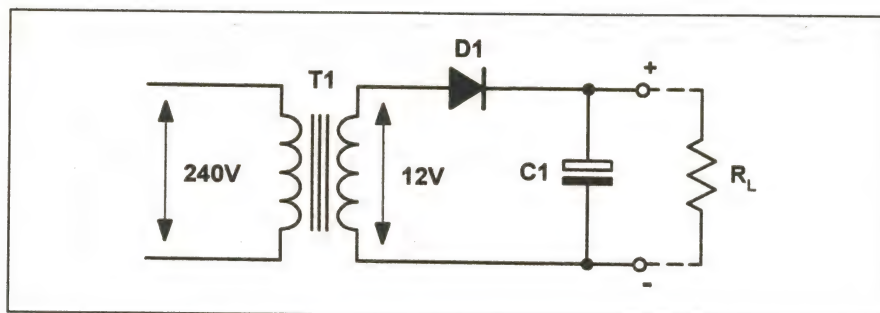


Fig. 3.12 Half-wave rectifier with reservoir capacitor.

constant (the series resistance multiplied by the capacitance value). In this circuit, the series resistance comprises the secondary winding resistance together with the forward resistance of the diode and the (minimal) resistance of the wiring and connections. Hence C1 charges very rapidly as soon as diode D1 starts to conduct.

The time required for capacitor C1 to discharge is, in contrast, very much greater. The discharge time constant is determined by the capacitance value and the load resistance, R_L . In practice, R_L is very much larger than the resistance of the secondary circuit and hence C1 takes an appreciable time to discharge. During this time, diode D1 will be reverse biased and will thus be held in its non-conducting state. As a consequence, the only discharge path for C1 is through R_L .

Capacitor C1 is referred to as a *reservoir capacitor*. It stores charge during the positive half-cycles of secondary voltage and releases it during the negative half-cycles. The circuit in Fig. 3.12 is thus able to maintain a reasonably constant output voltage across R_L . Even so, C1 will discharge by a small amount during the negative half-cycle periods from the transformer secondary. Fig. 3.13 shows the secondary voltage waveform together with the voltage developed across R_L with, and without C1 present. This gives rise to a small variation in the d.c. output voltage (known as *ripple*), as shown in Fig. 3.13.

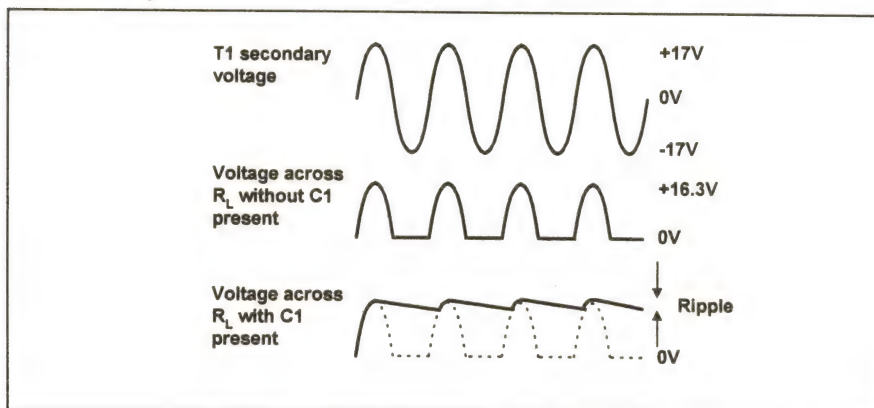


Fig. 3.13 Waveforms for half-wave rectifier circuits.

Since ripple is undesirable we must take additional precautions to reduce it. One obvious method of reducing the amplitude of the ripple is that of simply increasing the discharge time constant. This can be achieved either by increasing the value of capacitor C1 or by increasing the resistance value of R_L . In practice, however, the latter is not really an option because R_L is the effective resistance of the circuit being supplied and we don't usually have the ability to change it! Increasing the value of C1 is a more practical alternative and very large capacitor values (often in excess of 4700 μ F are typical).

A further refinement of the simple power supply circuit is shown in Fig. 3.14. This circuit employs two additional components, resistor R1 and capacitor C2, which act as a filter to remove the ripple. The value of C2 is chosen so that the component exhibits a negligible reactance at the ripple frequency (normally 50Hz). In effect, this circuit acts like a potential divider. The amount of ripple is reduced by a factor equal to:

$$\frac{X_C}{\sqrt{(R_1^2 + X_C^2)}}$$

Example

The R-C smoothing filter in a 50Hz mains operated half-wave rectifier circuit consists of $R_1 = 100\Omega$ and $C_2 = 1000\mu$ F. If 1V of

ripple appears at the input of the circuit, determine the amount of ripple appearing at the output.

First we must determine the reactance of the capacitor, C2, at the ripple frequency from:

$$X_C = \frac{1}{2\pi fC} = \frac{1}{6.28 \times 50 \times 1000 \times 10^{-6}} \\ = \frac{1000}{6.28 \times 50} = \frac{1000}{314}$$

Thus $X_C = 3.18\Omega$

The amount of ripple at the output of the circuit (i.e., appearing across capacitor C2) will be given by:

$$V_{\text{ripple}} = 1V \times \frac{X_C}{\sqrt{(R_1^2 + X_C^2)}} \\ = 1V \times \frac{3.18}{\sqrt{(100^2 + 3.18^2)}} \\ = 0.032V = 32mV$$

A further improvement can be achieved by using an inductor (L1) instead of a resistor (R1) in the smoothing circuit. This circuit also offers the advantage that the minimum d.c. voltage is dropped across the inductor (in the circuit of Fig. 3.14, the d.c.

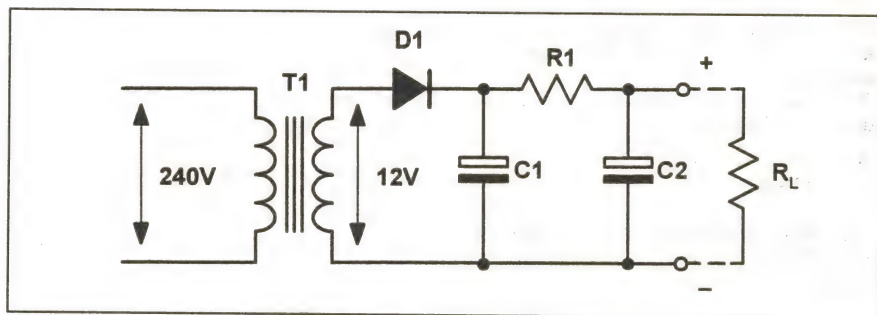


Fig. 3.14 Half-wave rectifier with R-C smoothing circuit.

output voltage is reduced by an amount equal to the voltage drop across R1).

The circuit of a half-wave power supply using L-C smoothing is shown in Fig. 3.15. At the ripple frequency, L1 exhibits a high value of inductive reactance whilst C1 exhibits a low value of capacitive reactance. The combined effect is that of an attenuator which greatly reduces the amplitude of the ripple whilst having a negligible effect on the direct voltage.

Example

The L-C smoothing filter in a 50Hz mains operated half-wave rectifier circuit consists of $L_1 = 10H$ and $C_2 = 1000\mu$ F. If 1V of ripple appears at the input of the circuit, determine the amount of ripple appearing at the output.

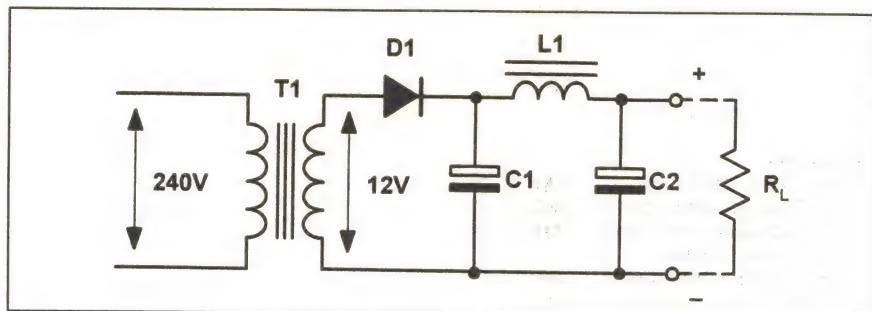


Fig. 3.15 Half-wave rectifier with L-C smoothing circuit.

Table 3.3 Measured values for Assignment 3.3.

Circuit under investigation	Measured voltage	
	output	ripple
No reservoir capacitor (step 4)		
100 μ F reservoir capacitor (step 5)		
470 μ F reservoir capacitor (step 6)		
470 μ reservoir plus 100 Ω and 470 μ smoothing filter (step 7)		
As above but with Zener diode regulator (step 8)		

output voltage was increased when the reservoir capacitor was fitted? Which circuit was most effective at removing the ripple? Why? Was the output voltage what you would have predicted? If not, why not?

FULL-WAVE RECTIFIERS

The half-wave rectifier circuit is relatively inefficient as conduction takes place only on alternate half-cycles. A better rectifier arrangement would make use of both positive and negative half-cycles. These full-wave rectifier circuits offer a considerable improvement over their half-wave counterparts. They are not only more efficient but are significantly less demanding in terms of the reservoir and smoothing components. There are two basic forms of full-wave rectifier; the bi-phase type and the bridge rectifier type.

BI-PHASE RECTIFIERS

A simple bi-phase rectifier circuit is shown in Fig. 3.22. Mains voltage (240V) is applied to the primary winding of a stepdown transformer (T1) which has two

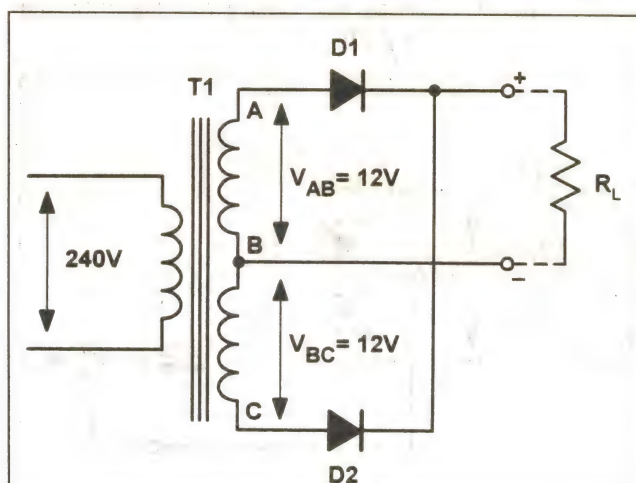


Fig. 3.22 Bi-phase rectifier.

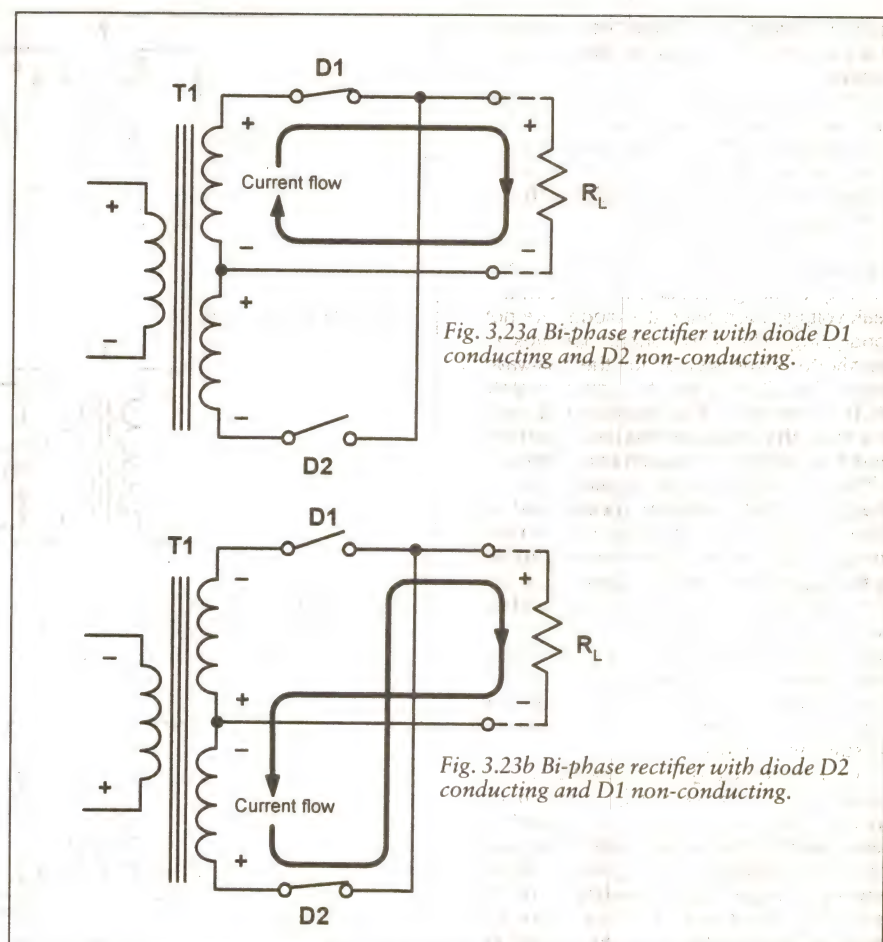


Fig. 3.23a Bi-phase rectifier with diode D1 conducting and D2 non-conducting.

Fig. 3.23b Bi-phase rectifier with diode D2 conducting and D1 non-conducting.

identical secondary windings, each providing 12V r.m.s. (the turns ratio of T1 will thus be 240/12 or 20:1 for each secondary winding).

On positive half-cycles, point A will be positive with respect to point B. Similarly, point B will be positive with respect to point C. In this condition diode D1 will allow conduction (its anode will be positive with respect to its cathode) whilst diode D2 will not allow conduction (its anode will be negative with respect to its cathode). Thus diode D1 alone conducts on positive half-cycles.

On negative half-cycles, point C will be positive with respect to point B. Similarly, point B will be positive with respect to point A. In this condition diode D2 will allow conduction (its anode will be positive with respect to its cathode) whilst diode D1 will not allow conduction (its anode will be negative with respect to its cathode). Thus

diode D2 alone conducts on negative half-cycles.

The bi-phase rectifier circuit in Fig. 3.23 shows the diodes of Fig. 3.22 replaced by switches. In Fig. 3.23a diode D1 is shown conducting on a positive half-cycle whilst in Fig. 3.23b diode D2 is shown conducting. The result is that current is routed through the load in the same direction on successive half-cycles. Furthermore, this current is derived alternately from the two secondary windings.

As with the half-wave rectifier, the switching action of the two diodes results in a pulsating output voltage being developed across the load resistor (R_L). However, unlike the half-wave circuit the pulses of voltage developed across R_L will occur at a frequency of 100Hz (not 50Hz). This doubling of the ripple frequency allows us to use smaller values of reservoir and smoothing capacitor to obtain the same degree of

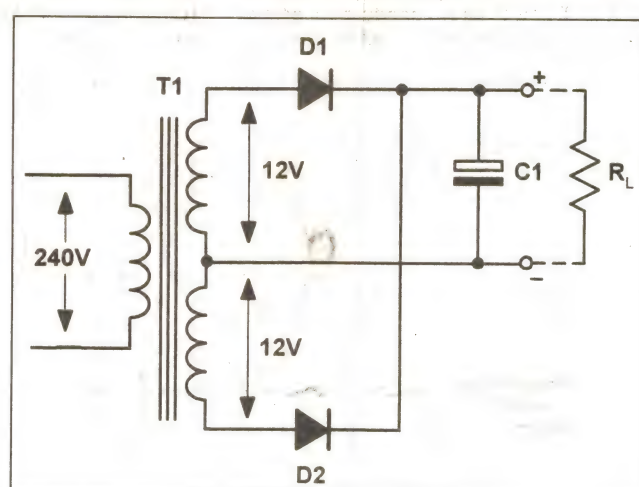


Fig. 3.24 Bi-phase rectifier with reservoir capacitor.

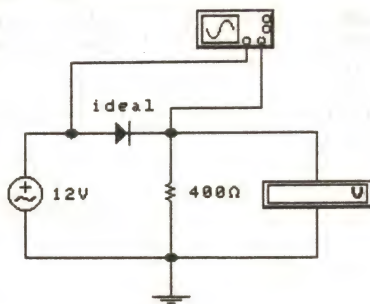


Fig. 3.16 Circuit for Assignment 3.3.

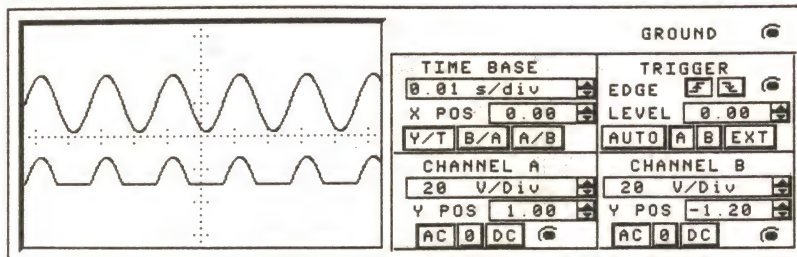


Fig. 3.17 Initial oscilloscope settings for Assignment 3.3

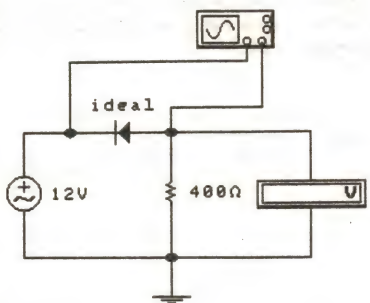


Fig. 3.18 Circuit of Fig. 3.16 modified for negative output.

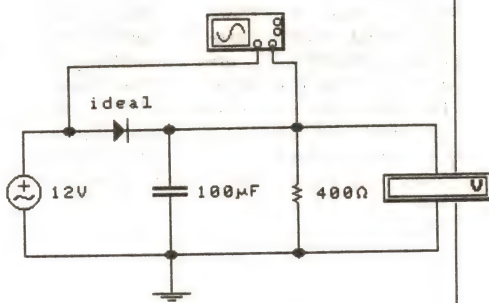


Fig. 3.19 Half-wave rectifier with reservoir capacitor (Assignment 3.3).

Once again, the reactance of the capacitor, C_2 , is 3.18Ω (see previous example).

The reactance of inductor L_1 at 50Hz can be calculated from:

$$X_L = 2\pi fL = 2 \times 3.14 \times 50 \times 10 = 3140\Omega$$

The amount of ripple at the output of the circuit (i.e., appearing across C_2) will be given by:

$$\begin{aligned} V_{\text{ripple}} &= 1V \times \frac{X_C}{\sqrt{(X_L^2 + X_C^2)}} \\ &= 1V \times \frac{3.18}{\sqrt{(3140^2 + 3.18^2)}} \\ &= 0.001V = 1mV \end{aligned}$$

It is worth comparing this value with that obtained from the previous example!

Practical assignment 3.3: Half-wave rectifiers

In this assignment you will investigate the behaviour of half-wave rectifier circuits. You will also investigate the operation of simple smoothing and Zener diode regulator circuits.

Objectives:

- 3.3.1 To investigate the action of a half-wave rectifier.
- 3.3.2 To use an oscilloscope to obtain waveforms for a half-wave rectifier.
- 3.3.3 To determine the effectiveness of an R-C smoothing circuit.
- 3.3.4 To investigate the action of a simple Zener diode regulator.

Instructions:

1. Connect the circuit shown in Fig. 3.16. The 400Ω resistor is used to simulate the load that would normally be connected to the power supply.
2. Display the input and output waveforms on the screen of the oscilloscope (see Fig. 3.17 for recommended initial set-

tings for the oscilloscope front-panel). Note the shape of the output waveform (you might like to make a sketch of it) and measure its peak-peak voltage using the vertical scale.

3. Reverse the diode connections (see Fig. 3.18). Repeat step 1 and note the difference in the output waveform (once again, you might like to make a sketch of it). Measure the peak-peak voltage and check this is the same as before.
4. Reconnect the circuit as shown in Fig. 3.16. Connect the voltmeter across the 400Ω resistor in order to measure the output voltage. Record the measured

value of the d.c. output voltage and the peak-peak ripple voltage (measured with the oscilloscope) in Table 3.3.

5. Now add a $100\mu F$ smoothing capacitor (Fig. 3.19). Once again display the input and output waveforms. Note the shape of the output waveform. As before, record the measured value of d.c. output voltage and the peak-peak ripple voltage measured with the oscilloscope.
6. Replace the $100\mu F$ capacitor with a $470\mu F$ capacitor and repeat step 5.
7. Next, add an R-C filter to the circuit by connecting a 100Ω resistor in series with the d.c. output from the rectifier and a second $470\mu F$ capacitor in parallel with the output (as in Fig. 3.20). Once again, note the shape of the output waveform and record the measured value of d.c. output voltage and the peak-peak ripple voltage.
8. Finally, add a 5-1V Zener diode in order to regulate the output voltage (see Fig. 3.21). Record the measured value of output voltage and peak-peak ripple voltage.

Conclusions:

To what extent have the objectives for this assignment been met? Can you explain, in your own words, how each part of the circuit works? (Hint: divide the circuit into three parts; the diode rectifier, the smoothing circuit, and the Zener diode regulator). Can you explain why the d.c.

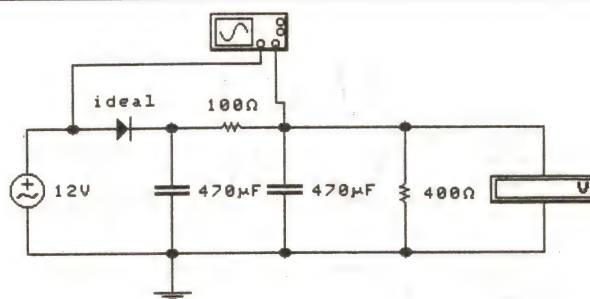


Fig. 3.20 Half-wave rectifier with smoothing filter.

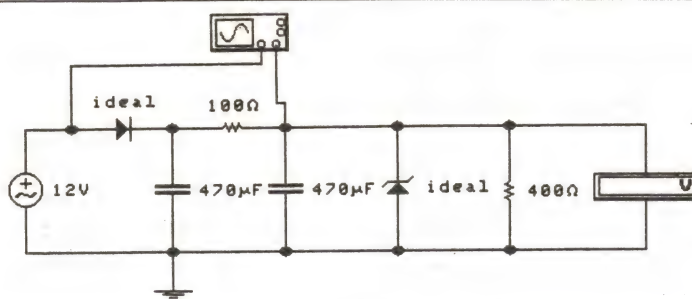


Fig. 3.21 Half-wave rectifier with smoothing filter and Zener diode regulator (Assignment 3.3).

ripple reduction (recall that the reactance of a capacitor is reduced as frequency increases).

As before, the peak voltage produced by each of the secondary windings will be approximately 17V and the peak voltage across R_L will be 16.3V (i.e., 17V less the forward threshold voltage of about 0.6V to 0.7V dropped by the diodes).

Fig. 3.24 shows how a reservoir capacitor (C1) can be added to ensure that the output voltage remains at, or near, the peak voltage even when the diodes are not conducting. This component operates in exactly the same way as for the half-wave circuit, i.e., it charges to approximately 16.3V at the peak of the positive half-cycle and holds the voltage at this level when the diodes are in their non-conducting states.

The time required for capacitor C1 to charge to the maximum (peak) level is determined by the charging circuit time constant (the series resistance multiplied by the capacitance value). In this circuit, the series resistance comprises the secondary winding resistance together with the forward resistance of the diode and the (minimal) resistance of the wiring and connections. Hence capacitor C1 charges very rapidly as soon as either diode D1 or diode D2 starts to conduct.

The time required for capacitor C1 to discharge is, in contrast, very much greater. The discharge time constant is determined by the capacitance value and the load resistance, R_L . In practice, R_L is very much larger than the resistance of the secondary circuit and hence capacitor C1 takes an appreciable time to discharge. During this time, diode D1 and diode D2 will be reverse biased and held in a non-conducting state. As a consequence, the only discharge path for capacitor C1 is through R_L . Voltage waveforms for the bi-phase rectifier, with and without C1 present, are shown in Fig. 3.25.

BRIDGE RECTIFIERS

An alternative to the use of the bi-phase circuit is that of using a four-diode bridge rectifier (see Fig. 3.26) in which opposite pairs of diode conduct on alternate half-cycles. This arrangement avoids the need to have two separate secondary windings.

Mains voltage (240V) is applied to the primary winding of a stepdown transformer (T1). The secondary winding provides 12V r.m.s. (approximately 17V peak) and has a turns ratio of 20:1, as before. On positive half-cycles, point A will be positive with respect to point B. In this condition diodes D1 and D2 will allow conduction whilst diodes D3 and D4 will not allow conduc-

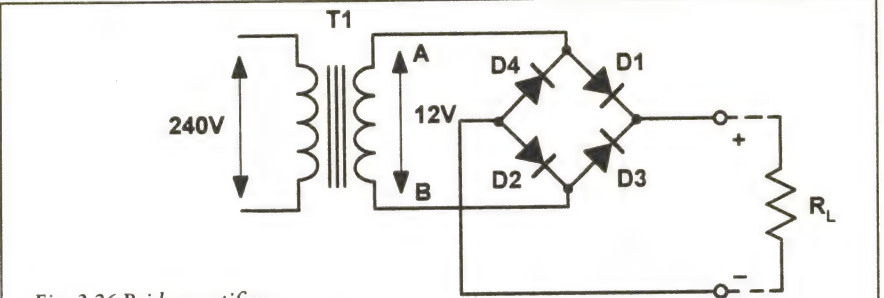


Fig. 3.26 Bridge rectifier.

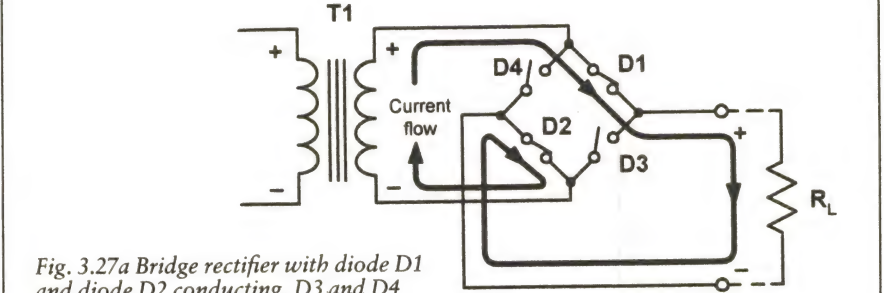


Fig. 3.27a Bridge rectifier with diode D1 and diode D2 conducting, D3 and D4 non-conducting.

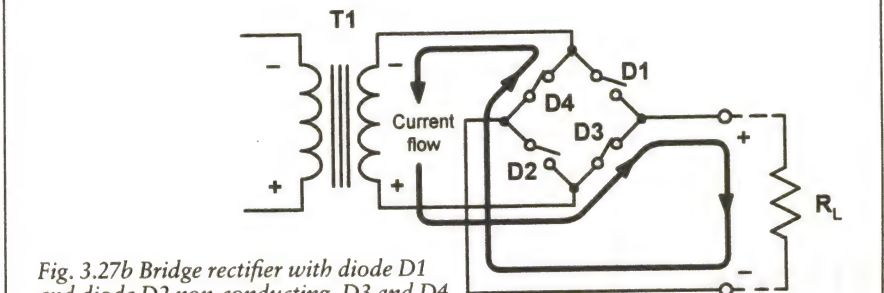


Fig. 3.27b Bridge rectifier with diode D1 and diode D2 non-conducting, D3 and D4 conducting.

tion. Conversely, on negative half-cycles, point B will be positive with respect to point A. In this condition diodes D3 and D4 will allow conduction whilst diodes D1 and D2 will not allow conduction.

The bridge rectifier circuit in Fig. 3.27 shows the diodes of Fig. 3.26 replaced by switches. In Fig. 3.27a diodes D1 and D2 are conducting on a positive half-cycle whilst in Fig. 3.27b diodes D3 and D4 are conducting. Once again, the result is that current is routed through the load in the same direction on successive half-cycles.

As with the bi-phase rectifier, the switching action of the two diodes results in a pulsating output voltage being developed across the load resistor (R_L). Once again, the peak output voltage is approximately 16.3V (i.e., 17V less the 0.7V forward threshold voltage).

Fig. 3.28 shows how a reservoir capacitor (C1) can be added to ensure that the output voltage remains at, or near, the peak voltage even when the diodes are not conducting. This component operates in exactly the same way as for the bi-phase circuit, i.e., it charges to approximately 16.3V at the peak of the positive half-cycle and holds the voltage at this level when the diodes are in their non-conducting states. This component operates in exactly the same way as for the bi-phase circuit and the voltage waveforms are identical to those shown in Fig. 3.25.

Finally, R-C and L-C smoothing circuits can be added to both the bi-phase and bridge rectifier circuits in exactly the same manner as those shown for the half-wave rectifier arrangement (see Fig. 3.14 and Fig. 3.15).

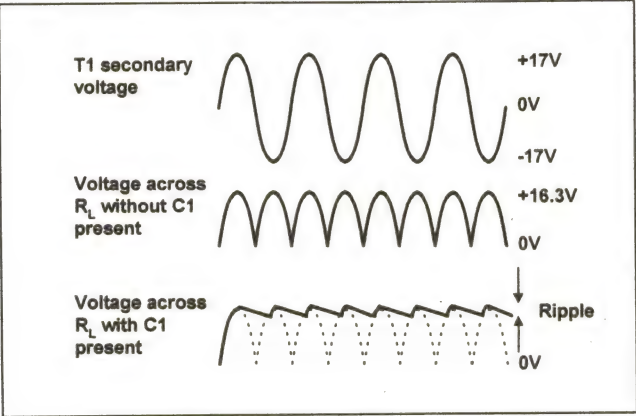


Fig. 3.25 Waveforms for the bi-phase rectifier.

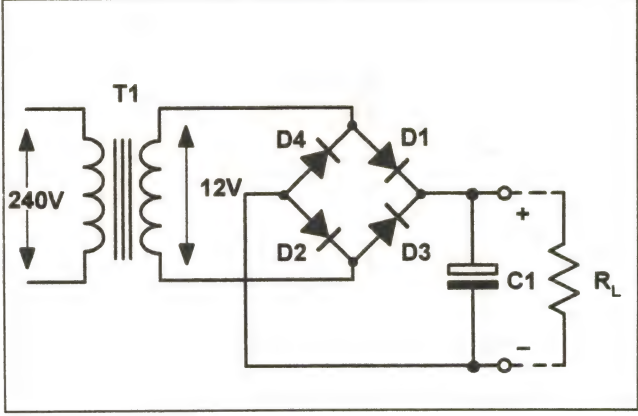


Fig. 3.28 Bridge rectifier with reservoir capacitor.

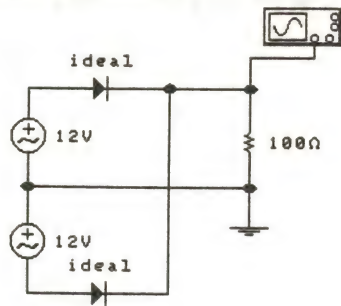


Fig. 3.29 Bi-phase rectifier circuit for Assignment 3.4.

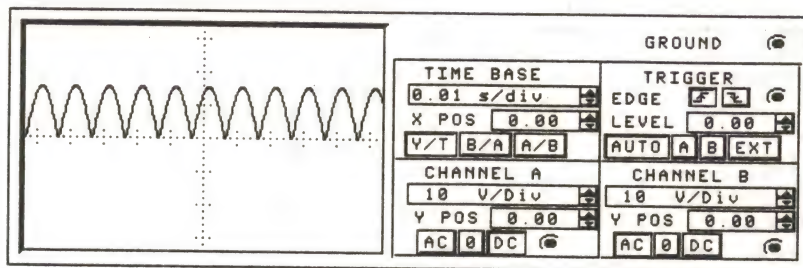


Fig. 3.30 Initial oscilloscope settings for Assignment 3.4.

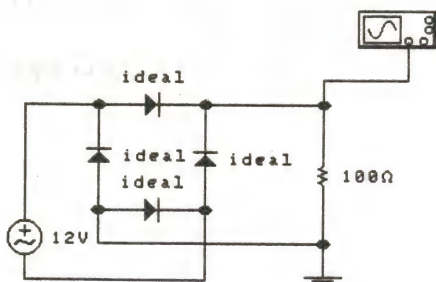


Fig. 3.31 Bridge rectifier circuit for Assignment 3.4.

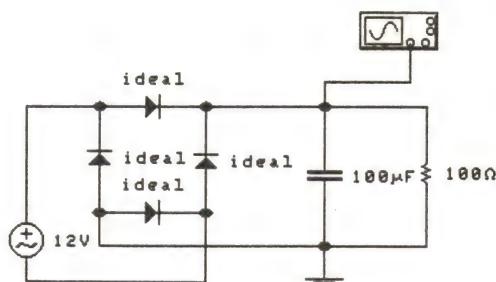


Fig. 3.32 Bridge rectifier with reservoir capacitor (Assignment 3.4).

Practical assignment 3.4:

Full-wave rectifiers

In this assignment you will investigate the behaviour of bi-phase and bridge rectifier circuits.

Objectives:

- 3.3.1 To investigate the action of full-wave rectifiers (both bi-phase and bridge types).
- 3.3.2 To use an oscilloscope to obtain waveforms for full-wave rectifiers (both bi-phase and bridge types).
- 3.3.3 To compare the effectiveness of R-C and L-C smoothing filters.

Instructions:

1. Connect the bi-phase rectifier circuit shown in Fig. 3.29. The 100Ω resistor is used to simulate the load that would normally be connected to the power supply. Note that this is a lower value of resistance (and thus a more severe load) than we used for the half-wave rectifier circuit. Note also that the transformer secondary windings are represented by two 12V 50Hz a.c. voltage sources.
2. Display the output waveform on the screen of the oscilloscope (see Fig. 3.30 for recommended initial settings for the oscilloscope front-panel). Note the shape of the output waveform (you
- might like to make a sketch of it) and measure its peak-peak voltage using the vertical scale. Record this measured value in Table 3.4.
3. Connect the bridge rectifier circuit shown in Fig. 3.31. Once again, the 100Ω resistor is used to simulate the load that would normally be connected to the power supply. This time you will only need a single 12V 50Hz a.c. voltage source.
4. Repeat step 2 (this time for the bridge rectifier).
5. Add a $100\mu\text{F}$ smoothing capacitor to the output of the bridge rectifier (as in Fig. 3.32). Once again display the output waveform and note its shape. Record the peak-peak ripple voltage in Table 3.4.
6. Replace the $100\mu\text{F}$ capacitor with a $470\mu\text{F}$ capacitor and repeat step 5.
7. Next, add an R-C filter to the circuit by connecting a 400Ω resistor in series with the d.c. output from the bridge rectifier and a second $470\mu\text{F}$ capacitor in parallel with the output (Fig. 3.33). Once again, note the shape of the output waveform and record the peak-peak ripple voltage in Table 3.4.
8. Finally, modify the filter circuit by replacing the 400Ω resistor with a 10H inductor (as in Fig. 3.34). Once again, note

the shape of the output waveform and record the peak-peak ripple voltage in Table 3.4.

Conclusions:

To what extent have the objectives for this assignment been met? Can you explain, in your own words, how each part of the circuit works? Did the two rectifier circuits produce identical output waveforms? If not, why not? Which smoothing circuit (R-C or L-C) was most effective at reducing the ripple? Why? Can you suggest another advantage of the L-C filter when compared with the R-C filter?

BRAIN TEASER

This month's challenge for those of you who are using the full *Electronics Workbench* package is to design a full-wave power supply that provides equal but opposite output voltages with a common earth (0V) connection. The circuit is to incorporate smoothing and each output voltage is to be stabilised using a parallel-connected 5V Zener diode. Use *Electronics Workbench* to test your circuit and check that it works correctly!

Answer to last month's Brain Teaser

Each branch of the circuit will produce a phase shift. Since the component values

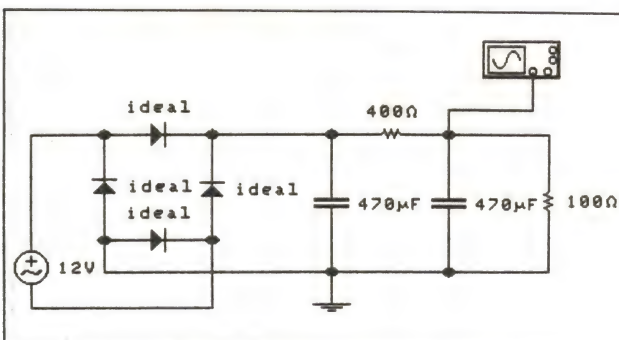


Fig. 3.33 Bridge rectifier with R-C smoothing filter.

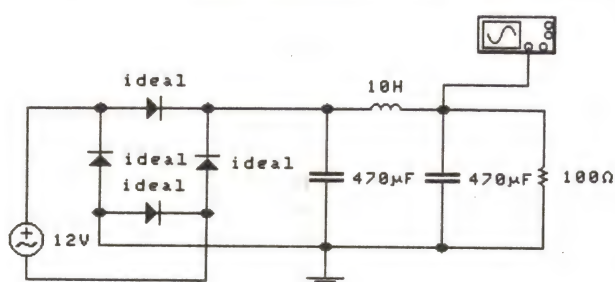


Fig. 3.34 Bridge rectifier with L-C smoothing filter.

Table 3.4 Measured values for Assignment 3.4.

Circuit under investigation	Measured ripple voltage
Bi-phase circuit without reservoir capacitor (step 2)	
Bridge circuit without reservoir capacitor (step 4)	
100µF reservoir capacitor (step 6)	
470µF reservoir capacitor (step 6)	
470µF reservoir plus 400Ω and 470µF smoothing filter (step 7)	
470µF reservoir plus 10H and 470µF smoothing filter (step 8)	

(1kΩ and 1µF) are identical but interchanged, an equal but opposite phase shift will be produced in the two branches. Thus, a 90° phase shift between A and B will be produced when each branch gives a phase shift of 45°.

The phase shift produced by a C-R circuit is given by:

$$\tan \theta = \frac{X_C}{R} = \frac{1/(2\pi f C)}{R} = \frac{1}{2\pi f C R}$$

Hence:

$$f = \frac{1}{2\pi C R \tan \theta}$$

Now when $\theta = 45^\circ$, $\tan 45^\circ = 1$ thus:

$$\begin{aligned} f &= \frac{1}{2\pi C R} \\ &= \frac{1}{6.28 \times 1 \times 10^{-6} \times 1 \times 10^3} \\ &= \frac{1000}{6.28} = 159\text{Hz} \end{aligned}$$

An easier way to solve the problem is to remember that a 45° phase shift will be produced at the frequency that makes $X_C = R$ (i.e., when the reactance is equal to the resistance). We can then say that:

$$X_C = R \text{ thus } \frac{1}{2\pi f C} = R \text{ or } f = \frac{1}{2\pi C R} \text{ as before.}$$

IMPORTANT NOTE:

If you have any problems installing *Electronics Workbench* please note the following points:

1. If you receive a "Mouse not installed" error message please ensure that you are using a Microsoft compatible mouse driver.
2. If you receive an "Incorrect registration" or "Access denied" error message please increase the FILES command in your CONFIG.SYS file by 20 (i.e., if the current setting of FILES is 20 you should increase FILES to 40).
3. If you receive a "Graphics card not recognized" error message and you are using an EGA monitor, you should edit the file EWB.OPT (using an ASCII text editor) and change the line "DISPLAY; VGA" to read "DISPLAY; EGA".

CORRECTION

In *Electronics from the Ground Up* Part 2 last month (EPE November 1994), at the bottom left of page 864, the capacitive reactance formula for X_C should read:

$$X_C = \frac{1}{2\pi f C} = \frac{1}{6.28 \times 2 \times 10^3 \times 10 \times 10^{-9}}$$

Electronics Workbench – Order/Enquiry Form

Please register me for the Upgrade disk of Assignments for the Entire Course
I am an Overseas reader, please advise me how to order *Electronics Workbench* and/or the Upgrade disk.

Please supply:

Full version of *Electronics Workbench*
Model Set 1 (disk)
150 Circuits (book plus disk)
Trouble Shooting (book plus disk)
Practical Teaching Ideas (book plus disk)

Special Offer

(Full EWB plus all 4 add-on modules)

Please Tick	Price*
☐	£9.50
☐	-
☐	£238.81
☐	£38.18
☐	£32.30
☐	£32.30
☐	£26.43
☐	£303.75

Total Payment £

*All prices include VAT at 17.5% and UK P&P.

From:

Name

Address.....

Post Code

CREDIT/DEBIT CARD NUMBER

Expiry Date

Signature

(Please supply name and address of Cardholder if different from address shown)

Payments in £ Sterling only please. Cheque/PO/Visa/Access/Switch

Simply phone, fax or send this form (or photocopy) to:

Robinson Marshall (Europe) PLC

Nadella Building, Progress Close, Leofric Building Park, Coventry CV3 2TF

Tel: 0203 233216 (International 044-203 233216)

Fax: 0203 233210 (International 044-203 233210)

TEACH-IN No. 7 Plus Free Software

ANALOGUE AND DIGITAL ELECTRONICS COURSE

(Published by *Everyday with Practical Electronics*)

Alan Winstanley and Keith Dye B.Eng(Tech)AMIEE

The highly acclaimed *Teach-In '92* series, which included the construction and use of the *Mini Lab* and *Micro Lab* test and development units, has been put together in book form. Additionally EPT Educational Software have developed a GCSE Electronics software program to compliment the course and a FREE DISK covering the first two parts of the course is included with the book.

An interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles.

If you are taking electronics or technology at school or college, this book is for you. If you just want to learn the basics of electronics then this book is for you. If you are teaching electronics or technology you must make sure you see it. *Teach-In No. 7* will be invaluable if you are considering a career in electronics or even if you are already training in one. The *Mini Lab* and software enable the construction and testing of both demonstration and development circuits. These learning aids bring electronics to life in an enjoyable and interesting way: you will both see and hear the electron in action! The *Micro Lab* microprocessor add-on system will appeal to higher level students and those developing microprocessor projects.

Available at the end of October. Price £3.95 – place an order with your newsagent NOW!

Techniques

ACTUALLY DOING IT!

by Robert Penfold

MOST hobbies are to some degree seasonal, and electronic project construction is no exception. No doubt there are many who follow the hobby all-year round, but for most it is a pastime that is pursued more avidly in the winter months.

By the time this piece gets into print we should be well under way with a new season of project building, and many potential "new recruits" will presumably be contemplating the construction of their first project. This inevitably gives rise to the question, "what is the minimum I need in order to get started?"

TOOLS FOR THE JOB

Even if you are in the fortunate position of having plenty of spare cash, it is probably not worthwhile going out and buying every tool and gadget you see. You will almost certainly end up wasting a lot of money on implements that you will rarely (if ever) use. It is much better to start with a fairly basic toolkit, and then add to it as and when the need arises. Start by building a couple of simple and straightforward projects from recent issues of *EPE*. It should be possible to construct these using just a few basic tools.

A lot of the tools you will require are the type of thing that is to be found in the average household toolbox anyway. These include such things as pliers, a hacksaw or junior hacksaw, screwdrivers, a centre punch, hammer, files, a hand or power drill, and a set of twist drill bits.

Some of these may not be ideally suited to electronic project building, which is mainly a small scale affair. For example, large screwdrivers are of no use when you need to tighten the tiny grub screw in a control knob. If you do not already have a couple of miniature electricians' screwdrivers you will certainly need to add them to your toolkit. The cost should be less than a pound for the two. It is also worth having a small cross-point (Phillips) screwdriver. Again, the cost of one these should be minimal.

Whilst in most cases I advocate purchasing the highest quality tools you can afford, this is not really essential in the case of twist drills. It is mostly soft plastics and aluminium that you will be working with, and even cheap drill bits should have a reasonably long life when used on these materials. If you have a set of HSS (High Speed Steel) drill bits with a good range of sizes

from about 2mm to 10mm in diameter these should cover virtually all your needs.

If you have to buy the drill bits it would probably be better to obtain individual drills in the sizes you will need, rather than buying a large set which is likely to contain numerous drills you will never use. I find that the vast majority of project drilling can be handled by these four sizes:

3.3mm – for holes that will take metric M3 or 6BA screws (e.g. mounting circuit boards).

5mm – mounting holes for sub-miniature toggle switches

6.35mm (0.25 inches) – mounting holes for many push button switches, miniature toggle switches, miniature potentiometers, various sockets, etc.

10mm – the standard mounting hole size for potentiometers, rotary switches, and many other controls.

In due course you will probably find the need for several other sizes, but provided you steer clear of unusual switches, sockets, etc., these drills should suffice initially.

Power drills are all right for project work, but I find them a bit awkward to use. When drilling soft materials such as plastics and aluminium there is a tendency for power drills to rip straight through almost instantly in a rather uncontrolled fashion. Particularly when drilling larger holes, there is a definite advantage in using a drill that can be set to a slow speed. These days I rarely use power drills when building projects. My preference is for a heavy duty hand drill for the small and medium sized holes, and a brace for the larger ones.

CLEAN CUT

For holes larger than 10mm in diameter a chassis punch is my preferred tool. A chassis punch is basically just a large nut and bolt, but the nut is also a circular cutting blade. First a hole of suitable diameter for the bolt is drilled. Then the bolt is fitted into the hole, and the nut is fitted onto the bolt and tightened. With the aid of an Allen key the nut is tightened so much that it is forced through the panel, punching a hole in its way. Although this sounds like a very crude

way of tackling the problem, it actually produces very high quality results very quickly. Even a well worn chassis punch seems to provide "cleaner" holes than any drill. Although only intended for use with metals such as steel and aluminium, chassis punches seem to work quite well with any non-brittle plastic.

Chassis punches having diameters of 12.5mm and 16mm are very useful for electronics work. These are suitable for punching the mounting holes for larger switches (especially toggle types) and DIN sockets respectively. Unfortunately, chassis punches are relatively expensive, so it is probably not worthwhile buying one unless you really need it, and are likely to go on using it. When only used on aluminium and plastics a chassis punch has an extremely long life, and is not expensive in the long term.

Probably the most useful type of file to have is a large half round type. A small flat type is also more than a little useful. In due course I would recommend buying a set of miniature files (needle files) as these are useful for correcting small errors, making irregular shaped cutouts, etc. An "Abrafile" is a good low cost alternative.

The type of pliers I find most useful are, not surprisingly, electricians' pliers. Virtually any type of pliers will do initially, provided you use them carefully, but it is a good idea to invest in a good pair of electricians' pliers before too long.

HOT STUFF

While a lot of the tools needed for electronic project construction are general purpose tools which you may have already, there are a few which do not form part of the average toolkit. The most obvious of these is the soldering iron. Most electronic component catalogues list a few soldering irons having ratings from about 12W to 50W.

For project construction an iron having a rating of about 17W to 25W is the most suitable. There is no need to bother with expensive temperature controlled irons. Something like an Antex model CS will provide very good results, will only set you back about £10, and (with occasional bit replacement) should last many years.

A soldering iron stand is an essential extra. It provides somewhere safe to keep the hot iron between soldering operations, and it also helps to remove excess heat from the iron during periods of inactivity. A matching stand for your particular soldering iron should cost no more than about £4.

You will also need some solder. Only use a 60 per cent tin/40 per cent lead solder containing a non-corrosive flux. This is listed in most catalogues in two thicknesses, which are 18 and 22 s.w.g. For modern project construction the 22 s.w.g. solder is the easier to use, and it is a good idea to buy a decent sized pack of this, or even a large reel. Buying solder in very small quantities is likely to be rather expensive in the long term, and you will inevitably find that you keep

running out when projects are 99 per cent complete! It is useful to have some 18 s.w.g. solder for larger joints, such as when wiring-up controls and sockets, but you can get by without it.

It is possible to buy soldering kits which consist of an iron, a matching stand, some solder, and a booklet on soldering techniques. At about £14 these offer good value for money, and are ideal for beginners.

ASNIP

Wire cutters and insulation strippers are tools that should be regarded as essential items. It is possible to improvise using scissors or a modelling knife, but the end result is usually a minor disaster. Scissors will soon be ruined if you cut wire with them. Also, they are simply too large and clumsy for a lot of wire cutting work.


Using a knife is likely to almost instantly ruin the blade, and there is a strong risk of cutting yourself. With both methods it is likely that the wire core or cores will be nicked and seriously weakened. Even with only a small amount of flexing the wire will almost certainly break.

A pair of combination wire strippers and cutters should only cost a pound or three, and can be adjusted so that they will not cut so deeply that the wire becomes damaged. I find that these combination tools are very good as wire strippers, and I actually prefer them to expensive wire stripping tools. As wire cutters they are perhaps less than ideal, but they are more than good enough to get you started.

In due course I would recommend purchasing a pair of "side cutters". Although miniature cutters might seem to be the most apposite for modern electronic work, I find a relatively substantial pair of six inch cutters much easier to use.

THE REST

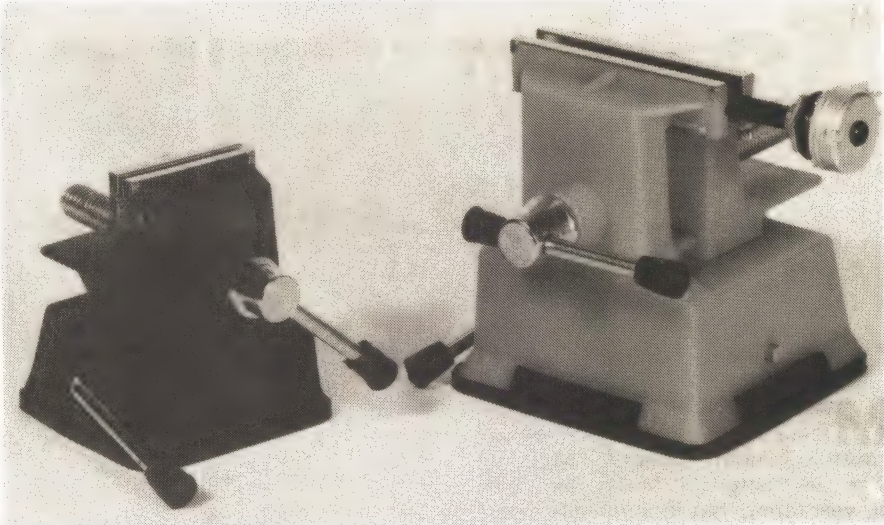In due course you will certainly need to add to your toolkit, but initially only a few other odds and ends are required. If your nails are cut (or bitten!) quite short you will probably find it very difficult to pick up small pieces of wire,



Little and large "Hobby" vices. They are fixed in place via a suction cup.

and the smaller components such as resistors. This may also be difficult if your fingers are not quite as nimble as they once were. A pair of tweezers should make life a lot easier when dealing with the more fiddly items.

Some sort of vice is more than a little useful. Even something as basic as a "hobby vice" will do to start with. In fact I find these unlikely gadgets to be extremely useful. A vice of this type is basically just a scaled-down version of a normal bench vice, but it is made of plastic with metal inserts on the jaws.

It is fixed to the worktop via a large suction clamp which provides a more secure fixing than you might expect. A vice of this type is very useful if you have to borrow the kitchen table for use as a temporary work-space when constructing projects.

A printed circuit work frame (also known as a mounting frame or a solder frame) is a worthwhile addition to the electronics workshop if you get involved in building fairly large printed circuit boards. The basic idea is to fit all the components in place on the board, and then clamp it into the frame. The frame is then clipped in the closed position, which presses the component side of the board into a thick piece of

heat-resistant foam material. This holds all the components in place while the leads are trimmed and the soldered joints are completed. Particularly with larger boards, this method is very much quicker and easier than dealing with the components one or two at a time.

As a good quality printed circuit frame costs about £40 or more it is probably not worth buying one initially, but for regular project builders it represents a sound investment.

Last but by no means least, no creative hobby can be pursued without some plasticine or Bostik Blu-Tack. This is useful for all manner of things, such as holding components in position while they are soldered in place, and generally sticking down anything that has a tendency to "walk" away.

Although electronics is sometimes accused of being an expensive hobby, it is difficult to justify this claim. Even if you have to start virtually from scratch when assembling a toolkit, I would guess that it would be possible to obtain the basic requirements plus the components for a small project, and still have change from £50. I doubt if it is possible to get started in many hobbies these days for this sort of money.

N. R. BARDWELL LTD (EPE)

200	Signal diodes 1N4148.....	£1.00
75	Rectifier Diodes 1N4001.....	£1.00
50	Rectifier Diodes 1N4007.....	£1.00
25	Rectifier Diodes 1N5401.....	£1.00
100	Asstd. Zeners.....	£1.00
10	NE555 Timer ICs.....	£1.00
30	BC478 Transistors.....	£1.00
30	BC547 Transistors.....	£1.00
30	BC558 Transistors.....	£1.00
30	MPSA92 Transistors.....	£1.00
30	5mm red l.e.d.s.....	£1.00
25	Asstd. high brightness l.e.d.s.....	£1.00
24	Miniature red l.e.d.s 3mm dia.....	£1.00
50	Axial l.e.d.s (Diode package) wide angle l.e.d.s.....	£1.00
12	Asstd. seven segment displays.....	£1.00
30	Asstd. IF transformers.....	£1.00
48	Asstd. coil formers.....	£1.00
100	Asstd. RF chokes (inductors).....	£1.00
30	Asstd. connectors edge-dil-sil etc.....	£1.00
10	4P 3W MBB min. rotary switches.....	£1.00
20	1 inch Glass reed switches.....	£1.00
20	Magnetic ear clips plus lead & plug.....	£1.00
20	Min SP/CO slide switches.....	£1.00
30	Asstd. d.i.l. sockets up to 40 pin.....	£1.00
20	24-way turned pin IC sockets.....	£1.00
24	24 pin d.i.l. wire wrap IC sockets.....	£1.00
2	ORP12 light dependant resistors.....	£1.00
200	Asstd. disc ceramic capacitors.....	£1.00
80	Asstd. capacitors 1nf to 1uf.....	£1.00
80	Asstd electrolytic capacitors.....	£1.00
80	1UF 16V Radial electrolytics.....	£1.00
80	4.7UF 16V Radial electrolytics.....	£1.00
75	4.7UF 63V Radial electrolytics.....	£1.00
80	10UF 16V Radial electrolytics.....	£1.00
50	10UF 50V Radial electrolytics.....	£1.00
40	22UF 25V Radial electrolytics.....	£1.00
60	33UF 16V Radial electrolytics.....	£1.00
80	100UF 10V Radial electrolytics.....	£1.00
50	220UF 16V Radial electrolytics.....	£1.00
60	470UF 10V Radial electrolytics.....	£1.00
20	1000UF 10V Axial electrolytics.....	£1.00
12	1000UF 25V Axial electrolytics.....	£1.00
1	1 Farad 5.5V memory back up capacitor.....	£1.00
100	4N7 Mini Axial capacitors.....	60p
100	5mm plastic l.e.d. holders (for tapered l.e.d.s).....	£2.00
1	10 watt Stereo amplifier, 4 controls plus data.....	£2.95

Prices include VAT, postage £1.25. Stamp for Lists
288 Abbeydale Road, Sheffield S7 1FL
Phone (0742) 552886 Fax (0742) 500689

NEW MARKET TRANSFORMERS LTD.

Unit 15, Craven Way Industrial Est., Newmarket, Suffolk. CB8 0AP
Telephone: (0638) 662989 Facsimile: (0638) 660799

TOROIDAL MANUFACTURERS
Primary 220/240v Two Secondaries

VA	Price	Dimensions
30	£11.30	70 x 35mm
50	£12.40	80 x 45mm
80	£13.90	90 x 35mm
120	£14.80	90 x 45mm
160	£17.85	110 x 45mm
225	£19.20	110 x 50mm
300	£19.86	110 x 60mm
500	£26.70	140 x 60mm
625	£28.90	140 x 70mm
800	£33.90	125 x 90mm
1000	£39.90	160 x 70mm

Prices include VAT & Carriage
For further information and quantity discounts, contact Michael Dornan
Phone: 0638 662989 Fax: 0638 660799

FOX REPORT

by Barry Fox



Dodo Apple

Is the Apple Mac now cast in the role played by Betamax in its last few years? Great picture, great sound, great features, but with a future as secure as a Dodo.

Do those who now buy into the Mac world risk becoming the victim of friends who joke about their being "the man who bought Mac when everyone else was buying PCs?"

Journalists like me, who kept banging on about Beta's superior benefits, finally had to face reality. When does the Mac press own up?

Even by now the Mac zealots amongst you will be fuming at the very suggestion of a parallel with Betamax. So will Apple's staff. But there is clear writing on the wall and there is no sign of Apple's top management addressing the problem.

Of course, lower and middle management make all the right reassuring noises. But without a sign from Apple's power-masters it means nothing. Frankly, just as when the Beta manufacturers like Toshiba and Sanyo started to make VHS recorders as well, it is hard to see what can now be done to halt the death spiral.

Consider the Facts

A few weeks ago, and for the first time since the Mac was launched, I was loaned a Mac (portable) to try for myself. Never in ten years had anyone from Apple ever said, "I've seen all the rude things you keep writing about the compatibility mess in PC

World, so why don't you try a Mac for a few days and see for yourself how much easier it is to plug in and use?"

Gradually it now seeps out that Apple has had an economy policy of restricting the number of Macs available for review. So they have been shuttled round bona fide reviewers, rather than journalists with a much more general approach. I was only loaned the portable, because I was involved with a highly respected, wide circulation, magazine's comparative review of portables.

Given the chance to use a Mac, I was struck immediately by the fact that using it was an easy pleasure. Five years ago it would have made a glorious change from struggling with early versions of Windows. But in those five years, the PC Windows world has aped the Mac world so effectively that the look and feel of the two worlds is now almost identical.

Multiply this situation across the board, and through the ranks of non-specialist journalists writing for just the kind of real world people the Mac is aimed at, and you have a massive missed opportunity.

Even semi-specialists like me who have invested tens of thousands of pounds into buying PC hardware are hardly going to pay the even higher price of Mac hardware and software just to give it a try.

If Microsoft gets its new Windows-style operating system, called Chicago, right and brings plug-and-play convenience to the PC world, what has the Mac world got left to offer the customer?

Certainly not chip speed, because both PCs and Macs are already running so fast that most of the time they just sit idle while their owners perform routine tasks.

The people who love their Macs are the people who have always used Macs. But the bridges that are now being built between Mac and Windows software will let corporate purchasing departments look only at price when the time for the next hardware update comes round. This will suck Apple ever deeper into a price war it can never win.

How can Apple compete on price against the mass manufacturing might of Korea, Taiwan and Mainland China? How can Apple compete on the size, weight and compactness of portables from miniaturization masters like Toshiba, Sharp, Sony and the clone manufacturers making for Gateway and Dell?

Apple can sub-contract, as it already does to Sony and Sharp, but this shaves the profit margins even tighter. Newton was a flop, with early models now being offered for sale at £100. The parallel with BetaMovie, the world's first genuinely portable camcorder, is inescapable.

Licence to Kill

This whole scenario is the direct cause of Apple's consistent refusal to license Mac technology to other companies. Initially this kept profits high. But it restricted sales volume and gave the PC World and Microsoft all those years it took them to get Windows working, and Chicago planned.

Remember how in the early days Sony was reluctant to license Betamax technology, while JVC threw VHS licences around like confetti? The parallels stack up.

From the outside looking in, there is only one way for Apple to stop the Mac becoming another Betamax. That is to move fast and license the technology to clone makers who could then offer a cheap alternative to the Pentium PC and Chicago. Apple would then become a licensing company.

There is no shame in this. Dolby Laboratories have very wisely never made a single piece of consumer equipment in their life, but grown rich on the licence fees paid by those who do. Microsoft has never made any consumer equipment either (except for a few sub-contracted mice etc). They grow fat on royalties from software.

With the launch of Chicago imminent, I'd say that Apple has just about six months left in which to shape its final future. And my bet is that Apple will do nothing, and sink into irreversible decline.

— Date with the Future —

I have been working on a feature for these pages which deals with the whole issue of data storage cards like smart cards. How they work, how much information they can store, what they can do with it and the security implications. One point that emerged early and clearly is that some people are very worried about any plan to bring in Identity Cards, especially using cards which can store very large volumes of information.

Witness the recent fuss about the government's scheme for a photo driving licence. This reminds one of the fuss which preceded launch of the licences currently in use.

After complaints about loss of privacy, age and sex were not listed. But when I hired a car in the US last year, the counter clerk wished me happy birthday. Date of birth and sex, the clerk pointed out, are buried in the innocent-looking six-figure Driver Number which is printed over the driver's name.

Since then I have found friends and work colleagues split between those who say "Oh everyone knows that" and those who say "I

never knew that". Even those who do know, do not know how to read the numbers.

Although it is easy to decode the date when you know the tricks, you first have to know the tricks. The date code varies with the month and is further disguised by the code used for sex. I checked a collection of friends' licences and birthdates to be sure I had fully cracked the code.

The first and last digits tell the year of birth. The third digit gives single figure months (January – September). But double figure months (October – December) use the second and third digits. The second digit has 5 added where the driver is female. The fourth and fifth digits give the day of the month.


So number 359149 tells that the holder is female and was born on 14 September 1939. Number 306107 tells that the driver is male and born on 10 June 1937.

Did you know that this information is available to any police officer who asks to see your driving licence? Does it bother you?

**"Electronics Workbench
is the best simulator to
design and verify circuits."**

*Gordon MacDonald
Production Engineer Technician*

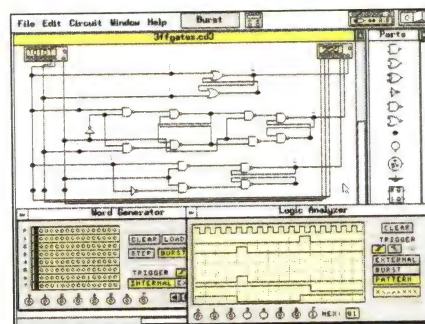
Electronics Workbench is a highly productive bench where you design and verify circuits in a fraction of the time. Connections are always perfect. Wires route themselves. And the simulated components and test instruments work just like the real thing.



Digital Module: Analyzing a logic circuit.

It's faster than building with actual components because you change connections and component values instantly. And since the simulated components are free, you don't need to replace burnt-out parts or keep an extensive inventory. The result: You save precious time and money. Guaranteed!

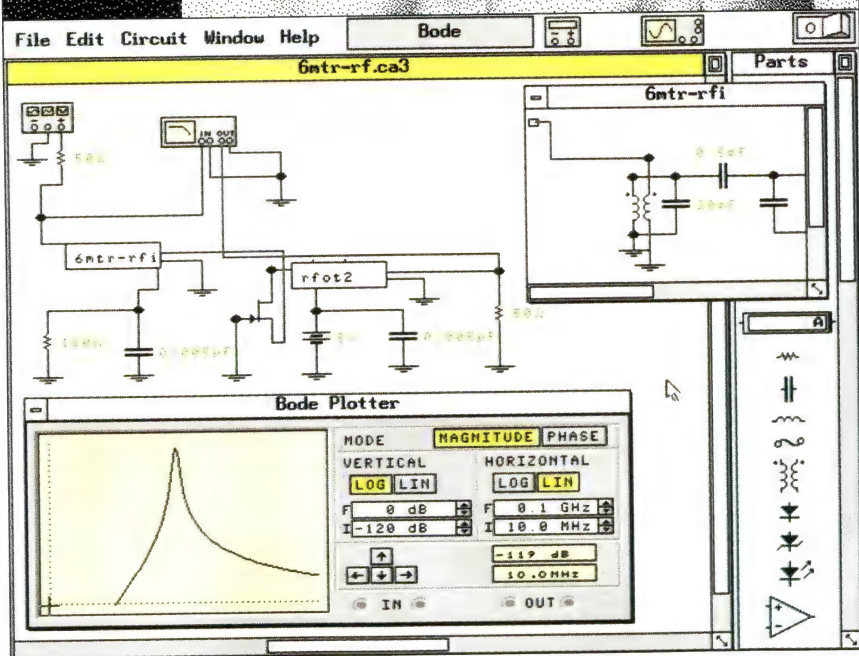The standard for simplicity and power for over six years, Electronics Workbench is the most popular tool of its kind. It has gained worldwide acclaim as the ideal complement to any test bench. **Fact: Over 90% of our customers recommend it to their friends and colleagues.**



Analog Module: Tuning an RF front end.

Electronics Workbench®

The electronics lab in a computer™

Call: 44 0203 233216

Robinson Marshall (Europe) PLC


Nadella Building, Progress Close, Leofric Business Park, Coventry, Warwickshire CV3 2TF
FAX: (44) 0203 233210

*30-day money-back guarantee.

Shipping charges - UK £4.99. All prices are plus VAT.

All trademarks are the property of their respective owners.

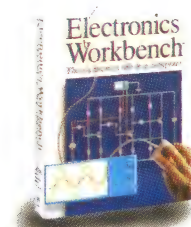**With the purchase of Electronics Workbench. Offer valid until October 15, 1994.



Just £199*
For DOS, Windows or Mac Version.



WHETHER ELECTRONICS IS YOUR HOBBY OR YOUR LIVELIHOOD... YOU NEED THE MODERN ELECTRONICS MANUAL

**ORDER NOW
and get a
FREE SUPPLEMENT
plus our
30 DAY MONEY BACK GUARANTEE**

When the input of the next counter (the carry output of the last counter) leads the time input and the carry ten leads the input of the hardware.


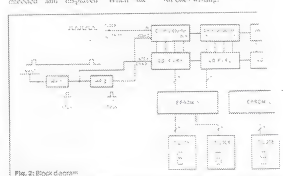


Fig. 2: Block diagram

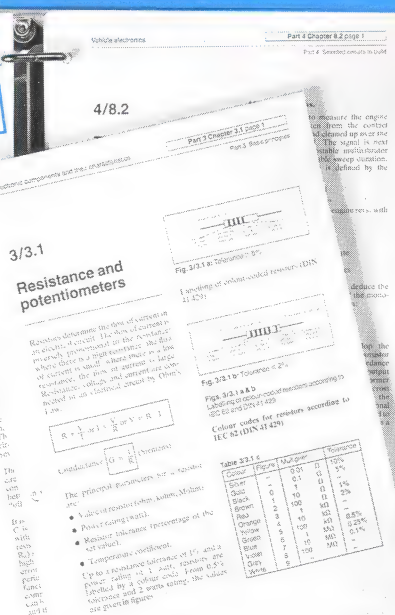

The essential reference Work

- Easy-to-use format
- Clear and simple layout
- Regular Supplements
- Sturdy ring-binder
- News of latest developments
- Full components checklist
- Extensive data tables
- Detailed supply information
- Ready-to-transfer PCBs
- Comprehensive subject range
- Detailed assembly instructions
- Professionally written

EVERYTHING YOU NEED TO KNOW ABOUT ELECTRONICS!

If the fascinating and fast-changing world of electronics is your livelihood, your study subject or simply your passion, the revised edition of **THE MODERN ELECTRONICS MANUAL** is the reference work for you to have at your side.

The Base Manual contains information on the following subjects:

BASIC PRINCIPLES: Symbols, components and their characteristics, passive component circuits, power supplies, acoustics and electroacoustics, the workshop, principles of metrology, measuring instruments, digital electronics, operational amplifiers, timers, physics for electronics.

CIRCUITS TO BUILD: Construction techniques, radio, telephony, microcomputing, measuring instruments, vehicle electronics, security, audio, power supplies, electronic music (over 25 different projects).

REPAIRS AND MAINTENANCE: Basic circuit operation for radio, television, audio/hi-fi, telephones.

DATA: Diodes, transistors, thyristors and triacs, digital and linear i.c.s, microprocessors.

The Manual also covers **Safety, Specialist Vocabulary with Abbreviations and Suppliers.**

OVER 1,000 pages, with over 900 diagrams and photographs, A4 looseleaf format weighing over 3.5kg.

ALL-IN-ONE AND EASY-TO-USE: A sturdy ring-binder allows you to use the Manual on your workbench. The looseleaf format also means you can slot in the regular supplements as they arrive – so all your information is there at a glance.

EXTENSIVE GLOSSARY: Should you come across a technical word, phrase or abbreviation you're not familiar with – simply turn to the glossary included in the Manual and you'll find a comprehensive definition in plain English.

GUARANTEE

Our 30 day money back guarantee gives you **complete peace of mind**. If you are not entirely happy with the Manual, for whatever reason, simply return it to us in good condition within 30 days and we will make **a full refund of your payment** – no small print and no questions asked. (Overseas buyers do have to pay the overseas postage charge).

Now – at last – the most comprehensive reference work ever produced at a price you can afford, the revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the essential information you need.

Over 1,000 pages of well-organised and clearly explained information is brought to you by an expert editorial team whose combined experience ensures the widest coverage.

Regular supplements to this unique publication, each around 160 pages, mean that you will always be kept abreast of the latest developments from around the world as they occur

REGULAR SUPPLEMENTS

Unlike a book or encyclopedia, the Manual is a living work – continuously extended with new material. Recent or upcoming supplements include radio, superconductors, electric motors, basic electronic building blocks for beginners which can be joined together to construct elaborate circuits, filters, IBM PC and compatibles (including updating/expanding PCs). Supplements are sent to you approximately every two months. Each supplement contains approximately 160 pages – all for only £23.50 + £2.50 p&p. You can of course return any supplement (within 10 days) which you feel is superfluous to your needs.

RESPONDING TO YOUR NEEDS

We are able to provide you with the most important and popular, up to the minute, articles in our supplements. Our unique system is based on readers


requests for new information. Through this service you are able to let us know exactly what information you require in your Manual. You can also contact the editor directly in writing if you have a specific technical request or query relating to the Manual.

ASSEMBLING ...

There's nothing to beat the satisfaction of creating your own project. From basic principles to circuit-building, the Manual describes clearly, with appropriate diagrams, how to assemble radios, loudspeakers, amplifiers, car projects, measuring instruments etc. The revised edition of The Modern Electronics Manual contains practical, easy-to-follow instructions for building a wide range of projects. It shows you how to make fun gadgets such as a remote control door opener and a digital rev. counter for your car. It also tells you how to construct useful devices like test gear, security and

baby alarms – plus – many more popular devices.

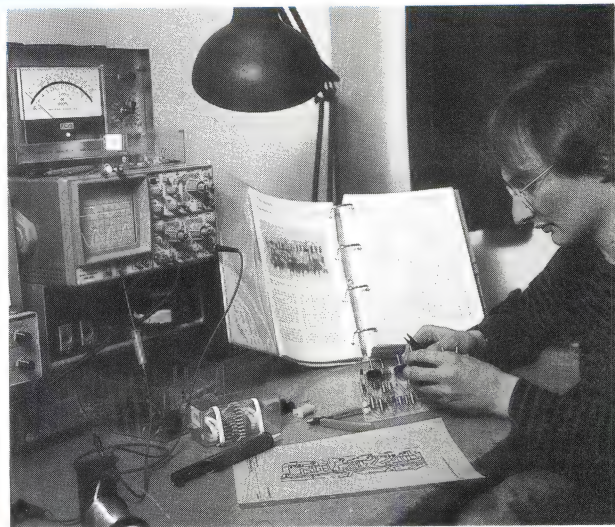**Wimborne Publishing Ltd.,
Allen House, East Borough,
Wimborne,
Dorset BH21 1PF
Tel: 0202 881749 Fax: 0202 841692**



THE MODERN ELECTRONICS MANUAL

Revised Edition of Basic Work: Now contains over 1,000 pages of information.

Regular Updates: Approximately 160-page supplements of additional information which are forwarded to you immediately on publication. These are billed separately and can be discontinued at any time.

Presentation: Durable looseleaf system in large A4 format (297mm × 210mm)

Price of the Basic Work: £39.95 + £5.50 p&p (to include a recent supplement free).

PLEASE send me **THE MODERN ELECTRONICS MANUAL** plus a **FREE SUPPLEMENT**. I enclose payment of **£45.45**

(£39.95 plus £5.50 postage and packing). Should I decide **not** to keep the Manual

I will return it to you in good condition within 30 days for a full refund of this payment. I shall also receive the appropriate supplements several times a year.

These are billed separately and can be discontinued at any time.

FULL NAME
(PLEASE PRINT)

ADDRESS

..... **POSTCODE**

SIGNATURE

☐ I enclose cheque/PO payable to Wimborne Publishing Ltd.

☐ Please charge my Visa/Mastercard/Access

Card No. **Card Ex. Date**

ORDER FORM

Simply complete and return the order form with your payment to the following address:

**Wimborne Publishing Ltd, Allen House,
East Borough, Wimborne, Dorset BH21 1PH**

We offer a 30 day MONEY BACK

GUARANTEE – if you are not happy with the Manual simply return it to us in good condition within 30 days for a full refund.

Overseas buyers do have to pay the overseas postage – see below.

OVERSEAS ORDERS: All overseas orders must be prepaid and are supplied under a money-back guarantee of satisfaction. If you are not entirely happy with the Manual return it within a month for a refund of the purchase price (you do have to pay the overseas postage). **SEND £39.95 PLUS THE POSTAGE SHOWN BELOW:**

EIRE	AIR MAIL ONLY £11
EUROPE (E.E.C. Countries)	AIR MAIL ONLY £20
EUROPE (non E.E.C.)	SURFACE MAIL £20, AIR MAIL £26
U.S.A. & CANADA	SURFACE MAIL £25, AIR MAIL £32
FAR EAST & AUSTRALIA	SURFACE MAIL £31, AIR MAIL £33
REST OF WORLD	SURFACE MAIL £25, AIR MAIL £44

Note surface mail can take over 10 weeks to some parts of the world. Each manual weighs about 4.5kg including the free supplement when packed.

All payments must be made in £'s Sterling payable to Wimborne Publishing Ltd. We accept Mastercard (Access) and Visa credit cards.

CIRKIT ELECTRONIC CONSTRUCTORS CATALOGUE

NEW WINTER '94/95 EDITION

- ▶ 280 pages packed with over 4000 products and now with news and features
- ▶ New additions to Cirkit's unique range of kits, including: IR Remote Control System, Combustible Gas Detector, Mains Carrier Audio Link, Mains Carrier Remote Control, Electrical Appliance Watt Meter, Breath Tester, TV Tuner
- ▶ Two feature projects, fully detailed articles for Hi-Fi quality Infra-red Cordless Headphones and 'Chiptester' a logic IC tester with full PC software, with full construction kits available for both
- ▶ 100s new products, including: mobile phone batteries and chargers, low cost thermometers, ICs, LEDs and books
- ▶ Available at most large newsagents or direct from Cirkit



Cirkit

Cirkit Distribution Ltd

Park Lane • Broxbourne • Hertfordshire • EN10 7NQ • Tel: Sales (01992) 448899 • Fax (01992) 471314



EMBEDDED CONTROLLERS

JOHN DAVIES B.Sc.

From fly-by-wire aircraft to automobiles and home control-systems, the applications for embedded controllers are increasing in number and complexity.

THESE days most people are familiar with personal computers in one way or another. They may use them at work, see them while shopping or, more often than not, play games on them. There is, however, another type of computer which is becoming more and more common and which comparatively few people are aware of. This other type is the *embedded controller* which usually has no human interface other than maybe a few flashing lights.

Before embarking on a tour of embedded controllers it is worth defining a few points. Firstly for the purposes of this article, the author has defined an embedded controller as a computer which is dedicated to one task only.

This task may be to control a washing machine a TV, or the ignition system of a car, as will be seen the possibilities are endless. Secondly, because the microprocessors used in embedded controllers contain many peripheral devices (interrupt controllers, memory, serial interfaces etc.) they are generally called microcontrollers.

The rest of this article looks at where and why embedded controllers are used, what the differences are between them and the average PC (Personal Computer) and what design problems are faced.

APPLICATIONS

The earliest application of an embedded controller that the author has discovered is the small computer developed for the *Apollo Lunar Programme* of the 1960s. This computer was designed to take control of the Lunar Module while it orbited behind the Moon and was thus unable to communicate with the computers on Earth.

Since then embedded controllers have been used in aircraft, initially for navigation and then for weapons control, and latterly for fly-by-wire systems whereby the entire aircraft is controlled by computer. Similar applications have been found in the shipping world and the latest P&O liner being built in Germany at the moment will be steered into port by means of a small joystick on the bridge.

One of the largest and most obvious applications, however, is in the car market. These applications were instigated by the demands of the motorsport industry for

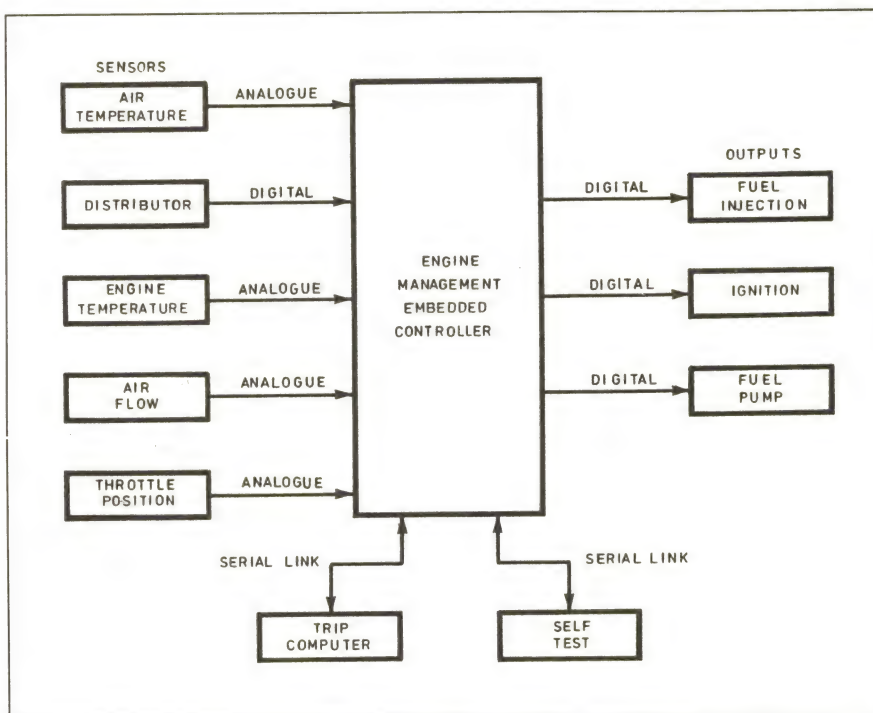


Fig. 1. Typical engine management system.

more and more power from existing engines and these developments have now spilled over into normal road cars. It is now very unusual for even middle of the range cars not to have an engine management system based on an embedded controller.

The boom over the past few years in the home entertainment industry has also seen the introduction of embedded controllers into televisions, video recorders etc.

Another area which has also been revolutionised by the availability of cheap embedded controllers is the design and application of alarm systems (both fire and intruder systems). Even cheap domestic alarm systems costing less than £100 will probably have a small microcontroller inside them. More sophisticated systems will even go to the length of having a microcontroller inside each sensor.

The smallest embedded controllers in use at the moment are the credit card sized "smart cards". They are used for a variety of applications, e.g. high security

identification cards, rechargeable cards for electricity meters etc., and usually contain a simple microcontroller and a small amount of memory.

MOTIVATION

There are three main reasons for introducing computer control. First, an improvement in performance in the equipment being controlled can usually be expected. The major boost in power and handling obtained by Formula One racing cars is due in no small part to the skill of the engineers who designed the on-car electronics. Indeed the power increase is so great that many of the electronic aids are now being banned.

Applications in road cars have also resulted not only in power increase but also more importantly in economy. Recently, however, the reduction in exhaust emissions has become essential and embedded controller applications are the only real way to make progress. Fig. 1 shows the

way in which a typical engine management system would work.

Phenomenal increases in speed and performance have also been obtained in modern warplanes which now have very sophisticated weapon systems which allow the attacking of multiple targets simultaneously.

The second reason for using embedded controllers is to provide features that could not be provided using conventional analogue based systems. Formula One cars' active suspension and traction control systems, for example, could not realistically be implemented any other way. Similarly, the sophisticated video recorder programming methods using on-screen menus, barcodes and code numbers could not be done without embedded controllers.

Finally, embedded controller based systems are usually more reliable and need less calibration than their analogue counterparts. Self test and diagnostic software can be built in to ease repair work and self calibration features can be used to minimise any adjustments required for measurement systems.

PC COMPARISON

The first and most obvious difference between a PC and an embedded controller is the lack of a keyboard or screen. The embedded controller's view of the world is obtained via analogue or digital signals. The digital signals can be represented by one bit of information, either on or off. An analogue signal, however, is slightly more complex in that it theoretically has an infinite range of values.

To simplify matters an analogue voltage is converted into a digital number before being read by the microcontroller. The resolution of the conversion process depends on the application. A simple volume control for a hi-fi may only need six bits of resolution, where one bit represents 1/64th of the maximum voltage.

High performance measuring equipment, however, may need up to 16 bits of resolution where one bit represents 1/65536th of the maximum voltage. Needless to say the more resolution needed the more expensive the analogue to digital converter devices and the more susceptible the circuit is to noise.

An average PC usually has at least 640Kbytes of RAM and more often anything up to 4Mbytes of RAM. The average embedded controller application, however, usually uses only hundreds of bytes of RAM with possibly a few Kbytes of EPROM for program storage. In addition, the average microprocessor chip used in embedded controllers packs in far more interfaces and peripheral devices than does say an 80386 or 80486 as used in many PCs.

Embedded controllers are also generally more rugged than the average PC, and this is discussed in more detail later.

PROBLEMS

The first and most obvious embedded controller problem is that of programming. How do you program a computer which has no keyboard, screen or disk drive and whose program is stored in an EPROM? Early embedded controller applications were programmed by hand coding the assembler software and entering it byte by byte into an EPROM programmer which was then used to program the EPROM. The controller was switched on and more often than not didn't work.

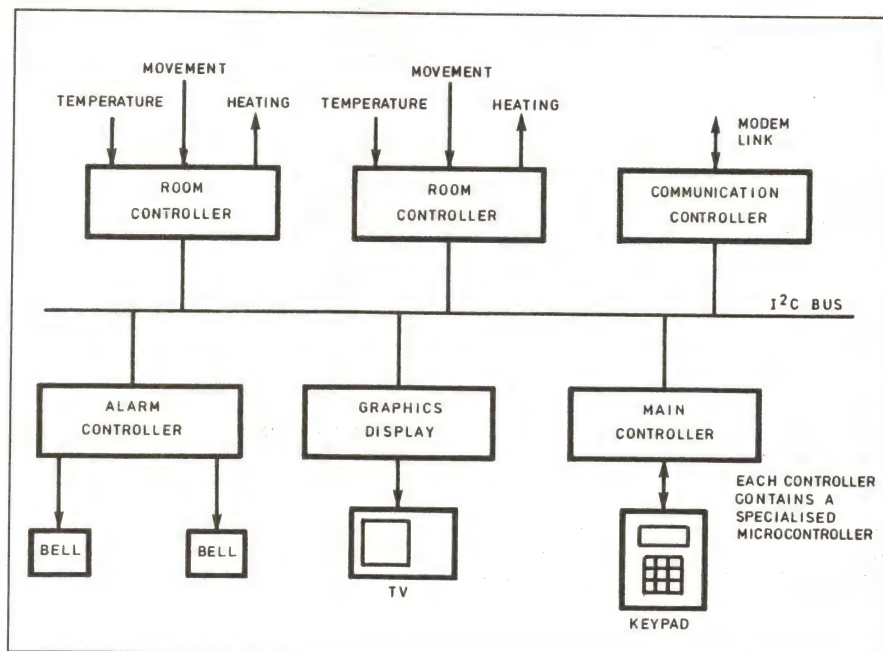


Fig. 2. Future home control system.

These days the software is written and assembled or compiled on a separate computer (usually a PC), traditionally in assembler but more and more in high level languages such as C. The PC is then normally attached to a separate piece of equipment called an emulator which has a pod which can be plugged into the circuit board in place of the microcontroller chip. The programmer can then download the software into the emulator and can control the operation of the microcontroller by single stepping through the program or setting breakpoints in much the same way as developing software to run on a PC.

Emulators for a simple microcontroller chip cost a few hundred pounds whereas emulators for specialist complex chips used for telecommunications applications can cost upwards of ten thousand pounds. When the program is running satisfactorily the emulator is removed, the microcontroller replaced and the software programmed into an EPROM.

The second major problem is that while the average PC will operate in a relatively benign office environment the average embedded controller application will face a more hostile climate. An engine management controller in a car, for example, will face an ambient temperature of -30°C in Norway in mid-Winter and an ambient temperature of $+50^{\circ}\text{C}$ in southern Spain in mid-Summer.

Very careful thermal design of the equipment and the use of rugged, almost military specification chips are needed to ensure reliable operation. The use of CMOS based low power devices is very important and most manufacturers of microcontrollers offer this option. Vibration can be a problem with extra restraints needed for any large components, e.g. capacitors, mounted on the printed circuit board (p.c.b.).

A less obvious problem is that of humidity and heat cycling. An alarm system in a warehouse, for example, can be quite cold overnight then warm up rapidly during the day as the heating is switched on and then cool down again overnight. This sort of heat cycling can lead to condensation forming on p.c.b.s and components usually with dire results. To overcome this problem the p.c.b.s may need to be sprayed with a waterproof coating.

LEGISLATIVE IMMUNITY

A further design problem which has only really been highlighted recently with European and worldwide legislation is that of Electromagnetic Compatibility or EMC. There are two main aspects to this legislation, namely susceptibility and emissions.

Susceptibility means that your embedded controller application must not be affected by other electrical equipment. Usually this means that the circuit must be unaffected by large voltage transients occurring in the vicinity. These can be the ignition system in a car, lightning strikes, switched mode power supplies or even the EHT in a television. The voltage transients may be conducted through the air or induced onto wires connecting to the equipment.

Emission legislation means that your application must not emit voltages such that it would be hazardous to other equipment. This may not seem to be a major problem for embedded controllers but there are two main areas of concern.

Firstly microcontrollers will operate at clock speeds up to 10MHz and the harmonics from digital signals at this frequency are large enough to interfere with radio equipment. Secondly, switched mode power supplies are usually used to reduce size and increase efficiency and these also radiate at high frequency, especially onto the mains power input which is usually run all around a building.

Compliance with the various new bits of legislation is now essential as from 1996 no new electrical equipment may be sold in Europe unless it passes the relevant EMC tests.

RUN-TIME ERRORS

A final problem which may not at first seem to be a problem is that of dealing with errors which occur while an embedded controller is running. If something goes astray with an expensive PC spreadsheet, for example, then the user can expect a reasonably friendly message explaining what has gone wrong and what the computer is going to do about it. With cheaper software the computer usually sulks and


the only remedy is the reset button or the on/off switch. This is mildly annoying but not normally a problem unless a large amount of data has just been lost.

With an embedded controller system, though, a message such as "Cannot find file.." or "MSDOS Error 2" is not very useful if the washing machine is busy emptying its contents over the floor or worse if you are landing your fly-by-wire fighter aircraft on an aircraft carrier in the dark.

A common error which can lead to such problems is to declare an array of "n" elements and then to try and access the "n+1th" element of that array. At best you get an incorrect result, at worst you overwrite some other vital data. Some languages, e.g. ADA which is used for military applications, will detect errors and allow the programmer to write software which will handle the errors if they occur. Most languages, though, don't have this feature and unless great care is taken over the software an error will cause the embedded controller to fail, usually disastrously.

A technique used to increase the reliability of embedded controller systems in life critical situations is to use more than one system for each function. Three systems are commonly used with three independent microcontrollers using a "majority vote" system to define any output. This means that an error in one controller will be overruled by the other two controllers if operating correctly.

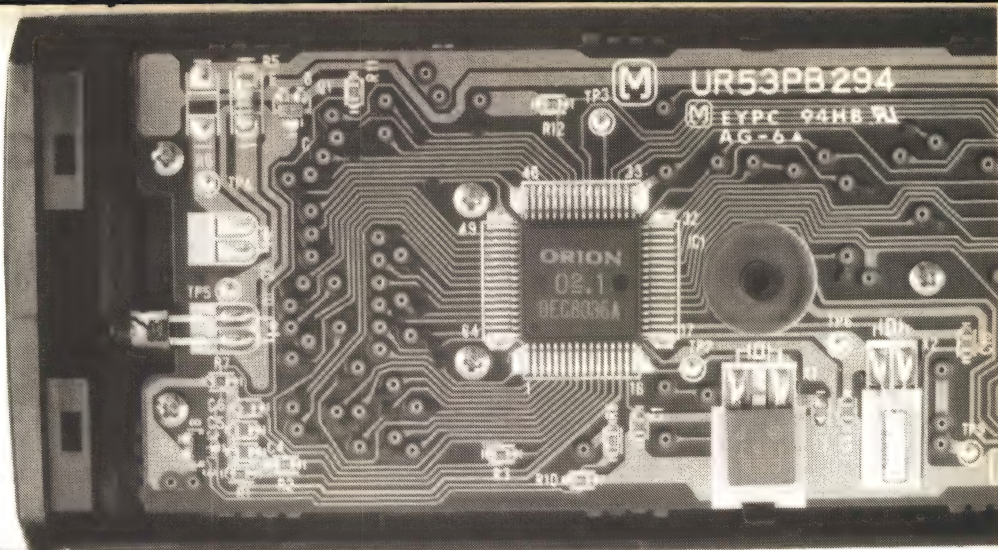One problem which will not be solved with this method is that any bugs in the software will be replicated in each controller so that although hardware failures will be handled, software bugs will not. A method of overcoming this last difficulty is to have three systems as before but to



Typical embedded controller application – TV remote controller.

have each system programmed by a different team so that hopefully software bugs are not replicated across the three systems. This method is used on projects such as the Airbus fly-by-wire systems.

FUTURE DEVELOPMENTS

Over the past decade the trend for microcontrollers has been to make them smaller and consume less power whilst packing in more features. There has also been a tendency over the past few years to provide microcontrollers with dedicated specialised functions. An example of this is a microcontroller which is able to drive an l.c.d. and to scan a keyboard for use in remote control handsets. Others provide specialist communication path interfaces, e.g. for telephones.

The interconnection of chips is also being changed from the traditional parallel address and data busses to using a simple serial link. The I²C bus pioneered by Philips is an example. Fig. 2 shows a possible future application for an integrated home control system using all the features described above.

Finally, what will undoubtedly change is the range of skills needed by the engineers who design and build these embedded controller systems. No longer will there be a clear cut distinction between hardware and software design and engineers will need both types of skills. The final system design for any embedded controller application will always be a compromise between hardware and software design and the most successful design will be the one which combines the best from each discipline. □

KARE ELECTRONICS

8051 In-Circuit Emulator




- Adapters for 8751, 8051(EA = 1), 80C451, 80C552, 80C562, 80C652 • Built-in assembler
- Optional EPROM and 8751, 8752, 87C552, 87C752 programmers available from £39
- 10 day money back guarantee.

Supported Devices:
8051/52
80C51/52
8031/32
80C31/32
(EA* = 0)

colour catalogue available

£264 INC

P.C. E(E)prom Programmer

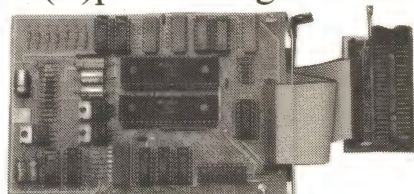

£145 INC
BEST EVER VALUE

For PC
XT, AT,
386, 486.

- Internal card for greater security • Reads, verifies & Program's devices to 4 Meg. • Fast Program's 64A in 10 sec.
- Binary, Intel Hex, Motorola S. Format • Colour software.
- Adaptors available for Micro's, 16 bit, Epson cards etc.

All prices include V.A.T. Please add £5 p&p and send cheque with order. Allow up to 10 days for delivery.

If you require any further information or demo disk please call.

32, Pear Tree Ave., Ditton, Aylesford, Kent ME20 6EB. Tel/Fax 0732 844633

89C51 Microcontrollers

£17.50 INC

Flash version of 87C51.

Z80 Controller Board (with Basic Interpreter).

- Fully programable in BASIC via RS232 on PC
- CMOS Z80 processor • Up to 64 I/O Ports
- 8k of User Memory • Eprom Blowing Facility.

£60.00
INC

80C552 Embedded Controller/ Development Board MA-012/32

£52.88
INC

- Microcontroller (Installed) 80C552 (MA-012)
- Credit card size PCB 5x7cm • 32K SRAM (62256)
- Ram backup – just connect 3.6V ni-card
- Eprom socket to take 2764/27256
- 96 interface connections
- Stackable with other modules providing additional facilities.

Development kit for above.

£11.75 INC

Monitor Eprom

(Not available separately)


- Ideal for students and enthusiasts
- Download Hex files • Edit both Data/Prog data and SFR's
- Full Monitor Facilities plus more.

Device Programmer


£349
INC

PLD, GAL, PALCE
As well as E(E)proms, Flash, Micro-controllers inc PIC's & Serial E(E)prom.

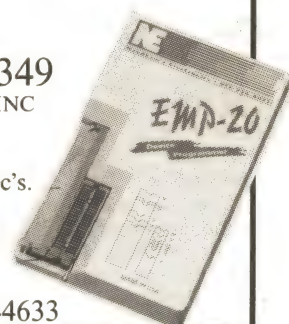Fast programming 27C040 4 meg 90 sec's.
Small enough for briefcase.
Made in U.S.A.



UNIVERSAL DIGITAL CODE LOCK

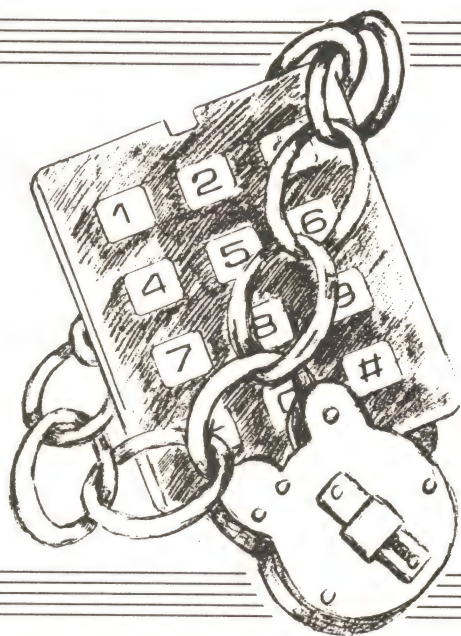

BART TREPAK

PIC and choose the code that keeps crooks from your pad.

EVER since the earliest civilisations, when men found that they were not all equal and some had more possessions than others, there has been a need for locks. Even the ancient Egyptians had one which, interestingly, worked on the same basic principle as the modern pin-tumbler lock mostly in use today for domestic applications, although theirs was much bigger and made mostly of wood. This simple affair, backed up no doubt by draconian punishments for offenders (such as chopping the hands off anyone caught stealing etc.) was presumably sufficient to keep one's valuables safe.

With the progress of civilisation and technology, the sophistication of the locksmith and the criminal has advanced to the stage where complicated mechanical locks with three, five or more levers are required to satisfy insurance companies while the more liberal approach to punishment ensures that even these are not always sufficient to deter the burglar.

KEY PROBLEMS

The "trick" with any lock design is to make it easy to open for the legitimate owner, but extremely difficult for everyone else. With mechanical locks this is done by providing the owner with a key which (hopefully) only he possesses.

The problem here is that while it is possible to buy a duplicate key or at least have one cut, it is not possible to buy a duplicate lock with the result that instead of having one key to open all your doors, a whole bunch is required. This may be better from the security point of view but it can be very annoying to have to carry around all this metal and then to fumble in the dark to find the correct key. (Ancient keys were very large, some up to a metre long so they must have had an even bigger problem and no electronics to offer a solution!)

Worse still, keys can be easily lost or left inside the premises and then the lock becomes more of an obstacle to the legitimate owner than to the burglar who feels less inhibited about, say, smashing a window to get in.

Those who have had the misfortune to lock themselves out of their car will know

the feeling of frustration, especially when told stories of "professionals" who can break into any car in 30 seconds. When keys are stolen the position is even worse since all the locks may have to be changed to ensure that a thief does not gain access.

Combination locks overcome most of these difficulties at a stroke because they eliminate the need for a key, but there remains the problem of changing the combination if the code is discovered. This can be difficult or even impossible with mechanical combination locks but is relatively simple with electronic ones. Over the years, some lock chips have appeared on the market which required the changing of a few links to alter the code, while later developments have a memory which can be re-programmed from the key pad.


These perform admirably but still have limitations which preclude their use in many applications. It was therefore decided to design a lock which would be virtually impossible to pick (unless one had the patience of a saint) and which would be useful in as wide a range of applications as

possible, from replacing your front door lock, to preventing the unauthorised use of your computer. It is worth mentioning at this point that there is no such thing as a totally secure lock as given sufficient time and a computer, any code can be cracked. Also, it should be remembered that a lock is only as good as the door to which it is fitted.

LOCK REQUIREMENTS

Combination locks are used in many different kinds of premises all of which can have different requirements, but common to all, is that they must be simple to use, difficult to open if the code is not known and easy to re-program. Not much more is required from a domestic lock but for one used in a hotel or guest house for example, two open codes would be an advantage. One could be given to the *customer* or guest which he or she could change at will, while the *management* would have another code which would allow the staff to enter rooms to clean or when the guest had left and omitted to leave the number that he had programmed.

The *customer* should be able to change only his own code while the *management* should be able to change either should

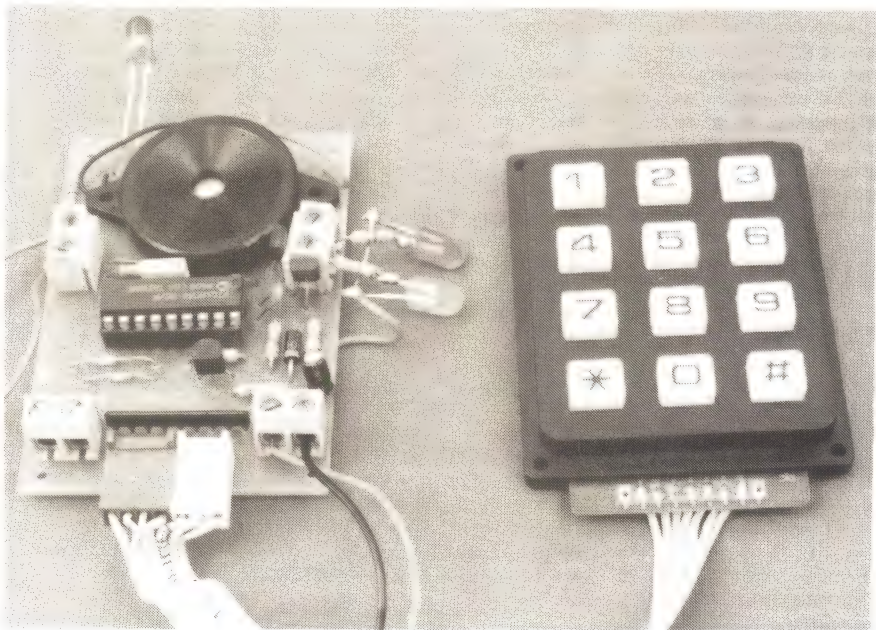

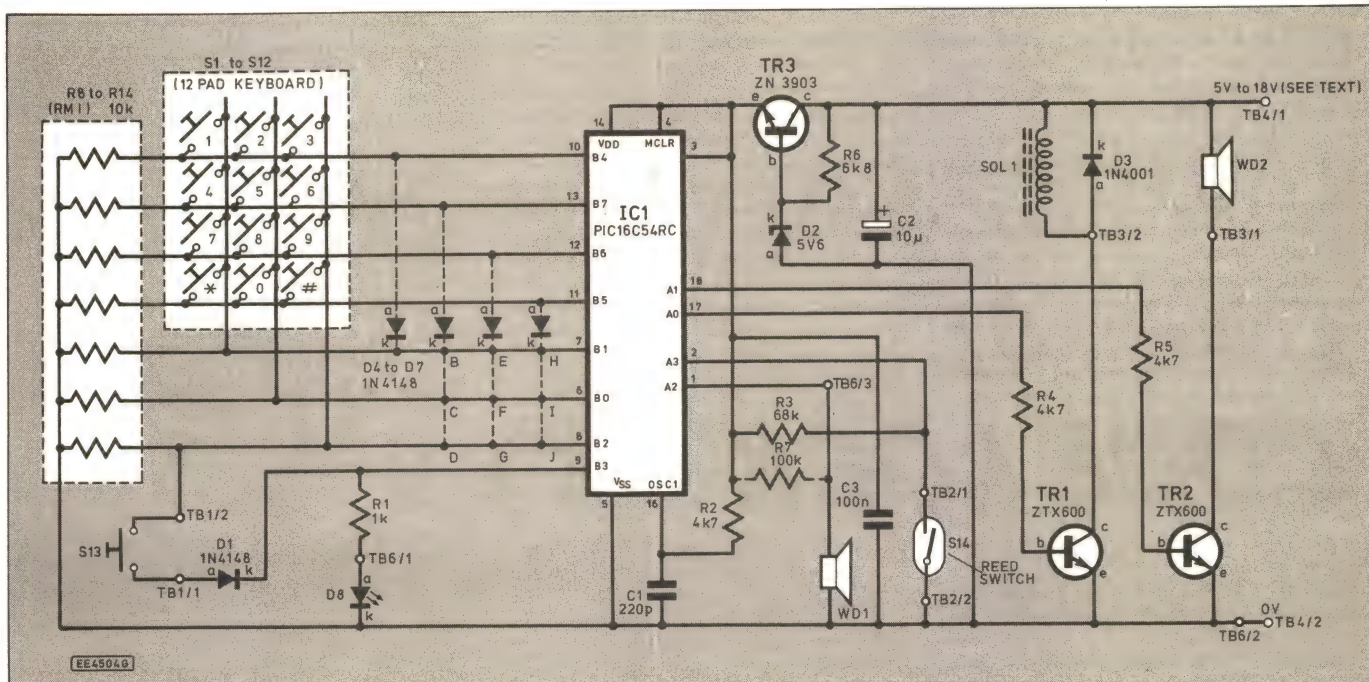


Fig. 1. Principal circuit diagram for the Universal Digital Code Lock.

this be required. In an office or research laboratory, the requirement could be similar but it may be useful to give cleaners or other people who need to have access for a limited period a special *temporary* code without the need to go around and re-program all the locks once they had gone. The lock to be described has a special temporary code which can be easily programmed and automatically cancels itself 15 minutes after it is last used.

Another requirement concerns the use to which the circuit is put. Most electric door release mechanisms require to be energised for a short period only to enable the door to be pushed open, but in some situations, such as arming or disarming a burglar alarm or car ignition, the output must remain latched in the open or closed state. The lock is designed to provide either type of output and this can be selected by means of a diode link.

In some applications, it could be useful to be able to connect a door contact enabling the unit to sense if the door was open or closed. A warning could then be given if the door were inadvertently left open, a desirable feature for fire doors or doors in security sensitive areas.

An external alarm could also be sounded if the door was forced, enabling the unit to function as a self contained alarm for the door or be connected to a more comprehensive alarm system covering the whole building. This feature has also been added to the circuit and may be used with a reed switch/magnet combination, the contacts being normally closed when the door is closed. If this feature is not required, the input may be permanently shorted with a wire link.

Programming should also be easy (for the legitimate owner) without the need to take the unit to bits or refer to a manual so this should be possible from the keypad using as few entries as possible. Some digital locks feature EEPROM memories to store the programmed open code if there should be a power failure. This is difficult to justify in terms of cost or even convenience especially if, as in this case, the lock control unit takes only a few seconds to re-program.

Since a battery would be required to power the solenoid to enable the user to enter during a power failure anyway, this battery could also retain the memory contents. The unit consumes so little current that a small battery would easily retain the memory contents for the duration of a power cut.

In this design, programming is carried out by simply entering the current code followed by two depressions of the star ("*") key while the output is open, keying in the new sequence and pressing the star key again. An l.e.d. is included which lights to show when the unit is in the "program mode".

Finally, to make the circuit compatible with any key pad, it should be possible to connect a piezo sounder to bleep each time a key is pressed. This is particularly useful with membrane keypads or those which have little or no tactile feedback. The sounder could then also form the local alarm in case of tampering and alert the user to any errors when programming.

HARD TO PIC

If the lock is to be easy to use, then the open combination should be limited to as few numbers as possible so that the owner does not have to remember long strings of digits or spend a long time entering them. Obviously, the longer the code, the more possible combinations there will be and the harder it will be for the intruder to chance on the correct one, so a compromise must be made.

Given a 12-way keypad, the number of possible three-digit codes is 1728 ($12 \times 12 \times 12$). The corresponding possibilities for four and five-digit codes are 20,736 and 248,832 respectively. If the prospect of trying nearly two thousand combinations sounds daunting, twenty thousand does not bear thinking about, so a four-digit combination was chosen.

To make things more difficult for the determined code breaker or the one who feels he has the time to spend trying every combination, the circuit is designed to sound a warning alarm for a short time and disable the keyboard for a slightly longer time following a preset number of incorrect

entries. This means that assuming that the keyboard lock out time has been set to 15 seconds and the alarm sounds after two incorrect entries, the intruder would only be able to enter at most six digits per minute (in fact, after the first two incorrect digits, every incorrect entry generates a 15 second delay so only four digits can be entered every minute) so that it would take him over three and a half days, working day and night to try them all.

Even ignoring the sheer boredom of this task and the inevitable breaks which would be required, this estimate is wildly optimistic. As there is no indication that the open sequence is a four-digit one and not a three, five, eight or some other number, or that the keyboard is being disabled for most of the time, the chances of someone discovering the combination by trial and error are virtually non-existent.

With so many requirements, the only realistic way of performing all these functions without resorting to twenty or thirty standard logic chips, or developing a custom chip, is to use a microcomputer. This circuit is based somewhat appropriately on a PIC microcontroller and all the above features have been incorporated.

The additional cost of adding any of these features to a basic lock circuit is only a few more lines of program code and many of them can be easily disabled should they not be required in a particular situation. This makes the circuit suitable for the majority of applications from controlling access to buildings or parts of buildings, including flats, hotels or offices, to preventing the unauthorised use of equipment such as computers, domestic alarm systems or car ignition immobiliser/alarm systems. The only modifications required will be the type of output device selected, such as a relay or solenoid, and which diode links are fitted.

CIRCUIT DETAILS

The circuit diagram for the digital code lock controller is shown in Fig. 1. The use of a pre-programmed microcontroller, IC1, reduces the circuit to almost trivial proportions consisting of little more than the chip, keyboard, programming indicator l.e.d.,

piezo sounder and output drivers together with a handful of resistors and diodes required mainly for selecting the various functions. The processor handles everything from the keyboard scanning to driving the outputs and piezo sounder and also contains the RAM which stores the open codes as well as the ROM which stores the program.

The chip includes a power on reset circuit which makes the computer execute its start up routine which consists of "reading" the diode links D4 to D7 and resistor R7, and initialising the memory, after which it settles down to scanning the keyboard and controlling the outputs as required. Resistor R2 and capacitor C1 control the timing of the on-chip oscillator, which in turn controls the bleep frequency and alarm time, etc.

Since none of these times are critical, an R/C oscillator was chosen so that the actual times quoted are only approximate. The prospective intruder is not going to complain if the alarm sounds for only 14 minutes and 35 seconds instead of the full 15 minutes quoted!

For use in a typical domestic lock application, the output would switch on and energise the lock solenoid SOL1 via transistor TR1 for approximately five seconds following the entry of the pre-programmed four digit combination. Each time a digit is entered, the sounder WD1 is beeped and an internal timer restarted so that if no digit is entered within the next five seconds, the digit counter is reset and the next digit is assumed to be the first in the sequence.

Incorrect entries are counted and when the count exceeds the preset number, the internal alarm is sounded and the keyboard is locked out for the preset time. Any further incorrect entries will also do this and will activate the external alarm WD2 via transistor TR2. This may be a loud siren or bell depending on the application and it will sound for approximately 15 minutes, or until the correct security code is entered.

Since the chip requires a 5V d.c. supply whilst most solenoids run at 9V or 12V, Zener diode D2 and transistor TR3 are included to supply the 5V from the higher voltage.

PROGRAMMING

Once the lock is open (i.e. the output is on), the unit may be re-programmed by entering "***" ("*" key twice). This will cause the program i.e.d. (D8) to light and the output to remain on (unlocked) indefinitely, or until the programming sequence is finished even if the unit is being used in the momentary mode. Care should therefore be taken not to leave the lock in this state as some solenoids may not be rated for continuous operation.

Depending on whether the *manager* or *customer* code was entered when opening the lock, (the *manager* code must always start with the "#" key followed by four digits while the *customer* code consists of only four digits) the next four numbers keyed will reprogram that code. The program mode is terminated by pressing the "*" key once, when the i.e.d. will switch off and the output will follow (if the unit is in the momentary mode).

If the "*" key is pressed after fewer than four keys had been entered, the sounder will beep three times and the unit will remain in the program mode until at least four digits have been entered. If more than four digits are entered before the "*" key is pressed, only the last four will form the new

code, so if you make a mistake in programming, simply key in the correct required number before pressing the "*" key.

To change the *customer* code after having entered the *manager* code to open the lock, the "*" key should be pressed twice (to enter the program mode) followed by the "#" key. The following digits will now modify the *customer* code with the "*" key returning the unit to its normal mode, the *manager* code remaining unchanged.

If this is done after the *customer* code is entered, the new code will form the *temporary* code and a 15 minute timer will start which will reset this code when it times out. The *temporary* code may be used to open or close the lock and will reset the timer each time it is used, but if this code is entered followed by "*" the unit will not enter the program mode so that it is impossible to change any codes if only this one is known.

Any of the digits zero to nine may be used in any combination with the same digits repeated if required. The "*" and "#" keys are not allowed as part of the code sequence and the only other limitation is that the *customer* and *temporary* codes must not start with the same digit, i.e. 5451 and 4451 is acceptable but 5451 and 5936 is not.

The same programming procedure is used when the unit is in the latched mode, the only difference being that the output will not switch off when the programming mode is finished by pressing "*" until the new valid code is entered.

The following examples should make the process clear:

Current *manager* code: 1066

Current *customer* code: 1234

Current *temporary* code: 5678

Key sequence entered:

1234 ** 0000 * *customer* code will now be 0000. Other codes remain unchanged.

Key sequence entered:

#1066 ** #0123456789 *

Customer code will change to 6789 (only the last four digits are stored).

Key sequence entered:

5678 ** #98765 ...

No change in any codes because program mode is disabled if temporary code is entered. Program indicator i.e.d. remains off.

Key sequence entered:

6789 ** #4321 *

Temporary code will change to 4321.

Key sequence entered:

#1066 ** 1111 *

Manager code will now be 1111 (enter #1111 to open or close the lock).

ALARM INPUT

As mentioned, the circuit also features an alarm input which may be connected to a normally closed contact such as a reed switch/magnet assembly S14 which opens when the door is opened. If the door is opened while the lock is in the closed mode (i.e. output is off) as would be the case if the door were forced, for example, the alarm is immediately activated (transistor TR2 switches on) and will sound for 15 minutes or until the correct code is entered. Closing the door once the alarm has gone off will, of course, have no effect.

If the lock is first opened and the door then pushed open, the alarm will not go off but the sounder will beep twice every twenty seconds to remind personnel that the door is still open even if the output turns off as it would in the momentary mode.

Once the door is open, closing the lock either manually or automatically while holding the door open will not activate the alarm as this will only be armed when the door is closed and the output (transistor TR1) is off. The door open reminder can be disabled if it is not required by omitting resistor R7. The alarm can be disabled by simply connecting a link in place of the reed switch. In this case resistor R3 may also be omitted.

There is, of course, one problem which occurs when a person already inside the room or building wants to leave, as opening the door (even from the inside) without first entering the open code would set off the alarm.

Another keypad could be provided on the inside but it would be tedious to have to keep entering numbers to leave as well as to enter, so a separate input for switch S13 (which would be mounted within the protected area) has been provided. Pressing this will disable the alarm while the door is opened and remove the need for an exit timer, which would also need to be user programmable to cater for different situations. The alarm is again enabled only after the door has been closed.

SELECTING OPTIONS

Functions such as momentary or latched output, keyboard lockout time (following incorrect entries), number of incorrect entries allowed without setting off the alarm, and initial open codes are selectable by means of diodes D4 to D7 as shown in Table 1. Note that only the pre-programmed *management* code selected is valid after power on so that the first entry must begin with the "#" key. These codes have been chosen to make them easy to remember and some readers may recognise them as important historical dates. 1805

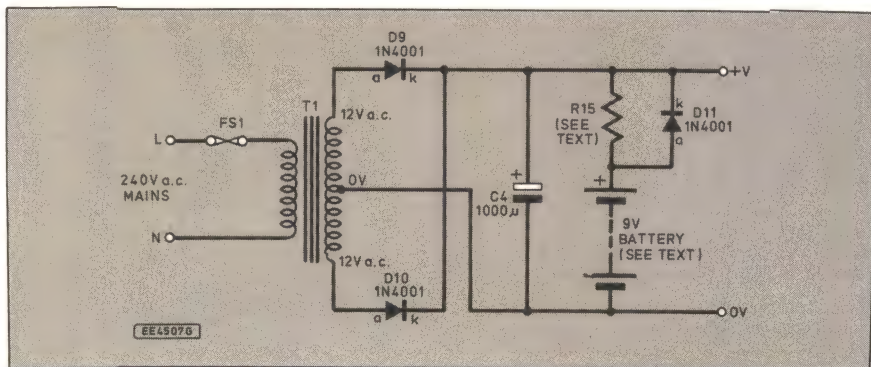


Fig. 2. Suggested power supply circuit.

was the Battle of Trafalgar, 1914 and 1939 the beginning of the First and Second World Wars and 1066 which should need no explanation.

Following initial power-up, customer or temporary codes can be entered and changed, as can the management code, only after the initial preset code has been entered. Note also that irrespective of the preset number of incorrect entries which have been selected, the circuit will give a warning after the first incorrect entry and an alarm following the second after the unit is powered up. This will change to the selected number once the correct sequence has been keyed in.

POWER SUPPLIES

The circuit will operate from any supply in the range 5V to 18V so the choice of supply will be determined largely by the supply requirements of the load and the use to which the unit is to be put.

For door locks and area access applications where a solenoid or electric latch are to be operated, a mains supply, such as that shown in Fig. 2, capable of supplying sufficient current to operate the solenoid will be required, plus per-

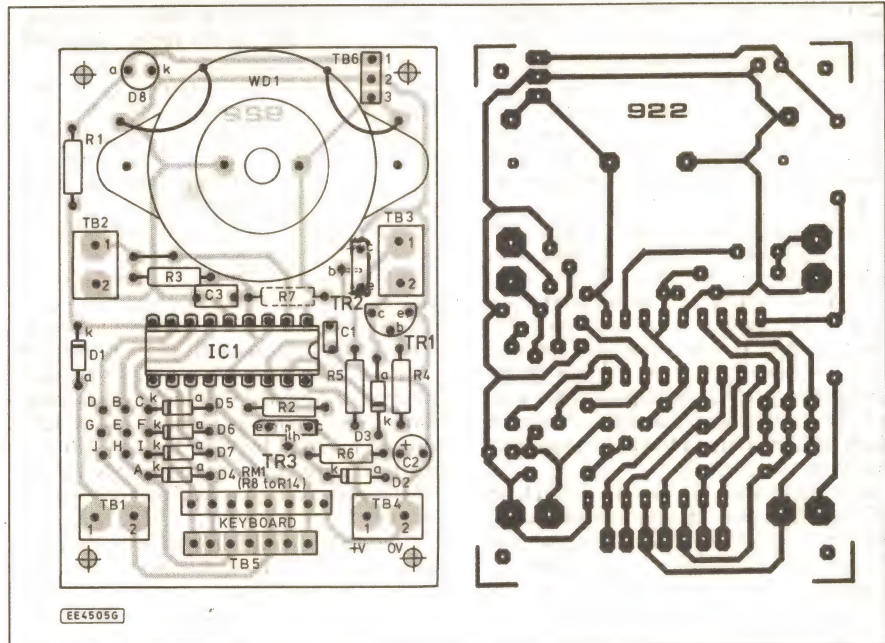


Fig. 3. Printed circuit board component layout and full size copper foil master track pattern.

haps a rechargeable battery with sufficient capacity to operate the solenoid in the event of power failure. This circuit could be treated as a small plug in d.c. power supply with a rechargeable PP3 battery in the case of some low power electric latch mechanisms. Alternatively, it could be a higher power d.c. supply and a stack of rechargeable C or D cells in the case of some heavy duty solenoids.

If the rectified d.c. supply has a slightly higher output voltage than the battery, then this may also be used to trickle charge it via resistor R15. The latter should have a value to limit the charging current to that recommended by the battery manufacturer (usually 0.1 times the amp-hour rating in the case of Ni-Cads). Non-rechargeable batteries should not be used with this circuit.

If the circuit is to be used to switch on a car alarm or disable the ignition, the 12V car battery would be the obvious power supply choice with the lock driving suitable 12V relays. It is not advisable to use the car horn as the external alarm as these are not normally rated for continuous use.

For restricting the use of other equipment such as computer systems,

photocopiers etc., similar power supply and output requirement considerations will apply.

CONSTRUCTION

It is recommended that the circuit is built on a printed circuit board (p.c.b.) as this will make construction quicker and much less error prone. Details of the component layout and full size copper foil master track pattern for the suggested p.c.b. are shown in Fig. 3. This board is available from the EPE PCB Service, code 922.

Care should be taken to ensure that all diodes, transistors, electrolytic capacitors and the integrated circuit are fitted to the board the correct way around. Note also that the resistor network module RM1 must be fitted the correct way around, the common connection usually being indicated by a dot on the component. The microprocessor IC1 is a CMOS type and although the input circuitry at the pins has been designed to protect the device from electrostatic damage it is best to fit a suitable i.c. socket to the board and insert the chip into this.

The order of assembly is of course immaterial but it is usually best to begin

with the low profile components such as resistors and diodes and then progress to the taller ones (capacitors, transistors, i.e.d. and terminal blocks). Resistor R7 should be omitted if the "door open" signal is not required and diode D7 fitted if a latched output is required. Diodes D4 to D6 should be fitted or omitted as required in accordance with Table 1.

The circuit is designed to operate with virtually any keyboard as long as it has matrix connections (i.e. rows

COMPONENTS

Resistors

R1	1k
R2, R4,	
R5	4k7 (3 off)
R3	68k
R6	6k8
R7	100k
R8 to R14	
(RM1)	7 × 10k s.i.l. resistor module
R15	see text

See
SHOP
TALK
Page

Capacitors

C1	220p ceramic
C2	10µ radial elect. 16V
C3	100n polyester
C4	1000µ radial elect. 25V

Semiconductors

IC1	PIC16C54RC
	pre-programmed microcomputer (see text)
TR1, TR2	ZTX600 npn Darlington transistor (2 off)
TR3	2N3903 npn transistor
D1, D4 to D7	1N4148 signal diode (5 off)
D2	BZY88C5V6 Zener diode
D3, D9 to D11	1N4001 rectifier diode (4 off)
D8	5mm red l.e.d.

Miscellaneous

Miniature piezo transducer, printed circuit board available from the EPE PCB Service, code 922; 2-way p.c.b. terminal block (4 off); 3-way terminal block; 18-pin i.c. socket; 7-way keyboard connector (see text); 4 × 3 matrix keyboard.

Optional

S1 push-to-make switch; S2 door contact (reed switch/magnet assembly); siren; solenoid/lock mechanism; power supply/battery (see text).

Approx cost
guidance only

£37

Table 1.

DIODE	POSITION	FUNCTION
D4	A Not fitted	Latched Output Momentary Output
D5	B C D Not fitted	# 1805 Code # 1914 Code # 1939 Code # 1066 Code
D6	E F G Not fitted	1 Incorrect Entry Allowed 2 Incorrect Entries Allowed 5 Incorrect Entries Allowed 255 Incorrect Entries Allowed
D7	H I J Not fitted	10 secs Lockout Time 15 secs Lockout Time 25 secs Lockout Time 5 secs Lockout Time
R7	Fitted Not fitted	DOOR OPEN Warning No Warning


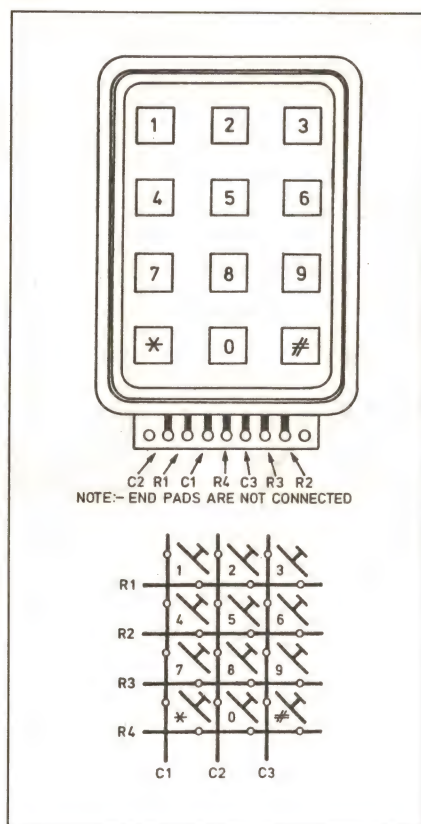


Fig. 4. Keyboard connection details.

and columns) and is not one with a common connection. These are easily distinguished as a 12-way keyboard with a common connection will have 13 terminals while a matrix connected keyboard will have only seven. The choice of keyboard will depend largely on the application, personal preference and of course cost. If the unit is to be mounted outside then a weather proof type should be used, but as long as it is not subjected to driving rain then a membrane type or the low cost conductive rubber type specified may suffice.

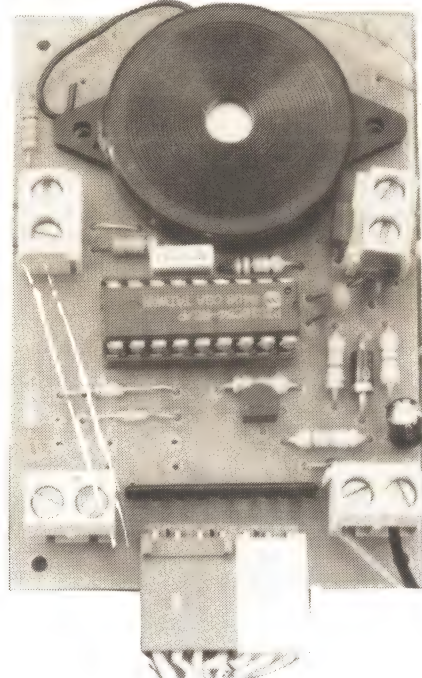The connections for the keyboard are shown in Fig. 4 but if your keyboard does not have the same connections this is not too important as long as the column connections of the keyboard are connected to the column connections on the printed



circuit board and likewise with the rows. In this case the circuit will work, although the numbers will be different and in particular the functions of the "*" and "#" keys may be performed by two of the numbered keys. The wiring details used by the author are shown in Fig. 5.

Although the keyboard could be wired directly to the board using short lengths of stiff copper wire, it is best from a security point of view to mount the keyboard remotely from the unit on a length of ribbon cable. This enables the circuit board to be mounted within the protected area with only the keyboard outside and prevents anyone from simply shorting out the output transistor on the printed circuit board to gain access, which could be easy to do if the whole unit were mounted outside.

KEY PLUGGED

Installation is also made much easier if a plug and socket are fitted to enable the keyboard to be "plugged" into the circuit. Any suitable miniature 7-way plug and socket such as a DIN or D-type connector may be used although a 7-way p.c.b. pin header and mating crimp socket are probably the simplest. These are available in 0.1in spacing in 2, 3 and 4-way versions so a 7-way version can be easily made up.

If other keyboards are used, such as membrane types or even ones made up from individual switches (as long as the switches are connected in a 4×3 matrix), the method of connection will need to be modified to suit. In some applications, it may be desirable to fit the l.e.d. and sounder near the keyboard so that a similar ribbon cable/plug and socket arrangement would be required. To prevent noise pick-up on the keyboard inputs, leads should be kept as short as possible.

Note that this circuit uses a piezo sounder or piezo element which should not be confused with piezo buzzers which, as well as the element, also contain an oscillator circuit to produce a sound when connected to a d.c. voltage. The p.c.b. has been designed to accommodate either a p.c.b. mounted sounder or one with flying leads.

TESTING

When assembly is complete the circuit may be tested using a 9V d.c. supply (or a 9V PP3 battery) with the correct polarity connected to terminal block TB4. Light emitting diodes with one kilohm series resistors may be connected from the terminals of TB3 to the positive line to simulate the solenoid and siren. A toggle or slide switch maybe used to replace the reed

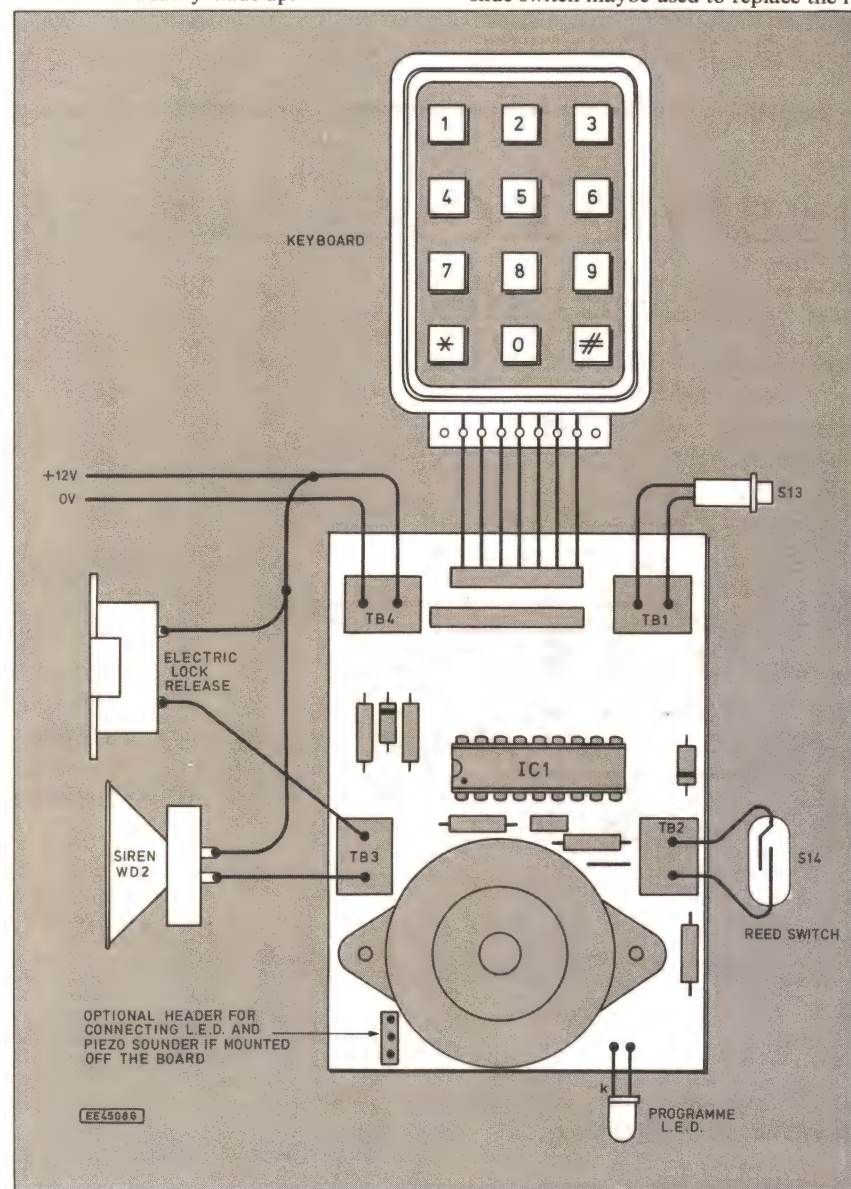


Fig. 5. Details of the interconnections between the printed circuit board and the other components.

switch and connected between the terminals of TB2. A push-to-make switch, S13, should also be connected to the terminals of TB1.

Before plugging in the chip, switch on and check with a voltmeter that you have +5V between pins 5(-) and 14(+) of the i.c. socket. If this is not the case, check the polarity of the Zener diode D2 and transistor TR3. If all is well, *switch off* and insert the chip into its socket.

Note the diode settings and switch on. All the l.e.d.s should be off and the operation of the circuit should be checked. If the circuit appears to go into alarm mode immediately on switch on, check that the switch substituting for the reed switch is closed. If the circuit appears to ignore any keyboard entry, check that diodes D4 to D7 (where fitted) are soldered the correct way around.


INSTALLATION

No details are given for enclosing the unit as so much will depend on how and where the circuit is to be used. For a door lock application, the circuit could be housed in a suitably sized plastic box which could also house the power supply and battery if used. This could be mounted conveniently near to the door to avoid long cable runs to the keyboard, electric lock mechanism, reed switch and siren. Switch S13 could be mounted on the

box. Whether or not the piezo sounder is mounted in the box will depend on if it can be heard from the location of the keyboard.

The keyboard could be mounted on some kind of decorative panel, on which the l.e.d. (and sounder) could also be mounted. The panel need not be particularly robust (such as the thick steel

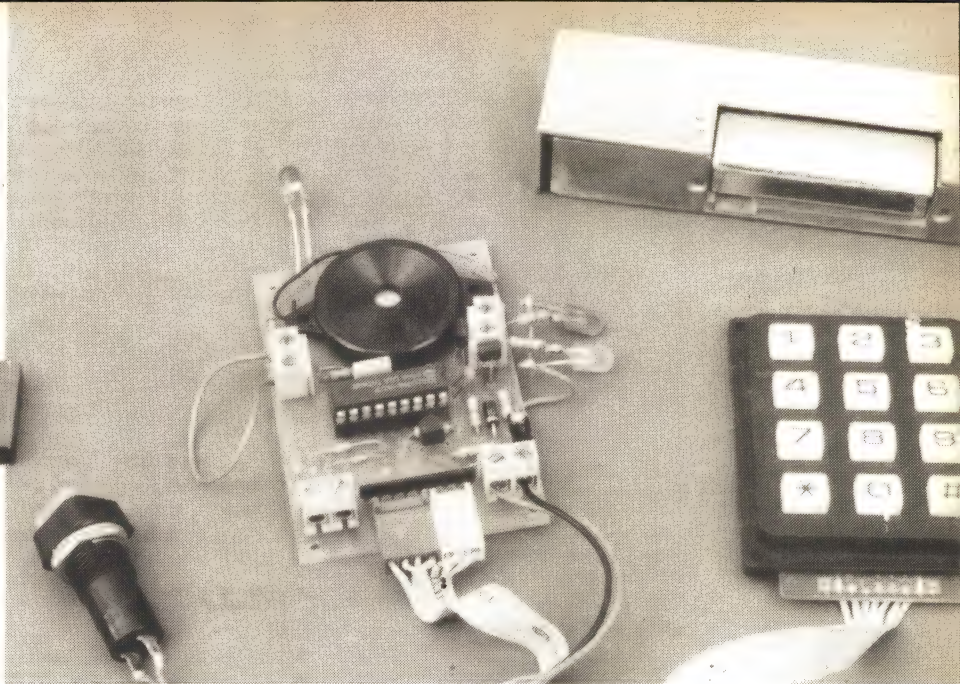
panels normally used in such applications) unless you are afraid of someone wilfully vandalising the keyboard out of sheer desperation at being unable to break the code. If the unit is constructed with the electronics separate as suggested above, removing or smashing the keyboard will only make entering numbers more difficult, making it even harder to get in. □



SEETRAX CAE - RANGER - PCB DESIGN

Ranger1 £100

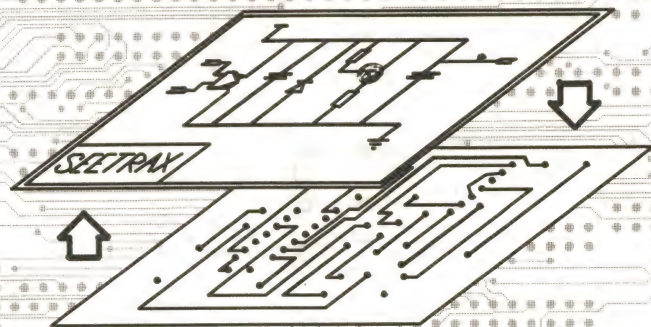- * Schematic capture linked to PCB
- * Parts and wiring list entry
- * Outline (footprint) library editor
- * Manual board layout
- * Full design rule checker
- * Back annotation (linked to schematic)
- * Power, mass and signal autorouter - £50



Ranger2 £599

All the features of Ranger1 plus

- * Gate & pin swapping (linked to schematic)
- * Track highlighting
- * Auto track necking
- * Copper flood fill
- * Power planes (heat-relief & anti-pads)
- * Rip-up & retry autorouter

Ranger3 £3500

All the features of Ranger2 plus

- * UNIX or DOS versions
- * 1 Micron resolution and angles to 1/10th degree
- * Hierarchical or flat schematic
- * Unlimited design size
- * Any-shaped pad
- * Split power planes
- * Optional on-line DRC
- * 100% rip-up & retry, push & shove autorouter

Outputs to:

- * 8/9 and 24 pin dot-matrix printers
- * HP Desk/Laser Jet, Canon BJet, Postscript (R3 only)
- * HP-GL, Houston Instruments plotters
- * Gerber photoplotters
- * NC Drill Excellon, Sieb & Meyer
- * AutoCAD DXF

All systems upward compatible. Trade-in deals available.

Call **Seetrax CAE** for further information/demo packs.

Tel 0705 591037

Fax 0705 599036

Seetrax CAE, Hinton Daubnay House, Broadway Lane,
Lovedean, Hampshire, PO8 0SG

All trademarks acknowledged.

New Technology Update

Glass-on-silicon and etched aerials are two of the latest developments in communications technology – Ian Poole reports.

THIS month we are taking a look at some of the developments which are taking place in radio communications. This technology is now a major growth area of the electronics industry. As people are finding they need more versatile mobile communications, developments in radio are taking place at an ever increasing rate.

New breeds of cellular phones and cheaper prices as well as developments in data transmission, and of course the rise in satellite television, have all fuelled a tremendous amount of development. Many of the new developments have already hit the market place and we are beginning to see the rewards. There are, though, still a very large number in the pipe line which promise some exciting improvements for the future.

Microwave I.C.s

The enormous growth in radio telecommunications has brought about a need for cheap high performance microwave i.c.s. In the past, microwave components have been notoriously expensive, but the increased markets have now given many manufacturers the incentives to start developing low cost components for these frequencies.

For some years now low cost MMICs (monolithic microwave i.c.s) have been available for operation at up to frequencies of 1GHz (1000MHz) and more. Now there is an increased demand for greater levels of integration at frequencies of up to 10GHz.

At these frequencies circuit losses become a significant problem. Even conventional glass fibre boards cannot be used because of their poor performance. This results in the use of expensive teflon or p.t.f.e. based boards. If further components could be integrated onto a single chip, then many of the losses could be reduced and costs cut.

Seeing the need for the development of lower cost and more integrated microwave circuits, the Microelectronics Division of M/A Com Inc. have developed a new glass microwave i.c. technology. This allows microwave i.c.s and discrete components to be placed onto the same substrate to give high performance for a relatively low cost.

When developing circuits for microwave applications there are a number of features which must be included which are not normally present for digital circuits. Low r.f. losses are obviously of paramount importance. In addition to this, tracks between many of the stages and components must form accurately matched transmission lines.

Glass-on-Silicon

To fulfil these requirements M/A Com devised a new structure. Their new glass-on-silicon wafer forms the basis of the new i.c.s. Standard thin film techniques can then be used to place the tracks and transmission lines and lay down the components, (Fig. 1.).

The ground plane is created by using a layer of silver or gold between the glass and silicon. It is then possible to connect to this layer by bringing the ground connection up through the glass using "via" holes similar to those seen in ordinary multi-layered printed circuit boards.

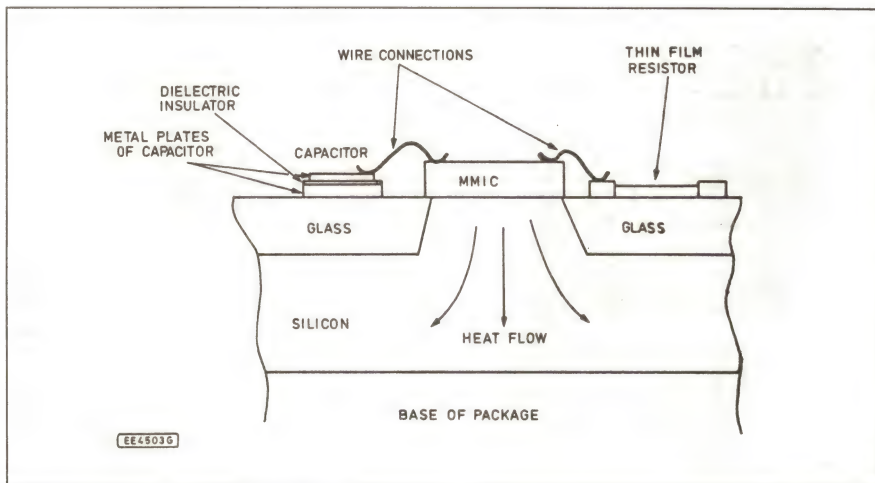


Fig. 1. Part of a typical glass-on-silicon i.c.

The silicon layer itself consists of heavily doped silicon, and this provides a highly conductive path to the outside package.

In the development of this technique, great attention was paid to the thermal aspects of the design. Many microwave i.c.s consume high levels of current, and this results in high levels of heat being generated in localised areas. The silicon itself has high thermal conductivity and it provides an efficient path for the heat to flow away from the i.c.s.

In addition to this, the thermal coefficients of expansion of the glass and silicon are closely matched. This significantly increases the reliability of the final circuit. If this were not so then the resultant stresses built up in the circuits could lead to early failure of some of the components.

These circuits, along with many other new ideas, should help to open up higher frequencies to mass produced products. New generations of cellular phones together with a host of other uses could all benefit as the lower frequencies become fully used and higher ones have to be used to cope with the demand.

New Dishes

Television aerials are a feature of our modern society. Most houses will have one attached to a chimney stack, and there are a growing number of satellite dishes appearing on building walls. In view of this, a number of companies have been working on developing methods of manufacturing less unsightly aerials for a variety of uses, commercial and domestic.

In one development being undertaken at the Georgia Institute of Technology a flat aerial which can be hung in a window, or incorporated into a roof has been developed. Although its current operating

range is between 500MHz and 4GHz it is expected to find widespread usage in a variety of applications including TV reception, cellular telephones and even satellite communications. Possible further developments may be able to extend its coverage up to satellite TV frequencies in the region of 12GHz.

The aerials are constructed out of a teflon or p.t.f.e. sheet and the conductors for the aerial are etched out of copper on the sheet using ordinary p.c.b. techniques. These conductors make up an array of dipoles, and by careful choice and calculation of the lengths and positions it is possible to alter the frequency bandwidth and directivity performance.


Once the basic aerial has been manufactured it is mounted in a layer of foam over a metal sheet. This construction ensures that the assembly does not distort and alter its properties.

To aid with the design of the individual aerials the development team use a computer program which enables the basic specifications for the aerial to be turned directly into the artwork needed to manufacture the aerial.

ELECTROMAIL

Bursting with new ideas
The 94/95 Electromail Catalogue
Now available

**OVER
53,000
PRODUCTS**

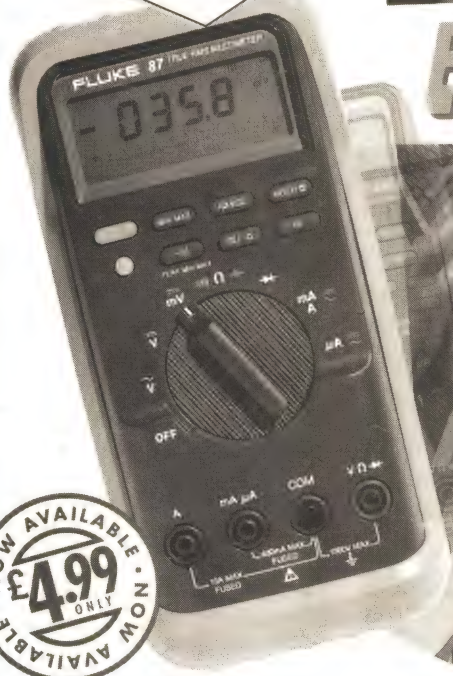

**NOW AVAILABLE
ONLY
£4.99
NOW AVAILABLE**

ELECT

ELECTROMAIL

**November 1994 -
October 1995**
**Prices guaranteed
to February 1995**
53,000 Products
**Largest range in
Europe**

Order by 'phone - pay by Access or Visa
PHONE 01536 204555 FAX

**ENTIRELY
NEW
11
SECTIONS**

Part 1

More ...

Semiconductors, Surface Mount Technology, fuses, batteries, potentiometers, capacitors

Part 2

More ...

Fire & security, wiring accessories, lights, plugs, fittings, Datacom products

Part 3

More ...

Hand tools, power tools, screwdrivers, wire cutters, drills, taps, workshop and machine tools

To Order: Phone: 01536 204555 OR Fax: 01536 405555 quoting your Access/Visa card number and expiry date. **OR Write:** Send written orders, accompanied by cheque, postal order or include your Access/Visa card number and expiry date, ensuring that your order is signed. Cheques and postal orders must be crossed and made payable to ELECTROMAIL.

DO NOT SEND CASH OR CREDIT CARD.

Electromail (Dept EPE) PO Box 33, Corby, Northants. NN17 9EL.
- RS, RS and Electromail are registered trademarks of RS Components Ltd.

Order by phone - pay by Access or Visa - it couldn't be easier
PHONE: 01536 204555 FAX: 01536 405555

**3 volumes that add up to the UK's biggest
technical superstore, at the end of your 'phone.**

INTERFACE

Robert Penfold



IN LAST month's *Interface* article the basics of fibre-optic data links were discussed. This month we will look at a practical fibre-optic RS232C interface capable of operation at up to 19200 baud.

This system is a simple direct coupled type,* and is not of the tone encoded/decoded variety. Consequently its range is not particularly large. However, I found that it was possible to obtain good results using a 10 metre length of fibre-optic cable, and this should be more than adequate for most purposes.

Bright Lights

The transmitter end of the system is really just an electronic switch driving a l.e.d. The transmitter circuit diagram is shown in Fig. 1. Transistor TR1 is a simple common emitter switching stage. It is driven by the serial input signal via the potential divider formed by resistors R1 and R2.

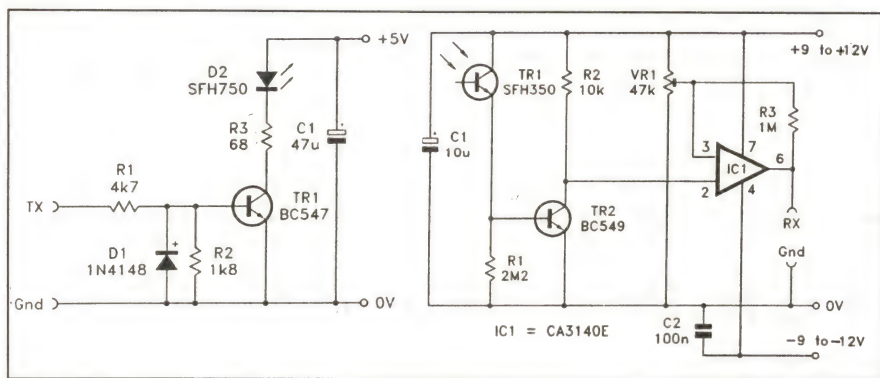


Fig. 1. Circuit diagram for the transmitter section of the fibre-optic data link.

When the input signal is high (at about +3V to +12V) TR1 is biased hard into conduction, and it drives the l.e.d. (D2) by way of current limiting resistor R3. The "on" l.e.d. current is a little over 40mA, but the average current consumption of the circuit will normally be no more than about 20mA.

When the input signal is low (at about -3V to -12V) TR1 is cut off, and it is protected against an excessive reverse base voltage by resistor R1 and diode D1. These limit the base voltage to about -0.7V. Incidentally, the input should be low under standby conditions, which results in the circuit having a negligible current consumption when it is not handling any data.

The circuit will work on a 9V or 12V supply, but the value of resistor R3 must be altered to suit the higher supply voltage, and maintain an "on" current of about 40mA or so: Use a 180 ohm resistor for a 9V supply, or a 270 ohm resistor for a 12V supply.

A direct coupled optical link is heavily dependent on a reasonable amount of light

from the transmitter reaching the photocell at the receiver. In order to achieve this, it is necessary to use a proper fibre-optic device at both ends of the system. Improvising with an ordinary l.e.d. and some Blu-Tack is unlikely to give usable results even over a range of a few millimetres!

The specified l.e.d. is a visible red type having a moulded-in orifice to accept a standard 2.2mm diameter cable. The system should work using any similar fibre-optic l.e.d., but I have only tested it using the specified device.

Seeing The Light

The circuit for the receiver is shown in Fig. 2. The photocell is phototransistor TR1, and this a special fibre-optic type which has a moulded-in receptacle for the cable. It is used as what is effectively an emitter follower stage driving a common emitter switch, transistor TR2.

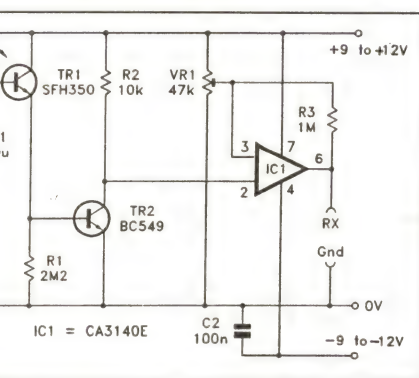


Fig. 2. Circuit diagram for the fibre-optic data link receiver.

Under standby conditions TR1 passes only minute leakage currents. The emitter load resistor (R1) ensures that these currents are insufficient to even partially bias TR2 into conduction. The pulses of light from the transmitter result in much greater leakage currents through TR1, causing TR2 to conduct strongly. Op.amp IC1 acts as a trigger circuit and level shifter. This gives an output signal that switches rapidly and cleanly at normal RS232C levels.

For IC1 to provide proper RS232C signal voltages it must have a negative supply of around -9V to -12V. In practice it may well be found that satisfactory results are obtained even if IC1 pin 4 is simply connected to the 0 volt supply rail, especially if only a short cable is used to connect the receiver to the peripheral device.

If dual supply operation proves to be necessary, the negative supply can be generated from the positive supply using the circuit of Fig. 3. Note that this circuit should not be used on a supply voltage of more than 10V. The receiver circuit only consumes about 3mA from each supply rail.

Clear-Cut

The correct cable to use with the SFH350 phototransistor and SFH750 l.e.d. is a single core type having an outer diameter of 2.2mm and an inner core 1mm in diameter. A fibre-optic cable will only operate efficiently if both ends are properly prepared.

Cables are not usually supplied with either end of the filament prepared and ready for use, and they are often very inefficient as supplied. The ends of the polymer filament can be polished, but there seems to be no real need to do this. Provided the ends of the cable are cut neatly and cleanly at right angles the cable should provide high transmission efficiency.

I find that the best way of doing this is to trim off the ends of the cable using a modelling knife fitted with a new blade. Place the end to be trimmed on a cutting board, and then cut through the cable in one go using plenty of pressure (but taking due care to cut nothing other than the cable). Make sure that the cut is at right angles to the cable. When both ends have been prepared, aim one end of the cable at a light source and check that plenty of light can be seen coming from the other end of the cable.

The SFH350 and SFH750 have holes into which the cable must be pushed fully home. They do not require any of the cable's outer sleeving to be removed. The cable is a simple push-fit, and it pulls out again just as easily as there is no form of built-in grip.

It should not be too difficult to devise a simple method of clamping the cable in place so that it is not continually being pulled out of the photocells, but be careful not to clamp it too tightly. Any damage to the polymer filament could seriously reduce the efficiency of the cable. Note that the clear casing of the SFH350 makes it sensitive to any ambient light. It must therefore be shielded from any bright light sources.

Adjustment

Preset potentiometer VR1 must be given a setting that will accurately retain the input waveform at high baud rates. At these baud rates, particularly 19200 baud, the collector

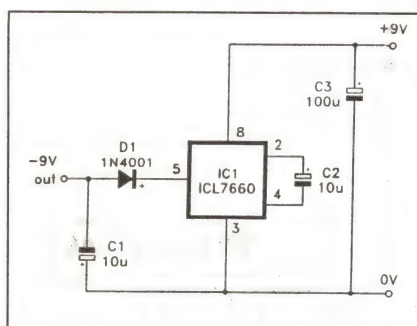


Fig. 3. Simple negative supply generator.

of transistor TR2 at the receiver switches relatively slowly from one level to the other.

Probably the easiest method of setting VR1 is to first measure the positive supply voltage of the receiver circuit. Then at the transmitter circuit, temporarily connect the "TX" input to the +5V supply rail so that i.e.d. D2 switches on.

Next measure the voltage at the collector of phototransistors TR1. This should be about 5V or more below the positive supply voltage. If the voltage drop is much less than this it is unlikely that the unit will work properly, especially at high baud rates.

Preset VR1 should be adjusted for a wiper potential that is half way between this voltage and the actual supply voltage. For example, if the voltage at the collector of TR2 is 5.6V, and the measured supply potential was 11.8V, VR1 should be adjusted for a wiper voltage of 8.7V ($5.6V + 11.8V = 17.4V$, $17.4V$ divided by $2 = 8.7V$). Alternatively, if a logic pulse generator and an oscilloscope are available, feed a 10kHz squarewave signal to the input of the transmitter, and then adjust VR1 for a 1-to-1 squarewave output from the receiver.

Handshaking

A single fibre-optic data link is only suitable for one-way (simplex) operation, and it does not support any form of handshaking. If two-way operation is needed it is necessary to build two complete systems, one for communication in each direction. The two links must use separate optical cables.

If handshaking is needed it is possible to accommodate it using additional links. This is not a particularly neat or cheap way of

handling the problem though. Where possible it is best to avoid handshaking altogether by using a low enough baud rate to ensure that the receiving device does not become overloaded with data. If some form of handshaking is essential, a two-way link and software handshaking may well be the simplest and most versatile solution.

Projects that connect to the serial port of a computer can usually be relied upon to bring in a few letters from readers who are experiencing difficulty in getting the computer to output any data. The problem does not usually arise when the serial port hardware is being controlled directly, and it is mainly when data is sent to the port via the computer's operating system that difficulties occur.

The important point to bear in mind here is that although your hardware add-on may not be using any form of hardware handshaking, it is quite likely that the computer's operating system will be monitoring and responding to the handshake lines. This means that it is often necessary to activate a handshake input (i.e. take it high) before the computer will output any data. If the handshake output or outputs are not being used, these usually represent the most simple way of activating one or more handshake inputs.

With the BBC computers, simply linking the two handshake lines enables data to be output from the RS423 port. With PCs the method of connection shown in Fig.4 should enable a flow of data from the port. In this case two sets of handshake lines must be linked (RTS to CTS, and DTR to DSR). Presumably the same general technique will work equally well with other computers.

Beating Time

A number of PC shareware companies are now distributing shareware and commercial demo disks that have a sort of built-in time-out function. The software works fine until a certain date is reached, and thereafter it refuses to run. Instead you simply get an on-screen message explaining that the disk is past its use-by date. This is fair enough, but many of these disks originate in the USA, and are near or past their expiry dates by the time they reach British users.

Fortunately, with most of these disks there is no difficulty in getting them to run so that you can try out the software. Simply using the computer's built-in setup program to set the clock/calendar back to a suitable date seems to do the trick. The programs are probably reading the MS/DOS clock/calendar rather than directly accessing the hardware clock, so it would probably be possible to fool these programs into action simply by using the usual MS/DOS DATE command.

Fibre-optic cable 2.2/1.0mm is available from Maplin (order code XR56L). The SFH350 phototransistor and SFH750 i.e.d. are available from ElectroValue.

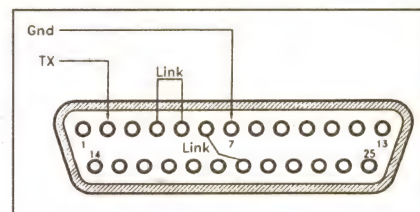


Fig. 4. A method of connection that permits an easy flow of data from a PC serial port.

A SAMPLING OSCILLOSCOPE AND LOGIC ANALYSER!

IN AN AFFORDABLE PORTABLE PACKAGE

- 10 Mega samples per second single channel DSO
- 1MHz analogue bandwidth
- 0.2V-50V input range
- Various Triggering options
- 10 Mega samples per second 8 channel logic analyser
- 5V TTL/4.5-15V CMOS logic level inputs
- Crisp, clear LCD screen
- Zoom and Scroll facilities (selected ranges only)
- Battery or mains adapter powered
- 12 Months Warranty (Built version only)
- "Get you working" service (kits only)

Write or phone for a free Information Pack to

AUDON

AUDON ELECTRONICS

36 Attenborough Lane, Chilwell, Nottingham NG9 5JW 0602 259737

The Miniscope




MINISCOPE KIT £139

MINISCOPE BUILT £179

MAINS PSU £3 P&P £3

PLEASE ADD VAT AT 17.5%

VIDEO MODULES HORIZONTAL WIPER

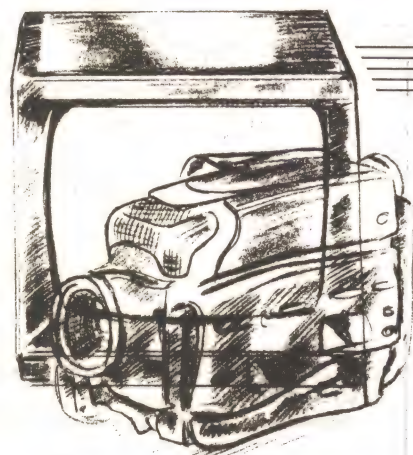

ROBERT PENFOLD **Part Two**

Your home videos will take on a whole new meaning if you build these low cost modules. Professional presentations couldn't be easier!
You can tailor the controller to meet your own special needs and budget.

- Simple and Improved Faders • Horizontal and Vertical Wipers
- Video Enhancer • 4-Channel Audio Mixer
- Audio Dynamic Noise Limiter • System PSU

LAST month we dealt with simple video faders and also gave details for a Video Enhancer to boost picture definition. This month we introduce the subject of video wipers plus we describe the construction of a simple 4-Channel Audio Mixer.

Video wipers offer an interesting alternative to faders. The two basic types of wiper are the horizontal and vertical types.

A wiper operates on the basis of having part of the screen showing a normal picture, and the other section completely blanked. The blanked part of the screen is normally black, but a wiper circuit could be designed to have the blanked area of screen white, or any shade of grey. The wipers featured here produce the usual black area of blanked screen.

With a vertical wiper the screen is progressively blanked from the top downwards until all the visible part of the screen has been blanked. At the beginning of the next scene the picture is restored from the bottom upwards.

Most vertical wipers offer the alternative of blanking from the bottom upwards, and restoring the picture from the top downwards. A horizontal wiper provides a side-to-side blanking and restoring action.

HOW IT WORKS

The block diagram of Fig. 9 helps to explain the way in which the Horizontal Wiper functions. This is similar in many respects to the Improved Fader circuit described last month, and the Horizontal Wiper has been developed from the Improved Fader circuit.

The input signal is split two ways, with part of the signal being fed to a synchronisation separator. This provides output pulses which trigger a monostable at the beginning of each line synchronisation pulse.

The monostable has a variable output pulse duration, and it is the pulse length potentiometer that acts as the wiper control. With the minimum pulse duration set, the pulse ends just as the luminance signal begins. With the maximum pulse duration set, the pulse finishes at the end of the current line scan.

In the other signal path there is a d.c. restoration circuit, an electronic switch, and an output amplifier. The electronic switch is controlled by the monostable, and it permits the input signal to pass through to the output of the unit only during a pulse from the monostable.

The waveform of Fig. 10a is a section of the input signal, and Fig. 10b is the processed output signal. Although there is a small gap between one pulse and the next, and a section of the signal is blanked, the missing section is very small. It does not carry any important picture information.

By shortening the pulse length slightly, the electronic switch is turned off just before the end of each line scan. This results in the extreme right hand section of the screen being blanked. If the monostable's pulse duration is set at about half its maximum length, the electronic switch will be turned off about half way through each line scan, and the right half of the screen will be blanked.

Reducing the pulse length to its minimum duration results in the switch being turned off just before the luminance signal commences, and the entire screen is then blanked. Waveforms Fig. 11 and Fig. 12 show the way in which this process operates.

CIRCUIT DETAILS

The full circuit diagram for the Horizontal Video Wiper is shown in Fig. 13. This has obvious similarities with the Improved Wiper circuit, including the same synchronisation separator circuit based on transistors TR1 and TR2.

This again drives a negative edge triggered monostable based on a 4047BE (IC1), but the C/R timing network is different. Resistor R8 sets the minimum pulse duration at a suitable figure, and VR1 is the Wiper control. Resistor R9 and preset VR2 are connected in parallel with VR1, and VR2 is used to trim the maximum pulse duration to precisely the correct figure.

The d.c. restoration, electronic switch, and output amplifier sections are also much the same as their equivalents in the Improved Fader circuit. The obvious difference is that the input of IC2b is simply wired to "earth", (0V) rather than being fed an the input signal via a "fader" potentiometer. The current consumption of the circuit is typically about 25mA.

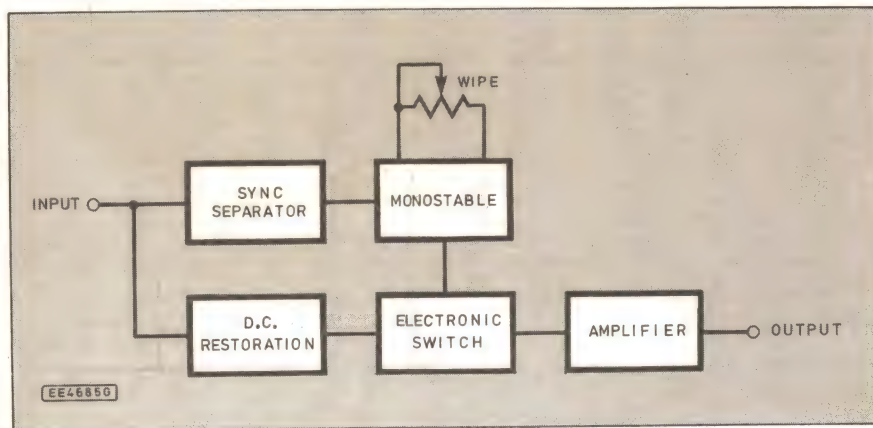


Fig. 9. Block diagram for a horizontal wiper.

COMPONENTS

HORIZONTAL WIPER

Resistor

R1, R19	470 (2 off)
R2, R3, R10	47k (3 off)
R4	18k
R5, R7, R13, R15, R18	4k7 (5 off)
R6, R9	33k (2 off)
R8	5k6
R11, R12	22k (2 off)
R14	1k
R16	220k
R17	12k
R20	68
All 0-25% carbon film	

See
SHOP
TALK
Page

Potentiometers

VR1	47k rotary carbon, linear
VR2	100k min. preset, horizontal

Capacitors

C1	220n polyester
C2	10µ radial elect. 25V
C3	10n polyester
C4	1n polyester
C5	100µ radial elect.
C6	100n ceramic
C7, C8, C9	100µ radial elect. 10V (3 off)

Semiconductors

IC1	4047BE CMOS timer
IC2	4016BE or 4066BE CMOS analogue switch
TR1	BC557 pnp silicon transistor
TR2, TR3, TR4, TR5	BC547 npn silicon transistor (4 off)
D1, D2	1N4148 signal diode (2 off)

Miscellaneous

SK1, SK2 phono socket (2 off)
Printed circuit board available from the *EPE PCB Service*, code 916; 14-pin i.c. holder (2 off); control knob; connecting wire; single-sided solder pins; solder etc.

Approx cost
guidance only

£14

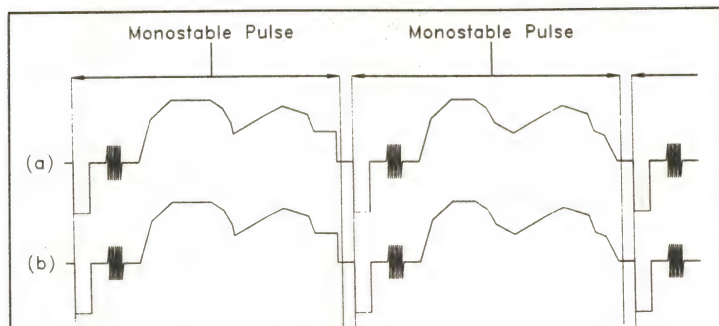


Fig. 10. With the maximum pulse length each line signal passes unprocessed.

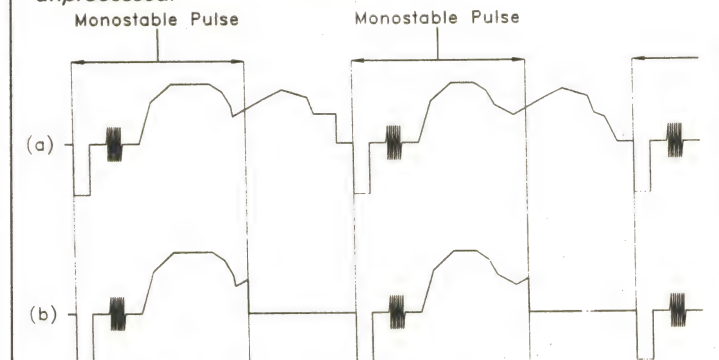


Fig. 11. The effect of the circuit with about half the maximum pulse duration.

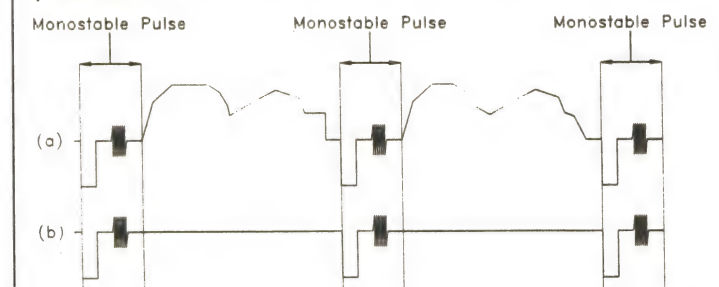


Fig. 12. The effect of the circuit with the minimum pulse length.

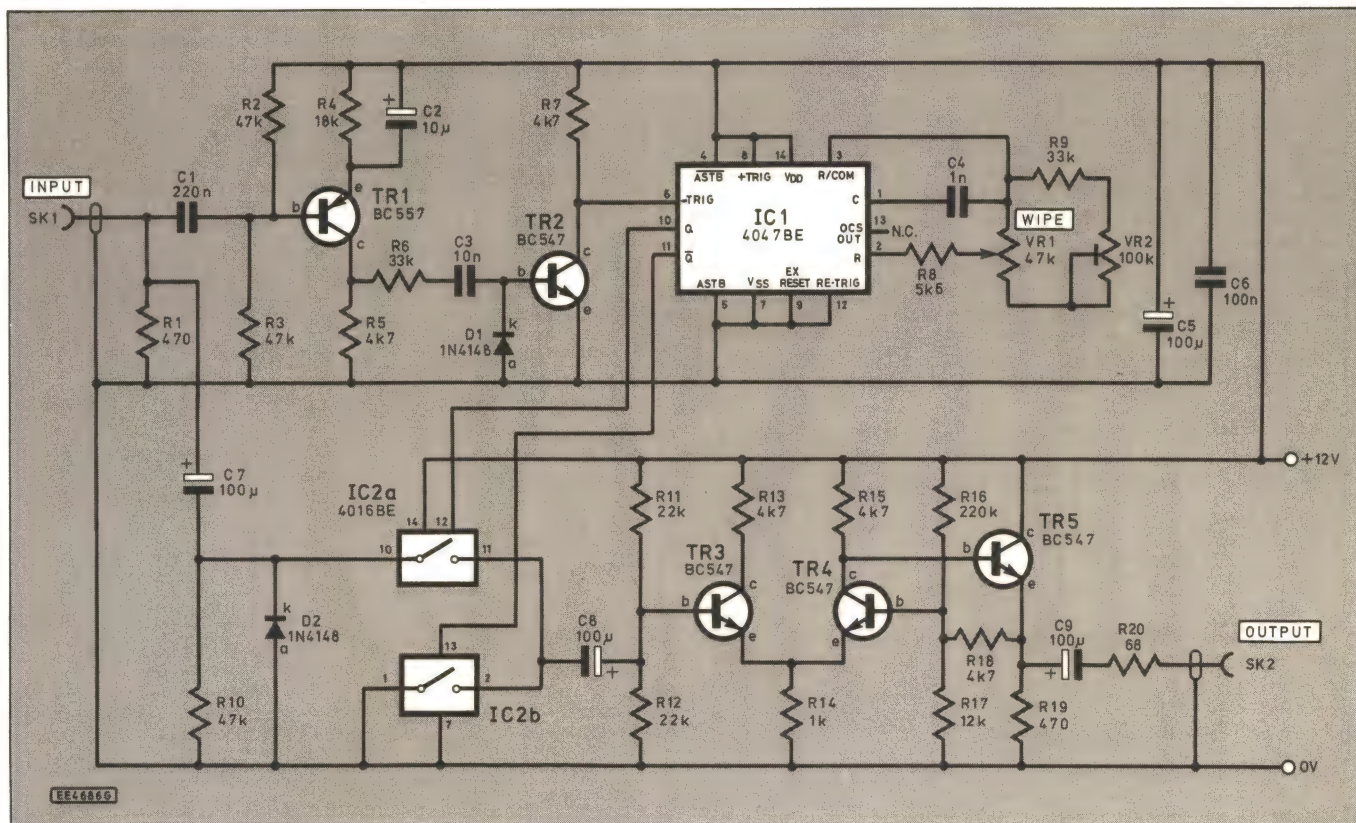


Fig. 13. Complete circuit diagram for the Horizontal Video Wiper.

CONSTRUCTION

The printed circuit board (p.c.b.) component layout and full size underside copper foil design for the Horizontal Wiper is shown in Fig. 14. This board is available from the *EPE PCB Service*, code 916.

As IC1 and IC2 are CMOS integrated circuits the normal anti-static handling precautions should be taken. Use holders for these two components, and do not plug them into the p.c.b. until the unit is complete.

Do not overlook the two link-wires (below IC2). Construction of the board is perfectly straightforward in all other respects. The small amount of hard wiring is also clearly illustrated in Fig. 14.

TESTING

To test the unit connect it between the video output of a camcorder and the composite video input of a suitable television or monitor. Start with preset VR2 at a roughly middle setting. The unit should function more or less correctly, but VR2 must be set so that none of the screen is blanked with Wipe control VR1 at maximum resistance. This is just a matter of setting VR1 at maximum resistance and adjusting VR2 for the correct picture.


If VR2 is set too low in value (too far in a clockwise direction) the right hand section of the screen will be blanked. If it is set too high in value the beginnings of every other line scan will be blanked, probably resulting in a severe loss of picture stability. There should be a narrow range of in-between settings that give the desired result.

It is just possible that with VR1 at minimum resistance there will be a very narrow band down the left hand side of the screen which is not blanked. Reducing the


value of resistor R8 to 4k7 should cure this problem.

If the monostable is set for the maximum pulse duration, the electronic switch is in the "on" state for what is virtually the

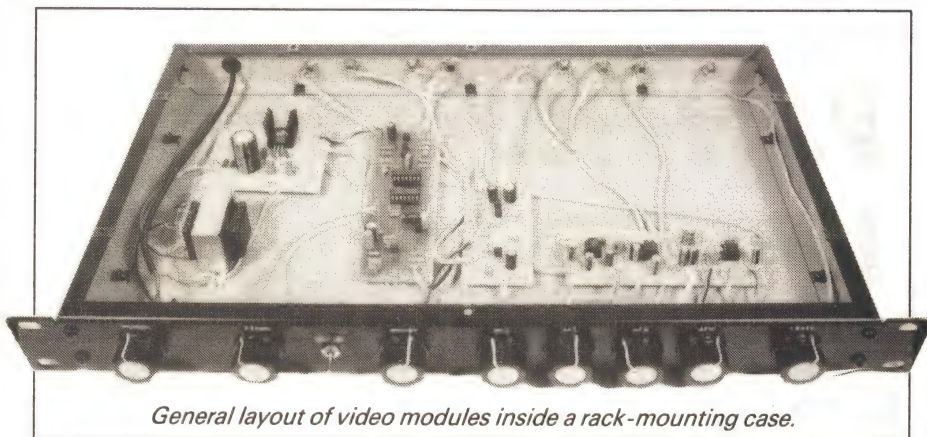whole of each line scan, and the input signal is effectively passed through to the output without any processing. The television or monitor therefore shows an unblanked screen. Fig. 10 helps to explain this process.



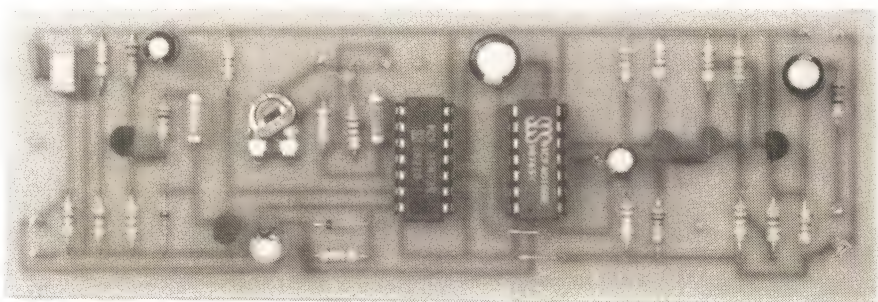General layout of video modules inside a rack-mounting case.



The completed Horizontal Wiper circuit board.


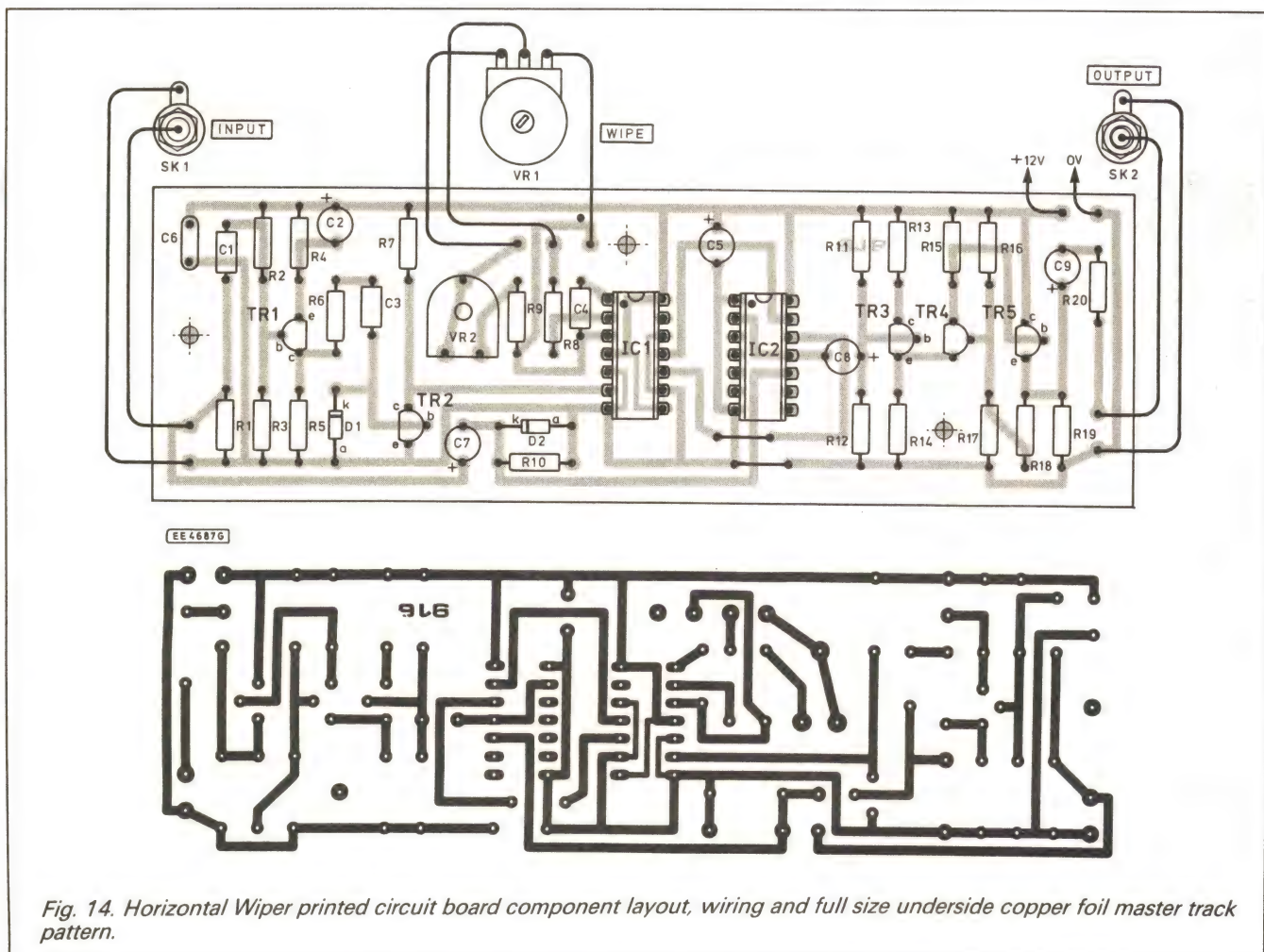


Fig. 14. Horizontal Wiper printed circuit board component layout, wiring and full size underside copper foil master track pattern.

VERTICAL WIPER

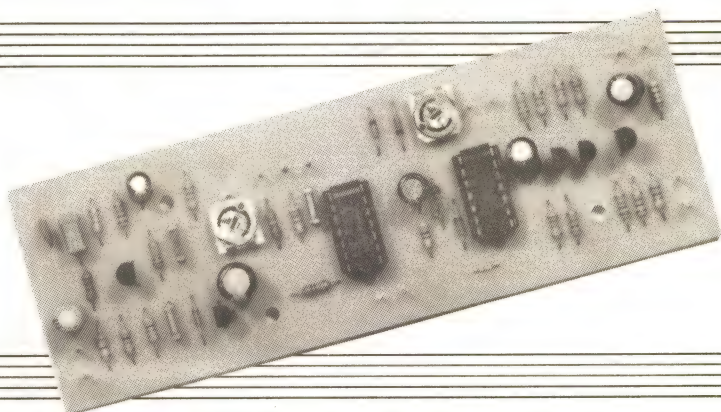

Blanking the television or monitor screen using the "frame-by-frame" technique.

A VERTICAL wiper operates in a manner which is not dissimilar to a horizontal type, but there are some important differences between the two types of circuit. Fig. 15 shows the block diagram for the Vertical Wiper module.

Like the Horizontal Wiper, this arrangement has part of the signal fed to a synchronisation separator, with the resultant output pulses driving a monostable multivibrator. This in turn controls an electronic switch.

The synchronisation separator used in this application is different to the one used in the Horizontal Wiper. This circuit must operate on a "frame-by-frame" basis, rather than using a line-by-line approach. Accordingly, the synchronisation separator produces a trigger pulse for the monostable at the beginning of each frame synchronisation pulse.

The pulse duration of the monostable can be varied via a potentiometer, and this acts as the Wipe control. As the blanking process is being applied to frames rather than to lines, the maximum pulse duration is much longer in this application. It is approximately equal to the duration of one frame, or about 20ms in other words.

ELECTRONIC SWITCH

The electronic switch is a changeover type, and one input is fed with the full composite input via a d.c. restoration circuit. The other input is fed via a luminance stripper circuit which removes the brightness modulation signal, but leaves the negative synchronisation pulses (both the frame and the line types).

With the monostable set for its minimum pulse duration the full composite signal is only switched through to the output for the first few lines. As these are not displayed on a correctly adjusted television or monitor, this has no effect on the displayed picture. For the rest of each frame the luminance stripped signal is fed through to the output. This gives a blanked screen, but it contains the line synchronisation signals that are necessary to maintain a stable picture.

As the monostable pulse duration is increased, more lines at the top of the screen have the luminance signal, and the picture is "wiped" onto the screen from the top downwards. With the maximum pulse duration only a few lines at the bottom of the screen are wiped. As these are not normally displayed, a normal picture appears on the screen of the television or monitor. Gradually shortening the pulse duration of the monostable has the opposite effect, and "wipes" the picture from the screen.

Although this setup "wipes" away the signal from the bottom upwards, and reintroduces it from the top downwards, it is easy to obtain the opposite effect.

Simply inverting the control signals to the electronic switch results in the picture being wiped from the top downwards, and reintroduced from the bottom upwards.

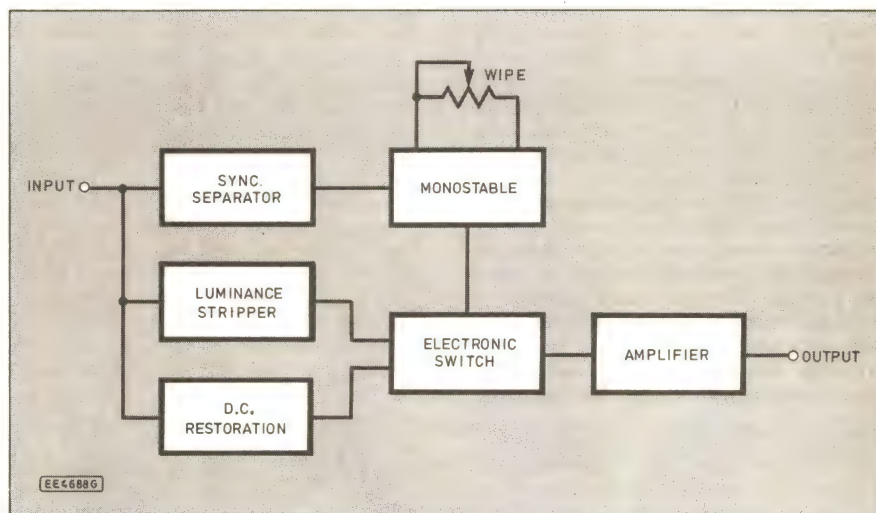


Fig. 15. The Vertical Wiper module block diagram.

COMPONENTS

Approx cost
guidance only

£15

VERTICAL WIPER

Resistors

R1	120
R2	390
R3, R4	47k (2 off)
R5	18k
R6, R8, R11,	
R12, R15,	
R17	4k7 (6 off)
R7	10k
R9	2k7
R10	560k
R13, R14	22k (2 off)
R16	1k
R18	220k
R19	12k
R20	5k6
R21	470
R22	68
All 0.25 5% carbon film	

Potentiometers

VR1	470k rotary carbon, linear
VR2, VR3	1M min. preset, horizontal (2 off)

Capacitors

C1	220n polyester
C2	10µ radial elect. 25V
C3	15n polyester

C4	1n polyester
C5	22n polyester
C6	100µ radial elect. 16V
C7	100n ceramic
C8, C9,	
C10, C11	100µ radial elect. 10V (4 off)

Semiconductors

IC1	4047BE CMOS timer
IC2	4016BE or 4066BE CMOS analogue switch
TR1	BC557 pnp silicon transistor
TR2, TR3,	
TR4, TR5	BC547 npn silicon transistor (4 off)
D1, D2,	
D3, D4	1N4148 signal diode (4 off)
D5	OA91 germanium signal diode

Miscellaneous

S1	d.p.d.t. min. toggle switch
SK1, SK2	phono socket (2 off)
Printed circuit board available from the EPE PCB Service, code 917; 14-pin i.c. holder (2 off); control knob; connecting wire; 1mm single-sided solder pins; solder etc.	

See
SHOP
TALK
Page

CIRCUIT DESCRIPTION


The full circuit diagram for the Vertical Wiper appears in Fig. 16. The synchronisation separator circuit is based on transistor TR1 and TR2. It is similar to the synchronisation separator used in the previous two circuits, but it incorporates low-pass filtering (R7 and C3) so that it will only respond to signals of suitably long duration. In other words, it is activated by the frame pulses, but it will ignore the much shorter line synchronisation pulses.

Once again, the monostable is a negative edge triggered type based on a CMOS 4047BE. In this case the values in the C/R timing network have been chosen to give much longer pulse durations. Resistor R9 sets the minimum pulse duration at a suitable figure of about 150µs. Potentiometer VR1 is the Wiper control, and this permits the pulse duration to be varied up to about 20ms. The series resistance of R10 and preset VR2 is connected in parallel with VR1, and VR2 is adjusted to limit the maximum pulse duration to a suitable level.

The electronic switch (IC2) is a change-over type, which is actually a pair of s.p.s.t. switches driven with anti-phase control signals so that the required s.p.d.t. action is obtained. Switch S1 governs the phasing of the control signals to IC2, and enables the unit to be switched between wiping from the top of the screen downwards and the bottom of the screen upwards.

One input of the electronic switch is fed with the normal composite signal via a simple d.c. restoration circuit based on diode D5. The other input is fed via a simple clipping circuit based on diodes D2 to D4.

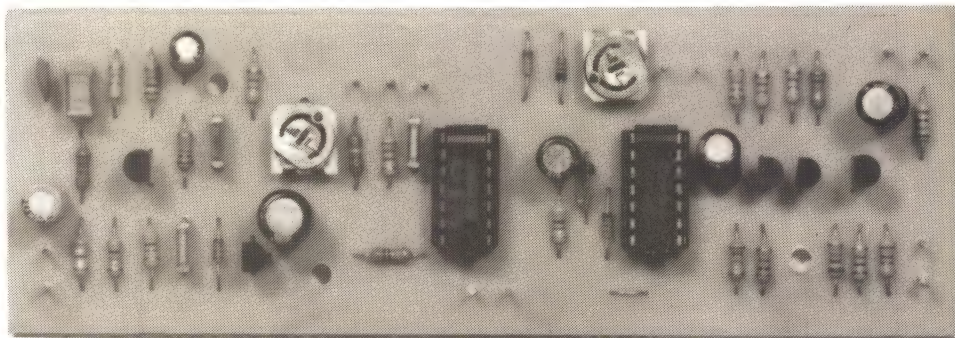This operates in the same manner as the basic Video Fader circuit described previously. Preset VR3 is the "fader" control, and in this application it is preset to



Component layout on the completed Vertical Wiper p.c.b.

give a fully faded signal, so that only the synchronisation pulses are passed through to IC2.

Transistors TR3 to TR5 are used in a buffer amplifier, at the output of the circuit. The current consumption of the circuit is typically a little under 25mA.

CONSTRUCTION

The printed circuit board (p.c.b.) component layout and underside copper foil master pattern for the Vertical Wiper module is shown in Fig. 17. This board is available from the *EPE PCB Service*, code 917.

Remember that IC1 and IC2 are CMOS integrated circuits, and that they require the standard anti-static handling precautions. Also bear in mind that the OA91 (D5) is a germanium diode, and that a component of this type is more vulnerable to heat damage than the more familiar silicon semiconductors.

It is not essential to use a heat-shunt when fitting D5, but the two soldered joints must be completed reasonably quickly. Do not omit the single link-wire just below D4 and IC2.

The point-to-point wiring is also il-

lustrated in Fig. 15. This is very straightforward, and should give no problems.

ADJUSTMENT

Like the units described previously, testing and setting up this device is easiest if it is connected between a camcorder and a suitable television set or monitor. With presets VR2 and VR3 set at roughly middle settings the unit should work to some degree. Preset VR3 should be adjusted for the lowest resistance that gives a properly "wiped" screen. In other words, it should be given the most clockwise setting that gives good results.

Preset VR2 must be set for the lowest resistance that enables the full screen to be "wiped". This should be carried out with switch S1 set for a "top downwards" wipe of the screen. If VR2 is set for too low a resistance it will not be possible to fully "wipe" the screen.

If VR2 is set for an excessive resistance, with VR1 at around maximum resistance the screen blanking will only occur on every other frame, giving a very flickery picture. Finding the right setting for VR2 is a matter of first setting VR1 at maximum resistance, and then using a bit of trial and error.

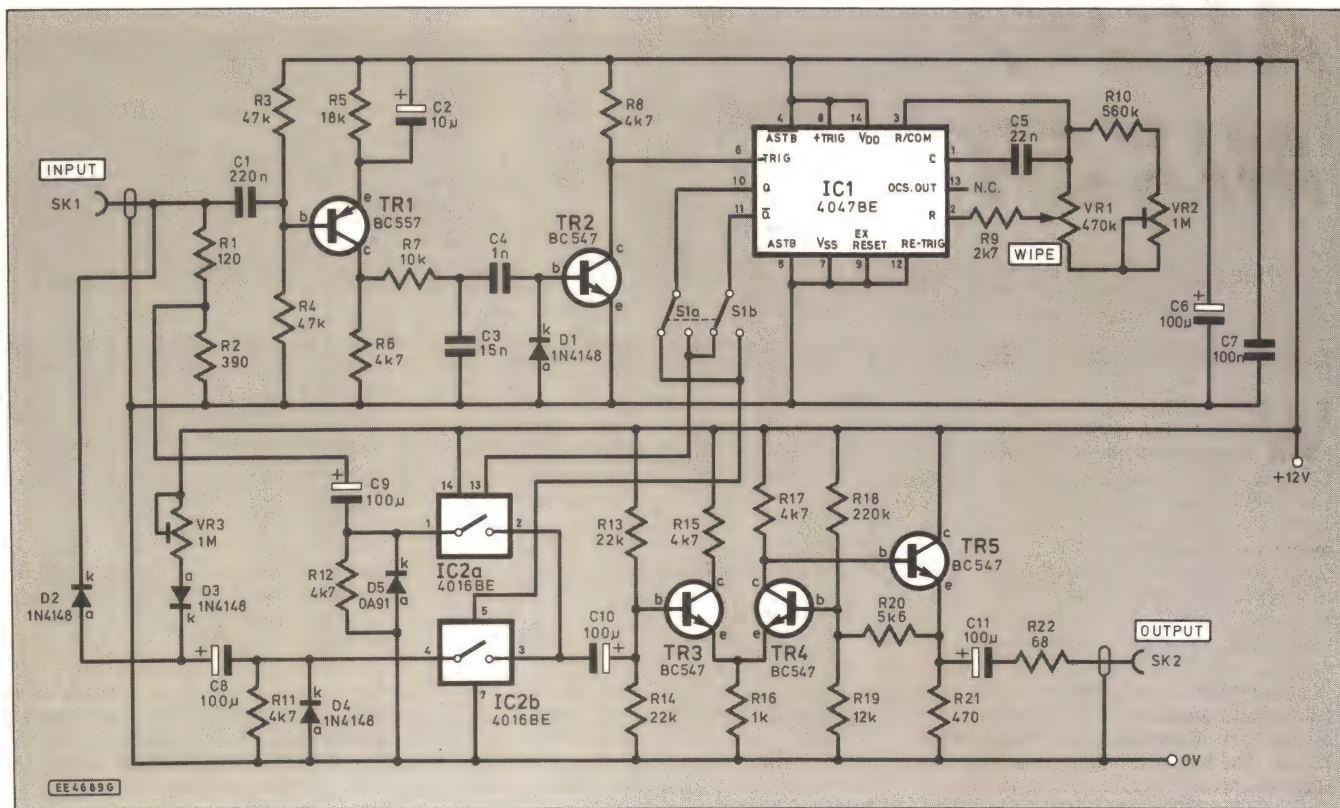


Fig. 16. Full circuit diagram for the Vertical Wiper module.


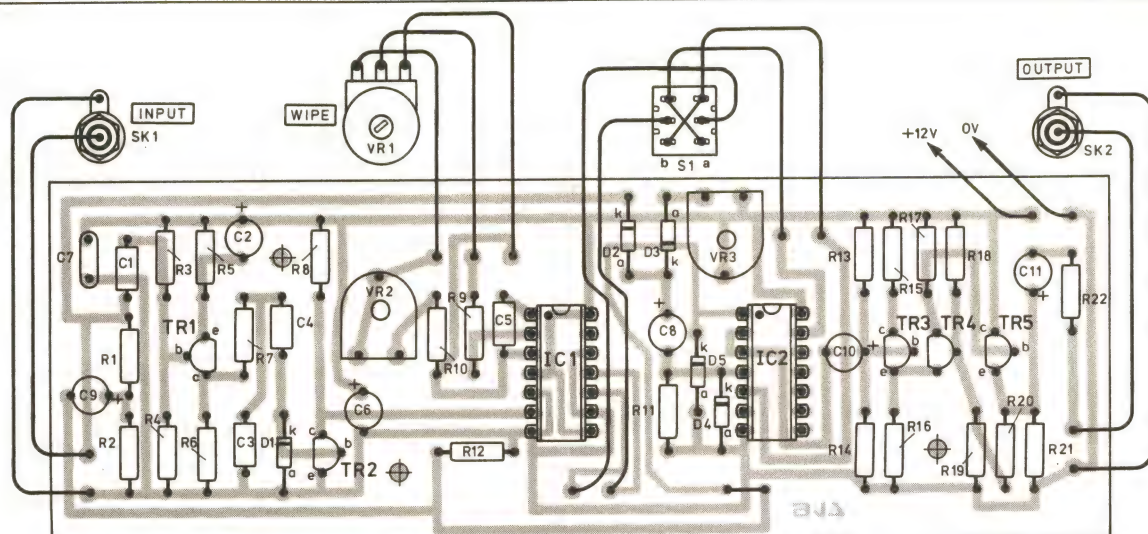


Fig. 17. Component layout, wiring and full size copper foil master for the Vertical Wiper p.c.b.

AUDIO MIXER

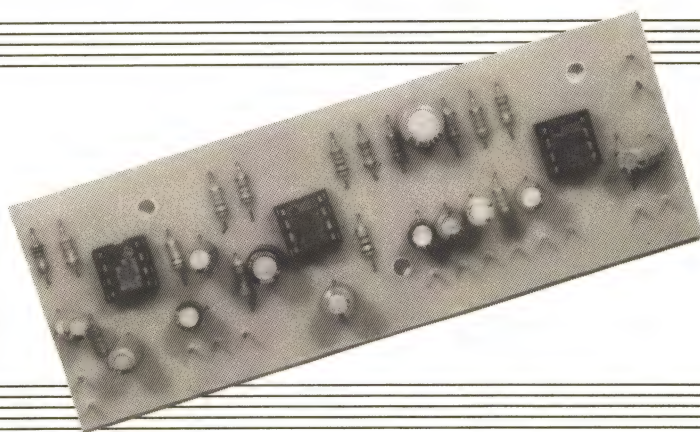

Dub a sound-track on your home videos.

WITH most camcorders and video recorders it is possible to do some doctoring of the sound when editing tapes. This usually consists of mixing some background music with the original sound track, and possibly adding a commentary of some kind as well.

An Audio Mixer is needed in order to accomplish this audio editing, but a sophisticated mixing desk is not needed. In fact a fairly basic mixer will handle the job very well.

The audio mixer featured here is a simple four-input (channel) type having one microphone input and three high level inputs. The latter can be fed from sources such as a Compact Disc player, a Cassette Deck, and the Camcorder itself.

The microphone input can be used with a low impedance (about 200ohms to one

kilohm) dynamic microphone, or any microphone which has comparable output characteristics. This includes most electret type microphones. The microphone input is easily modified for operation with high impedance (about 20k to 50k) dynamic microphones, or microphones which provide a similar output level.

STEREO

Although the mixer was designed as a mono unit, it can be built as a stereo mixer. It is basically just a matter of building *two* mixer boards, one for use in each stereo channel.

The "fader" potentiometers could then be dual-gang types so that the two channels can be adjusted simultaneously. An arrangement preferred by many is to have individual slider controls for the two chan-

nels, with each pair mounted side-by-side. It is then easy to adjust the two channels simultaneously, but it is also possible to adjust them individually if some correction of the channel balance should be required.

CIRCUIT DESCRIPTION

The circuit is basically just a standard summing mode circuit. The complete circuit diagram for the Four-Channel Audio Mixer is shown in Fig. 18.

The low-noise j.f.e.t. input op.amp IC3 is used as the basis of the mixer stage, and this is really a form of inverting mode amplifier. However, in this case there are four input resistors (R10 to R13), and the output of the circuit adjusts to balance the sum of the input voltages.

This gives the required mixing action, and it also gives almost complete isolation between the inputs due to the "virtual

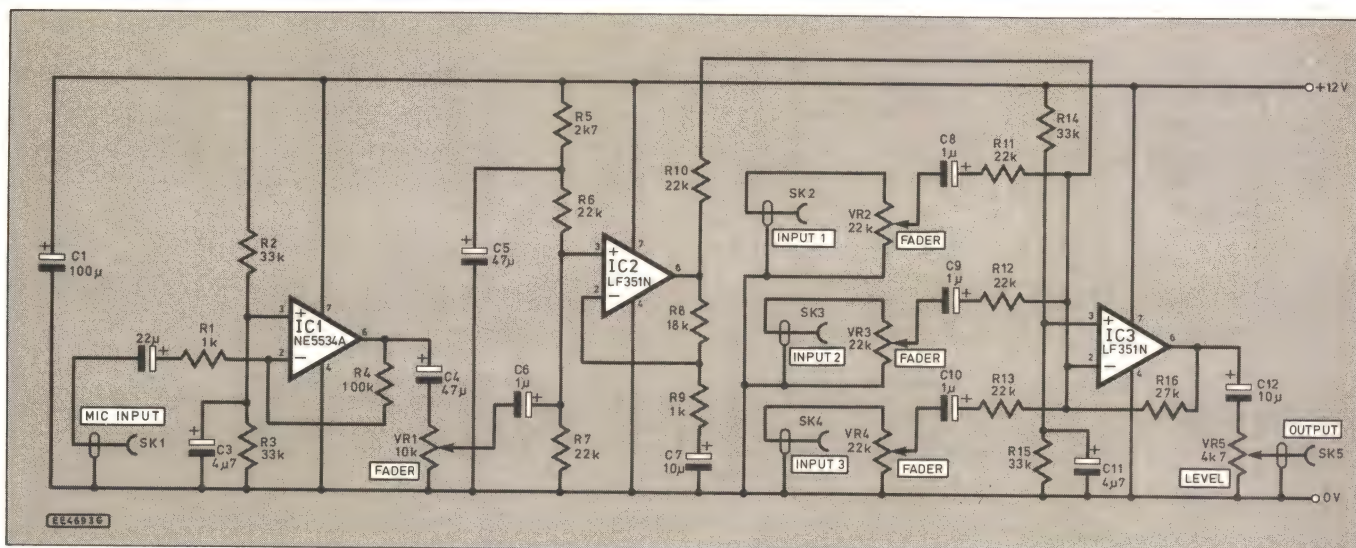


Fig. 18. Complete circuit diagram for the 4-Channel Audio Mixer. The input/output sockets can be mono or jack types.

earth" produced at the inverting input of IC3. This ensures that adjustments to the Fader control for one channel have no significant affect on the other three channels.

Sockets SK2 to SK4 are the high level inputs, and these feed three inputs of the mixer via "fader" potentiometers (VR2 to VR4). The maximum gain from each high level input to the output is a little over unity.

If necessary, slightly higher gain can be obtained by making resistor R16 slightly higher in value. The maximum voltage gain is actually equal to the value of R16 divided by 22k (the value of the input resistors). The input impedance at the high level inputs is around 15k.

MICROPHONE PREAMPLIFIER

The output level from a low impedance microphone is very low. In fact it is normally well under one millivolt r.m.s., which is about one to two thousand times less than the signal from a high level source such as a compact disc player. A high gain preamplifier is therefore used to boost the microphone signal to a level which is comparable to the signal level at the other inputs.

A very low noise bipolar operational amplifier, IC1, is used in the input stage of the preamplifier. This provides a much better signal to noise ratio than the standard 741C, or even a low noise bifet device such as the LF351N. In fact it gives a noise level which is only about one tenth of that provided by a 741C.

Good noise performance is important in an application such as this where very low input levels are involved. IC1 operates in the inverting mode, and has a closed loop voltage gain of about 100 (40dB). Resistor R1 sets the input impedance at approximately one kilohm (1k), which will give satisfactory results with any normal low impedance microphone.

For operation with a high impedance microphone R1 should be increased in value to 10k, and capacitor C2 should be reduced to 2µ2. This will give a closed loop voltage gain of 10 (20dB) and an input impedance of about 10k. This should give good results with virtually any high impedance dynamic microphone, or an electret type which has a built-in step-up transformer.

Further amplification is provided by IC2, and this is a non-inverting mode

circuit. It has a closed loop voltage gain of just under 20 (26dB), giving a total voltage gain of just under 2000 (66dB). This gives an output level of several hundred millivolts r.m.s. Potentiometer VR1 is the Fader control for the microphone input.

The output Level control VR5 would normally be set for maximum output. It provides an easy means of simultaneously fading *all* the input signals. The current consumption of the circuit is approximately 9mA.

CONSTRUCTION

The printed circuit board (p.c.b.) component layout and full size underside copper foil maser pattern are shown in Fig. 19. This board is available from the *EPE PCB Service*, code 918.

None of the integrated circuits are static-sensitive, but the NE5534A used for IC1 is not a particularly cheap device. It is strongly recommended that an i.c. holder is used for this component, and it would be advisable to use holders for the other two integrated circuits as well. Fit single-sided pins to the board at the numerous points where connections to off-board components will be made.


There is a substantial amount of hard wiring, and this is also illustrated in Fig. 19. The wiring to socket SK1 is very sensitive to stray pick up of mains "hum" and other electrical noise. Therefore, it is essential to use a *screened* cable to connect SK1 to the printed circuit board.

The wiring from the other input sockets to their respective Fader potentiometers is

COMPONENTS

Approx cost guidance only

£15

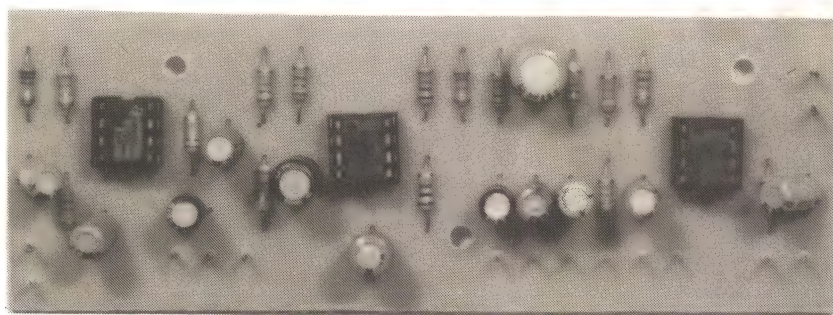

AUDIO MIXER

Resistors

R1, R9	1k (2 off)
R2, R3,	
R14, R15	33k (4 off)
R4	100k
R5	2k7
R6, R7,	
R10 to R13	22k (6 off)
R8	18k
R16	27k
All 0.25W 5% carbon film	

Potentiometers

VR1	10k rotary carbon, log.
VR2, VR3,	
VR4	22k rotary carbon, log. (3 off)
VR5	4k7 rotary carbon, log.

Capacitors

C1	100µ radial elect. 16V
C2	22µ radial elect. 16V

C3, C4,

C11	4µ7 radial elect. 63V (3 off)
-----	-------------------------------

C5

C6, C8, C9,	
-------------	--

C10	1µ radial elect. 63V (4 off)
-----	------------------------------

C7, C12	10µ10µ radial elect. 25V (2 off)
---------	----------------------------------

Integrated Circuits

IC1	NE5534A low noise op.amp
IC2, IC3	LF351N bifet op.amp (2 off)

Miscellaneous

Printed circuit board available from the *EPE PCB Service*, code 918; 8-pin i.c. holder (3 off); control knob (5 off); connecting wire; single-sided solder pins; solder etc.

See
SHOP
TALK
Page


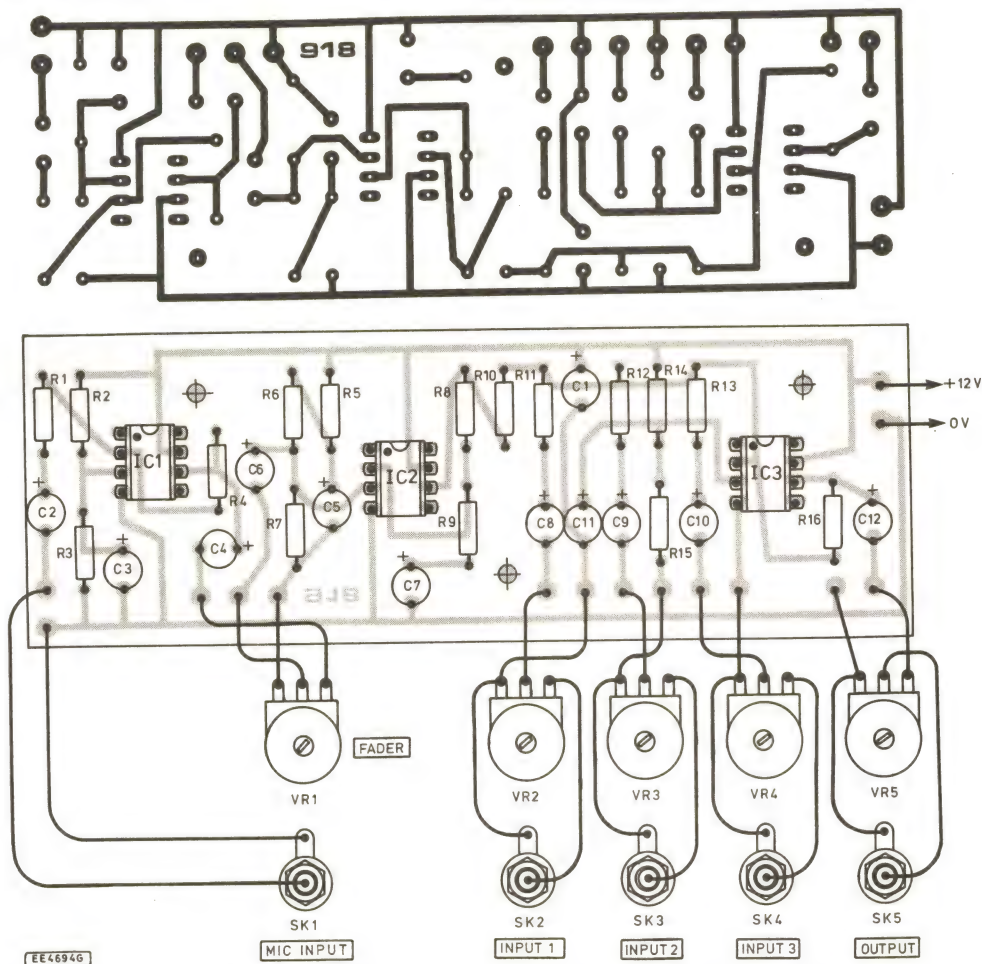


Fig. 19. Audio Mixer printed circuit board component layout, wiring and full size copper foil master.

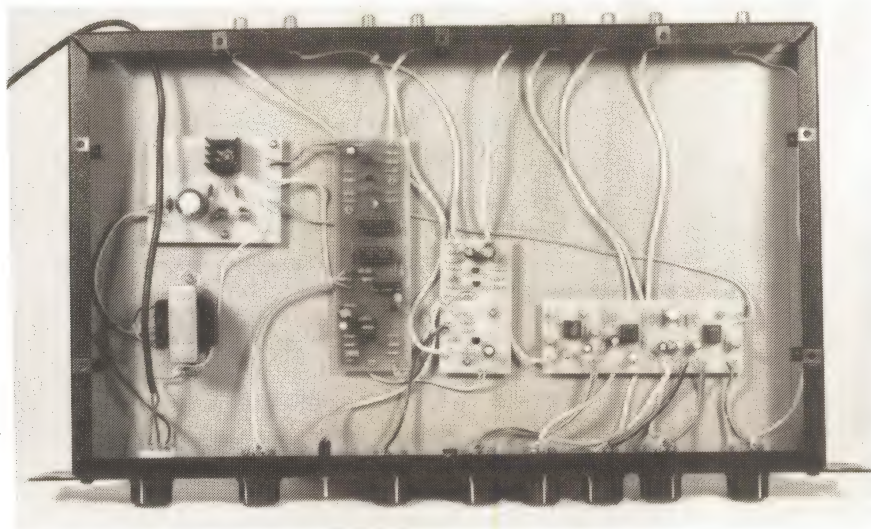

The Audio Mixer input and output sockets are mounted on the rear panel of the case.



Wiring to the Mixer module printed circuit board, using screened leads, can be seen in the right-hand corner of the metal case.

less prone to stray pick up, but it would still be advisable to use screened cables for these connections unless this wiring is very short. Similarly, screened cables should also be used to connect controls VR2, VR3, and VR4 to the p.c.b. unless this wiring is very short.

Phono sockets are shown for SK1 to SK5 in the wiring diagram Fig. 19, and this is the type of socket normally used for both the audio and video signals on amateur video equipment. However, it is obviously in order to use any type of audio connector which fits in well with your other equipment. For example, a 3.5mm jack socket might be a better choice for SK1.

TESTING

When initially testing the mixer it is probably best to feed its output to the *audio* input of a television set or monitor. You can then feed signals to the inputs, and check that the various controls have the correct effect.

When trying the microphone input remember that "howl-around" will almost certainly result if the microphone level control (VR1) is advanced too far. For this reason, when using the microphone input in earnest the audio output signal *should not* be monitored using a loudspeaker. It might be all right to monitor the signal using headphones, but even this can cause feedback problems.

Next Month: We conclude with a Dynamic Noise Limiter and the System Power Supply module.

ELECTRONICS PRINCIPLES II SOFTWARE

from E.P.T. Educational Software (Tel: 0376 514008)

If you are looking for a means of improving your knowledge of the basics of electronics then this software is for you.

Electronics Principles II covers:

- ★ Insulators, Conductors, Resistance
- ★ D.C. Circuits
- ★ Capacitance and Inductance
- ★ A.C. Series Circuits
- ★ A.C. Parallel Circuits
- ★ Reactance and Impedance
- ★ A.C. and D.C. Power
- ★ Frequency and Tuned Circuits
- ★ Using Numbers
- ★ Complex Numbers, Phase Angles
- ★ P.N. Junction Diode
- ★ Transistors
- ★ Operational Amplifiers
- ★ Logic Gates
- ★ Digital Number Systems
- ★ Combinational Logic
- ★ Flip Flops
- ★ Counters and Shift Registers
- ★ Memory
- ★ Microcomputer operation

Electronics Principles II is a major revision of the successful original version currently used by electronics hobbyists, schools, colleges, and for training within industry throughout the U.K. and overseas. Some of the modifications are as a result of feedback from teachers, but mostly the changes are due to making greater use of the available improvements in software development technology. Text has been removed from the screen and is now selected by the F1 key. This provides a larger screen area on which to develop the circuit diagrams and calculations, greatly improving the graphics presentation.

The individual sub-menus are changed to selection buttons, this makes all those topics available within a module, clearly visible to the user. The layout of the calculations is considerably enhanced, firstly by providing the formulae used and secondly by showing the calculation steps, exactly as in a textbook; the advantage here being that you can input your own values.

Mouse selection is improved by increasing the screen range over which the button may be clicked. There are several additional screens, developing further previous topics and a new program illustrating microprocessor registers and the operation of a micro-computer.

Having reviewed a dozen, or more, educational software packages designed to "teach" electronics, I was more than a little sceptical when I first heard about Electronics Principles: there seemed to be little that could be done that has not been done elsewhere. When I started to use the package my views changed. Indeed, I was so impressed with it that I quickly came to the conclusion that Everyday with Practical Electronics readers should have an opportunity to try the package out for themselves! — MIKE TOOLEY B.A. Dean of Faculty of Technology, Brooklands Technical College

Over 200 menu driven screens with interactive graphics enabling a learning by doing approach to encourage experimentation.

Complete package **Only £49.95** inc. VAT.

ELECTRONICS P.C. TOOLBOX VERSION 2.0

New extended and improved version of the popular Toolbox software. Presents commonly used formulae in a way that makes calculations easier thus encouraging experimentation in circuit design.

Covers D.C. Calculations from Ohm's Law to Loading a Potential Divider; Further D.C. Calculations from Power Ratio Decibels to Kirchhoff's Laws; A.C. Calculations from Average Peak Current to Filters and Admittance; Capacitance Calculations from values to RC Time Constants; Inductance Calculations from value to Selectivity; Binary Calculations from Addition to 2's Complement; Numbers and Phase Angles from addition to Polar to Rectangular; Operational Amplifiers from Inverting Op-Amp to Op-Amp Differentiator.

Only £19.95 inc. VAT

FREE While stocks last each Toolbox Version 2.0 ordered will be supplied with two different EPE "Calculation Corner" wall charts covering D.C. and A.C. Electricity.

These programs require a PC (or fully compatible system) running DOS with an 80286 or better processor and VGA (ideally colour) graphics. In addition you must have a hard disk, a high density (1.44Mb) floppy drive and at least 640K of RAM. We also recommend the use of a mouse. Site licences are available — please enquire.

Distributed by **Direct Book Service**, 33 Gravel Hill, Merley, Wimborne, Dorset BH21 1RW. (Mail Order Only).

Add £1 per order for UK post and packing. Make cheques payable to **Direct Book Service**.

Direct Book Service is a division of **Wimborne Publishing Ltd.** publishers of *Everyday with Practical Electronics*.

Tel: 0202 881749. Fax: 0202 841692.

Visa and Mastercard orders accepted (minimum credit card order £5) — please give card number, card expiry date and cardholders address if different to the delivery address. Orders are normally sent within seven days but please allow a maximum of 28 days — longer for overseas orders.

OVERSEAS ORDERS: Add £2 postage for countries in the E.E.C. Overseas readers, outside the E.E.C. countries add £3 for airmail postage.

Demonstration disk available
Electronic Principles II, GCSE Maths
or Mathematics Principles (state which)
send £2 (Overseas orders send £3)
— includes P&P

GCSE MATHS

A series of programs covering *all the major topics* required by the school syllabus. Designed to be user friendly enabling you to study or revise in what we believe is an interesting and enjoyable way. There are nearly one hundred and fifty menu driven screens with interactive graphics, enabling a 'learning through doing' approach to encourage experimentation. Now being used in many schools throughout the U.K.

Overseas customers or for those with a general interest in maths order **Mathematics Principles**

Only £49.95 inc. VAT for either package

VIDEOS ON ELECTRONICS

A range of videos designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They are proving particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc.

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

VT201 55 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more.

Order Code VT201

VT202 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits.

Order Code VT202

VT203 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained.

Order Code VT203

VT204 56 minutes. Part Four; Power Supplies. Guides you step by step through different sections of a power supply.

Order Code VT204

VT205 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc.

Order Code VT205

VT206 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits.

Order Code VT206

By the time you have completed VT206 you have completed the basic electronics course and should have a good understanding of the operation of basic circuit elements.

VCR MAINTENANCE

VT102 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output.

Order Code VT102

VT103 32 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path.

Order Code VT103

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier.
(All videos are to the UK PAL standard on VHS tapes)

Now for the digital series of six videos. This series is designed to provide a good grounding in computer technology.

VT301 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation.

Order Code VT301

VT302 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc.

Order Code VT302

VT303 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital design. Gets into multiplexers, registers, display devices, etc.

Order Code VT303

VT304 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital to analogue and analogue to digital converter circuits.

Order Code VT304

VT305 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices.

Order Code VT305

VT306 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work.

Order Code VT306

By now you should have a good understanding of computer technology and what makes computers work. This series is also invaluable to the computer technician to understand the basics and thus aid troubleshooting.

VT401 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system.

Order Code VT401

NEW VT402 58 minutes. F.M. Radio 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier; limiter and f.m. decoder stages of a typical f.m. receiver.

Order Code VT402

NEW VT403 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding.

Order Code VT403

NEW VT501 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers.

Order Code VT501



ORDERING: Add £1 p&p per order for UK orders. **OVERSEAS ORDERS:** Add £2 postage for countries in the EEC. Overseas orders outside the EEC countries send £25.49 (price less VAT) plus £3 per tape airmail postage (or £5 per order surface mail postage). All payments in £ sterling only (send cheque or money order drawn on a UK bank).

Visa and Mastercard orders accepted – please give card number, card expiry date and cardholder's address if different from the delivery address. Orders are normally sent within seven days but please allow a maximum of 28 days – longer for overseas readers.




Send your order to: **Direct Book Service, 33 Gravel Hill, Merley, Wimborne, Dorset BH21 1RW (Mail Order Only)**

Direct Book Service is a division of Wimborne Publishing Ltd., Publishers of *Everyday with Practical Electronics*. Tel: 0202 881749. Fax: 0202 841692

£29.95
each inc. VAT

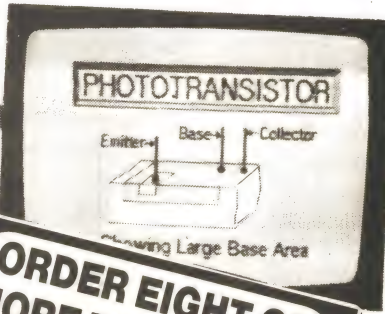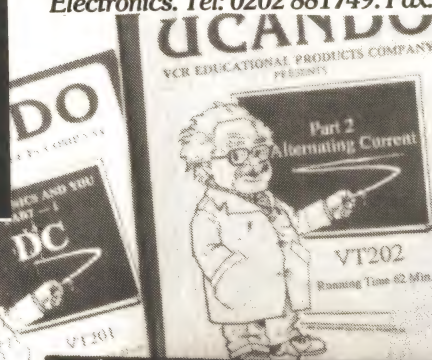

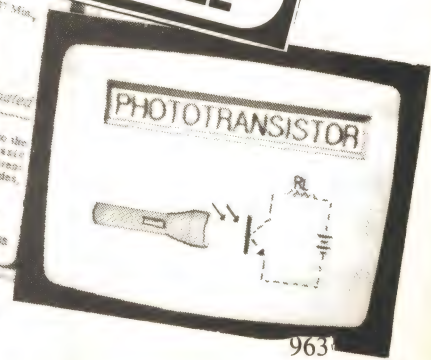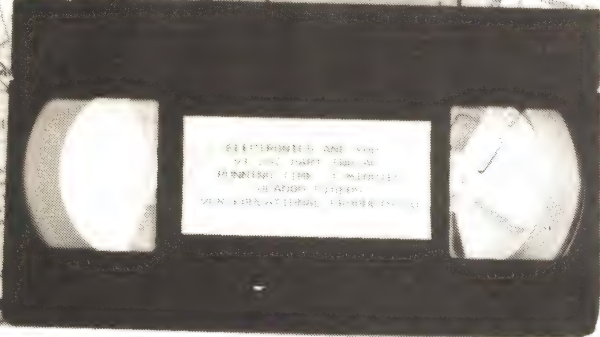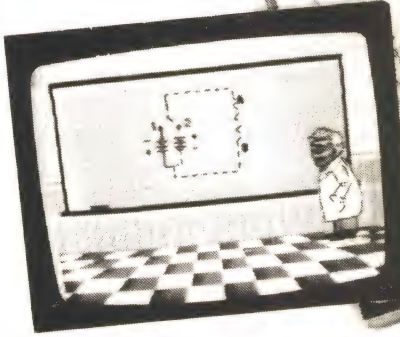ORDER EIGHT OR MORE TOGETHER - GET ONE FREE



RODENT REPELLER

TERRY de VAUX-BALBIRNIE

A flashy but soundly conservationist way to rid your rooms of rodents – goodbye Mr. Mouse!

THIS project was born out of the need to produce a simple but effective means of repelling some unwelcome visitors to the attic – the Mouse Family.

Some people lay down poison and others set traps. Some are not so brave and wish the rotten rodents would go away without having to kill them. The idea of a poisoned animal wandering off and dying somewhere is repugnant to many people.

Also, a trap sometimes leaves the terrified creature caught by the tail and releasing it can be a gruelling experience. Humane traps are available which catch the mouse alive but these would need to be checked regularly if the occupant is not going to starve to death – also, not everyone can pluck up the courage to carry the trap containing the terrified creature within to release it.

PACK YOUR BAGS

The Rodent Repeller will be found best at keeping mice away. However, it should also be successful at making the established “Mouse Family” pack their bags and seek hospitality elsewhere. It works by using a brilliant intermittent flashing light and a high-pitched whistle – a combination which frightens Ronald Rodent and family and deprives them of a good night’s sleep.

Although not very suitable for the general living area of the house, it could be used there to keep mice at bay while away on holiday. It works well in cupboards, roof spaces and other dark places since then the light appears particularly bright. The flashing lamp and sounder operate together at varying intervals to keep Mr. Mouse on his toes – the effect is not truly random because the timing cycle repeats after three but these animals are not thought to be good at their arithmetic.

The Rodent Repeller is mains-operated so may be left connected continuously for very little cost. Although in the prototype, the flashing light and audible warning device are part of the main unit, it would be a simple matter to mount them remotely on a subsidiary plastic box.

It would then be possible to site the main section in a convenient location – possibly more accessible to the mains supply – so that it could be switched on and off as required. The inter-connecting wire could be of any light-duty twin type of any reasonable length.

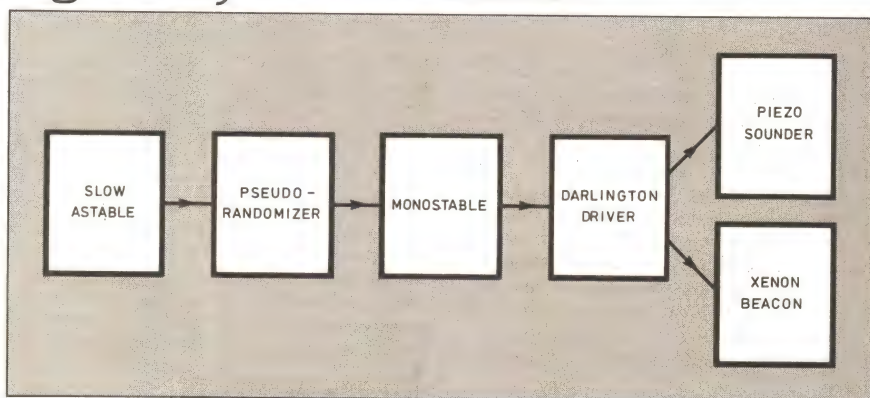


Fig. 1. Block diagram of the Rodent Repeller.

XENON TUBE

The light source is a xenon flash tube (of the type used in small photographic flash guns). This is part of a ready-made unit – a xenon beacon – which is often to be seen mounted on the external housings of burglar alarm sirens. A clear (uncoloured) beacon is best for this project. When activated, these devices flash between once and three times per second which makes them effective for the present purpose.

The sounder is a piezo-electric buzzer. A high-pitched sounder is most effective and

it should be chosen to be as loud as possible. It is also important to use the correct type and more will be said about this later. The sounder specified in the components list will be found very suitable although other types could be tried.

It is recommended that a frequency no lower than 2.4kHz is used – the higher the better. High-pitched sounds appear to be particularly annoying to mice. Also, high frequency sound does not “carry” very well to the human living area since it is easily absorbed by intervening objects.

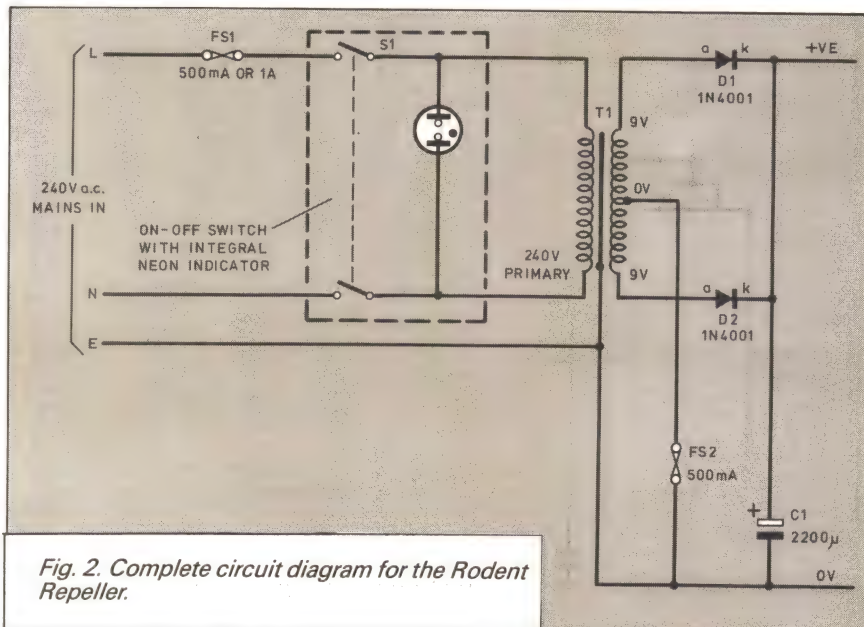


Fig. 2. Complete circuit diagram for the Rodent Repeller.

This means that it will be very loud where the mice live, but less likely to disturb paying occupants some distance away.

Although useful as a rodent repeller, this is a versatile circuit and some readers will, no doubt, find alternative uses for it. Other 12V output devices could be connected, up to a total maximum loading of 250mA.

BLOCK DIAGRAM

The Rodent Repeller is illustrated in block diagram form in Fig. 1. The first section consists of a slow astable. This produces a regular chain of pulses at a rate of between one every 13 seconds and one every 22 minutes approximately, depending on adjustment and component tolerances.

These pulses are applied to the second section which *pseudo-randomizes* them. New pulses are then delivered after a certain number of input pulses have been counted. These will be provided at twice, three times and five times the frequency of the astable. The cycle then repeats indefinitely.


At minimum adjustment, therefore, there will be output pulses at intervals of 26, 39 and 65 seconds approximately. At maximum, the nominal timings will be 44, 66 and 110 minutes.

The next section is a monostable. The "randomized" pulses trigger this so that, with the arrival of each one, an output is provided of between five and 50 seconds duration, depending on the adjustment. This output operates the final part of the circuit which is a Darlington driver having sufficient current-handling capacity to power the piezo-sounder and xenon beacon.

POWER SUPPLY

The complete circuit diagram for the Rodent Repeller project is shown in Fig. 2. Power is derived from the 240V a.c. mains supply by a conventional arrangement of step-down transformer, T1, twin full-wave rectifier diodes, D1 and D2 and smoothing capacitor, C1. There is a double-pole ON-OFF switch with integral neon indicator, S1, in the mains feed and fuses are included in both the mains circuit (FS1) and low-voltage section (FS2).

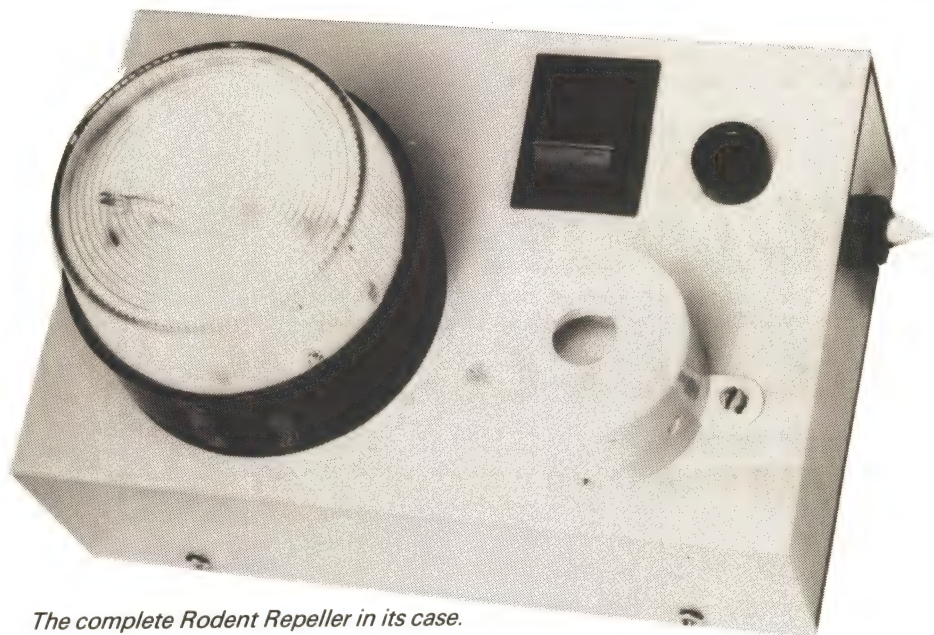Note that a 9V transformer is sufficient to provide a nominal 12V supply since capacitor C1 charges up to the *peak* voltage



The complete Rodent Repeller in its case.

of the rectified waveform. This is approximately 1.4 times the nominal output provided by the transformer secondary winding – giving 13V approximately.

However, there is the forward voltage drop (0.7V approximately) across the rectifier diodes to take into account and an additional voltage drop caused when the load of the flashing beacon and sounder is applied. The specified audible warning device will operate over a wide voltage range and tests show that the xenon beacon will work on less than 10V so the operating voltage is not particularly critical.

COUNTING PULSES

The astable section is centred on IC1 – a ZN1034E precision timer integrated circuit. IC1 differs from the common "555 timer" type device by using digital techniques to allow a very slow pulse repetition frequency to be obtained without the need for high-value timing components which would be bulky and costly.

With a supply connected to IC1 pins 4 and 5 through resistor R3, a precision 2.6V output is produced by an on-chip regulator. This is available at pin 14.


Capacitor C2 charges up from this precision supply through preset potentiometer

VR1 and resistor R1. The time taken to do this is set by the values of VR1, R1, R2 and C2. Thus, with R1, R2 and C2 fixed in value, the rate at which C2 charges can be varied by adjustment to VR1.

As capacitor C2 charges, the voltage across it rises and, at a pre-determined threshold level, a count of one is clocked-up by an on-chip binary register. It then discharges to begin a further cycle. When 4095 ($2^{12} - 1$) counts have been registered, output pin 2 goes from *low* (0V) to *high* (+5V) and output pin 1 goes from *high* to *low*. This marks the end of the timing cycle.

When this happens, the low state of pin 1 resets the i.c. by taking pin 3 low via resistor R4. Timing begins once again and the cycle repeats as long as a supply exists. Since precise timings are not required in this circuit, an inexpensive ceramic capacitor may be used in the C2 position. Capacitor C3 is required for stable operation of the i.c.

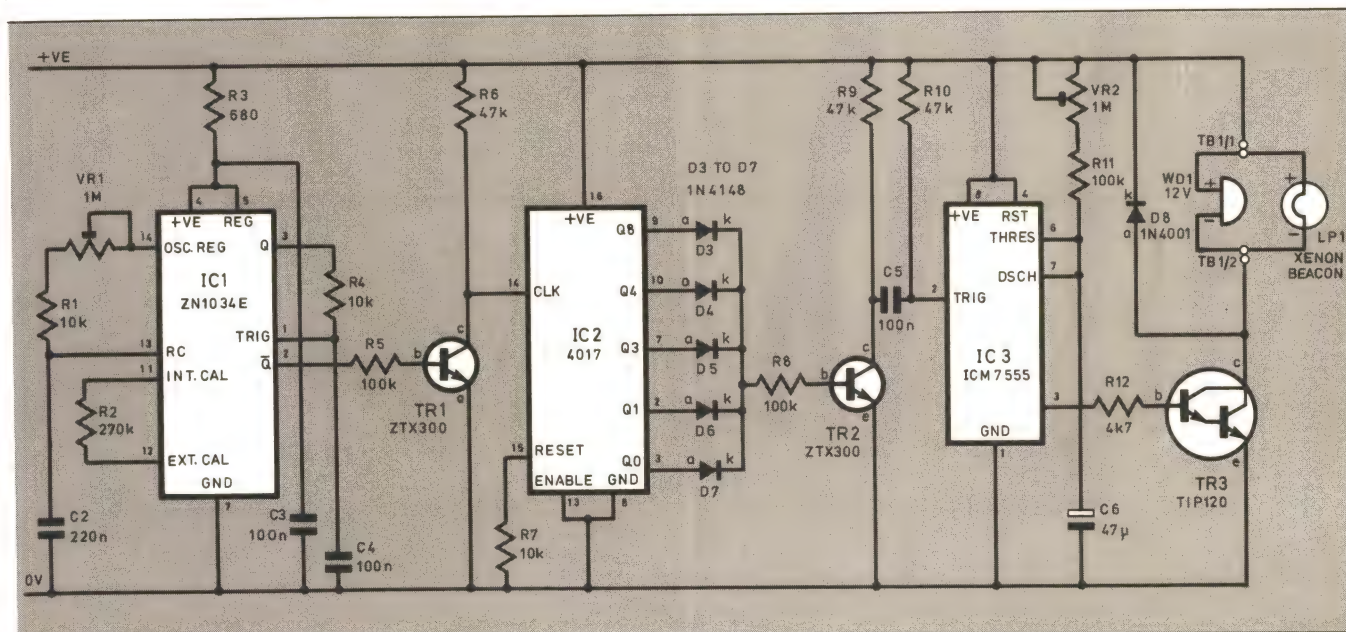The randomizing section centres on decade counter IC2. This accepts pulses applied to its clock input, pin 14, these being derived from IC1 output pin 2. However, these pulses are not of a sufficient voltage level to be used directly. This is because they arrive from IC1 at +5V rather than at +12V as required by IC2.



The voltage is therefore amplified by applying the pulses to the base of transistor TR1 through current-limiting resistor R5. Thus, with the arrival of each pulse, the transistor switches on and its collector – and hence IC2 clock input pin 14 – goes low. While the transistor is turned off, IC2 pin 14 is held high (+12V) via resistor R6. Clock input pin 14 is therefore pulsed between long high and short low states.

IC2 has ten fully decoded outputs 0 to 9. With the arrival of positive-going pulses at pin 14, each of the outputs goes high in turn. When all outputs have cycled, the chip automatically begins counting again from zero.

KEEP 'EM GUESSING

When any of the connected outputs, Q0, Q1, Q3, Q4 or Q8, goes high, current is directed through one of the diodes D3 to D7 as appropriate and flows through current-limiting resistor, R8, to the base of transistor TR2. The transistor will therefore turn on at varying time intervals. Note, however, that there is no further effect if TR2 base remains high, only if it goes low before becoming high again. The outcome is that the collector of transistor TR2 goes low successively at twice, three times and five times the basic clock frequency.

If, for example, VR1 is adjusted so that IC1 produces 10-minute pulses, then TR2 will turn on at 20, 30 and 50 minutes then repeat – good enough to keep Mr. Mouse guessing. This particular arrangement of used IC2 outputs gives good results with the prototype but other combinations could be tried if desired.

The low transitions occurring at TR2 collector are applied, via capacitor C5, to

the monostable circuit centred on IC3. Thus, when trigger input pin 2 goes low, output pin 3 goes high for a time determined by the values of preset potentiometer VR2, resistor R11 and capacitor C6. The output then reverts to a low level.

Adjustment to the timing is provided by VR2 and with the specified values this will lie between about five and 50 seconds. It could be easily extended by increasing the value of resistor R11 or capacitor C6 if required.

It is a characteristic of this type of timer that a low pulse is required at the trigger input rather than a high one. IC3 Pin 2 is normally held high through resistor R10 and this prevents false triggering. Between pulses, capacitor C5 discharges rapidly through resistors R9 and R10, ready for further operation.

While high, IC3 output pin 3 directs current to the base of Darlington transistor TR3 through current-limiting resistor R12. Collector current then flows through audible warning device WD1 and xenon beacon LP1 connected in parallel.

A Darlington device consists of two interconnected transistors in the same package. It is equivalent to a single transistor with a high input impedance and an exceptionally high current gain. Thus, a very small base current is sufficient to provide a large collector output.

Note that TR3 is amply-rated to drive the specified AWD and xenon lamp and does not require a heat sink. Diode D8 is included as a precaution in case an inductive load, such as a relay, is ever connected to the output. If this were done, the collapse of the magnetic field on switching off could generate a high-voltage pulse which could damage semiconductor components in the circuit. Certain types of audible warning device could have a similar effect.

MAINS POWER

Important Safety Warning: Construction of this project involves making mains connections. It is therefore essential for any reader who is not certain of being able to make a safe job to seek professional advice. Before removing the lid of the case to make adjustments to the timings or for any other reason, the unit must first be unplugged from the mains.

The Rodent Repeller is designed to be plugged into a standard mains wall socket. It should not be permanently wired-in. Note also that the completed project must be housed in an earthed metal box and correctly fused in both transformer primary and secondary circuits as indicated.

It is important to use a good quality transformer of adequate current rating (see components list). This will remain cool in operation and be suitable for continuous use.

Some cheap transformers have an excessive off-load voltage. The theory is that the voltage drops to the nominal value when a full load is applied. These transformers should be avoided in this application since, between operations of the beacon and sounder, very little current is drawn from the transformer – that is, it is almost off-load. The output voltage could then be sufficiently high to cause damage to the circuit.

CONSTRUCTION

One further practical point is that the chosen sounder must be of the type with internal drive circuitry. Other types will not work. The correct type will be described as being suitable for 12V d.c. operation (or a range of d.c. voltages spanning 12V).

Most of the components for the Rodent Repeller are mounted on a single-sided

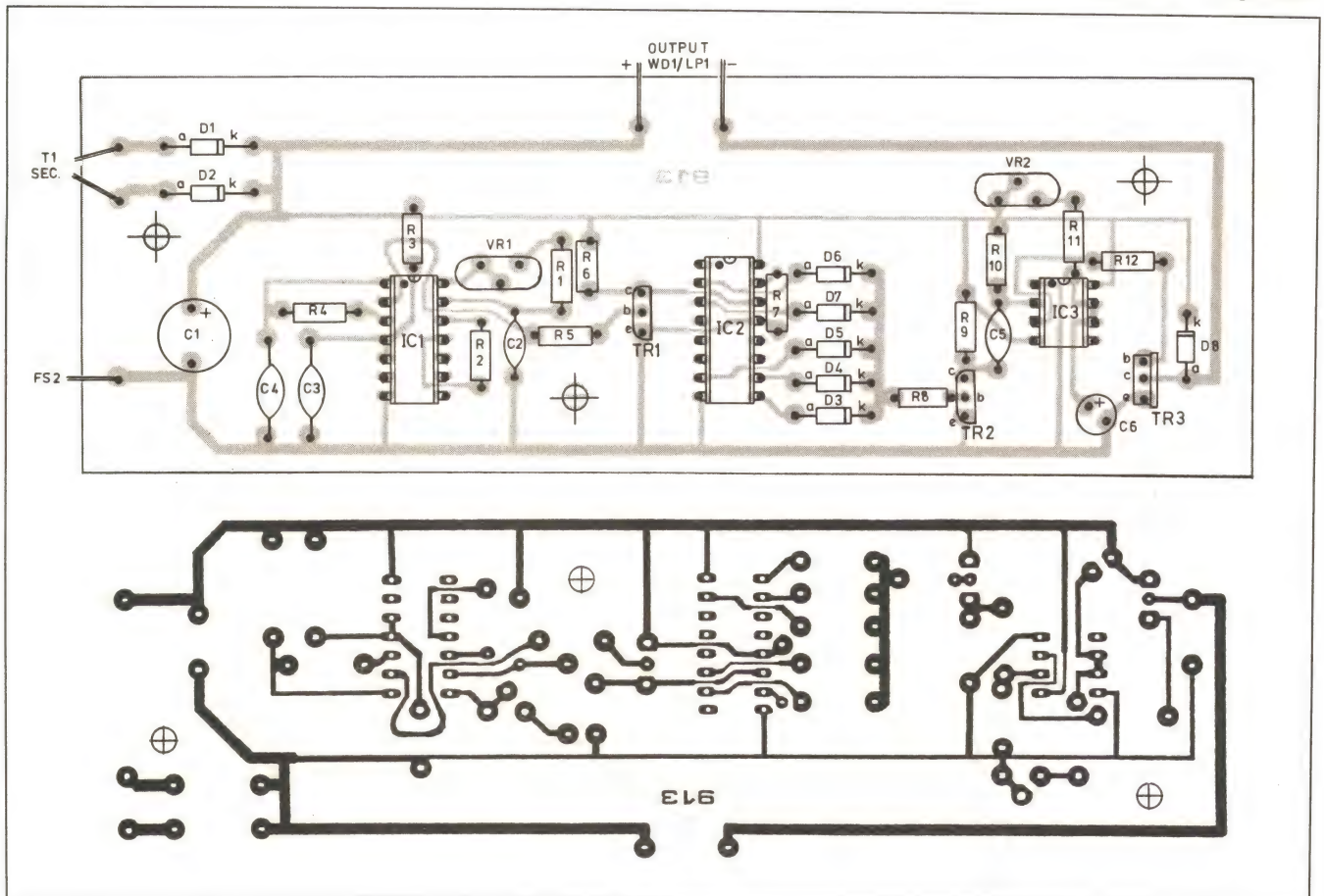


Fig. 3. Printed circuit board component layout and full size copper foil master track pattern.

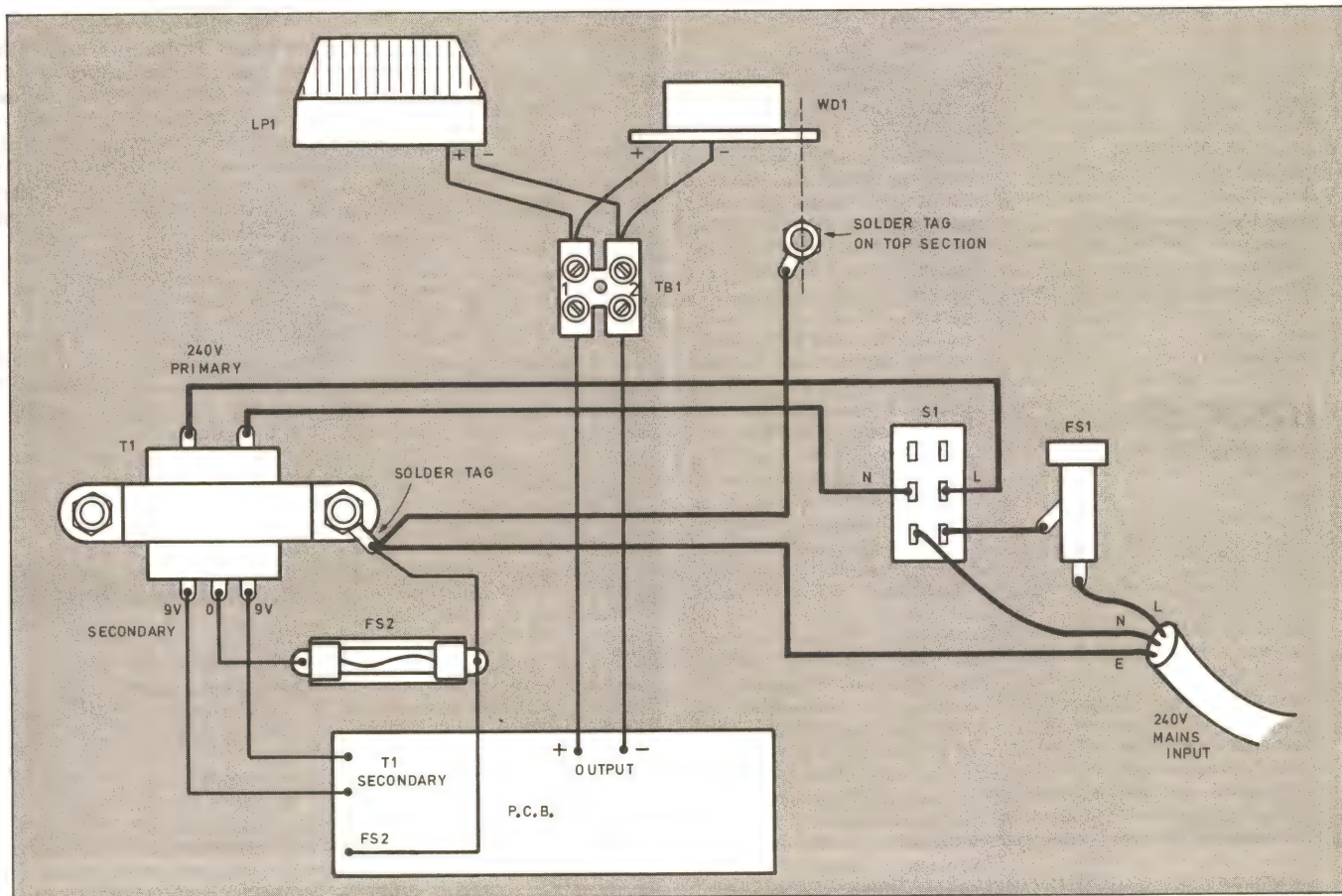


Fig. 4. Wiring details for the Rodent Repeller.

printed circuit board (p.c.b.). A full-size copper foil master track pattern and component layout details are shown in Fig. 3. This board is available from the *EPE PCB Service*, code 913.

Begin construction by drilling the three mounting holes in the circuit board, 2mm in diameter, at the positions indicated. The recommended assembly order is as follows. Firstly, solder in the three i.c. sockets followed by resistors, non-electrolytic capacitors (C2 to C5) and diodes – all mounted flat to the board. Next, mount the transistors and the two preset potentiometers. Finally, solder in electrolytic capacitors C1 and C6. Take particular care over the polarity of the diodes, transistors and electrolytic capacitors.

Adjust the presets fully anti-clockwise (as viewed from the top edge of the circuit board) – this will provide the shortest timings which will be convenient for testing purposes. Solder a temporary wire 10cm long to either position labelled “T1 sec” on the circuit board and a similar piece of wire to the position marked “FS2”. Solder two further pieces of wire to the output pads and secure the two-section piece of screw terminal block to the free ends of these.

The terminal block will eventually be used for the sounder and beacon connections. However, it is better if a small 12V bulb (an MES type of 2.2W rating in a suitable lamp holder for example) is used for the moment. It is then possible to test the p.c.b. using a 9V or 12V battery without the encumbrance of having to observe mains safety precautions. Any small problems may then be solved before attempting to the mains-operated section.

A PP3 battery is not really up to this job. It would be better to use a PP9 type or, perhaps, six “AA” size cells in a suitable battery holder.

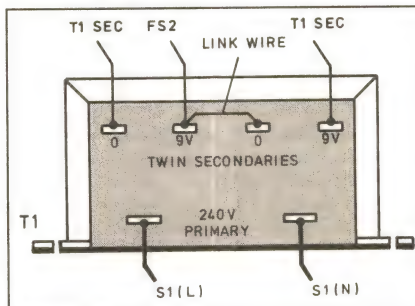


Fig. 5. Alternative transformer wiring.

Insert the i.c.s into their sockets taking care over the orientation. Since these are all CMOS devices, they could possibly be damaged by excessive static charge which might exist on the body. It would therefore be wise to touch something which is earthed, for example, a water tap, before removing them from their packaging and touching the pins.

Now, using crocodile clips or other reliable method, connect the battery negative terminal to the wire leading to the position marked “FS2” on the circuit board. Connect the positive terminal to the wire leading to diode D1 or D2. IC3 often triggers when power is first applied so the lamp will probably come on immediately and go off a few seconds later.

Leave the battery connected and check that the light operates at roughly the correct time intervals. As a guide these will be 26, 39 and 65 seconds, then repeat. Note that on powering-up, IC2 may begin with any one of its outputs high so the cycle may not begin as expected. If the circuit operates correctly in this basic test, attention may be given to preparing the case for the printed circuit board and other internal components.

JUST IN CASE

Prepare the box by drilling three holes in the base section to correspond with those already made in the circuit board. Drill holes also for transformer T1, chassis fuse holder FS2, and a further one of sufficient diameter to accommodate the strain relief bush to be used on the mains input lead. Drill holes in the top section of the case for on-off switch S1, panel fuse holder FS1 and terminal block TB1 mounting (see photograph).

Further holes will need to be drilled in the top of the case to mount the sounder and xenon beacon, depending on the type. Holes will also be needed for their connecting wires to pass through. If these components are to be mounted remotely, a hole will be needed for a small socket (for example, a 3.5mm mono jack-type socket) to enable them to be connected through a matching plug and length of twin wire.

TRANSFORMER MOUNTING

Mount the mains transformer (only loosely at the moment if the connections are difficult to reach with the soldering iron) noting the solder tag at one of its fixings. **This will be used for earthing the case and transformer core and is essential for safety reasons.** It will probably be necessary to de-solder the temporary wires which were previously connected to the circuit panel for testing purposes. However, those connected to the output pads will be used.

Make the three connections from the circuit board to the transformer secondary. If the transformer is of the type having a “9V-0V-9V” secondary (sometimes called a centre-tapped secondary), proceed by referring to Fig. 4. Here, the transformer is shown having three secondary wires, or

tags. These may be marked "9V, 0V, 9V" or similar. If coloured, there may be two white ones and one black. The two of similar colour will be the 9V connections and should be connected as such to the "T1 secondary" positions on the circuit board. The black wire is the 0V one and is connected to fuse FS2.

COMPONENTS

Resistors

R1, R4,	
R7	10k (3 off)
R2	270k
R3	680
R5, R8,	
R11	100k (3 off)
R6, R9,	
R10	47k (3 off)
R12	4k7
All 0.25W 5% carbon film or better	

See
**SHOP
TALK**
Page

Potentiometers

VR1, VR2	1M vertical sub-min. preset (2 off)
----------	--

Capacitors

C1	2200µ 25V radial elect. 25V
C2	220n disc ceramic
C3, C4,	
C5	100n disc ceramic (3 off)
C6	47µ radial elect. 25V

Semiconductors

IC1	ZN1034E precision timer
IC2	4017 decade counter
IC3	ICM7555 CMOS timer
D1, D2,	
D8	1N4001 50V 1A rectifier diode (3 off)
D3 to D7	1N4148 signal diode (5 off)
TR1, TR2	ZTX300 npn transistor (2 off)
TR3	TIP120 (or TIP121 or TIP122) npn Darlington transistor

Miscellaneous

T1	miniature transformer with 240V primary and 9V-0V-9V (or twin 9V secondaries) 250mA minimum
S1	d.p.s.t. rocker switch with 1A minimum mains-rated contacts and integral neon indicator
FS1	20mm panel fuse holder with 1A or 500mA ceramic mains fuse to fit
FS2	20mm chassis fuse holder with 500mA glass fuse to fit
TB1	2A screw terminal block - 2 sections required
WD1	12V piezo sounder suitable for 10V to 12V operation, 3kHz operation and 103dB output at 1 metre
LP1	clear xenon beacon (burglar alarm type) - 12V operation up to 200mA rating - see text.

Printed circuit board available from EPE PCB Service, code 913; aluminium box size 155mm x 105mm x 45mm; 8-pin d.i.l. socket; 14-pin d.i.l. socket; 16-pin d.i.l. socket; 3.5mm jack plug and socket (see text); 3-core 3A mains wire; strain relief bush, rubber grommets (2 off); heat shrinkable sleeving, cable ties, solder tags (2 off), nuts, bolts, connecting wire, solder, etc.

Approx cost
guidance only

£39

If the transformer has twin 9V secondaries, follow Fig. 5. Again, it will be clear either by colour-coding or printing on the body which wire or tag is which. It will be seen in Fig. 5 that one of the 0V wires and one of the 9V ones are linked together to form the new "0V" line which connects to FS2. The 9V wire or tag left over together with its 0V counterpart are connected to the "T1 sec" positions on the circuit board (either way round).

INTERWIRING

Referring back to Fig. 4, mount all remaining internal components including the circuit board itself. This should be attached using small fixings through the holes already drilled for the purpose. Use 5mm long plastic stand-off insulators on the bolt shanks - these should ensure that all connections on the copper track side remain clear of the metal-work. If necessary, place a piece of thick cardboard between the p.c.b. and the bottom of the case as an additional precaution.

Attach the sounder and xenon beacon. Connecting wires passing through the box must be protected using a rubber grommet. Note the solder tag at one of WD1 fixings. This will be used to provide reliable earthing of the case top section. If this position is not convenient, a small hole should be drilled elsewhere in the top section and the solder tag secured with a small fixing.

Complete the internal wiring apart from the mains input lead. Use a piece of mains-type wire to interconnect the solder tags in the base and top sections of the case. **Note that all wiring shown drawn in thicker lines in Fig. 4 must be mains type of 3A rating minimum.**

If the transformer has exposed primary tags, make a cardboard or plastic shield for these. Transformers having "flying lead" connections, of course, do not need this. Heat-shrinkable sleeving should be used to insulate the connections at the on-off switch S1 and fuseholder FS1.

MAINS LEAD

Make up the mains input lead using a sufficient length of 3-core mains-type wire of 3A rating minimum. Fit a standard mains plug on the end and insert a 2A fuse. Pass the other end through the strain relief grommet and secure it. Complete the mains wiring using more heat shrinkable sleeving to insulate otherwise exposed connections. **Make certain that all connections are secure and cannot pull free in service.**

The wiring may be tidied up by grouping wires into bundles and using cable ties or spiral wire wrap on them. Tighten the transformer fixings firmly. Insert a 500mA glass fuse in the chassis fuse holder (FS2) and a 500mA or 1A mains-type ceramic fuse in the panel fuseholder (FS1). Note that glass fuses are not suitable for direct mains use.

ADJUSTMENT AND TESTING

It is probably best to continue using the small lamp already connected to terminal TB1 until the unit has been tested on the mains supply and to enable the operating times to be set conveniently. Pass the lamp holder wires through one of the holes which have already been drilled for the beacon or buzzer wires so that testing may be undertaken with the lid of the case in position.


Plug in the unit, switch on and check for correct operation. If all is well, adjust the preset potentiometers clockwise for the required delays and operating time. This could be the subject of experiment over the next few days. Setting the wiper of preset potentiometer VR1 to approximately mid-track position should provide a basic clock rate of about one pulse every 10 minutes so the lamp will operate at 20, 30 and 50 minutes then repeat. This is just a guide and the actual timings will depend to some extent on component tolerances.

With VR2 adjusted to mid-track position, an operating time (beacon and sounder on time) of some 30 seconds would be expected. However, the actual value of capacitor C6 is often higher than its nominal value so the timing is likely to be rather longer than that calculated. When the timings are set to satisfaction, the test lamp may be removed and the beacon and buzzer connected to terminal TB1 with the correct polarity.

FLASH LIFE


The rated life of the flash tube is approximately one million operations. Taking into account the fact that the unit operates only intermittently, the service life of the xenon beacon will be in excess of 12 months. Since it is unlikely that the unit will be used for more than a few weeks in the year, the potential life will be several years.

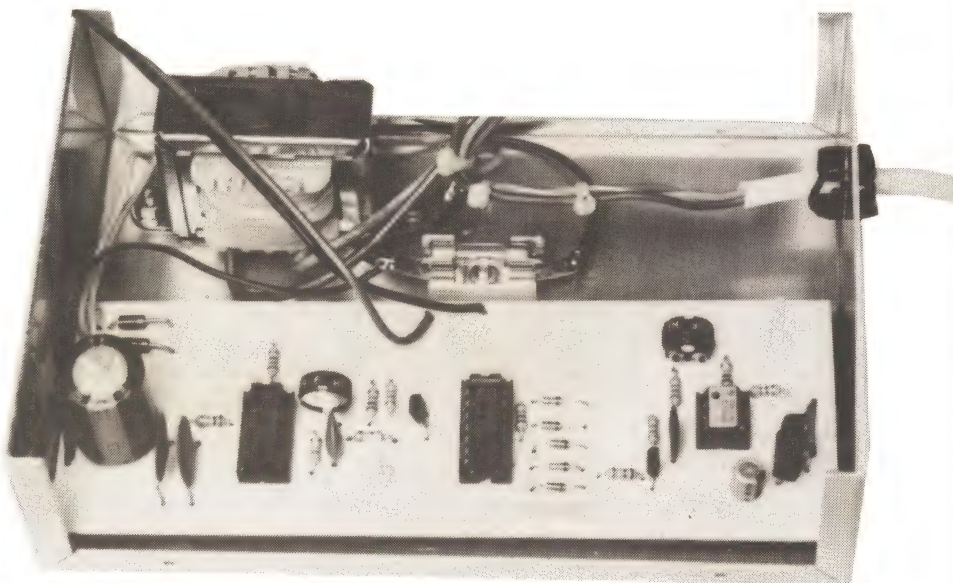Experiment to find the best position for the unit - near where the Mouse Family nest and forage. Goodbye Mr. Mouse! □



POWERFUL SCHEMATIC CAPTURE, PCB DESIGN AND AUTOROUTING ALL FOR JUST £395...

PROPAK AR for DOS provides all the features you need to create complex PCB designs quickly and easily. Draw the circuit diagram using the powerful facilities of ISIS DESIGNER+ and then netlist into ARES AUTOROUTE for placement, autorouting and tidy up. Advanced real time design rule checks guarantee that the final PCB will correspond exactly with the schematic thus saving you from costly layout errors and time consuming debugging.

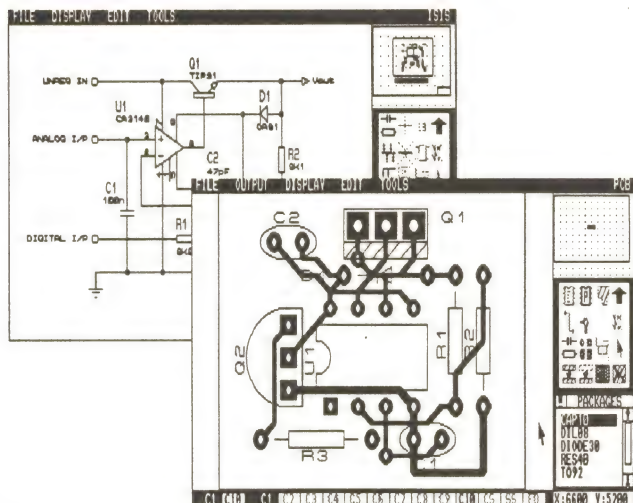

- Attractive, easy to use graphical interface.
- Object oriented schematic editor with automatic wire routing, dot placement and mouse driven place/edit/move/delete.
- Netlist generation for most popular CAD software.
- Bill of Materials and Electrical Rules Check reports.
- Two schemes for hierarchical design.
- Automatic component annotation and packaging.
- Comprehensive device libraries and package libraries including both through hole and SMT parts.
- User definable snap grids (imperial and metric) and Real Time Snap to deal with tricky SMT spacings.
- Manual route editing features include Auto Track Necking, Topological editing and Curved tracks.
- Autorouting for single, double and multi-layer boards.
- Non autorouting PROPAK is available for just £250 if you do not need or want the router.
- Full connectivity and design rule checking.
- Power plane generator with thermal relief necking.
- Graphics support to 800x600 Super VGA.
- Output to dot matrix and laser printers, HP and Houston plotters, Postscript devices, Gerber and Excellon NC machines plus DXF and other DTP file formats.

CADPAK

Two Programs for the Price of One

ISIS SUPERSKETCH

A superb schematic drawing program for DOS offering Wire Autorouting, Auto Dot Placement, full component libraries, export to DTP and much more.

Only
£79

Exceptionally easy and quick to use. For example, you can place a wire with just two mouse clicks - the wire autorouter does the rest.


PCB II

High performance yet easy to use manual PCB layout package. Many advanced features including curved tracks, auto track necking, DXF export, Gerber and NC file generation, Gerber viewing and more.

Alan Chadwick writing in ETI (January 94) concluded...
"At £79 I thought this was an excellent buy."

ISIS ILLUSTRATOR

Schematic Drawing for Windows

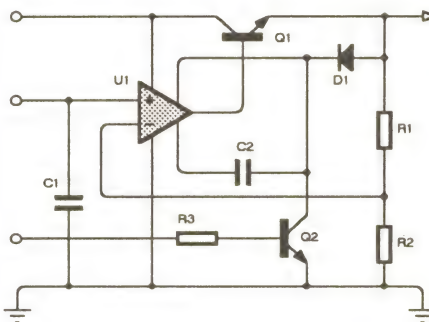

From
£99

Running under Windows 3.1, ISIS ILLUSTRATOR lets you create presentation quality schematic drawings like you see in the magazines. Furthermore, when the drawing is done, transferring it to another document is just a matter of pasting it through the Clipboard.

Now used by a number of prominent technical authors to illustrate their latest books and magazine articles.

labcenter
Electronics



WE HAVE MOVED - NOTE NEW ADDRESS

Call us today on 0756 753440 or fax 0756 752857 for a demo pack - state DOS or Windows. Multi-copy and educational discounts available.

Prices exclude p&p (£5 for U.K.) and VAT. All manufacturers' trademarks acknowledged.

53-55 Main St, Grassington, North Yorks. BD23 5AA.

£1 BARGAIN PACKS - List 1

1,000 items appear in our Bargain Packs List - request one of these when you next order.

- 1 x 12V Stepper Motor. 7.5 degree. Order Ref: 910.
- 1 x 10 pack Screwdrivers. Order Ref: 909.
- 2 x 5 amp Pull Cord Ceiling Switches. Brown. Order Ref: 921.
- 5 x reels Insulation Tape. Order Ref: 911.
- 4 x 14mm Bull-races. Order Ref: 912.
- 2 x Cord Grip Switch Lamp Holders. Order Ref: 913.
- 1 x DC Voltage Reducer. 12V-6V. Order Ref: 916.
- 1 x 10 amp 40V Bridge Rectifier. Order Ref: 889.
- Lightweight Stereo Headphones. Moving coil so superior sound. Order Ref: 896.
- 2 x 25W Crossovers. For 4ohm loudspeakers. Order Ref: 22.
- 2 x NiCad Constant Current Chargers. Easily adaptable to charge almost any NiCad battery. Order Ref: 30.
- 18V-0-18V 10VA mains transformer. Order Ref: 813.
- 2 x White Plastic Boxes. With lids, approx. 3" cube. Lid has square hole through the centre so these are ideal for light operated switch. Order Ref: 132.
- 2 x Reed Relay Kits. You get 8 reed switches and 2 coil sets. Order Ref: 148.
- 12V-0-12V 6VA mains transformer, p.c.b. mounting. Order Ref: 938.
- 1 x Big Pull Solenoid. Mains operated. Has 1/2" pull. Order Ref: 871.
- 1 x Big Push Solenoid. Mains operated. Has 1/2" push. Order Ref: 872.
- 1 x Mini Mono Amp. 3W into 4 ohm speaker or 1W into 8 ohm. Order Ref: 495.
- 1 x Mini Stereo 1W Amp. Order Ref: 870.
- 15V DC 150mA p.s.u., nicely cased. Order Ref: 942.
- 1 x In-Flight Stereo Unit is a stereo amp. Has two most useful mini moving coil speakers. Made for BOAC passengers. Order Ref: 29.
- 1 x 0-1mA Panel Meter. Full vision fact 70mm square. Scaled 0-100. Order Ref: 756.
- 2 x Lithium Batteries. 2.5V penlight size. Order Ref: 874.
- 2 x 3m Telephone Leads. With BT flat plug. Ideal for 'phone extensions, fax, etc. Order Ref: 552.
- 1 x 12V Solenoid. Has good 1/2" pull or could push if modified. Order Ref: 232.
- 4 x In-Flex Switches. With neon on/off lights, saves leaving things switched on. Order Ref: 7.
- 2 x 6V 1A Mains Transformers. Upright mounting with fixing clamps. Order Ref: 9.
- 2 x Humidity Switches. As the air becomes damper, the membrane stretches and operates a micro switch. Order Ref: 32.
- 5 x 13A Rocker Switch. Three tags so on/off, or changeover with centre off. Order Ref: 42.
- Mini Cassette Motor. 9V. Order Ref: 944.
- 1 x Suck or Blow-Operated Pressure Switch. Or it can be operated by any low pressure variation such as water level in tanks. Order Ref: 67.
- 1 x 6V 750mA Power Supply. Nicely cased with mains input and 6V output lead. Order Ref: 103A.
- 2 x Stripper Boards. Each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers, etc. Order Ref: 120.
- 12 Very Fine Drills. For PCB boards etc. Normal cost about 80p each. Order Ref: 128.
- 5 x Motors for Model Aeroplanes. Spin to start so needs no switch. Order Ref: 134.
- 6 x Microphone Inserts. Magnetic 400 ohm, also act as speakers. Order Ref: 139.
- 6 x Neon Indicators. In panel mounting holders with lens. Order Ref: 180.
- 1 x In-Flex Solderstat. Keeps your soldering iron etc always at the ready. Order Ref: 196.
- 1 x Mains Solenoid. Very Powerful as 1/2" pull, or could push if modified. Order Ref: 199.
- 1 x Electric Clock. Mains operated. Put this in a box and you need never be late. Order Ref: 211.
- 4 x 12V Alarms. Makes a noise about as loud as a car horn. All brand new. Order Ref: 221.
- 2 x (6" x 4") Speakers. 16 ohm 5 watts, so can be joined in parallel to make a high wattage column. Order Ref: 243.
- 1 x Panostat. Controls output of boiling ring from simmer up to boil. Order Ref: 252.
- 2 x Oblong Push Switches. For bell or chimes, these can switch mains up to 5A so could be foot switch if fitted in pattrass. Order Ref: 263.
- 50 x Mixed Silicon Diodes. Order Ref: 293.
- 1 x 6 Digit Mains Operated Counter. Standard size but counts in even numbers. Order Ref: 28.
- 2 x 6V Operated Reed Relays. One normally on, other normally closed. Order Ref: 48.
- 1 x Cabinet Lock. With two keys. Order Ref: 55.
- 6 1/2 8 1/2 5 Watt Speaker. Order Ref: 824.
- 1 x Shaded Pole Mains Motor. 3/4" stack, so quite powerful. Order Ref: 85.
- 2 x 5 Aluminium Fan Blades. Could be fitted to the above motor. Order Ref: 86.
- 1 x Case, 3 1/2 x 2 1/4 x 1 1/4 with 13A socket pins. Order Ref: 845.
- 2 x Cases. 2 1/2 x 2 1/4 x 1 1/4 with 13A pins. Order Ref: 565.
- 4 x Luminous Rocker Switches. 10A mains. Order Ref: 793.
- 4 x Different Standard V3 Micro Switches. Order Ref: 340.
- 4 x Different Sub Min Micro Switches. Order Ref: 313.

BARGAINS GALORE

MULTI TESTER. 19 range, ex-British Telecom, reconditioned. These measure AC and DC volts, DC milliamps and have 3 resistance ranges made to BT specification and 20,000 opv movement. Complete with test prods, £8.50, Order Ref: 8.5P3. Carrying case with handle £2 extra.

FIELD TELEPHONES. Ex-GPO, reconditioned, just join together with almost any length twin wire, £15 each, Order Ref: 15P62.

HEAVY DUTY TIME SWITCH (Smiths). Will switch on up to 100A, ex-electricity board, reconditioned, £10, Order Ref: 10P14.

TIME ON SWITCH. Can be set anywhere from 0 to 90 mins. with calibrated knobs, £2, Order Ref: 2P158.

FLASHING BEACON. Ideal for putting on a van, a tractor or any vehicle that should always be seen. Uses a XENON tube and has an amber coloured dome. Separate fixing base is included so unit can be put away if desirable. Price £10, Order Ref: 10P123.

1/2rd HORSE POWER 12V MOTOR (Sinclair C5) £29.50, Order Ref: 29.5P1.

SPEED CONTROLLER Suitable for the C5 or other DC 12V motor. Complete kit £18, Order Ref: 18P8, already made £29.50, Order Ref: 29.5P2.

LEAD LAMP. Ideal for motorists, normal handgrip and hanging hook, takes 60W bulb protected by glass cover, £4, Order Ref: 4P31.

POWER UNIT. Ideal model controller. Mains operated, totally enclosed so safe. Control arm reverses the polarity and varies the voltage from 6V to 8V to 10V to 12V DC. Price £2, Order Ref: 2P3.

WATERPROOF HEATING WIRE. Nicrome element surrounded by PVC casing. Ideal for putting around pipes to stop them freezing. 15m, the right length for mains working, £5, Order Ref: 15P109.

ULTRASONIC CAR OR HOUSE ALARM. Operates from its own battery, nicely cased, is reasonably loud and can be coupled to external horn, £10, Order Ref: 10P76.

CLOCK MODULE. 2" LCD display, requires 1.5V battery, goes back to zero when switched off so ideal for timing operations, £2, Order Ref: 2P307.

QUARTZ CLOCK MECHANISMS. Complete with 2 sets of hands, modern or period, made up ready to work, £3, Order Ref: 3P111.

12V-6V REDUCER. Plugs into car socket to work radio, etc, £2, Order Ref: 2P318.

DIMMER REPLACEMENT FOR WALL SWITCH up to 250W, £2.50, Order Ref: 2.5P9. Coloured so please state colour required.

MAINS AXIAL FAN. Approximately 4x4, top quality German make (PAPST) £8, Order Ref: 8P35.

MINI BLOW HEATER. 1kW, ideal under desk, etc, but needs simple case, £5, Order Ref: 5P23.

ANOTHER 12V-0V-12V TRANSFORMER is a 50VA and is suitable for dropping through the chassis or as it is fitted with 4 pillars it can be mounted above the chassis. Also should you want a 12V 4A transformer, then this one should be quite suitable, you use just one half of the secondary. Price £3.50, Order Ref: 3.5P7.

0-2A PANEL METER. Circular, approximately 1 1/2" diameter, ideal for battery charger, or for variable voltage instrument, only £2, Order Ref: 366.

POWER CONTROLLER. 0 to 250W, serve as a light dimmer, very simply mounted through circular hexagonal nut, £2, Order Ref: 2P362.

SHARP DISK DRIVE. Made to work with the Sharp computer M2700 or M2800. Price £20, Order Ref: 20P25.

PHONE LEADS. 3M long with the standard flat BT plug one end. We've got a lot of these and we want to clear them so are offering 20 leads for £5, Order Ref: 5P246.

0V-20V DC PANEL METER. This is a nice size 65mm sq. It is ideal if you are making a voltage variable instrument or battery charger. Price £3, Order Ref: 3P188.

COAL EFFECT HEATER. This is a blow heater with switch control alongside, made to look like a coal fire. It has a fibreglass cover with a light underneath (but it doesn't smoke!) It's on curved iron legs, is free standing and comes complete with flex, ready to go. It looks quite effective, is very efficient and can easily be moved from room to room. Two heat settings, price £12.99, plus £5 special packing, Order Ref: 13P2.

LOCAL HEATING. Where it is impossible to heat the whole building, consider using quartz glass elements. These are 115V 360W so you would have to use 2 in series which would give you 720W or 4 to give you twice that heat. You could incorporate a simple switch to cut it down on the not so cold days. You can have these quartz elements at a bargain price of 2 for £1, Order Ref: 907.

INSULATION TESTER WITH MULTIMETER. Internally generates voltages which enables you to read insulation directly in megohms. The multimeter has four ranges, AC/DC volts, 3 ranges milliamperes, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50, yours for only £7.50 with leads, carrying case £2 extra, Order Ref: 7.5P4.

The same meter but slightly faulty, will not operate on all ranges, probably repairable. We supply diagram, £3, Order Ref: 3P176.

TOUCH DIMMERS. 40W-250W, no knob to turn, just finger on front plate, will give more, or less light, or off. Silver plated on white background, right size to replace normal switch, £5, Order Ref: 5P230.

LCD 3 1/2 DIGIT PANEL METER. This is a multi-range voltmeter/ammeter using the A-D converter chip 7106 to provide 5 ranges each of volts and amps. Supplied with full data sheet. Special snip price of £12, Order Ref: 12P19.

2MW LASER. Helium neon by Philips, full spec, £30, Order Ref: 30P1. Power supply for this in kit form with case is £15, Order Ref: 15P16, or in larger case to house tube as well, £18, Order Ref: 18P2. The larger unit, made up, tested and ready to use, complete with laser tube, £69, Order Ref: 69P1.

PHILIPS 9" HIGH RESOLUTION MONITOR. Black and white in metal frame for easy mounting. Brand new, still in maker's packing, offered at less than price of tube alone, only £15, Order Ref: 15P1.

15W 8 OHM 8" SPEAKER & 3" TWEETER. Made for a discontinued high quality music centre, gives real hi-fi and only £4 per pair, Order Ref: 4P57.

£1 BARGAIN PACKS - List 2

This is the £1 Bargain Packs List 2 - watch out for lists 3 and 4 next month.

- 3 x Battery Model Motors, tiny, medium and large, Order Ref: 35.
- 2 x Tuning Capacitors for medium wave radios, Order Ref: 36.
- Miniature 12V Relay with low current consuming coil, 2 x 3A changeover contacts, Order Ref: 51.
- 2 x Ferrite Slab Aerials with medium wave coils. Ideal for building small radio, Order Ref: 61.
- 2 x 25W 8 OHM Variable Resistors. Ideal for loudspeaker volume control, Order Ref: 69.
- 2 x Wirewound Variable Resistors in any of the following values, 18, 35, 50, 100 ohms, your choice, Order Ref: 71.
- 4 x 30A Procelain Fuse Holders. Make your own fuse board, Order Ref: 82.
- 2 x 6 1/2" Metal Fan Blades for 5/16" shaft, Order Ref: 86/6 1/2.
- Mains Motor to suit the 6 1/2" blades, Order Ref: 88.
- 1 x 4.5V 150mA DC Power Supply. Fully enclosed so quite safe, Order Ref: 104.
- 10 each red and black small size Crocodile Clips, Order Ref: 116.
- 15m Twin Wire, screened, Order Ref: 122A.
- 100 Plastic Headed Cable Clips, nail in type, several sizes, Order Ref: 123.
- 4 x MES Batten Holders, Order Ref: 126.
- Complete Pocket Size MW Radio, believed OK but not tested, Order Ref: 133R.
- 4 x 2 Circuit Micro Switches (Licon) Order Ref: 157.
- 1 x 13A Switch Socket, quite standard but coloured, Order Ref: 164.
- 1 x 30A Panel Mounting Toggle Switch, double-pole, Order Ref: 166.
- 2 x Neon Numicator Tubes, Order Ref: 170.
- 100 x 3/8 Rubber Grommets, Order Ref: 181.
- 6 x BC Lamp Holder Adaptors, Order Ref: 191.
- 8 x Superior Type Push Switches. Make your own key-board, Order Ref: 201.
- Mains Transformer 8V-0V-8V 1/4A, Order Ref: 212.
- 2 x Sub Min Toggle Switches, Order Ref: 214.
- High Power 3" Speaker (11W 8ohm) Order Ref: 246.
- Medium Wave Permeability Tuner. Its almost a complete radio with circuit, Order Ref: 247.
- 6 x Screwdown Terminals with through panel insulators, Order Ref: 264.
- LCD Clock Display, 1/2" figures, Order Ref: 329.
- 10 x Push-On Long Shafted Knobs for 1/4" spindle, Order Ref: 339.
- 2 x ex-GPO Speaker Inserts, ref 4T, Order Ref: 352.
- 100 x Sub Min 1F Transformers. Just right if you want coil formers, Order Ref: 360.
- 1 x 24V 200mA PSU, Order Ref: 393.
- 1 x Heating Element, mains voltage 100W, brass encased, Order Ref: 8.
- 1 x Mains Interference Suppressor, Order Ref: 21.
- 3 x Rocker Switches, 13A mains voltage, Order Ref: 41.
- 1 x Mini Uni-Selector with diagram for electronic jig-saw, Order Ref: 56.
- 2 x Appliance Thermostats, adjustable up to 15A, Order Ref: 65.
- 1 x Mains Motor with gearbox giving 1 rev per 24 hrs, Order Ref: 89.
- 10 x Round Pointer Knobs for flatted 1/4" spindles, Order Ref: 295.
- 1 x Ceramic Wave Change Switch, 12-pole, 3-way with 1/4" spindle, Order Ref: 303.
- 1 x Tubular Hand Mike, suits cassette recorders, etc. Order Ref: 305.
- 2 x Plastic Stethosets, take crystal or magnetic inserts, Order Ref: 331.
- 20 x Pre-set Resistors, various types and values, Order Ref: 332.
- 6 x Car Type Rocker Switches, assorted, Order Ref: 333.
- 10 x Long Shafted Knobs for 1/4" flatted spindles, Order Ref: 339.
- 1 x Reversing Switch, 20A double-pole or 40A single-pole, Order Ref: 343.
- 4 x Skirted Control Knobs, engraved 0-10, Order Ref: 355.
- 3 x Luminous Rocker Switches, Order Ref: 373.
- 1 x 1000W Tubular Heating Elements with terminal ends, Order Ref: 376.
- 1 x Mains Transformer Operated NiCad Charger, cased with leads, Order Ref: 385.
- 2 x Clockwork Motors, run for one hour, Order Ref: 389.

Prices include VAT. Send cheque/postal order or ring and quote credit card number.
Add £3 post and packing.
Orders over £25 post free.

M & B ELECTRICAL SUPPLIES LTD

Pilgrim Works (Dept. E.E.)
Stairbridge Lane,
Sussex RH17 5PA

Telephone: 0444 881965

(Also fax but phone first)

Callers to 12 Boundary Road,
Hove, Sussex.

DIRECT BOOK SERVICE

The books listed have been selected by *Everyday with Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page. For another selection of books see next month's issue.

ELECTRONIC PROJECTS - BOOK 1

Published by *Everyday Electronics* in association with *Magenta Electronics*.

Contains twenty of the best projects from previous issues of EE each backed with a kit of components. The projects are: Seashell Sea Synthesiser, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three Channel Sound to Light, BBC 16K Sideways Ram, Simple Short Wave Radio, Insulation Tester, Stepper Motor interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser Isolator, Bat Detector, Acoustic Probe, Mains Tester and Fuse Finder, Light Rider - (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.

128 pages (A4 size) **Order code EP1 £2.45**

ELECTRONICS TEACH-IN 88/89 - INTRODUCING MICROPROCESSORS

Mike Tooley BA (published by *Everyday Electronics*)

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc. Starting with basic terminology, integrated circuits, logic families and numbering systems the text builds in stages, with revision and assessments built in, up to programming, languages, flow charts, etc. The course is ideal for the newcomer to the subject.

80 pages (A4 size) **Order code TI-88/89 £2.45**

Special Everyday Electronics Books

ELECTRONICS TEACH-IN No.5 GUIDE TO BUILDING ELECTRONIC PROJECTS

Published by *EVERYDAY ELECTRONICS*

Due to the demand from students, teachers and hobbyists we have put together a range of articles from past issues of *Everyday Electronics* that will assist those involved with the construction of electronic projects.

The book contains the complete *Project Development* for GCSE series.

Contents: Features - First Steps in Project Building; Building with Vero; Project Development for GCSE; Getting your Project Working; Guide to Printed Circuit Boards; Choosing and Using Test Equipment - The Multimeter, The Oscilloscope, P.S.U.s, Logic Probes, Digital Frequency Meters, Signal Generators, etc; **Data** - Circuit Symbols; Component Codes; Resistors; Identifying Components; Capacitors; Actually Doing It - Understanding the Circuit Diagram, Component Codes, Mounting circuit boards and controls, Understanding Capacitors; **Projects** - Lie Detector; Personal Stereo Amplifier; Digital Experiments Unit; Quizmaster; Siren Effects Unit; UV Exposure Unit; Low-cost Capacitance Meter; Personal Radio.

88 pages (A4 size) **Order code TI5 £2.95**

ELECTRONICS TEACH-IN No. 6 DESIGN YOUR OWN CIRCUITS

(Published by *Everyday with Practical Electronics*)

Mike Tooley B.A.

This book is designed for the beginner and experienced reader alike, and aims to dispell some of the mystique associated with the design of electronic circuits. It shows how even the relative newcomer to electronics can, with the right approach, design and realise quite complex circuits.

Fourteen individual p.c.b. modules are described which, with various detailed modifications, should allow anyone to design and construct a very wide range of different projects. Nine "hands-on" complete DIY projects have also been included so readers can follow the thinking behind design, assembly, construction, testing and evaluation, together with suggested "mods" to meet individual needs. The practical projects have each been designed to stand on their own as complete items of equipment. P.C.B.s for all the modules and projects are available by mail order.

The subjects covered in each chapter of the book are: Introduction and Power Supplies; Small Signal Amplifiers; Power Amplifiers; Oscillators; Logic Circuits; Timers; Radio; Power Control; Optoelectronics.

The nine complete constructional projects are: Versatile Bench Power Supply; Simple Intercom; Bench Amplifier/Signal Tracer; Waveform Generator; Electronic Die; Pulse Generator; Radio Receiver; Disco Lights Controller; Optical Communications Link.

136 pages **Order code TI6 £3.45**

TEACH-IN No. 7. Plus Free Software ANALOGUE AND DIGITAL ELECTRONICS COURSE

(Published by *Everyday with Practical Electronics*)


Alan Winstanley and Keith Dye B.Eng(Tech)AMIEE

The highly acclaimed *Teach-In '92* series, which included the construction and use of the *Mini Lab* and *Micro Lab* test and development units, has been put together in book form. Additionally EPT Educational Software have developed a GCSE Electronics software program to complement the course and a FREE DISC covering the first two parts of the course is included with the book.

An interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles.

If you are taking electronics or technology at school or college, this book is for you. If you just want to learn the basics of electronics then this book is for you. If you are teaching electronics or technology you must make sure you see it. *Teach-In No. 7* will be invaluable if you are considering a career in electronics or even if you are already training in one. The *Mini Lab* and software enable the construction and testing of both demonstration and development circuits. These learning aids bring electronics to life in an enjoyable and interesting way; you will both see and hear the electron in action! The *Micro Lab* microprocessor add-on system will appeal to higher level students and those developing microprocessor projects.

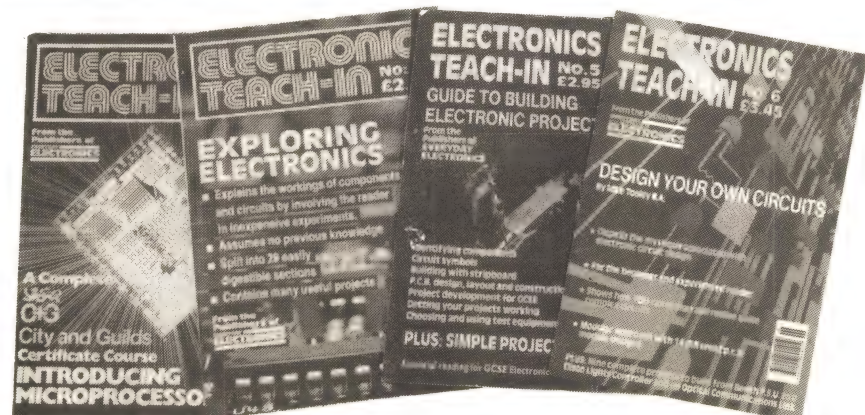160 pages (A4 size) **Order code TI7 £3.95**



Computers and Computing

HOW TO CHOOSE A SMALL BUSINESS COMPUTER SYSTEM

D. Weale

This book is for anyone intending to buy an IBM compatible computer system, whether it is their first system or a replacement. There are sections on hardware, application and systems programs and how to actually make your choice as well as sections on the law, ergonomics and a glossary of common terms.

The text contains many useful tips and some warnings (which could save much effort and expense).

114 pages **Order code BP323 £4.95**

UNDERSTANDING PC SPECIFICATIONS

R. A. Penfold

If you require a microcomputer for business applications, or a high quality home computer, an IBM PC or compatible is often the obvious choice. They are competitively priced, and are backed up by an enormous range of applications programs, hardware add-ons, etc. The main difficulty for the uninitiated is deciding on the specification that will best suit his or her needs. PCs range from simple systems of limited capabilities up to complex systems that can happily run applications that would have been considered beyond the abilities of a microcomputer not so long ago. It would be very easy to choose a PC system that is inadequate to run your applications efficiently, or one which goes beyond your needs and consequently represents poor value for money.

This book explains PC specifications in detail, and the subjects covered include the following: Differences between types of PC (XT, AT, 80386, etc); Maths co-processors; Input devices (keyboards, mice, and digitisers); Memory, including both expanded (EMS) and extended RAM; RAM disks and disk caches; Floppy disk drive formats and compatibility; Hard disk drives (including interleaved factors and access times); Display adaptors, including all standard PC types (CGA, Hercules, Super VGA, etc); Contains everything you need to know if you can't tell your EMS from your EGA!

104 pages **Order code BP282 £4.95**

AN INTRODUCTION TO 68000 ASSEMBLY LANGUAGE

R. A. & J. W. Penfold

Obtain a vast increase in running speed by writing programs for 68000 based micros such as the Commodore Amiga, Atari ST range or Apple Macintosh range etc., in assembly language. It is not as difficult as one might think and this book covers the fundamentals.

112 pages **Order code BP184 £2.95**

MULTIMEDIA ON THE PC

Ian R. Sinclair

In this book, you'll find out what a CD ROM is, how it works, and why it is such a perfect add-on for a PC, allowing you to buy programmes, text, graphics and sound on a CD. It also describes the installation of a CD ROM drive and a sound card, pointing out the common problems that arise, and then shows how to use them to create a complete multimedia presentation that contains text, photos, a soundtrack with your own voice recorded as a commentary, even animation and edited video footage.

184 pages **Order code PC112 £11.95**

A CONCISE INTRODUCTION TO MS-DOS

N. Kantaris

This guide is written with the non-expert, busy person in mind and, as such, it has an underlying structure based on "what you need to know first, appears first". Nonetheless, the guide is also designed to be circular, which means that you don't have to start at the beginning and go to the end. The more experienced user can start from any section.

The guide covers versions 3.0, 3.1 and 3.2 of both PC-DOS and MS-DOS as implemented by IBM and other manufacturers of "compatible" microcomputers.

64 pages **Order code BP232 £2.95**

MAKING MS-DOS WORK FOR YOU (covers version 6.2)

N. Kantaris & P. R. M. Oliver

This book was written with the busy person in mind and, as such, it has an underlying structure based on "what you need to know first, appears first". Nonetheless, the

book has also been designed to be circular, which means that you don't have to start at the beginning and go to the end.

The book explains: How to write customised batch files which allow you to display what you want on your screen, and in the form and order you want it, instead of being forced to use the DOS prompt on a blank screen. How to design and set up a fast interactive and professional looking menu system, so that you or anyone else can run utility applications or commercial software packages easily. How the ANSI.SYS display and keyboard commands can be used to position the cursor on any part of the screen, change the intensity of the displayed characters or change their colour. How the Edit screen editor or the Edlin line editor can be used to enter ESCAPE (ANSI.SYS) commands into simple ASCII files to allow control of both your screen display and your printer. How to control the operation of the two main types of printers in use today, Epson compatible dot matrix and HP compatible laser printers. How to use several useful routines, such as moving and finding files, protecting files from accidental erasure, a simplified backup process, a screen saver, and a disc cataloguing system.

The Debug program and how it can be used to create, see and change the contents of any file, including those of programs written in assembler code. This includes how to find your way around the names and tasks of the CPU registers and the meaning of some simple assembler mnemonics.

182 pages **Order code BP319 £4.95**

AN INTRODUCTION TO CP/M

R. A. Penfold

In order to run and use programs operating under CP/M it is not essential to have an understanding of the system, but a reasonable knowledge of the subject can certainly be of immense help when minor problems occur, and also in fully exploiting the possible potential of the system. This book tells the story!

84 pages **Order code BP183 £2.95**

Audio and Music

ACOUSTIC FEEDBACK – HOW TO AVOID IT

Feedback is the bane of all public address systems. While feedback cannot be completely eliminated, many things can be done to reduce it to a level at which it is no longer a problem.

Much of the trouble is often the hall itself, not the equipment, but there is a simple and practical way of greatly improving acoustics. Some microphones are prone to feedback while others are not. Certain loudspeaker systems are much better than others, and the way the units are positioned can produce or reduce feedback. All these matters are fully explored as well as electronic aids such as equalizers, frequency-shifters and notch filters.

The special requirements of live group concerts are considered, and also the related problem of instability that is sometimes encountered with large set-ups. We even take a look at some unsuccessful attempts to cure feedback so as to save readers wasted time and effort duplicating them.

Also included is the circuit and layout of an inexpensive but highly successful twin-notch filter, and how to operate it. 92 pages **Order code BP310 £3.95**

PRACTICAL MIDI HANDBOOK

R. A. Penfold

The Musical Instrument Digital Interface (MIDI) is surrounded by a great deal of misunderstanding, and many of the user manuals that accompany MIDI equipment are quite incomprehensible to the reader.

The Practical MIDI Handbook is aimed primarily at musicians, enthusiasts and technicians who want to exploit the vast capabilities of MIDI, but who have no previous knowledge of electronics or computing. The majority of the book is devoted to an explanation of what MIDI can do and how to exploit it to the full, with practical advice on connecting up a MIDI system and getting it to work, as well as deciphering the technical information in those manuals. 128 pages **Order code PC101 £6.95**

PREAMPLIFIER AND FILTER CIRCUITS

R. A. Penfold

This book provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases).

The preamplifier circuits featured include:- Microphone preamplifiers (low impedance, high impedance, and crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier (for use with compact cassette systems).

Other circuits include:- Audio limiter to prevent overloading of power amplifiers. Passive tone controls. Active tone controls. PA filters (highpass and lowpass). Scratch and rumble filters. Loudness filter. Audio mixers. Volume and balance controls. 92 pages **Order code BP309 £3.95**

AN INTRODUCTION TO LOUDSPEAKERS AND ENCLOSURE DESIGN

V. Capel

This book explores the various features, good points and snags of speaker designs. It examines the whys and wherefores so that the reader can understand the principles involved and so make an informed choice of design, or even design loudspeaker enclosures for him or herself. Crossover units are also explained, the various types, how they work, the distortions they produce and how to avoid them. Finally there is a step-by-step description of the construction of the Kapellmeister loudspeaker enclosure. 148 pages **Order code BP256 £2.95**

COMPUTERS AND MUSIC – AN INTRODUCTION

R. A. Penfold

Computers are playing an increasingly important part in the world of music, and the days when computerised music was strictly for the fanatical few are long gone.

If you are more used to the black and white keys of a synth keyboard than the QWERTY keyboard of a computer, you may be understandably confused by the jargon and terminology bandied about by computer buffs. But fear not, setting up and using a computer-based music making system is not as difficult as you might think.

This book will help you learn the basics of computing, running applications programs, wiring up a MIDI system and using the system to good effect, in fact just about everything you need to know about hardware and the programs, with no previous knowledge of computing needed or assumed. This book will help you to choose the right components for a system to suit your personal needs, and equip you to exploit that system fully. 174 pages **Order code PC107 £8.95**

ELECTRONIC PROJECTS FOR GUITAR

R. A. Penfold

This book contains a collection of guitar effects and some general purpose effects units, many of which are suitable for beginners to project building. An introductory chapter gives guidance on construction.

Each project has an introduction, an explanation of how it works, a circuit diagram, complete instructions on strip-board layout and assembly, as well as notes on setting up and using the units. Contents include: Guitar tuner; Guitar preamplifier; Guitar headphone amplifier; Soft distortion unit; Compressor; Envelope waa waa; Phaser; Dual tracking effects unit; Noise gate/expander; Treble booster; Dynamic treble booster; Envelope modifier; Tremolo unit; DI box. 110 pages **Order code PC110 £8.95**

HIGH POWER AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold

Practical constructional details of how to build a number of audio power amplifiers ranging from about 50 to 300/400 watts r.m.s. Includes MOSFET and bipolar transistor designs. 96 pages **Order code BP277 £3.95**

Theory and Reference

ELECTRONIC HOBBYISTS HANDBOOK

R. A. Penfold

Provides an inexpensive single source of easily located information that the amateur electronics enthusiast is likely to need for the day-to-day pursuance of this fascinating hobby. Covers common component colour codes. Details the characteristics and pinouts of many popular semiconductor devices, including various types of logic ICs, operational amplifiers, transistors, FETs, unijunctions, diodes, rectifiers, SCRs, diacs, triacs, regulators and SMDs, etc. Illustrates many useful types of circuits, such as timers and oscillators, audio amplifiers and filters, as well as including a separate section on power supplies. Also contains a multitude of other useful data. 88 pages **Order code BP233 £4.95**

FROM ATOMS TO AMPERES

F. A. Wilson

Explains in crystal clear terms the absolute fundamentals behind electricity and electronics. Really helps you to discover and understand the subject, perhaps for the first time ever.

Have you ever: Wondered about the true link between electricity and magnetism? Felt you could never understand the work of Einstein, Newton, Boltzmann, Planck and other early scientists? Just accepted that an electron is like a little black ball? Got mixed up with e.m.f. and p.d.? Thought the idea of holes in semiconductors is a bit much?

Then help is at hand with this inexpensive book, in as simple a way as possible and without too much complex mathematics and formulae. 244 pages **Temporarily out of print**

ELECTRONICS – A "MADE SIMPLE" BOOK

G. H. Olsen

This book provides excellent background reading for our *Introducing Digital Electronics Teach-In* Book and will be of interest to everyone studying electronics. The subject is simply explained and well illustrated and the book assumes only a very basic knowledge of electricity. 330 pages **Order code NE10 £6.95**

A REFERENCE GUIDE TO PRACTICAL ELECTRONICS TERMS

F. A. Wilson

Electronic devices surround us on all sides and their numbers are increasing without mercy. Ours is the problem therefore in keeping up with this relentless expansion. Unfortunately we cannot know it all and most

of us do not wish to afford the cost of large reference books which explain many concepts in fair detail. Here is an answer, an inexpensive reference guide which explains briefly (but we hope, well) many of the underlying electronics features of practical devices, most of which, to a certain extent, control our lives.

This book is in effect more than just a dictionary of practical electronics terms, it goes a stage further in also getting down to fundamentals. Accordingly the number of terms may be limited but the explanations of the many which are included are designed to leave the reader more competent and satisfied – and this is without the use of complicated mathematics which often on first reading can even be confusing.

For those who also wish to get right down to the root of the matter, there is a second volume entitled *A Reference Guide to Basic Electronics Terms* (BP286), each of the books referring to its companion as necessary.

A reference guide for practically everybody concerned with electronics. 432 pages **Order code BP287 £5.95**

NEWNES ELECTRONICS POCKET BOOK

E. A. Parr

Newnes Electronics Pocket Book has been in print for over twenty years and has covered the development of electronics from valve to semiconductor technology and from transistors to LSI integrated circuits and microprocessors. To keep up to date with the rapidly changing world of electronics, continuous revision has been necessary. This new Fifth Edition takes account of recent changes and includes material suggested by readers of previous editions. New descriptions of op.amp. applications and the design of digital circuits have been added, along with a totally new chapter on computing, plus other revisions throughout. 315 pages (hard cover) **Order code NE02 £12.95**

ELECTRONIC MODULES AND SYSTEMS FOR BEGINNERS

Owen Bishop

This book describes over 60 modular electronic circuits – how they work, how to build them, and how to use them. The modules may be wired together to make hundreds of different electronic systems, both analogue and digital. To show the reader how to begin building systems from modules, a selection of over 25 electronic systems are described in detail, covering such widely differing applications as timing, home security, measurement, audio (including a simple radio receiver), games and remote control. 200 pages **Order code BP266 £3.95**

Project Building

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING


R. A. Penfold

We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects. 96 pages **Order code BP110 £2.95**

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold

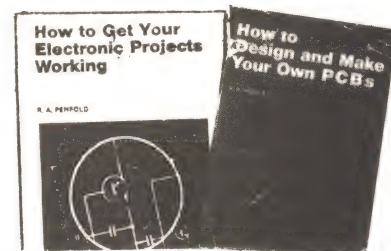Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s. 80 pages **Order code BP121 £2.50**



A BEGINNERS GUIDE TO MODERN ELECTRONIC COMPONENTS

R. A. Penfold

The purpose of this book is to provide practical information to help the reader sort out the bewildering array of components currently on offer. An advanced knowledge of the theory of electronics is not needed, and this book is not intended to be a course in electronics theory. The main aim is to explain the differences between components of the same basic type (e.g. carbon, carbon film, metal film, and wire-wound resistors) so that the right component for a given application can be selected. A wide range of components are included, with the emphasis firmly on those components that are used a great deal in projects for the home constructor. 166 pages **Order code BP285 £3.95**

BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS

R. A. Penfold

Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also include examples in the form of simple projects. 112 pages **Order code 227 £1.95**

ELECTRONICS SIMPLIFIED – CRYSTAL SET CONSTRUCTION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M. Especially written for those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. It is designed for all ages upwards from the day one can read intelligently and handle simple tools. 80 pages **Order code BP92 £1.75**

GUIDE TO BUILDING ELECTRONIC PROJECTS


Published by *Everyday Electronics*

See the first page of books – *ELECTRONICS TEACH-IN* No.5 – for full details.

ELECTRONICS PROJECT BOOK

Published by *Everyday Electronics* in association with *Magenta Electronics*.

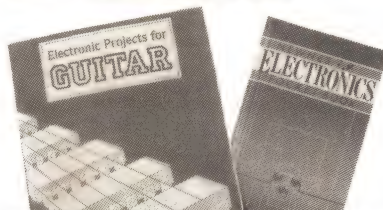See the first page of books for full details.



Testing and Test Gear

HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT

R. A. Penfold

This book explains the basic function of an oscilloscope, gives a detailed explanation of all the standard controls, and provides advice on buying. A separate chapter deals with using an oscilloscope for fault finding on linear and logic circuits. plenty of example waveforms help to illustrate the control functions and the effects of various fault conditions. The function and use of various other pieces of test equipment are also covered, including signal generators, logic probes, logic pulsers, and crystal calibrators. 104 pages **Order code BP267 £3.50**

Circuits and Design

PRACTICAL ELECTRONIC FILTERS

Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

88 pages **Order code BP299** £4.95

ELECTRONIC ALARM CIRCUITS MANUAL

R. M. Marston

One hundred and forty useful alarm circuits, of a variety of types, are shown in this volume. The operating principle of each one is explained in concise but comprehensive terms, and brief construction notes are given where necessary.

Aimed at the practical design engineer, technician and experimenter, as well as the electronics student and amateur.

124 pages **Order code NE11** £13.95

DIGITAL LOGIC GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages **Order code PC106** £8.95

ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS

Robert Penfold

Robots and robotics offer one of the most interesting areas for the electronics hobbyist to experiment in. Today the mechanical side of robots is not too difficult, as there are robotics kit and a wide range of mechanical components available. The micro controller is not too much of a problem either, since the software need not be terribly complex and many inexpensive home computers are well suited to the task.

The main stumbling block for most would-be robot builders is the electronics to interface the computer to the motors, and the sensors which provide feedback from the

robot to the computer. The purpose of this book is to explain and provide some relatively simple electronic circuits which bridge this gap.

92 pages **Order code BP179** £2.95

ELECTRONIC POWER SUPPLY HANDBOOK

Ian R. Sinclair

This book covers the often neglected topic of electronic power supplies. All types of supplies that are used for electronics purposes are covered in detail, starting with cells and batteries and extending by way of rectified supplies and linear stabilisers to modern switch-mode systems, IC switch-mode regulators, DC-DC converters and inverters.

The devices, their operating principles and typical circuits are all dealt with in detail. The action of rectifiers and the reservoir capacitor is emphasised, and the subject of stabilisation is covered. The book includes some useful formulae for assessing the likely hum level of a conventional rectifier reservoir supply.

136 pages **Order code PC108** £7.95

50 SIMPLE LED CIRCUITS

R. N. Soar

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components – the light-emitting diode (LED). Also includes circuits for the 707 common anode display.

64 pages **Order code BP42** £1.95

BOOK 2 50 more l.e.d. circuits **Order code BP87** £1.95

CIRCUIT SOURCE BOOK 1

A. Penfold

Written to help you create and experiment with your own electronic designs by combining and using the various standard "building block" circuits provided. Where applicable, advice on how to alter the circuit parameters is given.

The circuits covered in this book are mainly concerned with analogue signal processing and include: Audio amplifiers (op.amp and bipolar transistors); audio power amplifiers; d.c. amplifiers; highpass, lowpass, bandpass and notch filters; tone controls; voltage controlled amplifiers and filters; triggers and voltage comparators; gates and electronic switching; bargraphs; mixers; phase shifters, current mirrors, hold circuits, etc.

Over 150 circuits are provided, which it is hoped will be useful to all those involved in circuit design and application, be they professionals, students or hobbyists.

182 pages **Order code BP321** £4.95

CIRCUIT SOURCE BOOK 2

R. A. Penfold

This book will help you to create and experiment with your own electronic designs by combining and using the various standard "building blocks" circuits provided. Where applicable, advice on how to alter the circuit parameters is provided.

The circuits covered are mainly concerned with signal generation, power supplies, and digital electronics.

The topics covered in this book include: 555 oscillators; sinewave oscillators; function generators; CMOS oscillators; voltage controlled oscillators; radio frequency oscillators; 555 monostables; CMOS monostables; TTL monostables; precision long timers; power supply and regulator circuits; negative supply generators and voltage boosters; digital dividers, decoders, etc.; counters and display drivers; D/A and A/D converters; opto-isolators, flip/flops, noise generators, tone decoders, etc.

Over 170 circuits are provided, which it is hoped will be useful to all those involved in circuit design and application, be they professionals, students or hobbyists.

192 pages **Order code BP322** £4.95

HOW TO USE OP-AMPS

E. A. Parr

This book has been written as a designer's guide covering many operational amplifiers, serving both as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

160 pages **Order code BP88** £2.95

A BEGINNERS GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in "real world" applications.

142 pages **Order code BP332** £4.95

DIRECT BOOK SERVICE

ORDERING DETAILS

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Add £1 to your total order for postage and packing (overseas readers add £2 for countries in Europe, or add £5 for all countries outside Europe, surface mail postage) and send a PO, cheque, international money order, (£ sterling only) made payable to Direct Book Service or credit card details (including the card expiry date), Visa or Mastercard (Access) – minimum credit card order is £5 – quoting your name and address, the order code and quantities required to DIRECT BOOK SERVICE, 33 GRAVEL HILL, WIMBORNE, DORSET BH21 1RW (mail order only).

Although books, videos and software are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of *Everyday with Practical Electronics*) before ordering from old lists.

Note – our postage charge is the same for one book or one hundred books!

MORE BOOKS NEXT MONTH

Direct Book Service is a division of Wimborne Publishing Ltd

Tel: 0202 881749

Fax: 0202 841692

Radio, TV, Satellite

PROJECTS FOR RADIO AMATEURS AND S.W.L.S.

R. A. Penfold

This book describes a number of electronic circuits, most of which are quite simple, which can be used to enhance the performance of most short wave radio systems.

The circuits covered include: An aerial tuning unit; A simple active aerial; An add-on b.f.o. for portable sets; A wavetrapp for combat signals on spurious responses; An audio notch filter; A parametric equaliser; C.W. and S.S.B. audio filters; Simple noise limiters; A speech processor; A volume expander.

Other useful circuits include a crystal oscillator, and RTTY/C.W. tone decoder, and a RTTY serial to parallel converter. A full range of interesting and useful circuits for short wave enthusiasts.

92 pages **Order code BP304** £3.95

AN INTRODUCTION TO AMATEUR RADIO

I. D. Poole

Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the century.

This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages **Order code BP257** £3.50

SIMPLE SHORT WAVE RECEIVER CONSTRUCTION

R. A. Penfold

Short wave radio is a fascinating hobby, but one that seems to be regarded by many as an expensive pastime these days. In fact it is possible to pursue this hobby for a minimal monetary outlay if you are prepared to undertake a bit of d.i.y., and the receivers described in this book can all be built at low cost. All the sets are easy to construct, full wiring diagrams etc. are provided, and they are suitable for complete beginners. The receivers only require simple aerials, and do not need any complex alignment or other difficult setting up procedures.

The topics covered in this book include: The broadcast bands and their characteristics; The amateur bands and their characteristics; The propagation of radio signals; Simple aerials; Making an earth connection; Short wave crystal set; Simple t.r.f. receivers; Single sideband reception; Direct conversion receiver.

Contains everything you need to know in order to get started in this absorbing hobby.

88 pages **Order code BP275** £3.95

AN INTRODUCTION TO AMATEUR COMMUNICATIONS SATELLITES

A. Pickford

Communications and broadcast satellites are normally inaccessible to individuals unless they are actively involved in their technicalities by working for organisations such as British Telecom, the various space agencies or military bodies, even those who possess a satellite television receiver system do not participate in the technical aspects of these highly technological systems.

There are a large number of amateur communications satellites in orbit around the world, traversing the globe continuously and they can be tracked and their signals received with relatively inexpensive equipment. This equipment can be connected to a home computer such as the BBC Micro or IBM compatible PCs, for the decoding of received signals.

This book describes several currently available systems, their connection to an appropriate computer and how they can be operated with suitable software.

102 pages **Order code BP290** £3.95

AERIAL PROJECTS

R. A. Penfold

The subject of aerials is vast but in this book the author has considered practical aerial designs, including active, loop and ferrite aerials which give good performances and are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.

Also included are constructional details of a number of aerial accessories including a pre-selector, attenuator, filters and tuning unit.

96 pages **Order code BP105** £2.50

INTERNATIONAL RADIO STATIONS GUIDE

P. Shore

Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed to guide him or her around the ever more complex radio bands. This new edition has been completely revised and rewritten and incorporates much more information which is divided into the following sections:

Listening to Short Wave Radio; Choosing a Short Wave Radio Receiver; How to Use the IRSG; Abbreviations; Country Codes; Worldwide Short Wave Radio Stations; European, Middle Eastern and African Long Wave Radio Stations; European, Near and Middle Eastern and African Medium Wave Radio Stations; Canadian Medium Wave Radio Stations; USA Medium Wave Radio Stations; Broadcasts in English; Programmes for DXers and Short Wave Listeners; UK FM Radio Stations; Time Differences From GMT; Wavelength/Frequency Conversion.

226 pages **Order code BP255** £5.95

BABANI BOOKS

We now supply *all* the books published by Bernard Babani (Publishing) Ltd. We have always supplied a selected list of Babani books and you will find many of them described on the previous pages or in next month's issue of *Everyday with Practical Electronics* (all books with a BP prefix to the order code are Babani books).

Many readers have asked us to also supply various other Babani books, which have a reputation for value for money. Our customers tell us they appreciate our speedy service and low postage charge and they

would like to be able to purchase all the books from us and thus keep the postage charge to an absolute minimum (£1.00 for UK p&p no matter how many books you buy). We are pleased to be able to respond; with the aid of Michael Babani (M.D.) we are now able to meet all your requirements for their books. *If it's Babani and in print we can supply it.* Babani presently list over 160 different technical titles those *not* described in detail on the previous *Direct Book Service* pages or in next month's issue are listed below:

Code	Title	Price	Code	Title	Price	Code	Title	Price
BP37	50 Projects using Relays, SCRs and TRIACs	£2.95	BP245	Digital Audio Projects	£2.95	BP303	Understanding PC Software	£4.95
BP39	50 (FET) Field Effect Transistor Projects	£2.95	BP246	Musical Applications of the Atari ST's	£5.95	BP305	Learning CAD with AutoSketch for Windows	£5.95
BP44	IC 555 Projects	£2.95	BP247	More Advanced MIDI Projects	£2.95	BP306	A Concise Introduction to AmiPro 3	£4.95
BP48	Electronic Projects for Beginners	£1.95	BP249	More Advanced Test Equipment Construction	£3.50	BP307	A Concise Introduction to QuarkXPress	£4.95
BP49	Popular Electronic Projects	£2.50	BP250	Programming in FORTRAN 77	£4.95	BP308	A Concise Introduction to Word 5.1 on the Macintosh	£5.95
BP56	Electronic Security Devices	£2.95	BP251	Computer Hobbyists Handbook	£5.95	BP311	An Introduction to Scanners and Scanning	£4.95
BP74	Electronic Music Projects	£2.95	BP258	Learning to Program in C (revised edition)	£4.95	BP312	An Introduction to Microwaves	£3.95
BP76	Power Supply Projects	£2.50	BP259	A Concise Introduction to UNIX	£2.95	BP313	A Concise Introduction to Sage	£3.95
BP78	Practical Computer Experiments	£1.75	BP260	A Concise Introduction to OS/2	£2.95	BP314	A Concise Introduction to Quattro Pro 3.0	£4.95
BP84	Digital IC Projects	£1.95	BP261	A Concise Introduction to Lotus 1-2-3 (revised edition)	£3.95	BP315	An Introduction to the Electromagnetic Wave	£4.95
BP90	Audio Projects	£2.50	BP262	A Concise Introduction to WordPerfect (revised edition)	£3.95	BP320	Electronic Projects for Your PC	£3.95
BP94	Electronic Projects for Cars and Boats	£1.95	BP264	A Concise Advanced User's Guide to MS-DOS (revised edition - covers version 6.2)	£4.95	BP322	Circuits Source Book 2	£4.95
BP95	Model Railway Projects	£2.95	BP269	An Introduction to Desktop Publishing	£5.95	BP324	The Art of Soldering	£3.95
BP122	Audio Amplifier Construction	£2.95	BP272	Interfacing PCs & Compatibles	£3.95	BP326	An Introduction to Satellite Communications	£5.95
BP125	25 Simple Amateur Band Aerials	£1.95	BP273	Practical Electronic Sensors	£4.95	BP327	DOS One Step at a Time (covers version 6.2)	£3.95
BP126	BASIC & PASCAL in Parallel	£1.50	BP274	A Concise Introduction to SuperCalc5	£4.95	BP328	Sage Explained	£5.95
BP132	25 Simple SW Broadcast Band Aerials	£1.95	BP276	Short Wave Superhat Receiver Construction	£2.95	BP330	A Concise User's Guide to Lotus 1-2-3 Release 2.4	£4.95
BP136	25 Simple Indoor and Window Aerials	£1.75	BP280	Getting the Most From Your PC's Hard Disk	£3.95	BP331	A Beginners Guide to MIDI	£4.95
BP144	Further Practical Electronics Calculations & Formulae	£4.95	BP283	A Concise Introduction to SmartWare II	£4.95	BP334	Magic Electronics Projects	£4.95
BP145	25 Simple Tropical and MW Band Aerials	£1.75	BP284	Programming in QuickBASIC	£4.95	BP336	A Concise Users Guide to Lotus1-2-3 Release 3.4	£5.95
BP148	Computer Terminology Explained	£1.95	BP287	A Reference Guide to Basic Electronics Terms	£5.95	BP337	A Concise Users Guide to Lotus1-2-3 for Windows	£5.95
BP171	Easy Add-on Projects for Amstrad CPC 464, 664, 6128 and MSX Computers	£2.95	BP291	A Concise Introduction to Ventura	£3.95	BP338	A Concise Introduction to Word for Windows	£5.95
BP176	A TV-DXers Handbook (revised edition)	£7.95	BP292	Public Address Loudspeaker Systems	£3.95	BP339	A Concise Introduction to WordPerfect 5.2 for Windows	£5.95
BP182	MIDI Projects	£2.95	BP293	An Introduction to Radio Wave Propagation	£3.95	BP343	A Concise Introduction to Microsoft Works for Windows	£5.95
BP190	More Advanced Electronic Security Projects	£2.95	BP294	A Concise Introduction to Microsoft Works (revised edition)	£4.95			
BP192	More Advanced Power Supply Projects	£2.95	BP298	A Concise Introduction to the Mac System & Finder	£3.95			
BP193	LOGO for Beginners	£2.95	BP301	Antennas for VHF and UHF	£4.95			
BP196	BASIC & LOGO in Parallel	£2.95						
BP198	An Introduction to Antenna Theory	£2.95						
BP230	A Concise Introduction to GEM	£2.95						
BP243	BBC BASIC86 on the Amstrad PCs and IBM Compatibles - Book 1: Language	£3.95						
BP244	BBC BASIC86 on the Amstrad PCs and IBM Compatibles - Book 2: Graphics and Disk Files	£3.95						

IF NO PRICE IS SHOWN THE BOOK IS OUT OF PRINT (O.O.P.)
SEE PREVIOUS PAGE FOR FULL ORDERING DETAILS

PCB SERVICE

Printed circuit boards for certain EPE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday with Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF.** Cheques should be crossed and made payable to *Everyday with Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are now held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail.

Back numbers or photostats of articles are available if required - see the Editorial page for details.

Please check price and availability in the latest issue.

Boards can only be supplied on a payment with order basis.

SALE! 1/2 PRICE
All p.c.b.s on THIS page reduced to

(Just send half the price shown, while stocks last.)
PCBs ON OPPOSITE PAGE: PRICES AS SHOWN

PROJECT TITLE	Order Code	Cost
Suntan Timer	AUG'88 610	£3.07
Doorbell Delay	NOV'88 616	£3.56
Sound-to-Light Interface	MAR'89 637	£6.24
Midi Pedal	639	£7.00
Midi Merge	640	£3.00
Audio Lead Tester	641	£5.77
Light Sentinel: Main Board	APR'89 632	£9.20
4-Channel Auto-Fader Interface	642	£6.80
Electronic Spirit Level	AUG'89 649	£3.85
Music on Hold	OCT'89 646	£3.85
Power Supplies - 25V 700mA	656	£4.35
Logo/Lego & Spectrum Interface	NOV'89 664	£5.60
Quick Cap Tester	FEB'90 668	£3.92
Superhet Receiver/Tuner/Amp	MAR'90 679/680	£4.22
Stereo Noise Generator	APR'90 681	£4.24

PROJECT TITLE	Order Code	Cost
Amstrad Speech Synthesiser	MAY'90 689	£4.68
Hand Tally: Main Bd and Display Bd	SEP'90 699/700	£10.95
Ghost Walker	OCT'90 703	£4.32
Frequency Meter	704	£5.25
Spatial Power Display	JAN'91 714	£5.33
Amstrad PCW Sound Generator	715	£5.03
Simple Basic Alarm	MAR'91 731	£4.50
Humidity Tester	APR'91 716	£4.97
Model Train Controller (double-sided)	736	£9.75
Digital LCD Thermostat	MAY'91 740	£4.05
- Control Board	741	£3.76
- Power Relay Board		£5.00
Control and Power Relay Boards together		
Modular Disco Lights - Simple Chaser	JUN'91 745	£5.00
Sweeper Module	746	£5.17
Automatic Light Control - PSU Board	747	£4.88
Logic Board	748	£5.17
Mod. Disco Lights	NOV'91 771	£6.91
Superchaser (Double-sided)	772	£8.26
Supersweep (Double-sided)	773	£5.01
Bicycle Alarm		
Knockerbox	DEC'91 775	£5.35
Signal Generator - Main Board	776	£7.46
Mind Machine - Main Board	778	£7.00
Auto Nightlight	779	£5.03
Mind Machine - Programmer Board	JAN'92 780	£7.39
Transistor Checker	781	£4.63
Stepping Motor Driver/Interface	782	£10.39
Micro-Sense Alarm	783	£5.42
Telesound	FEB'92 784	£4.66
Programmable Timer	785	£4.63
Auto Garage Light	MAR'92 786	£6.10
Versatile BBC Computer Interface	787	£11.59
Economy Seven Timer	788	£5.20
Sonic Continuity Tester	APR'92 789	£4.79
Telephone Ringer	790	£5.46
Experimental Weighing Scale	MAY'92 792	£5.17
12V Drill Charger/PSU (both boards)	793	£5.31
Digital Servo Interface	JUNE'92 791	£4.73
Tie Pulser	794	£5.19
CCD Reverb Unit	795	£6.39
Switch-Mode Power Supply	796	£7.01

PROJECT TITLE	Order Code	Cost
UV Exposure Timer JULY'92	797	£5.33
Cricket Game	798	£6.77
Quick Prom	799	£5.61
Gas Alarm AUG'92	800	£5.47
Dual Metronome	801	£6.74
Ultrasonic Tape Measure SEP'92	802	£6.06
Quicktest	803	£4.82
Extended Range Capacitance Meter OCT'92	804	£5.63
Traffic Lights System	806	£5.04
Mini Lab NOV'92	MINI LAB	£14.95
EPE Altimet (Altimeter)	807	£6.30
Personal Stereo Amplifier	808	£6.47
Universal Infra-Red Remote Control DEC'92	811T/811R	£6.55
Combination Switch	812	£5.68
Christmas Lights Colour Spectrum	813	£5.97
TV/UHF Aerial Amp (double-sided) JAN'93	814	£7.23
Continuously Variable Balanced Power Supply	815	£5.65
Emergency Lighting Unit	816	£6.77
Biomet Pulse Monitor FEB'93		
Sensor	817	£6.30
Display	818	£6.30
Biomet Pulse Monitor MAR'93		
– ADC Interface (double-sided)	819	£7.11
Car Electric Window Enhancer	821	£5.00
Simplify Atari STFM Interface	822	£5.55
Personal Stereo Amp. Add-On	823	£3.90
Electronic Fire APR'93	820	£4.84
Mind Machine MkII – Signal Generator	824	£5.57
Ventilation Fan Timer	825	£4.70
Universal Data Logger	826	£5.88
Mind Machine MkII – Magic Lights MAY'93	827	£6.58
Superhet Radio Control Receiver	828	£5.93
Guitar Preamp and Distortion Unit	829	£5.46
Linear Clock – Timing Board	830	£8.00
Display Board	831	£7.00
Universal Alarm Module	9070	£3.00
Electronic Snooker Scoreboard JUNE'93	832	£9.17
Mind Machine MkII JULY'93		
– Computer Interface	833	£6.39
Xenon Strobe	834	£5.84
Electronic Gong	835	£7.50
Micro Lab – p.c.b., EPROM, PAL and booklet	MICRO	£35.00
Bike Odometer (pair of boards) AUG'93	836/7	£7.00
Amstrad PCW A to D Converter (double-sided)	838	£9.85
Experimental Electronic Pipe Descaler	839	£5.50
Sound Activated Camera Trigger SEP'93	840	£5.34
L.E.D. Sandglass OCT'93		
Main and Display boards	841/2	£7.30
Kettle Alert	843	£5.19
Linear Power Supply (double-sided)	844	£9.77
Multi-Purpose Audio System		
Six Channel Stereo Mixer	845	£11.98
Multi-Purpose Audio System NOV'93		
Microphone Pre-Amp module	846	£4.88
RIAA Pre-Amp module	847	£5.11
20 Metre Receiver	848	£6.63
Multi-Purpose Audio System DEC'93		
Tone Control and 1W Stereo Amplifier	849	£6.09
Tone Control	850	£5.12
1W Stereo Amplifier	851	£4.88
Three-Way Christmas Tree Lights Flasher	853	£5.65
Auto Alarm	854	£5.49
250W/600W Battery to Mains Inverter	855	£13.92
Multi-Purpose Audio System JAN'94		
10W + 10W Stereo Power Amplifier		
Amplifier	852a	£5.65
Power Supply	852b	£5.49
Pond Heater Thermostat	856	£5.77
Timer/NiCad Capacity Checker	857	£6.30
Multi-Purpose Audio System FEB'94		
Balanced Microphone Preamplifier	858	£5.30
Balanced Microphone Power Supply	859	£5.14
Whistle Controlled Light Switch	860	£5.19
Battery to Mains Inverter – U.P.S. charger board	862	£7.38
Three Phase Generator MAR'94	861	£5.95
Visual Doorbell	863	£5.80
CCD TV Camera – Control Board (double-sided, plated-through-hole)	865	£15.00
Telephone Ring Detector APR'94	864	£4.72
CCD TV Camera		
Combined Video, Test & Ext Plug Boards	866a/e	£11.00
Frame Grab Control (double-sided plated-through-hole)	867	£15.00
EPE Sound DAC PC Sound Board	868	£4.77
MOSFET Variable Bench Power Supply	869	£5.80

PROJECT TITLE	Order Code	Cost
L.E.D. Matrix Message Display Unit MAY '94		
Display Board	870	£18.00
CPU Board	871	£7.20
Stereo Noise Gate	873	£6.14
Simple TENS Unit	875	£5.84
Capacitance/Inductance Meter	876	£6.44
Advanced TENS Unit JUN '94	877	£6.56
Digital Water Meter – Scaler	878	£11.19
Counter/Display	879	pair
L.E.D. Matrix Message Display Unit		
Keypad	872	£5.19
PC Interface	880	£5.82
Microprocessor Smartswitch	881	£5.61
Microcontroller P.I. Treasure Hunter	882	£6.60
Print Timer JULY '94	874	£5.82
Watering Wizard	883	£6.60
Simple NiCad Charger	884	£4.98
Voxbox	885	£6.90
Stereo HiFi Controller – 1 Power Supply	886	£5.66
Stereo HiFi Controller – 2 AUG '94		
Main Board	887	£7.39
Expansion/Display Boards (pair)	888	£9.80
Dancing Fountains – 1		
Pre.amp	889	£5.28
Pump Controller	890	£5.41
Filter	891	£5.23
6802 Microprocessor Development Board	894	£9.15
Dancing Fountains – 2 SEPT '94		
PC-Compatible Interface (double-sided)	892	£10.90
Automatic Greenhouse Watering System	895	£5.33
Seismograph – 1 Sensor/Filter	895	£6.23
Clock/Mixer	897	£5.87
3-Channel Lamp Controller	899	£8.17
Seismograph – 2 OCT '94		
PC-Compatible Interface (double-sided)	898	£10.72
Visual/Audio Guitar Tuner	900	£7.55
Digilogue Clock	901	£12.50
Hobby Power Supply	902	£5.00
Audio Auxplexer		
Control Board	903	£7.72
Receiver	904	£6.24
Power Controller NOV '94	905	£4.99
1000V/500V Insulation Tester	906	£5.78
Active Guitar Tone Control	907	£4.50
TV Off-er (pair)	908/909	£7.25
Video Modules – 1 Simple Fader	910	£5.12
Improved Fader	911	£6.37
Video Enhancer	912	£5.15
Rodent Repeller DEC '94	913	£6.26
EPE Fruit Machine	914	£8.14
Video Modules – 2 Horizontal Wiper	916	£6.23
Vertical Wiper	917	£6.35
4- Channel Audio Mixer	918	£6.20
Spacewriter Wand	921	£4.00
Universal Digital Code Lock	922	£6.25

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
------------	---------	----------	-------

Name.....

Address.....

I enclose payment of £.....(cheque/PO in £ sterling only) to:



Everyday with
Practical Electronics



Access (MasterCard) or Visa No.
Minimum order for credit cards £5


[illegible]

Signature.....Card Exp. Date.....

Please supply name and address of cardholder if different from the address shown

REPORTING AMATEUR RADIO

Tony Smith G4FAI

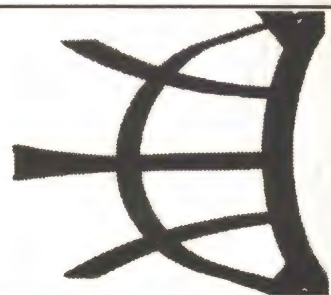

CIS CALLSIGNS

There has been some confusion over the amateur callsigns of ex-USSR stations since the break-up of the Soviet Union. Some countries immediately reclaimed their pre-WW2 prefixes, for example Estonia, ES, Latvia, YL, and Lithuania, LY. There were official new allocations from 1st January 1994, but some stations have continued to use previously issued calls now allocated to other countries.

Callsigns are allocated in series by the International Telecommunications Union (ITU). Countries are allocated blocks of prefixes beginning with a single letter, a pair of letters, or a number and a letter. Sometimes a block covers all possible prefixes with the same beginning, sometimes a half-series is allocated so that two countries share the same prefix. Swaziland, for example, has 3DA-3DM and Fiji 3DN-3DZ. Other countries, with many radio amateurs, have several prefix blocks.

The following is a list of the new ITU allocations for the countries of the ex-Soviet Union, including their previous calls for ease of reference.

BLOCKS ALLOCATED	COUNTRY	PREFIXES NEW	OLD
EKA-EKZ	Armenia	EK	UG
EMA-EOZ	Ukraine	EO	UB/UT/UY
ERA-ERZ	Moldava	ER	UO
ESA-ESZ	Estonia	ES	UR
EUA-EWZ	Belarus	EV	UC
EXA-EXZ	Kyrgystan	EX	UM
EYA-EYZ	Tajikistan	EY	UJ
EZA-EZZ	Turkmenistan	EZ	UH
LYA-LYZ	Lithuania	LY	UQ
RAA-RZZ	Russia	RA	UA
UAA-UIZ	Russia	UA	UA
UJA-UMA	Uzbekistan	UM	UI
UNA-UOZ	Kazakhstan	UN	UL
URA-UZZ	Ukraine	US/UT/ UX/UY	UB/UT
YLA-YLZ	Latvia	YL	UP
4JA-4KZ	Azerbaijan	4J/4K	UD
4LA-4LZ	Georgia	4L	UF
R1F	Franz Josef Land	R1F	4K2

YEAR IN REVIEW

I have been looking back over the last twelve months at some of the matters reported in this column to see if any conclusions can be drawn from them. I have chosen only one subject from each issue although there are of course several topics discussed each month.

In December 1993, an extract from the Radiocommunications Agency's Annual Report showed that there were fewer radio amateurs in 1992/93 than in the previous year. Numbers dropped from 61,442 in March 1992 to 59,242 a year later, a loss of 2,200. Publication of this year's Report has been delayed but I hope to have the 1994 figures next month.

January's column reported that the Radio Society of Great Britain's representatives at the IARU Region 1 Conference in the previous September had abstained from voting on the issue of the amateur Morse test. Apparently they had no mandate on this subject despite a recent RSGB survey in which a large majority of those voting had supported retention of the test.

February's column recorded that an Ariane launch vehicle had recently carried no less than seven amateur satellites into orbit.

March carried the finally released official Morse test survey results, showing that 67.5% of those taking part voted "No" to the concept of a code-free licence while 32.5% voted "Yes".

April highlighted the Young Operators' International Radio Club, a Russian based international organisation of young people under 30, which seeks to promote friendship and a better understanding of each other by sharing ideas and information about radio and other hobbies through radio communication and a newsletter.

COMMEMORATION

May saw news of "Operation Maquis", an amateur radio special event associated with the D-Day celebrations. Special French stations planned to be on the air to commemorate the WW2 clandestine radio links between France and Britain, and to honour the memory of those who died undertaking this dangerous work.

In June, there was a report on the work of Australian radio amateurs who provided communications support for the firefighters during the bush fires in New South Wales in January.

July carried the reassuring news that the Report of the Stage 3 Radio Spectrum Review Committee, covering 28MHz to 470MHz, "having noted the value of amateur radio to the community" proposed, for the foreseeable future, no change in the amateur radio frequency allocations.

In August this column reported, before any specialised amateur radio publication carried the news, that the International Amateur Radio Union had appointed a special sub-committee to examine the issues related to the amateur Morse test, and to propose the position the IARU should take on this controversial matter.

September saw a report on the first course run by STELAR (Science and Technology through Educational links with Amateur Radio) for teachers from schools with no current amateur radio programme.

In October, we delved into the fascinating world of "numbers stations", an intriguing aspect of short wave listening involving mysterious stations labelled with such names as the "Lincolnshire

Poacher", Bulgarian Betty", "Bugle Station", and "Russian Counting Man".

In November there were details of changes in the terms and conditions of the amateur radio licence. These introduced some new privileges, including the use of higher power in the 1.8MHz and 50MHz bands; and some restrictions including a requirement that unattended packet operation should have the facility to close-down rapidly when other services were being interfered with.

CONCLUSIONS

So what conclusions can be drawn from this brief review of a year of "Reporting Amateur Radio"? It seems clear that the question of the amateur Morse test is the one issue that won't go away. A survey of amateurs resulted in a substantial "retain it" majority, yet the RSGB would not adopt that viewpoint as its policy. Now the IARU is trying to decide what its policy should be at international level.

The annual figures show that the numbers of licensees are decreasing, and there is a view that this trend could be reversed if only the Morse test were abolished. As the survey showed, there is also a substantial contrary view so this particular controversy is likely to continue for some time yet.

Frequent references to rules and regulations emphasise that amateur radio is very much a disciplined hobby governed by detailed terms and conditions. In a world where "breaking the rules" is a common occurrence, radio amateurs who do this can lose their licences and few choose to take the risk.

ABOVE ALL IT'S FUN

My limited selection of topics gives some indication of the scope of amateur radio. A look back at the actual pages, however, widens the perspective and shows very clearly that it is not just one but many hobbies rolled into one, offering enjoyment and satisfaction at many levels.

None of this is parochial either. Amateur radio is international, with many activities involving contact with amateurs in other countries, often resulting in lasting friendships with them.

This column seeks to emphasise how easy it is for beginners to make a start in amateur radio. Once they have studied for and acquired their licences, newcomers are welcomed by the "specialists" who are more than pleased to help them start and make progress in the various branches of the hobby.

If you have a radio with facilities for listening to amateurs, try listening to them on the international bands over the festive season when they catch up with old friends, and make new ones. You will begin to get some idea of what it's all about. It's an absorbing activity, satisfying and rewarding. Above all it's fun. Happy Christmas!

SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

Genuine SUMA kits available only direct from Suma Designs. Beware inferior imitations!

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including: mic. 3-12V operation. 500m range.....£16.45

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter
Just 17mm x 17mm including mic. 3-12V operation. 1000m range.....£13.45

STX High-performance Room Transmitter

Hi performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6-12V operation, 1500m range.....£15.45

VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9-12V operation. 3000m range.....£16.45

VXT Voice Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range...£19.45

MYX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply for long-term monitoring. Size 30mm x 35mm. 500m range.....£19.45

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range.....£22.95

SCSX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range.....£23.95

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9-12V operation.....£22.95

ATR2 Micro Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line.....£13.45

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversation transmitted. Powered from line. 500m range.....£15.95

TLX700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range.....£13.45

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range.....£16.45

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation.....£22.95

CD400 Pocket Bug Detector/Locator

LED and piezo bleeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation.....£30.95

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation.....£50.95

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180 MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range.....£40.95

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range.....£40.95

QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m.....£35.95

QRX180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as a pre-built and aligned module ready to connect on board so no difficulty setting up. Outpt to headphones. 60mm x 75mm. 9V operation.....£60.95

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft and add £5.00 per order for shipment. Credit card orders welcomed on 0827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.

★★★★ Specials ★★★★★

DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way dit switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits).....£50.95
Individual Transmitter DLTX.....£19.95
Individual Receiver DLRX.....£37.95

MBX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle. Size 27mm x 60mm. 9V operation. 250m range.....£20.95

**SUMA
DESIGNS**

DEPT. EE

THE WORKSHOPS, 95 MAIN ROAD,
BAXTERLEY. NEAR ATHERSTONE,
WARWICKSHIRE CV9 2LE

VISITORS STRICTLY BY APPOINTMENT ONLY



Tel/Fax:
0827 714476

EXPRESS COMPONENTS

MAINS IONIZER KIT. Very useful kit that increases the flow of negative ions, helps clear cigarette smoke, dust, pollen etc. Helps reduce stress and respiratory problems. £15. kit, £20 built.

COMBINATION LOCK. Electronic 9 key combination lock suitable for alarms, cars, houses etc, easily programmable. Includes mains 2A relay o/p. 9v operation. £10 kit, £14 built.

VARIABLE POWER SUPPLY. Stabilized, short circuit protected. Gives 3-30v DC at 2.5A, ideal for workshop or laboratory. £14 kit, £18 built. 24VAC required.

LEAD ACID CHARGER. Two automatic charging rates (fast and slow), visual indication of battery state. Ideal for alarm systems, emergency lighting, battery projects etc. £12 kit, £16 built.

PHONE LINE RECORDER. Device that connects to the 'phone line and activates a cassette recorder when the handset is lifted. Ideal for recording 'phone conversations etc!. £8 kit, £12 built.

ROBOT VOICE. Turns your voice into a robot voice! answer the phone with a different voice!. £9 kit, £13 built.

PHONE BUG DETECTOR. This device will warn you if somebody is eavesdropping on your 'phone line. £6 kit £9 built.

PHONE BUG. Small bug powered by the telephone line. Only transmits when the phone is used. Popular surveillance product. £8 kit, £12 built.

STROBE LIGHT. Bright strobe light with an adjustable frequency of 1-60hz. (a lot faster than conventional strobes!) £16 kit, £20 built.

4W FM TRANSMITTER. 3 RF stages, audio preamp. 12-18vDC. Medium powered bug £20 kit, £28 built.

3 CHANNEL LIGHT CHASER. 3x 800w output, speed and direction controls, can be used with 12 led's (supplied) or TRIACS for mains lights (also supplied). 9-15v DC. £17 kit, £23 built.

25W FM TRANSMITTER. 4 stage, a preamp will be required. (Our preamp below is suitable) £79 built. (no kits). **SOUND EFFECTS GENERATOR.** Produces any thing from bird chips to sirens! add sounds to all sorts of things £9 kit £13 built.

FM/AM SCANNER. Well not quite, you have to turn the knob yourself but you will hear things on this radio (even TV) that you would not hear on an ordinary radio! A receiver that covers 50-160MHZ both AM and FM. Built in 5w amplifier. £15 kit, £20 built.

CAR ALARM SYSTEM. Works on vibration and/or voltage drop from door etc being opened. Entry and exit delays plus adjustable alarm duration. Low cost protection! £12 kit, £16 built.

15W FM TRANSMITTER. 4 stage, high power bug. You will need a preamp for this (see our preamp below which is ok) £69 built. (no kits).

1W FM TRANSMITTER. 2 stage including preamp and mic. Good general purpose bug. 8-30VDC. £12 kit, £16 built.

50 I/C's for £1.50
Nice mix of chips at a bargain price!

CERAMIC CAPACITOR PACK
Good mixed pack of 100 capacitors for just £1.00

ELECTROLYTIC PACK 1
100 small mixed electrolytic capacitors just £1.00

ELECTROLYTIC PACK 2
50 larger electrolytic mixed capacitors

RESISTOR PACK NO 1
250 low wattage resistors, ideal for most projects etc. Just £1.00

RESISTOR PACK NO 2
Hi wattage pack, good selection of mixed wattages and values 50 in all, bargain price just £1.00

PRESET PACK
Nice selection of 25 mixed preset pots for just another £1!

RELAY PACK NO 1
6 mixed relays for £1, that's just 17p each.

CONNECTOR PACK
10 different connectors, again for £1

FUSE PACK NO 1
40 mixed 20mm fuses, ideal for repairs etc, or just to stock up the spares box! Just £1.00

FUSE PACK NO 2
30 mixed 1.25" fuses again ideal for spares etc. Just £1.00

WIRE PACK
25 Metres of insulated wire for just £1.00, good for projects etc.

SLEEVING PACK
100 assorted pieces of sleeving for connectors etc. Yours for just £1.00

DIODE PACK
100 assorted diodes for just £1.00

LED PACK
20 light emitting diodes for £1.00

TRANSISTOR PACK
50 mixed transistors, another bargain at £1.00

BUZZER PACK
10 things that make a noise for just £1.00!

POT PACK
10 pots for £1, (5 different types) a snip at £1.00

DISPLAYS
10 seven segment displays for £1.00

ORDER 10 PACKS OR MORE AND CHOOSE ONE FREE PACK!!
FREE COMPONENT CATALOGUE WITH EVERY ORDER!!

BULK PACKS

99p
Post

KITS 'N MODULES

PREAMP MIXER. 3 channel input, independent level and tone controls. Ideal for use with the hi power FM transmitters. £15 kit, £19 built.

TREMBLER ALARM. Designed for bikes etc, adjustable sensitivity, preset alarm time, auto reset. Could be adapted for all sorts of "borrowable" things £12 kit, £16 built.

ULTRASONIC RADAR. A project that can be used as a movement detector in an enclosed space. Range about 10 metres, 12vDC. Good basis for car, shed, caravan alarm etc. £14 kit, £19 built.

PHONE CALL RELAY. Very useful kit that incorporates a relay that operates when the phone rings. Can be used to operate more bells, signalling lights etc. Good for noisy environments or if you have your headphones on! £10 kit, £14 built.

PORTABLE ALARM SYSTEM. Small 9v alarm system based on a mercury switch. The alarm continues to sound until disabled by the owner. Buzzer included. £11 kit £15 built.

800W MUSIC TO LIGHT EFFECT. Add rhythm to your music with this simple sound to light kit. £8 kit, £12 built.

MOSQUITO REPELLER. Modern way to keep the midges away! Runs for

about a month on one 1.5v battery. Frequency is set to drive away mosquitos etc. £7 kit, £11 built.

3 CHANNEL SOUND TO LIGHT. Can be used anywhere as no connection is made to hi fi. Separate sensitivity controls for each channel, 1,200W power handling. Microphone included. £14 kit, £19 built.

MINI METAL DETECTOR. Detects pipes, wires etc up to 20cm deep. Useful before you drill those holes! £8 kit, £12 built.

0-5 MINUTE TIMER. Simple time switch adjustable from 0-5 mins, will switch 2A mains load. 12v op. Ideal for laboratory, photographic projects etc. £7 kit, £11 built.

7 WATT HI FI AMPLIFIER. Useful, powerful amplifier 20hz-15khz, 12-18vdc. Good for intercoms, audio systems, car etc. £7 kit £11 built.

INCAR SOUND TO LIGHT. Put some atmosphere in your car with this kit. Each channel has 6 led's that create a beautiful lighting effect! £10 kit, £14 built.

VOX SWITCH. This is a sound activated switch, ideal for use on transmitters, CB's, tape recorders etc. Adjustable sensitivity, built in delay. Mic input. £7 kit, £11 built.

LIQUID LEVEL DETECTOR.

Useful item, can be used to detect fluid levels in watertanks, baths, ponds, fishtanks etc. Could also be used as rain alarm with an easily constructed sensor. £5 kit, £9 built.

FM TRANSMITTER. Mini FM transmitter 2 transistor, comes with FET miniature mic and is tuneable from 63 to 130MHZ. £7 kit, £11 built.

FUNCTION GENERATOR. Generates sinusoidal, saw tooth and square waveforms from 20hz up to 20khz. Separate level controls for each waveform. 24vac. £15 kit, £20 built.

5 WATT SIREN. Powerful siren kit with an impressive 5 watts output. Ideal for alarms etc. £6 kit £10 built.

TELEPHONE AMPLIFIER. Very sensitive amplifier which using a 'phone pickup coil (supplied) will let you fol-

low a telephone conversation without holding the handset to your ear! £11 kit £15 built.

SWITCH PACK
10 switches for just £1.00

12v FLOURESCENT. A useful kit that will enable you to light large flourescent tubes from your car battery etc. 9v mains transformer required. £8 kit, £12 built.

KNOB PACK
10 knobs for just £1.00

REMEMBER! YOUR FREE COPY OF OUR CUT PRICE COMPONENTS CATALOGUE SENT WITH EVERY ORDER!!!

How to place your order.....

By phone.....0273 771156

By FAX.....0273 206875

By Post...PO box 517 Hove Sussex BN3 5QZ

Payment by ACCESS, VISA, CHEQUE OR POSTAL ORDER.

Cheques and postal orders should be payable to Express Components.

ALL PRICES ARE SUBJECT TO 99p POST AND VAT. Some of our products may be unlicensable for use in the UK (particularly the FM transmitters.)

EVERYDAY WITH PRACTICAL ELECTRONICS

The No 1 Magazine for Electronic & Computer Projects

JANUARY 1994 TO
DECEMBER 1994

Pages	Issue	Pages	Issue
1-88	January	489-560	July
89-176	February	561-644	August
177-248	March	645-716	September
249-332	April	717-808	October
333-404	May	809-892	November
405-488	June	893-984	December

VOLUME 23 INDEX

CONSTRUCTIONAL PROJECTS

ACTIVE GUITAR TONE CONTROL <i>by John Chatwin</i>	842	MICROPROCESSOR SMARTSWITCH <i>by Bart Trepak</i>	452
ADVANCED TENS UNIT <i>by Andy Flind</i>	460	MOSFET VARIABLE BENCH POWER SUPPLY	
AMPLIFIER, QUAD II POWER, REBUILD	112, 134	<i>by Mark Stuart</i>	262, 362
AMPLIFIER, VALVE	112, 134	MULTI-PURPOSE AUDIO SYSTEM <i>by Max Horsey</i>	56, 156
AUDIO AUXILEXER <i>by William E. Chester</i>	770	NiCAD CAPACITY CHECKER	35
AUDIO GUITAR TUNER, VISUAL/	742	NiCAD CHARGER, SIMPLE	512
AUDIO MIXER	959	NIGHTLIGHT	16
AUDIO/R.F. MONITOR <i>by Ian Hickman</i>	198	NOISE CANCELLING UNIT, EXPERIMENTAL	574
AUDIO SYSTEM, MULTI-PURPOSE	56, 156	PAIN RELIEF UNITS	346, 460
AUTOLIGHT <i>by Terry de Vaux-Balbirnie</i>	16	PC STEPPING MOTOR DRIVER	388
BATTERY CHECKER, TIMER and NiCAD	35	POND HEATER THERMOSTAT <i>by Alan Winstanley</i>	70
BATTERY TO MAINS INVERTER	42, 69, 134	PORTABLE AUTOLIGHT <i>by Terry de Vaux-Balbirnie</i>	16
BENCH POWER SUPPLY, MOSFET	262, 362	POWER CONTROLLER <i>by Alan Winstanley</i>	870
CAPACITANCE/INDUCTANCE METER <i>by Doug Kennedy</i>	356	POWER SUPPLY, HOBBY	766
CAR ALARM, PROTECTOR PLUS	658	POWER SUPPLY, MOSFET VARIABLE BENCH	262, 362
CAR IMMOBILISER	190	PRINT TIMER <i>by Andrew Chadwick</i>	536
CCD TV CAMERA <i>by John Becker</i>	210, 300, 362, 618	PROTECTOR PLUS CAR ALARM <i>by Terry de Vaux-Balbirnie</i>	658
CHARGED-UP <i>by Ken Lee</i>	596	QUAD II POWER AMPLIFIER REBUILD	112, 134
CHARGER, NiCAD	512	RECORDING BOARD, VOXBOX VOICE	502
CLOCK, DIGILOGUE	730	REVIVING THE VALVE SOUND <i>by Jake Rothman</i>	112, 134
COMPUTER SOUND CARD, EPE SOUNDAC	280	R.F. MONITOR/AUDIO	198
CONTROLLER, STEREO HI FI	546, 628	RODENT REPELLER <i>by Terry de Vaux-Balbirnie</i>	964
DANCING FOUNTAINS <i>by John Becker</i>	590, 696	SEISMOGRAPH, EXPERIMENTAL	676, 786
DIGILOGUE CLOCK <i>by John Scott Patterson</i>	730	SIMPLE NiCAD CHARGER <i>by Steve Knight</i>	512
DIGITAL CODE LOCK, UNIVERSAL	944	SIMPLE TENS UNIT <i>by Andy Flind</i>	346
DIGITAL WATER METER <i>by John Becker</i>	430	SMART-KEY IMMOBILISER <i>by Nicholas Watkins</i>	190
DISPLAY, L.E.D. MATRIX MESSAGE	370, 468	SMARTSWITCH, MICROPROCESSOR	452
DOORBELL, VISUAL	222	SOUNDAC, COMPUTER SOUND BOARD <i>by Phil Green</i>	280
DUAL STEPPING MOTOR DRIVER FOR PCs	388	SPACEWRITER WAND <i>by Mark Stuart</i>	906
ENHANCER, VIDEO	835	STEPPING MOTOR DRIVER FOR PCs	388
EXPERIMENTAL NOISE CANCELLING UNIT <i>by Robert Penfold</i>	547	STEREO HF CONTROLLER <i>by David Geary</i>	546, 628
EXPERIMENTAL SEISMOGRAPH <i>by John Becker</i>	676, 786	STEREO NOISE GATE <i>by John Chatwin</i>	380
FADER, VIDEO	830, 833	TELEPHONE RING DETECTOR <i>by Andy Flind</i>	320
FISH POND HEATER THERMOSTAT	70	TENS UNIT, ADVANCED	460
FOUNTAIN, DANCING	590, 696	TENS UNIT, SIMPLE	346
FRUIT MACHINE, EPE, <i>by Brett Gossage & Julian Ilett</i>	909	THERMOSTAT, POND HEATER	70
GAME MACHINE, FRUIT	909	THREE-CHANNEL LAMP CONTROLLER <i>by Andy Flind</i>	687
GARDEN WATERING WIZARD	525	THREE-PHASE GENERATOR <i>by R.T. Irish</i>	230
GENERATOR, THREE-PHASE	230	TIMER, COUNTDOWN MICROCONTROLLER	134
GREENHOUSE WATERING SYSTEM <i>by Mike Richards</i>	668	TIMER, PRINT	536
GUITAR, STEREO NOISE GATE	380	TIMER and NiCAD CAPACITY CHECKER <i>by Andy Flind</i>	35
GUITAR TONE CONTROL, ACTIVE	842	TONE CONTROL, ACTIVE GUITAR	842
GUITAR TUNER, VISUAL/AUDIO	742	TREASURE HUNTER, MICROCONTROLLER PI	418
HOBBY POWER SUPPLY <i>by Terry de Vaux-Balbirnie</i>	766	TV CAMERA, CCD	210, 300, 362, 618
HORIZONTAL WIPER, VIDEO	954	TV SWITCH-OFF TIMER <i>by Chris Brown</i>	878
IMPULSE CLOCK MASTER UNIT <i>by Huw Griffiths</i>	316	UNINTERRUPTABLE POWER SUPPLY, 250W/600W	
INDUCTANCE/CAPACITANCE METER	356	INVERTER	42, 69, 134
INSULATION TESTER, 1000V/500V	822	UNIVERSAL DIGITAL CODE LOCK <i>by Bart Trepak</i>	944
INTRODUCTION TO MICROCONTROLLERS - TIMEOUT		VERTICAL WIPER, VIDEO	957
<i>by Peter Crowcroft</i>	128	VIDEO MODULES <i>by Robert Penfold</i>	830, 954
INVERTER, BATTERY TO MAINS	42, 69, 134	VISUAL/AUDIO GUITAR TUNER <i>by Robert Penfold</i>	742
LAMP CONTROLLER, THREE-CHANNEL	687	VISUAL DOORBELL <i>by Andy Flind</i>	222
L.E.D. MATRIX MESSAGE DISPLAY		VOXBOX VOICE RECORDING BOARD	
<i>by Julian Ilett & Brett Gossage</i>	370, 468	<i>by Guy Dance & Jeremy Austin</i>	502
LIGHTSWITCH, WHISTLE CONTROLLED	104	WAND, SPACEWRITER	906
LOCK, DIGITAL CODE	944	WATERING SYSTEM, GREENHOUSE	668
MACHINE, EPE FRUIT	909	WATERING WIZARD <i>by Terry de Vaux-Balbirnie</i>	525
MESSAGE DISPLAY, L.E.D. MATRIX	370, 468	WATER METER, DIGITAL	430
METAL DETECTOR	418	WHISTLE CONTROLLED LIGHTSWITCH <i>by Bart Trepak</i>	104
METER, DIGITAL WATER	430	0V to 25V at 0 to 2.5A MOSFET VARIABLE PSU	262, 362
MICROCONTROLLER PI TREASURE HUNTER		10W plus 10W STEREO POWER AMPLIFIER	56
<i>by Mark Stuart</i>	418	13A POWER CONTROLLER	870
MICROPHONE PREAMPLIFIER	156	250W/600W INVERTER & UNINTERRUPTABLE POWER	
MICROPROCESSOR DEVELOPMENT	608	SUPPLY - 2 <i>by Mark Daniels</i>	42, 69, 134
		1000V/500V INSULATION TESTER <i>by Mark Stuart</i>	822
		6802 DEVELOPMENT BOARD <i>by Richard Stone</i>	608

SPECIAL SERIES

ACTUALLY DOING IT, TECHNIQUES <i>by Robert Penfold</i>	76, 164, 234, 384, 400, 449, 624, 876, 934	Train Sound Effects	517
AMATEUR RADIO <i>by Tony Smith G4FA1</i>	84, 172, 244, 328, 466, 556, 640, 713, 804, 888, 976	Water Probe	672
		Zener Diodes	26
		555 Timer Triggers	516
BEST OF BRITISH		ELECTRONICS FROM THE GROUND UP	
<i>by Terry de Vaux-Balbirnie</i>	274, 364, 438, 520, 622	<i>by Mike Tooley, B.A.</i>	748, 854, 924
CIRCUIT SURGERY <i>by Alan Winstanley</i>	26, 120, 202, 293, 360, 428, 516, 605, 672, 738, 920	1 - Introduction	748
Aquarium Thermostat	517	2 - Capacitance, Inductance, A.C. Circuits	854
Astable and Monostable Timing	293	3 - Semiconductors	924
Battery Back-Up	120, 294, 605	INGENUITY UNLIMITED	846
Bilge Pump Controller	429, 673	Auto Power Down	846
Bistable Briefing	361	L.E.D. Voltmeter	848
Capacitor Problem	360, 605	Liquid Crystal Display Tester	846
Car Battery Monitor	607	Simple Lights-On Alert	847
Car Electrics Probe	516, 674	Voltage Drop Car Alarm	847
Coil Winding	920		
Education Service	295	INTERFACE <i>by Robert Penfold</i>	
D.C. Motor Controller	738	54, 144, 226, 298, 392, 476, 540, 616, 704, 794, 844, 952	
Fuses	203		
Halogen Lamp Protector	428	CALCULATION CORNER <i>by Steve Knight</i>	
Lamp Dimmer, Mains	204	50, 146, 219, 312, 352, 442, 542, 598, 684, 780	
Light Box for PCBs	921	1 - Getting to Know the Basics	50
Low Voltage Monitor	27	2 - Ohm's Law	146
Marine Battery Back-Up	605	3 - Work, Energy and Power	219
NiCad Charger Conversion	739	4 - Measuring Instruments	312
Power Factors	672	5 - Capacitors	352
Printed Circuit Boards	921	6 - Time Constants	442
Reed Relays	120	7 - Getting to Know Decibels	542
Regulator Protection	606	8 - Kirchoff's Law	598
Semiconductors, Checking Unmarked	202	9 - A.C. Theory	684
Shock Horror	361	10 - A.C. Theory continued	780
Shed Some Light	429	SAFETY FIRST <i>by Terry de Vaux-Balbirnie</i>	28, 150, 206

GENERAL FEATURES

CHICAGO CONSUMER SHOW <i>by Barry Fox</i>	838	I'LL BE SEEING YOU <i>by Alan W. Rudge</i>	586
DOWN TO EARTH <i>by George Hylton</i>	796, 867	INVISIBLE FORCE, THE <i>by Mike Crow</i>	694
EDITORIAL	15, 103, 189, 261, 345, 417, 501, 573, 657, 729, 821, 905	NEWS	22, 108, 194, 270, 355, 425, 509, 582, 664, 736, 826, 916
ELECTRONICS WORKBENCH REVIEW <i>by Mike Tooley</i>	285	NEW TECHNOLOGY UPDATE <i>by Ian Poole</i>	24, 110, 196, 272, 386, 426, 510, 584, 666, 765, 828, 950
ELECTRONIC TESTING AND FAULT DIAGNOSIS	64	NTC OPEN LEARNING COURSE REVIEW	64
EMBEDDED CONTROLLERS <i>by John Davies</i>	941	PLEASE TAKE NOTE	69, 362
EUROPEAN INTERNATIONAL AUDIO & VISUAL FAIR	122	Battery to Mains Inverter	69
FOX REPORT <i>by Barry Fox</i>	68, 132, 236, 319, 398, 458, 508, 702, 784, 936	CCD TV Camera	362
HOME BASE <i>by Terry Pinnell</i>	154, 238, 296, 534, 625	Christmas Tree Lights Flasher, Three-Way (Dec '93)	69
		MOSFET Variable Bench PSU	362
		Waterproof Delay Switch (Dec '93)	69
		SHOPTALK <i>with David Barrington</i>	69, 143, 225, 295, 362, 465, 518, 581, 674, 783, 868, 918

SPECIAL OFFERS AND SERVICES

ADVERTISERS' INDEX	88, 176, 248, 332, 404, 488, 560, 644, 716, 808, 892, 984	DIRECT BOOK SERVICE	79, 167, 239, 323, 395, 479, 551, 635, 707, 799, 883, 971
COMPONENT CATALOGUE		DISPLAY ELECTRONICS NEWS (32-page)	between 44/45
(Bull Electrical '95 96-page)	banded with Dec '94	ELECTRONICS FORMULAE - 1 Wall Chart	Free with Mar '94
COMPONENT CATALOGUE		ELECTRONICS FORMULAE - 2 Wall Chart	Free with April '94
(Display Electronics 32-page)	between 44/45	ELECTRONICS PRINCIPLES	34, 133, 228, 378, 484, 535, 634, 712, 798, 866, 962
COMPONENT CATALOGUE		ELECTRONICS VIDEOS	78, 166, 229, 292, 379, 448, 554, 604, 706, 764, 852, 963
(Greenweld '95 196-page)	banded with Nov '94	ELECTRONICS WORKBENCH SOFTWARE DISC	Cover Mounted - Oct '94
COMPONENT CATALOGUE		PRINTED CIRCUIT BOARD SERVICE	82, 170, 242, 327, 399, 482, 555, 638, 711, 802, 886, 975
(Greenweld 48-page Summer)	between 524/525		
COMPONENT CATALOGUE			
(Greenweld 32-page Winter)	between 132/133		

PCB Designer

For Windows 3.1
Runs on any PC running
Windows in standard or
enhanced mode
with 2MB
RAM

Only
£49
All
Inclusive

- ✓ Produce *Single* or *Double* sided PCBs.
- ✓ Print out to *any* Windows supported printer.
- ✓ *Toolbar* for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pads sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Positive reviews by Robert Penfold and Paul Stenning, copies available on request.

Phone (0432) 355 414 (Access and Visa welcome)

Niche Software

22 Tavistock Drive, Belmont, Hereford, HR2 7XN.

Please Note: Since PCB designer is so easy to use, and to keep costs down, PCB Designer has an On-Line manual, in Windows Help format. A FREE tutorial is also supplied.

Inverter toroidal transformers 225VA 10.5-0-10.5V
primary 0.260-285V secondary £29.95
LEDs 3mm or 5mm red or green 6p each, yellow
11p each. High intensity red, green or yellow,
5mm 30p each.
Cable Ties 1p each, £5.95 per 1000, £49.50 per
10,000.

High quality photo resist copper
clad epoxy glass boards
Dimensions single-sided double-sided
3x4 inches £1.09 £1.23
4x8 inches £2.75 £2.99
6x12 inches £6.20
12x12 inches £12.25

RECHARGEABLE BATTERIES
AA (HP7) 500mAh £0.99
AA 700mAh £1.75
C 2AH with solder tags £3.60
D 4AH with solder tags £4.95
1/2AA with solder tags £1.55
AAA (HP16) 180mAh £1.75
AA 500mAh with solder tags £1.55
C (HP12) 1.2AH £2.20
D (HP21) 2.8AH £2.60
PP3 8.4V 110mAh £4.95
Sub C with solder tags £2.50
1/3 AA with tags (Philips CTV) £1.95
Standard charger, charges 4 AA cells in 5 hours
or 4Cs or Ds in 12 to 14 hours + 1xPP3 (1, 2, 3
or 4 cells may be charged at a time) £5.95
High power charger, as above but charges the
Cs and Ds in 5 hours, AAs, Cs and Ds must be
charged in twos or fours £10.95
Nickel Metal Hydride AA cells, high capacity
with no memory, 1000mAh £3.85, 1200mAh £4.40

**SPECIAL OFFERS - PLEASE CHECK
FOR AVAILABILITY**
42mm x 16mm dia. 1.2V £1.45
Stick of 4 171mm x 16mm dia., with red
and black leads 4.8V £5.95
Computer grade capacitors with screw terminals,
38000µF 20V £2.50, 87000µF 10V £1.95,
68000µF 15V £2.95, 10000µF 16V £1.50,
58000µF 60V £4.95
7-segment common anode l.e.d. display,
12mm £0.45
LM2931 AT 5.0 low drop out 5V
regulator TO220 package £0.85
7812 and 7812 12V 1A regulators £26.00 per 100
LM337K TO3 case variable regulator £1.95
100 + £1.44 each
GaAs F.E.T. low leakage current S8873 £12.95
each, £9.95 10 +, £7.95 100 +
BS250 p-channel MOSFET £4.50
BC559 transistor £3.95 per 100
74LS05 Hex inverter £10.00 per 100
Used 8748 Microcontroller £3.50
SL952 UHF Limiting amplifier, LC 16 surface
mounting package with data sheet £1.95
AM27502 £1.25 each, 90p 100 +
CD4007UB £1.00 100 +, 6p 1000 +
Sinclair light gun terminated with a jack plug and
PP3 clip gives a signal when pointed at 50Hz
flickering light, with output waveform chart £3.95
DC-DC converter, Reliability model V12PS, 5V
200mA out, 300V input to output isolation,
with data £4.95 each or pack of 10 £39.50
Hour counter used 7 digit 240V ac. 50Hz £1.45

QWERTY keyboard, 58 key good quality switches,
new £5.00
Airpax A82903-C large stepping motor 14V
7.5" step, 27 ohm, 68mm dia body, 6.3mm
shaft £8.95 or £200.00 for a box of 30
Polyester capacitors, box type, 22.5mm lead pitch
0.9µF 250V d.c. 18p each, 14p 100 +, 9p 1000 +
1µF 250V d.c. 20p each, 15p 100 +, 10p 1000 +
2.2µF 250V d.c. 30p each, 20p 100 +, 15p 1000 +
3.3µF 100V d.c. 30p each, 20p 100 +, 15p 1000 +
1µF 50V bipolar electrolytic axial leads, 15p each,
7.5p 1000 +
0.22µF 250V polyester axial leads, 15p each,
100 + 7.5p each
Polypropylene 1µF 400V d.c. (Wima MKP10)
27.5mm pitch, 32 x 29 x 17mm case, 75p each,
60p 100 +
Philips 123 series solid aluminium axial leads,
33µF 10V & 2.2µF 40V 40p each, 25p 100 +
Philips 108 series 22µF 63V axial
100p each, 30p each, 15p 1000 +
Multilayer AVX ceramic capacitors, all 5mm
pitch, 100V 100pF, 150pF, 220pF, 10,000pF
(10n) 10p each, 5p 100 +, 3.5p 1000 +
500pF compression trimmer £0.60
40µF 370V ac. motor start capacitor (dielectric type
containing no p.c.b.s.) £5.95 or £49.50 for 10
Welwyn W23 9W 120 ohm 35p each, 24p 100 +
680 ohm 2W metal film resistor
Solid carbon resistors, very low inductance, ideal
for r.f. circuits, 27ohm 2W, 68ohm 2W 25p each,
15p each 100 +
we have a range of 0.25W, 0.5W, 1W and 2W
solid carbon resistors - please send SAE for list
P.C. 400W PSU (Intel part 201035-001) with
standard motherboard and 5 disk drive
connectors, fan and mains inlet/output
connectors on back and switch on the side (top
for tower case), dims. 212 x 149 x 149mm
excluding switch, £26.00 each, £138.00 for 6
MX180 Digital multimeter 17 ranges, 1000V
d.c. 750V ac. 2Mohm 200mA transistor Hfe 9V
and 1.5V battery test £12.95
AMD 27568 3 EPROMS £2.00 each, £1.25 250 +
CV2486 gas relay 30mm x 10mm dia. with
3 wire terminals, will also work as a neon
light £2.00 each, £2.50 per 100
A231 12V battery for car alarms or lighters
75p each, £50 100 +
All products advertised are new and unused unless
otherwise stated.
Wide range of CMOS TTL 74HC 74F Linear
Transistors kits, rechargeable batteries, capacitors,
tools etc. always in stock.
Please add £1.95 towards P&P
VAT included in all prices

JPG ELECTRONICS
276-278 Chatsworth Road
Chesterfield S40 2BH
Access/Visa Orders: (0246) 211202
Callers welcome

LÔÖKING FOR...

**ICs ★
TRANSISTORS ★ SEMIs?**
especially those hard to find?
Why not give us a buzz?

WE STOCK A MASSIVE RANGE

We specialise in devices with the following prefix
(to name but a few):

**2N 2SA 2SB 2SC 2SD 2SJ 2SK AN BA BC BD BDT BF
BFR BFY BFX BU BUK BUT BUV BUW BUZ CA DTA
HA IRF LA LB LC LF LM M MC MJ MJE MM MPS
MPSA MPSU NE RC SAA SAB SDA SI SL SN STA
STK STR TA TBA TC TDA TIP TEA TL UAA ULN UPC
XR ZN ZTX ... plus daily arrival of new numbers.**

ALSO

**RESISTORS ★ CAPACITORS ★ CHOKES ★ CABLES
LEADS ★ CONNECTORS ★ VIDEO HEADS ★ DRIVE BELTS
SWITCHES ★ TTL ★ CMOS ★ OP AMPS ★ VOLTAGE REGS
SPECIAL FUNCTION ★ TRANSFORMERS ETC ETC ETC**

**WE SPECIALISE IN PHONE & FAX MAIL ORDERS
BY CREDIT CARD**

Callers & Mail orders welcome



CRICKLEWOOD ELECTRONICS

40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
TEL: 081 452 0161 & 081 450 0995 FAX: 081 208 1441

!!! CATALOGUE DUE OUT AUTUMN 1994 !!!

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES
Available from £200 - PLUS INS SOLD SEPARATELY
TEKTRONIX 485 Dual Trace 350MHz Delay Sweep £750
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep £500
TEKTRONIX 465B Dual Trace 100MHz Delay Sweep £500
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep £400
TEKTRONIX SC504 Dual Trace 80MHz in TMS038 £450
TEKTRONIX 455 Dual Trace 50MHz Delay Sweep £450
WATSON S557 11C 4 Channel 100MHz Delay with DMM £300
TRIO CS2070 4ch 70MHz Delay Sweep £450
HITACHI V650F Dual Trace 60MHz Delay Sweep £350
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep £400
TELEQUINT DB3 Dual Trace 50MHz Delay £200
COULD 051100 Dual Trace 30MHz £160
WATSON S55702 Dual Trace 30MHz £300
COULD CS2508 Dual Trace 15MHz £125
TRIO CS1566A Dual Trace 20MHz £200
H.P. 1741A Dual Trace 100MHz Delay Sweep Analogue Storage £350

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE
HEWLETT PACKARD 1740A OSCILLOSCOPES
100MHz Dual Trace, Delay Sweep... For Only £350
MARCONI 2018 Synthesised AM/FM Sig Gen 80kHz-520MHz £700
H.P. 8640B Sig Gen 500kHz-1024MHz £1000
H.P. 8620C Sweep Oscillator with 86245A 5.9-12.4GHz £400
SYSTRON DONNER 1702 Synth AM/FM Sig Gen 100Hz-1GHz £600
RACAL 9081 Synthesised Sig Gen 5-520MHz £500
MARCONI TF2028 AM/FM Sig Gen 10kHz-510MHz £200
MARCONI TF2015 AM/FM Sig Gen 10kHz-510MHz £200
MARCONI TF2016 With Synchronizer TF2171 (lock box) £350
MARCONI TF2016 FM Sig Gen 10kHz-120MHz £250
PHILIPS PM5326 AM/FM Sig Gen 100kHz-110MHz £300
MARCONI TF2022 AM/FM Sig Gen 10kHz-80MHz with Dig Sync £1500
H.R. SMITH ANTENNA Type 12-602-4 £200
MARCONI 6500 Automatic Amplitude Analyser £1500
RACAL INSTRUMENT RECORDER type Store 4DN £500
H.P. 3575A Gen Phase Meter 1Hz-15MHz £400
SAVOSA Automatic Modulation Meter type 252B £125
RACAL 9104 RF Power Meter 1MHz-1GHz 10mW-300W £400
RACAL 9100 Automatic Wattmeter 15MHz-520MHz 300mW £100
TEKTRONIX CP2520 Trip Output PSU 2x20V 50A 5V2A Fxd £225
TEKTRONIX CP2520 Function Gen 0.2Hz-2MHz Sine/SQ Tri etc £225
TEKTRONIX CDMS20 Digital Multimeter 3 digit LED £180

SPECTRUM ANALYSERS
H.P. 8556A 001-220Hz £5000
H.P. 3580A LED 0.5MHz-50kHz £1000
POLARAD 641-1 10MHz-180Hz £1500
ANDAC AC281 with AC2811 1700MHz £1500
H.P. 182 with 8558B 100kHz-1500MHz £1500
H.P. 141T with 8558B & 8552B 500kHz-1250MHz £1200
H.P. 141T with 8553B & 8552A 1kHz-110MHz £800
MARCONI TF2370 30kHz-110MHz £1000
H.P. 8444 & 8443 Tracking Generators Available from £300
H.P. 141T Main Frames Only Good Tubes £700

Used Equipment - Guaranteed. Manuals supplied if possible.
This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before
ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Tel: 0734 268041 Fax: 0734 351696 Callers welcome 9am to 5.30pm MON-FRI (UNTIL 8pm THURS)

H.P. 3456A 6 digit DC True RMS AC Res HPB £600
EPO DANA 3510 Microwave Frequency Counter 20Hz-18GHz £500
H.P. 5541A Frequency Counter 50MHz-15GHz LED £300
MARCONI 2435 Digital Frequency Meter 20Hz £400
RACAL 1998 Freq. Counter 130Hz Ippons GPIB & High Stabl £300
RACAL 1991 Universal Counter/Timer 180MHz 9 digit £150
MARCONI 2437 Universal Counter/Timer DC-100MHz 8 digit £175
MARCONI 2431A Frequency Counter 10Hz-200MHz 8 digit £150
MARCONI 2430A Frequency Counter 10Hz-80MHz 8 digit £125
RACAL 9918 Frequency Counter 10Hz-520MHz 8 digit £200
RACAL 9913 Frequency Meter 10Hz-200MHz 8 digit £125
RACAL 9901 Universal Counter/Timer DC-50MHz 6 digit £100
RACAL 9901 Frequency Meter 10Hz-120MHz 7 digit £100
DARTON 1081A 6.5 digit Autocal Multimeter True RMS AC/Current £200
H.P. 3490A 5 digit Multimeter AC/DC/Ohms £750
H.P. 3435A 3.5 digit Multimeter AC/DC/Ohms/Current LED £100
PHILIPS PM2534 Multi Function DMM 3.5-6.5 digit GPIB/IEEE £450
SOLARTRON 7150 6.5-5.5 digit DMM with IEEE £600
SOLARTRON 7045 4.5 digit Multimeter Volts/Amps/Ohms £80
WAYNE KERR 8905 Automatic Precision Bridge 0.05% £400
MARCONI TF2700 Universal Bridge Battery Operated from £125
MARCONI TF1313A Universal LCR Bridge 0.1% £150
HEATHKIT IB RLC Bridge £60
BRADLEY 192 Oscilloscope Calibrator £500
WITRON 560 Scaler Network Analyser with Detectors £1000
H.P. 5050A Signature Analyser £250
FARNELL H30/100 30V 10A Metered £200
FARNELL TV570/M2 70V 5A/35V 10A Metered £200
FARNELL B30/10 30V 10A Variable £200
FARNELL L30C 0-30V 0-5A Metered £175
MARCONI W601 TF215A 0-50V 1A 0-15V 2A 0-75V 4A Metered £125
FARNELL H30/100 30V 10A Metered £200
BRANDENBURG 472R PSU - / - 2kV £260
FEEDBACK FG600 Sine/SQ/Tri 0.01Hz-100kHz £600
LYONS PC71N Pulse Gen. PRF 1Hz-20MHz 10mSec £75
FARNELL L011 M2B Audio Analyser £300
LINCOLN LA1 M2B Audio Analyser £350
UNIAHOM EP501 Audio Analyser £1250
RADFORD LD04 Low Distortion Oscillator £300
RADFORD LDMS2 Low Distortion Measuring Set £300
MARCONI TF2163 Attenuator DC-1GHz £100
MARCONI TF9938 Audio Power Meter Sine/Mod £250
H.P. 1650D Logic Analyser 45ch £750
H.P. 8405A Vector Voltmeter 1-1000MHz from £300

NEW EQUIPMENT
HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz £847
Daytime base £353
HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay Sweep £353
HAMEG OSCILLOSCOPE HM205-3 Dual Trace 30MHz Comp. Tester £392
HAMEG OSCILLOSCOPE HM205-3 Dual Trace 20MHz Digital Storage £555
All other models available. All oscilloscopes supplied with 2 probes
BLACK STAR EQUIPMENT (P&P all units £5)
APOLLO 10 100MHz Counter Timer Ratio/Period/Time Int. etc £222
APOLLO 100 100MHz (as above with more functions) £325
METEOR 100 FREQUENCY COUNTER 100MHz £119
METEOR 600 FREQUENCY COUNTER 600MHz £189
METEOR 1000 FREQUENCY COUNTER 1GHz £148
JUPITOR 300 FUNCTION GEN. 0.1Hz-500kHz Sine/SQ/Tri £119
ORION COLOUR BAR GENERATOR Pal/TV/Video £229
All other Black Star equipment available
OSCILLOSCOPE PROBES Switched X1 X10 (P&P £3) £12

EVERYDAY WITH PRACTICAL ELECTRONICS

Everyday with Practical Electronics reaches twice as many UK readers as any other independent monthly hobby electronics magazine, our audited sales figures prove it. We have been the leading independent monthly magazine in this market for the last nine years

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday with Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Advertisements, Everyday with Practical Electronics, Holland Wood House, Church Lane, Great Holland, Essex CO13 0JS. Phone/Fax (01255) 850596.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

*** SURVEILLANCE KITS ***

MRT1 MICRO TRANSMITTER, 26mm x 20mm including sensitive electret microphone, tuneable 80-115MHz, 500M range. Kit £4.95, Assembled £8.95.

MTT1 TELEPHONE TRANSMITTER, 35mm x 10mm, powered from line, transmits all conversations, 500M range, 80-120MHz. Kit £5.95, Assembled £10.95.

All prices include p&p. Send 2x2nd class stamps for Catalogue. Cheques/P.O.s payable to:

EXCEL PRODUCTS (Dept. EPE)

Unit 14, Sunningdale, Bishop's Stortford, Herts CM23 2PA

BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING

THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT AN EQUAL OPPORTUNITIES PROGRAMME

O.N.C., O.N.D. and H.N.C.

Next course commences

Monday 9th January 1995

FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept EPE) 20 PENYERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: 071-373 8721



ASTRA Desk Top Accounting™

Overture - Invoicing, Sales, Nominal, VAT, etc
Premier - plus Stock, Jobs, EPOS, etc
Professional - plus Multi-Currency/Depts, etc

S&S Systems Ltd, Bretton Court, Manor Road, Wales
Sheffield, S31 8PD, UK. (Software distributors and Apple dealers)
Tel: (01909) 773399 • Fax: (01909) 773645 • Int Code: 444 1909

The Amazing CLEANFIT wirefree Alarm System

- Protects homes, cars and outbuilding.
- Advanced radio technology linked detectors
- DTI Approval type MPT 1340
- Fitted in under 2 hours
- Full remote control operation


LOWEST PRICES IN UK

Free Info Pack. Tel: 0246 240800 or Fax 0246 240400

THE VINTAGE ELECTRONICS AND WIRELESS LISTING

Published regularly, contains for sale hundreds of old, modern and out of print Electronics and Wireless Books, Magazines. Surplus and obsolete components, spares, valves, semiconductors, electronic and wireless equipment. Send six first class stamps for next catalogue or £3.75 for next four issues.

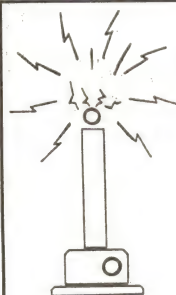Dept. E. CHEVET SUPPLIES LTD.,
157 Dickson Road, Blackpool FY1 2EU.
Tel: 0253 751858 Fax: 0253 302979



Solid State
Lightning Generator
100,000 Volts DC
Operates from 12-15V DC
Lab quality device
Caution required
Complete kit £119.50
Assembled and tested
£189.50

Cheque and postal orders to A. Radley
12 Orford Avenue, Warrington,
Cheshire WA2 7QL

CLASSIFIED

MINI C.C.D. CAMERA

Mini C.C.D. camera only
32x32mm complete with
3.8mm wide view lens and 9v
power supply. Plugs directly
into most types of video
recorders using the video
input. Min. illumination 0.3 Lux.
Standard mini board camera
(uncased) only

£195 including carriage.

ALSCO

Astley House,
Johnson St Tyldesley,
Manchester,
M29 8AB.

Tel. 0942 893573

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY

1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1 1/2 amps d.c. Fully stabilised. Twin panel meters for instant voltage and current readings. Overload protection

Fully variable.

Operates from

240V a.c.

Compact unit.

Size 9 x 5 1/2 x 3 in.

NEW MODEL. Up to 38volts d.c. at 6 amps. 10 amps peak. Fully variable

Twin panel meters. Size 14 1/2 x 11 x 4 1/2 in. £96 inc VAT. Carr £6.



£45 inc. VAT

+ Post and insurance £4

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON
SURREY, U.K. Tel: 081-684 1665

List. Large SAE. Delivery 7 days. Callers welcome. Closed Wednesday

THE BRITISH AMATEUR ELECTRONICS CLUB

exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.

For membership details, write to the Secretary:

**Mr. J. F. Davies, 70 Ash Road, Cuddington,
Northwich, Cheshire CW8 2PB.**

Space donated by Everyday with Practical Electronics

FRASER ELECTRONICS

NEW CATALOGUE/PRICE LIST
NOW AVAILABLE - 76 PAGES

3000 items at competitive prices!

Batteries • Buzzers • Cable • Displays
Capacitors • Cases • Connectors • LDR
CMOS • Crystals • Data switches • Diodes
Displays • Fuses • Integrated circuits
Knobs • LEDs • Loudspeakers • Relays
Resistors • Solder equipment • Switches
Transformers • Transistors • Triacs • etc

For your copy, send your name and
address, with 50p (stamp) towards
cost of carriage to:

FRASER ELECTRONICS

42 Elm Grove, Southsea, Hants PO5 1JG

Miscellaneous

PROTOTYPE PRINTED CIRCUIT BOARDS
one offs and quantities, for details send s.a.e. to
B. M. Ansbro, 38 Poynings Drive, Hove, Sussex
BN3 8GR, or phone Brighton 883871.

G.C.S.E. ELECTRONICS KITS, at pocket
money prices. S.A.E. for FREE catalogue.
SIR-KIT Electronics, 70 Oxford Road, Clacton,
CO15 3TE.

PLDs AND EPROMS copied or programmed.
We supply logic devices/convert discrete logic to
PLDs. Also PCBs designed. Send for details to
PO Box 1561 Bath (0225 444467).

**PROTECT YOURSELF AGAINST
COMPUTER/T.V. EMANATIONS.** Fix our
Harmonisers to your instruments/sets. Small,
innovative, different. Future Concepts, 19
Wellfield Avenue, London, N10 2EA. 081-883
0767.

AUDIO COMPRESSOR/EXPANDER KIT. All
components supplied. Input 10mV-1V. Output
90mV r.m.s. (nominal). Power requirements 6
volts d.c. 10mA (typical). £12.95 inc. postage. Star
Designs, 67 Medoc Close, Cheltenham GL50 4SP.

SOLAR TECHNOLOGY CATALOGUE. New,
3rd edition, 50 pages with wide range of security
lights, portable lamps, battery chargers, in-
dividual solar cells, small motors and many other
components. Send £5 (£3 refund on order) to:
SPI Ltd/EPE, 21a Broadwalk, Pinner Road,
North Harrow, Middlesex HA2 6ED. Tel:
081-424 0262 (Fax: 424 0824).

VALVE ENTHUSIASTS: Capacitors and other
parts in stock. For free advice/lists please ring,
Geoff Davies (Radio), Tel: 0788 574774.

**PRINTED CIRCUIT BOARDS - QUICK
SERVICE.** Prototype and Small Production. We
can raise your artwork from magazines or your
draft designs at low cost. PCB's also designed
from schematics. For details send to P. Agar, 54
Forthill Street, Enniskillen, BT74 6AJ or phone
0365 326800 (7 days).

OSCILLOSCOPE. Farnell DTV 60 3 Channel
8 Trace 60MHz with manual probes and soft
case. Current model, in absolute pristine condi-
tion. Cost £779 sell for £365. Tel: evenings 0272
407599.

**FREE Variable Power Supply + 12 project
catalogue £1 P&P.** Poweramps, 60 watt £5, TO3
heatsink, ex-equipment. K.I.A., 1 Regent Road,
Ilkley.

HUNDREDS of unusual items cheap! Send £1
coin for interesting samples and list. Grimbsy
Electronics, Lambert Road, Grimsby.

This 2 1/2 cm space in
**Everyday with
Practical Electronics**
Would ONLY cost you
£20 + VAT

1000 MIXED VALUE RESISTORS

Intelligent mix 1/4w 5% CR25 **£7.50 Inc.**
Carbon film. Full E12 range. VAT & p&p
4R7 to 10M 64 different values.

Satisfaction Guaranteed.

KARE ELECTRONICS

32 Pear Tree Avenue, Ditton, Aylesford,
Kent ME20 6EB. 0732 844633.

MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 10 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 100 years experience in home-study courses, and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for **FREE INFORMATION** on the course of your choice. (Tick one box only!)

GCSE/A' LEVEL over 20 examination subjects to choose from. Ask for details.

Electronics ☐	TV, Video & Hi-Fi Servicing ☐
C & G Basic Electronic Engineering ☐	Refrigeration & Air Conditioning ☐
Electrical Engineering ☐	PC Repair ☐
Electrical Contracting/Installation ☐	Computer Programming ☐

Mr/Mrs/Miss/Ms

Address

P.Code

ICS International Correspondence Schools, Dept. ECS C4, 312/314 High Street, Sutton, Surrey SM1 1PR. Tel: 041-221 7373 (24 hours). Fax: 041-221 8151.

VISA



Cooke International

SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS, GENERATORS, OSCILLOSCOPES, POWER METERS, ETC. ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE
COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME
SEND LARGE S.A.E. (50p POSTAGE) FOR LISTS OF EQUIPMENT & MANUALS
ALL PRICES EXCLUDE VAT AND CARRIAGE
DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED

OPEN MONDAY TO FRIDAY 9AM-5PM

Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis,
West Sussex, PO22 0EB

Tel (+44) 0243 545111/2 Fax (+44) 0243 542457

EQUIPMENT & ACCESSORIES PURCHASED

MARAPET ELECTRONIC COMPONENTS

Tel: 0452 526883

Spares for TV ★ Video ★ Audio ★ Computer Equipment

VIDEO SPARES
We can supply Pinch Rollers, Idlers, Belt Kits, Heads & many other Service & Specific parts for over 160 makes.

TV - SATELLITE
Switches, Transformers, Semiconductors, etc., etc. Large range available.

EQUIPMENT MANUALS
Large selection of Manufacturers Service & User information available. Original manuals supplied if possible.

SEMICONDUCTORS
We can supply thousands of different Custom & Industry Standard devices.

REMOTE CONTROL HANDSETS
Very large range available from... £10.99

PHONE for a 'PRICE & AVAILABILITY' on your requirements, or send S.A.E. for more information on our service.

Order by Post or Phone. We accept Credit Cards, DELTA & SWITCH. (Please give Validity Dates & Issue No.'s). Add: £1.20 (UK) P&P (+50p for LOPTX's) & 17.5% VAT. (NB: VAT is also due on P&P - Manuals are zero-rated).



Mail Order to:- MEC
1 HORNBEAM MEWS
GLOUCESTER GL2 0UE

INFOTECH & STREE

76 Church St, Larkhall, Lanarks, ML9 1HE

Phone (0698) 883334/888343 or Fax (0698) 884825

Remember: Not only do we have every sheet ever produced, but we also have

The World's Largest Collection of SERVICE MANUALS & CIRCUITS

We are now successfully running a Library Service which allows you to borrow any manual you want for as long as you want, and when you need another manual, just return the one you have, plus a £4.95 exchange fee and tell us what you want next.

Borrow any Service Manual for £4.95
regardless of its size or normal cost

The cost of this service is a yearly subscription fee of only £59.95. Join now & get a free 'Data Ref Guide'.

SERVICE MANUALS

We have what is probably the largest range of Service Information available anywhere.

From the Earliest Valve Wireless to the Latest Video Recorders. Colour Televisions, Test Gear, Audio, Computers, Amateur Radio in fact practically anything.

Write, Fax or Phone for immediate Quote. Originals or Photostats as available.

Also available. Our FREE catalogue detailing Hundreds of Technical Books and Repair Guides available.

STOP PRESS

Now Available. Our Service Manuals Index on P.C. Disc (3.5") for use on your Computer. Just £3.50 with FREE everlasting Updates. Order MP-285.

MAURITRON TECHNICAL SERVICES (EPE),
8 Cherry Tree Road, Chinnor, Oxon, OX9 4QY.

Tel:- 01844-351694. Fax:- 01844 352554.

Please forward your latest catalogue for which I enclose 2 x 1st Class Stamps. or £3.50 for the Technical Books Catalogue plus Manuals Index on PC Disc(s).

NAME

ADDRESS

POSTCODE

If you do not wish to cut your magazine photocopy this coupon or use a separate sheet

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60
OUTPUT 0-260V

	Price	P&P
0.5KVA 2.5 amp max	£31.90	£6.00
	(£44.53 inc VAT)	
1 KVA 5 amp max	£41.15	£7.00
	(£56.58 inc VAT)	
2KVA 10 amp max	£59.40	£8.50
	(£79.78 inc VAT)	
3KVA 15 amp max	£78.65	£8.50
	(£102.40 inc VAT)	
5KVA 25 amp max	£139.15	(Plus Carriage)

Buy direct from the Importers. Keenest prices in the country
COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO
110-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

WIDE RANGE OF XENON FLASH TUBES

Write/Phone your enquiries

ULTRA VIOLET BLACK LIGHT FLOURCESCENT TUBES

4ft 40 watt £12.00 (callers only)	(£14.10 inc VAT)
2ft 20 watt £7.44 + £1.25 p&p	(£10.21 inc VAT)
12in 8 watt £4.80 + 75p p&p	(£6.52 inc VAT)
9in 6 watt £3.96 + 50p p&p	(£5.24 inc VAT)
6in 4 watt £3.96 + 50p p&p	(£5.24 inc VAT)

230V AC BALLAST KIT
For either 6in, 9in or 12in tubes £6.05 + £1.40 p&p (£8.75 inc VAT)

400 WATT UV LAMP
Only £38.00 + £4.00 p&p (£49.35 inc VAT)

160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB
Available with B.C. or E.S. fitting. Price inc VAT & p&p £25.55

12V D.C. BILGE PUMPS
500 GPH 15ft head 3 amp £19.98
1750 GPH 15ft head 9 amp £34.55

Also now available:
24V D.C. 1750 GPH 15ft head 5 amp £35.55

All designed to be used submerged. PRICES INCLUDE P&P & VAT

EPROM ERASURE KIT
Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angstrom Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£19.98 inc VAT)

SUPER HY-LIGHT STROBE KIT
Designed for Disco, Theatrical use etc. Approx 16 joules. Adjustable speed £50.00 + £3.00 p&p (£62.28 inc VAT)

Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)

SAE for further details including Hy-Light and industrial Strobe Kits.



SERVICE TRADING CO
57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

TEL: 081-995 1560 FAX: 081-995 0549

ACCOUNT CUSTOMERS MIN. ORDER £10



Ample Parking Space

"BOFFINS SPECIAL" - UNIQUE OFFER

Surplus Precision Medical Unit, internally in excellent condition. Designed primarily to eject a precise controllable amount of fluid from a medical syringe (latter not supplied). Contains the following removable components: Dual Micro Processor Boards and EPROMS. Escap Precision 12V DC Motor with 300:1 Gear Box and optical encoder coupled to a precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad A.A. cells back-up. L.C.D. Digital read-out 17mm high with legends. Audible warning.

These are sold for the dismantling of the exceptional quality components. Regret no Circuits available. Ridiculously low price: £20.00 + £4.00 p&p (£28.20 inc VAT).

12V D.C. GEARED MOTOR

12V D.C. Reversible precision-built Motor Output speeds no load approx. 12V-26 rpm; 9V-20 rpm; 6V-12 rpm. Will work at lower voltages and still retain a reasonable torque. Ideal for robotics etc. Size: L. 40mm. W. 29mm. H. 39mm. Shaft: 3mm dia x 10mm long. Price: £8.00 + 50p p&p (£10.00 inc VAT)

240V AC CENTRIFUGAL BLOWER

New Manuf. Surplus Skeleton Blower suitable for mounting inside an enclosure to cool equipment. Overall size 130 x 110 x 85mm. Outlet 80 x 35mm. Impeller 60mm dia. x 60mm long. Price £14.10 inc p&p & VAT.

SEWING MACHINE MOTOR

Brand new 220/240V AC/DC SEW-TRIC 2 lead Brush Motor Size L. 100mm x H. 70mm x W. 55mm. Spindle 1/4 in. dia. x 1 in. long. Price £14.10 inc p&p & VAT.

GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £27.73.

SOLID STATE EHT UNIT

Input 230/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

SAVE POUNDS !!!

Build your own forged bank note detector. Can detect counterfeit amongst a quantity of notes. Complete kit of parts less case. 240V a.c., including 6" µV black light tube, starter and holder, a pair, bi-pin tube holders. Total price including p&p & VAT only £13.99.

MICROSWITCH

Pye 15 amp changeover lever microswitch, type S171. Brand new, price £5 for £7.05 inc VAT & p&p

WASHING MACHINE WATER PUMP

Brand new 240V AC fan cooled. Can be used for a variety of purposes. Inlet 1 1/2 in., outlet 1 in. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

Mixed metal/carbon film resistors 1/4W E12 series 10 ohms to 1 Megohm	2p
Carbon Film resistors 1/4W 5% E24 series 0.51 R to 10MΩ	1p
100 off per value - 75p. even hundreds per value totalling 1000	£6.00
Metal Film resistors 1/4W 10R to 1 MΩ 5% E12 series - 1 1/2p. 1% E24 series	2p
Mixed metal/carbon film resistors 1/4W E24 series 1R to 10MΩ	1 1/2p
1 watt mixed metal/Carbon Film 5% E12 series 4R7 to 10 Megohms	5p
Linear Carbon pre-sets 100mW and 1/4W 100R to 2MΩ E6 series	7p
Miniature polyester capacitors 250V working for vertical mounting	
.015, .022, .033, .047, .068-4p. 0.1 - 5p. 0.12, 0.15, 0.22 - 6p. 0.47 - 8p. 0.68 - 8p. 1.0 - 12p	
Mylar (polyester) capacitors 100V working E12 series vertical mounting	
1000p to 8200p - 3p. .01 to .068 - 4p. 0.1 - 5p. 0.12, 0.15, 0.22 - 6p. 0.47/50V - 8p	
Submin ceramic plate capacitors 100V wkg vertical mountings. E12 series	
2% 1.8pf to 47pf - 3p. 2% 56pf to 330pf - 4p. 10% 390p - 4700p	4p
Disc/plate ceramics 50V E12 series 1P0 to 1000P, E6 Series 1500P to 47000P	2p
Polystyrene capacitors 63V working E12 series long axial wires	
10pf to 820pf - 5p. 1000pf to 10,000pf - 6p. 12,000pf	7p
741 Op Amp - 20p. 555 Timer - 20p. LM3900	80p
CMOS 4001 - 20p. 4011 - 22p. 4017 - 40p. 4069UB unbuffered	20p
DIL holders, 8-pin 9p; 14-, 16-, 18-pin 12p; 24-pin 18p; 28-pin 20p; 40-pin 25p.	
ALUMINIUM ELECTROLYTICS (Mfds/Volts)	
1/50, 2/250, 4/750, 10/25, 10/50	5p
22/16, 22/25, 22/50, 33/16, 47/16, 47/25, 47/50	6p
100/16, 100/25, 100/50	12p
220/16, 220/25, 220/50 10p; 470/16, 470/25	11p
1000/25 25p; 1000/35, 2200/25 35p; 4700/25	70p
Subminiature, tantalum bead electrolytics (Mfds/Volts)	
0.1, 0.22, 0.47, 1.0, 2.2, 3.3 @ 35V - 4.7/16, 6.8/10, 10/6, 10p; 6.8/35, 12p.	
4.7/25, 6.8/16, 10/6, 11p; 15/16, 22/6, 33/10, 15p; 10/25, 16p; 10/35, 22/16, 20p.	
47/10, 20p; 47/16, 25p; 47/20, 30p; 47/35, 32p; 100/3, 18p; 100/6, 22/6, 20p.	
VOLTAGE REGULATORS	
1A + or - 5V, 8V, 12V, 15V, 18V & 24V - 55p. 100mA 5.8, 12, 15, V +	30p
DIODES (piv/amps)	
75/25mA 1N4148 2p. 800/1A 1N4006 4p. 400/3A 1N5404 14p. 115/15mA OA91	8p
100/1A 1N4002 3p. 1000/1A 1N4007 5p. 60/1.5A 1SM1 5p. 100/1A bridge	25p
400/1A 1N4004 4p. 1250/1A BY 127 10p. 30/150mA OA47 gold bonded	18p
Zener diodes E24 series 3V3 to 33V 400mW - 6p. 1 watt	10p
Battery snaps for PP3 - 7p for PP9	12p
L.E.D. s 3mm, & 5mm. Red, Green, Yellow - 10p. Grommets 3mm - 2p. 5mm	2p
Red flashing L.E.D.'s require 9-12V supply only, 5mm	50p
Mains indicator neons with 220k resistor	10p
20mm fuses 100mA to 5A. O. blow 6p. A/surge 10p. Holders, chassis, mounting	15.00
High speed pc drill 0.8, 1.0, 1.3, 1.5, 2.0mm - 40p. Machines 12V dc	£4.50
HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs	£6.50
AA/HP7 Nicad rechargeable cells 90p each. Universal charger unit	£1.10 per pack
AA/HP7 zinc/carbon batteries in packs of 4	20p
Glass reed switches with single pole make contacts - 8p. Magnets	70p
0.1" Stripboard 2 1/2" x 1" 9 rows 25 holes - 25p. 3 1/4" x 2 1/2" 24 rows 37 holes	10p
Jack plugs 2.5 & 3.5mm - 14p. Sockets Panel Mtg. 2.5 & 3.5mm	£1.50
Ear pieces 2.5 & 3.5mm, dynamic - 20p; 3.5mm crystal	
Multi cored solder, 22G - 8p yard, 18G - 14p yard.	
TRANSISTORS	
BC107/8/9 - 12p. BC547/8/9 - 8p. BC557/8/9 - 8p. BC182, 182L, BC183, 183L,	
BC184, 184L, BC212, 212L - 10p.	
BC327, 337, 337L - 12p. BC727, 737 - 12p. BD135/6/7/8/9 - 25p. BCY70 - 18p.	
BFY50/51/52 - 20p.	
BFX88 - 15p. 2N3055 - 55p. TIP31, 32 - 30p. TIP41, 42 - 40p. BU208A - £1.50, BF195, 197 - 12p.	
Ionisers with seven year guarantee, 240V AC, list price £16.95 or more	£12.50
Do not add VAT. Postage 30p (free over £5). Stamp for list.	
THE CR SUPPLY CO	
127 Chesterfield Rd., Sheffield S8 0RN Tel: 0742 557771 Return posting	

SHERWOOD ELECTRONICS

7 Williamson Street, Mansfield, Notts. NG19 6TD

SPECIAL OFFER - choose 2 x £1 packs **FREE** with every 12 purchased

SP1	15 x 5mm Red Leds	SP37	15 x 100/35V radial elect caps
SP2	15 x 5mm Green Leds	SP42	200 x Mixed 0.25W C.F. resistors
SP3	12 x 5mm Yellow Leds	SP47	5 x Min. push button switches
SP4	10 x 5mm Amber Leds	SP102	20 x 8 pin DIL sockets
SP10	100 x 1N4148 diodes	SP103	15 x 14 pin DIL sockets
SP11	30 x 1N4001 diodes	SP104	15 x 16 pin DIL sockets
SP12	30 x 1N4002 diodes	SP112	5 x Cmos 4093
SP18	20 x BC182 transistors	SP125	10 x 1000/16V radial elect caps
SP19	20 x BC183 transistors	SP130	100 x Mixed 0.5W C.F. resistors
SP20	20 x BC184 transistors	SP133	20 x 1N4004 diodes
SP22	20 x BC214 transistors	SP134	15 x 1N4007 diodes
SP23	20 x BC549 transistors	SP137	4 x W005 1.5A bridge rectifiers
SP24	5 x Cmos 4001	SP138	20 x 2.2/50V radial elect caps
SP28	5 x Cmos 4011	SP142	2 x Cmos 4017
SP29	4 x Cmos 4013	SP147	5 x Stripboard 9 strips x 25 holes
SP36	25 x 10/25V radial elect caps	SP165	2 x LF351 Op-amps

RESISTOR PACKS - 0.25W C.Film	
RP3	5 each value - total 365
RP7	10 each value - total 730
RP10	1000 popular values

Catalogue available £1 or **FREE** with first order over £5

Cheques or P.O. to **SHERWOOD ELECTRONICS** NO VAT
Please add £1.25 P&P to all orders

Millions of quality components at lowest ever prices!

Plus Tools, Watches, Fancy Goods, Toys.
Mail order UK only.

All inclusive prices -
NO VAT to add on.

Send 43p stamped self addressed label or envelope for catalogue/clearance list.

At least 2,100 offers to amaze you.

Brian J Reed
6 Queensmead Avenue, East Ewell
Epsom, Surrey KT17 3EQ
Tel: 081-393 9055

VALVES	
30L15, £4; ECC804, £3;	
ECH84/EF85/EH90/EY86/	
PCF801/PCF806/PC188/	
PL81/PL83/PY82.....All £1 ea*	
5 1/4" to 3 1/2" floppy converter	
leads.....	£1.50 ea*
STC p.s.u. 240V Input; 5V 6A	
Output, (converts to 12V 3A,	
details supplied).....	£5.95
Temperature probes, with	
data.....	£3.95*
Universal Timer (10 min.	
delay and 20 min. cut-off	
functions).....	£3.95*
TRANSISTORS	
BDX42/BDY91/BD237/	
BUX85/BSS52.....All 50p ea*	
12V 400mW Zeners, ...£1 - 100*	
MOSFETS, 10A 450V,	
10A 500V.....	£2.50 ea*
UM1287 sound and video	
modulator.....	£2.50 ea*
3AMP mains filters.....	£1.00 ea*
12V counters.....	£1.00 ea*
40 Character x 1-line dot	
matrix display.....	£4.95 ea*
Car Dashboard Display (shows	
lights, indicators, doors,	
on picture of car).....	£4.95*
4-digit clock display.....	£2.50*
4-digit l.c.d. with 7211	
driver.....	£3.50*
17-digit v.f. display.....	£2.95*
Giant 2 digit v.f. display.....	£2.95*
12V stepper motors, 48 steps	
per rev., 7.3° step angle.....	£3.95*
250 off mixed electrolytic	
caps.....	£4.95*
250 off polyester caps.....	£4.95*
1000 off mixed resistors	
1/4W.....	£4.95*
100 off phono plugs.....	£2.95*
50 off mixed terminal	
blocks.....	£2.50*
25 off buzzers & sounders.....	£3.50*
25 off mixed relays.....	£4.95*
50 off mixed switches.....	£7.50*
250 off i.c. sockets.....	£3.95*
1000 off Ceramic caps.....	£7.50*
5 off 3V Lithium memory	
back-up batteries.....	£2.00*
100 off 2200µF 25V caps.....	£6.00*
100 off 4-7µF 25V caps.....	£2.50*
3lb mixed component pack.....	£4.95
Jumbo component pack.....	£10
Crystal oscillators	
10/12Mhz.....	£1 ea
5V DPCO D.I.L. relay.....	60p ea*
5V SPCO S.I.L. reed relay.....	40p ea*
12V Piezoelectric Sounders.....	50p ea
DIL Switches 3/4/6 and	
12-way.....	35p ea*
3-5mm jack plugs.....	10 for £1*
100 off Zener diodes, mixed.....	£2*
21-piece mini screwdriver	
set.....	£3.95*
Universal test lead kit.....	£3.95*
10 crocodile clip leads.....	£3.50*
20 off mixed R.F. Filters,	
Crystals, etc.....	£4.95*
100m P.V.C. sleeving.....	£4.50*
QUANTITY DISCOUNTS	
AVAILABLE PLEASE RING.	
We also buy all forms of electronic components, p.s.u.s, disk drives etc.	
Lists to below address.	
ALL PRICES INCLUDE V.A.T.	
PLEASE ADD £2.00 p&p EXCEPT	
ITEMS MARKED* WHICH ARE 50P.	
SAE FOR BULK BUYING LIST	
PAYMENT WITH ORDER TO:	
Dept EE, COMPELEC,	
14 Constable Road,	
St. Ives, Huntingdon,	
Cambs PE17 6EQ	
Tel/Fax: 0480 300819	

ADVERTISERS INDEX


AUDON ELECTRONICS.....	953
N. R. BARDWELL.....	935
B.K. ELECTRONICS.....	Cover (iii)
BRIAN J. REED.....	984
BULL ELECTRICAL.....	Cover (ii)
CHATWIN GUITARS (JCG).....	900
CIRKIT DISTRIBUTION.....	940
COMPELEC.....	984
COOKE INTERNATIONAL.....	983
CRICKLEWOOD ELECTRONICS.....	981
CR SUPPLY COMPANY.....	984
DISPLAY ELECTRONICS.....	894
ELECTROMAIL (RS COMPONENTS).....	951
ESR ELECTRONIC COMPONENTS.....	904
EXPRESS COMPONENTS.....	978
FRASER ELECTRONICS.....	982
GREENWELD ELECTRONICS.....	899
HART ELECTRONIC KITS.....	896
ICS.....	983
INFOTECH & STREE.....	983
JPG ELECTRONICS.....	981
KARE ELECTRONICS.....	943
LABCENTER.....	969
MAGENTA ELECTRONICS.....	902/903
MAPLIN ELECTRONICS.....	Cover (iv)
MARAPET ELECTRONIC COMPONENTS.....	983
MAURITRON.....	983
M&B ELECTRICAL SUPPLIES.....	970
MQP ELECTRONICS.....	900
NATIONAL COLLEGE OF TECHNOLOGY.....	900
NEWMARKET TRANSFORMERS.....	935
NICHE SOFTWARE.....	981
NUMBER ONE SYSTEMS.....	919
OMNI ELECTRONICS.....	918
PICO TECHNOLOGY.....	897
POWERWARE.....	898
QUANTEK ELECTRONICS.....	918
ROBINSON MARSHALL.....	937
SEETRAX CAE.....	949
SERVICE TRADING.....	983
SHERWOOD ELECTRONICS.....	984
STEWART OF READING.....	981
SUMA DESIGNS.....	977
TANDY.....	923
TSIEN.....	901

POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

★ PRICES INCLUDE V.A.T. ★ PROMPT DELIVERIES ★ FRIENDLY SERVICE ★ LARGE (A4) S.A.E., 60p STAMPED FOR CATALOGUE ★

OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

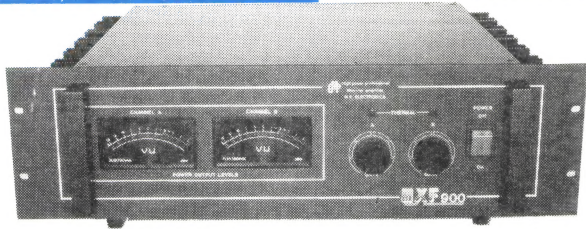THOUSANDS PURCHASED
BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)

MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.


USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
MXF400 W19" x H5 1/4" (3U) x D12"
MXF600 W19" x H5 1/4" (3U) x D13"
MXF900 W19" x H5 1/4" (3U) x D14 3/4"

PRICES:- MXF200 £175.00 MXF400 £233.85

MXF600 £329.00 MXF900 £449.15

SPECIALIST CARRIER DEL. £12.50 EACH

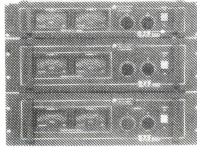

OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER




Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3.5/5KHz, all at 24dB per octave. Bass invert switches in each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE

★ ECHO & SOUND EFFECTS ★

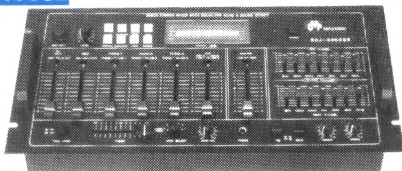STEREO DISCO MIXER with 2 x 7 band & R graphic equalisers with bar graph LED Vu meters. MANY OUTSTANDING FEATURES:- including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.



SIZE: 482 x 240 x 120mm

Price £144.99 + £5.00 P&P

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series. FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.

TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

TYPE 'A'

TYPE 'B'

TYPE 'C'

TYPE 'D'

TYPE 'E'

TYPE 'F'

TYPE 'G'

TYPE 'H'

TYPE 'I'

TYPE 'J'

TYPE 'K'

TYPE 'L'

TYPE 'M'

TYPE 'N'

TYPE 'O'

TYPE 'P'

TYPE 'Q'

TYPE 'R'

TYPE 'S'

TYPE 'T'

TYPE 'U'

TYPE 'V'

TYPE 'W'

TYPE 'X'

TYPE 'Y'

TYPE 'Z'

TYPE 'AA'

TYPE 'AB'

TYPE 'AC'

TYPE 'AD'

TYPE 'AE'

IBI FLIGHT CASED LOUDSPEAKERS

New range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 2" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET
FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

ibi FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR

ibi FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR


SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00

Delivery £6.00 per pair



N-CAR STEREO BOOSTER AMPS

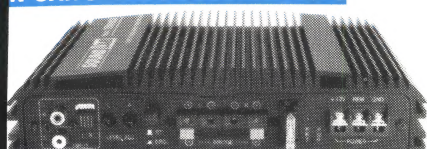

PRICES: 150W £49.99 250W £99.99

400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER
CAR STEREO BOOSTER AMPLIFIERS
150 WATTS (75 + 75) Stereo, 150W
Bridged Mono
250 WATTS (125 + 125) Stereo, 250W
Bridged Mono
400 WATTS (200 + 200) Stereo, 400W
Bridged Mono
ALL POWERS INTO 4 OHMS

Features:

★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES


SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



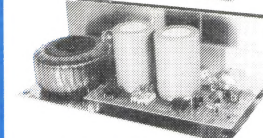OMP/MF 100 Mos-Fet Output power 110 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
-3dB, Damping Factor >300, Slew Rate 45V/uS,
T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R.
-110 dB, Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 200 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
-3dB, Damping Factor >300, Slew Rate 50V/uS,
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
-110 dB, Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
-3dB, Damping Factor >300, Slew Rate 60V/uS,
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
-110 dB, Size 300 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P




OMP/MF 450 Mos-Fet Output power 450 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
-3dB, Damping Factor >300, Slew Rate 75V/uS,
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
-110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2
Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P



OMP/MF 1000 Mos-Fet Output power 1000 watts
R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms,
frequency response 1Hz - 100KHz -3dB, Damping
Factor >300, Slew Rate 75V/uS, T.H.D. typical
0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan
Cooled, D.C. Loudspeaker Protection, 2 Second
Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS:
STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz.
PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS
775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS

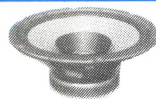

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS
AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER
GRILLES, CROSS-OVERS AND HIGH POWER, HIGH
FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E.
(60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE:- INSTRUMENTS, P.A., DISCO, ETC

ALL EMINENCE UNITS 8 OHMS IMPEDANCE

8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P
RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P
RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P
RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.64 + £3.50 P&P
RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.
12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. PRICE £36.67 + £3.50 P&P
RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB.
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P
RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB.
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P
RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB.
15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P
RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB.
15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P
RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)

BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
8" 50WATT EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.
10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5 1/4" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 99dB.
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE
PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS
COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL
PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm. SUPPLY 12V @ 0.5AMP.
PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH
VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 45mm, SUPPLY 9V BATTERY.
PRICE £8.80 + £1.00 P&P

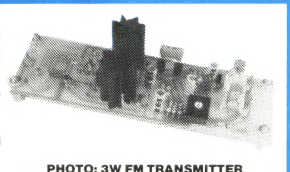


PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHEAD-ON-SEA,
ESSEX, SS2 6TR.

Tel.: 0702 - 527572 Fax.: 0702 - 420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL
ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC.
PRICES INCLUSIVE OF V.A.T. SALES COUNTER. VISA AND
ACCESS ACCEPTED BY POST, PHONE OR FAX.



NEW

FULL COLOUR GUIDE TO ELECTRONIC PRODUCTS


Sept 1994–Aug 1995

Maplin



BS 5750
Part 2 1987

Level B:
Quality Assurance
RS12750

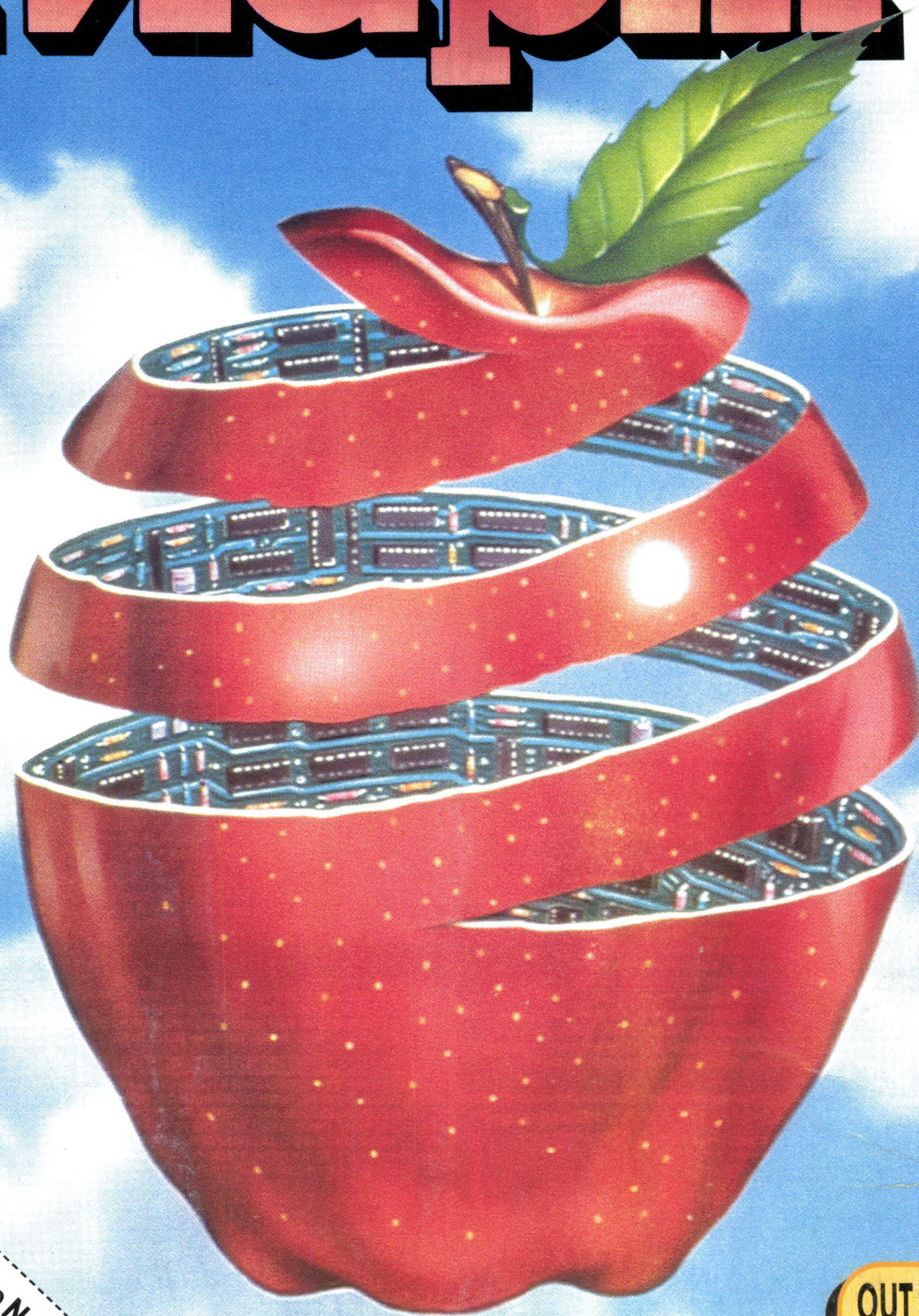

Order your copy of the New MAPLIN Catalogue on sale NOW!

Pick up a copy from any branch of WHSMITH, branches of John Menzies in Scotland ONLY, Eason & Son in N. Ireland ONLY, and Maplin stores nationwide for just £3.45 inc. p&p. If you live outside the UK, send £7.30 or 18 IRCs for Airmail in Europe (including Republic of Ireland); £6.50 or 16 IRCs for surface mail outside Europe; or £12.30 or 30 IRCs for Airmail outside Europe.

I enclose £3.95/£7.30/£6.50/£12.30 (delete as applicable).

Name

Address

Post Code

Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex, England
SS6 8LR

Over 800 colour packed pages
with hundreds of Brand New
Products at Super Low Prices.

OUT OF THIS WORLD
ON SALE NOW
ONLY
£3.45

Available from all branches of WHSMITH, John Menzies in Scotland ONLY, Eason & Son in N. Ireland ONLY, and Maplin stores nationwide. The Maplin Electronics 1995 Catalogue – OUT OF THIS WORLD